

1&2	W	/10
3	20	/20
4 & 5	20	/20
6	30	/30
7	20	/20
Total	100	/100


Note: problems 1 and 2 are a little trickier than last semester! Read carefully!

1) Given  $F = A'B' + CD'$

a. Write  $F'$  in product of sums notation

$$\overline{F} = \overline{A'B' + CD'} = (\overline{A'B'}) (\overline{CD'}) = (A+C)(\overline{C}+D)$$

 b. Implement  $F$  using as few 2 input NOR gates as possible. Assume that only the true literals (A,B,C,D) are available, not their complements (A', B', C', D').




2) Given  $G = (A'+B')(C+D')$

a. Write  $G'$  in sum of products notation.

$$\overline{G} = \overline{(A'+B')(C+D')} = \overline{(A'+B')} + \overline{(C+D')} = AB + \overline{C}D$$

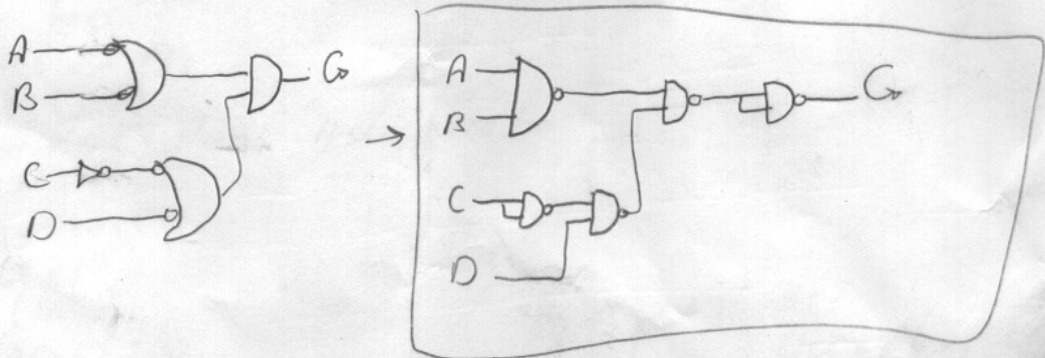b. Implement  $G$  using as few 2 input NAND gates as possible. Assume that only the true literals are available, not their complements.



3) Answer the following questions for the FSM below:

a. Briefly describe the function of this sequence detector. When is the output 1?

1? The seq. det. outputs a 1 when {it receives a 1 as input that was not immediately preceded by a 1} and a 0 otherwise.

b. Write a Verilog module which would implement this FSM for input variable "In" and output variable "Out." Use the same standard format as was presented in the Lab 3 lecture and used in Lab 3. (Define your states; use one always block for next state and output; use one always block for state transition)

```
module FSM(Reset, Clock, In, Out);
```

```
input Reset, Clock, In;
```

```
output Out;
```

```
reg [1:0] curr;
```

```
reg [1:0] next;
```

```
reg Out;
```

```
parameter Star = 2'b00;
```

```
parameter Ray = 2'b01;
```

```
parameter Mo = 2'b10;
```

```
always @(posedge Clock) begin
```

```
if (Reset)
```

```
curr <= Star;
```

```
else
```

```
curr <= next;
```

```
end //always
```

```
always @(curr or In) begin
```

```
next = curr; //default -> stay here
```

```
case (curr)
```

```
Star: begin
```

```
Out = 1'b0;
```

```
if (In)
```

```
next = Ray; //stay here for In
```

```
end //Star
```

```
Ray: begin
```

```
Out = 1'b1;
```

```
if (In)
```

```
next = Mo;
```

```
else
```

```
next = Star;
```

```
end //Ray
```

```
Mo: begin
```

```
Out = 1'b0;
```

```
if (!In)
```

```
next = Star; //stay here for In = 1
```

```
end //Mo
```


```
default:
```

```
Out = 1'bX; //stay in current state until reset, output X
```


```
end case
```

```
end //always
```

```
end module //FSM
```

 

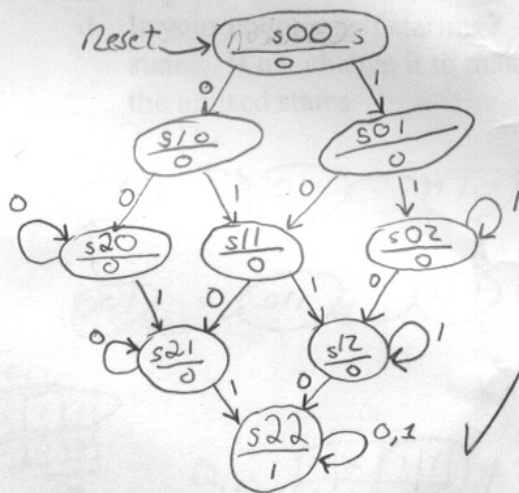
- 4) A finite state machine has one input and one output. The output becomes 1 and remains 1 thereafter when at least two 0s and at least two 1s have occurred as inputs, in any order after reset. Draw a state diagram of this FSM as a Moore machine. Try to minimize the number of states.



State "sxy" means  
 x zeroes and  
 y ones have been seen  
 (saturating at 2 in each case)

Notes: all states transition to s00 upon Reset, overriding In-driven transitions.

 - 5) A Moore machine has one input and one output. The output should be 1 if the total number of 0s at the input is odd, and the total number of 1s at the input is an even number greater than 0. Draw a state diagram. Try to minimize the number of states.




Assumed no Reset signal and initial state = init. If Reset signal required, Reset causes transition to init from any state as in previous FSM.

even zeros, no ones





odd zeros, odd ones etc

 6) Design a 3 FlipFlop counter which transitions through states  $Q_2Q_1Q_0 = 000, 100, 110, 111, 011, 001$  and then repeats.

- Draw the state diagram and state transition table
- Draw the Karnaugh maps, clearly indicating the implicants that you use in your covers of the next-state functions.
- Implement the counter using D flip flops and whatever gates you like.
- Is your counter self starting? If yes, show the transitions of the unused states. If no, change it to make it self starting, and show the transitions of the unused states.



$Q_2$	$Q_1$	$Q_0$	$Q_{2+}$	$Q_{1+}$	$Q_{0+}$
0	0	0	1	0	0
0	0	1	0	0	0
0	1	0	x	x	x
0	1	1	0	0	1
1	0	0	1	1	0
1	0	1	x	x	x
1	1	0	1	1	1
1	1	1	0	1	1

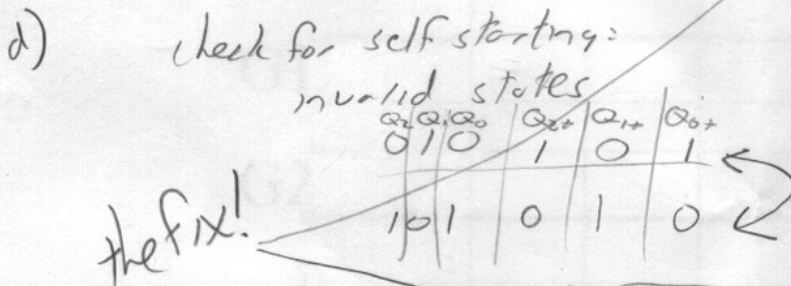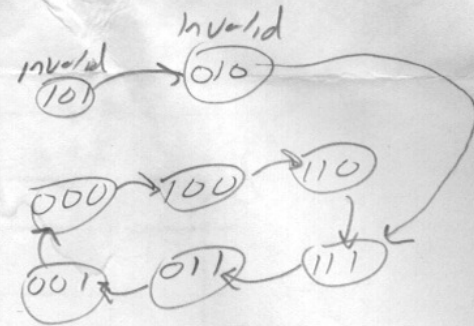  

bad news - each invalid state goes to other invalid state  
**∴ NOT SELF STARTING!**


- To fix, change  $Q_{1+}$  from  $Q_2$  to  $Q_{2+} \overline{Q_0} Q_1$ , ie
- since changed an X to a 1, valid states unaffected. Retry state transitions for invalid states

$Q_2$	$Q_1$	$Q_0$	$Q_{2+}$	$Q_{1+}$	$Q_{0+}$
0	1	0	1	1	1
1	0	1	0	1	0

now it's self starting -

$010 \rightarrow 111$  (good) } **PROVED TO BE SELF STARTING**  
 invalid invalid  
 $101 \rightarrow 010 \rightarrow 111$  (good)  
 invalid invalid valid

7) 20

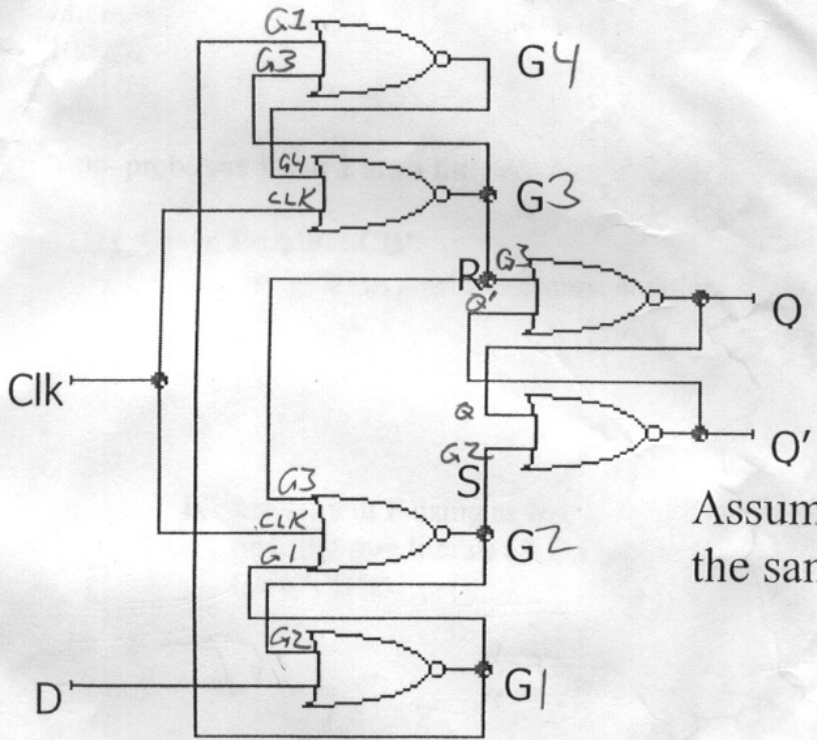

Assume all gates have exactly the same delay.

1 gate delay

