

Name:

SID:

Problem 1 _____ Points of 20

Problem 2 _____ Points of 20

Problem 3 _____ Points of 20

Problem 4 _____ Points of 20


Problem 5 _____ Points of 20

Score _____ %

- Closed book, closed notes
- One pocket calculator permitted (no PDAs, laptops, cell phones, or other electronic devices)
- Show derivations to get partial credit in case of numerical errors
- Cross out incorrect attempts (no partial credit for ambiguous derivations)
- Write results into boxes
- Take off hats or caps and leave backpacks and electronic devices in isle
- Verify that an assistant receives your completed exam!


1. Calculate the value of current i_x . Parameter $I_1 =$ mA, $V_2 =$ V, $V_3 =$ V, $R_1 =$ k Ω , $R_2 =$ k Ω , $R_3 =$ k Ω and $R_4 =$ k Ω .

$i_x =$ 20 pts.
0

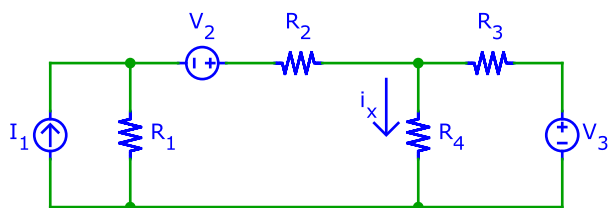


2. Find the value of the voltage v_x . Parameter $I_1 =$ mA, $I_2 =$ mA, $V_3 =$ V, $R_1 =$ k Ω , $R_2 =$ k Ω , $R_3 =$ k Ω , $R_4 =$ k Ω , $R_5 =$ k Ω and $R_6 =$ k Ω .

$v_x =$ 20 pts.
1

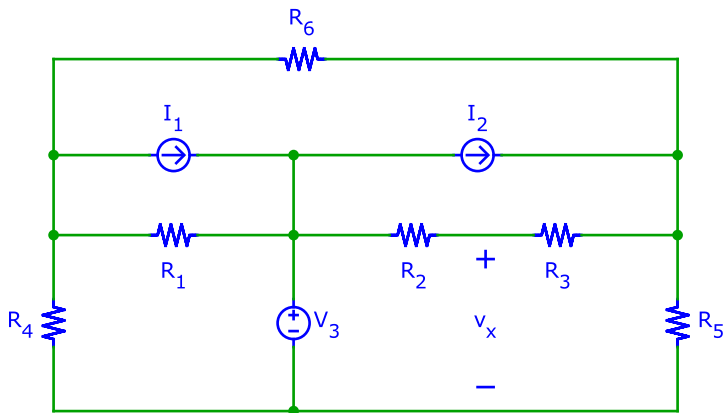

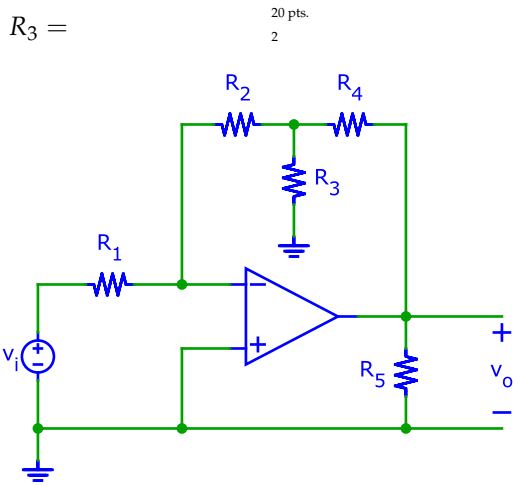3. Opamp circuits with high closed-loop gain require large resistor ratios. On integrated circuits these take up significant area and are therefore costly. The circuit below uses a so-called T-network to reduce the required resistor ratio.

Calculate the value of resistor R_3 such that $v_o/v_i = 10$. Use $R_1 = 10 \text{ k}\Omega$, $R_2 = R_4 = 10 \text{ k}\Omega$ and $R_5 = 10 \text{ k}\Omega$.



4. The output voltage of a temperature sensor element is

$$v_t(T) = -2 \frac{\text{mV}}{^\circ\text{C}} \times T$$

where T is the temperature in degrees Celsius.

Design a thermometer circuit with output voltage

$$v_o(T) = 10 \frac{\text{mV}}{^\circ\text{C}} \times T$$

using the sensor, resistors, and ideal opamps. Your circuit should produce the correct output independent of the output resistance R_o of the temperature sensor, which is in the range $50 \text{ k}\Omega \dots 100 \text{ k}\Omega$. Draw the schematic diagram in the space provided below. Specify the values of all resistors (except R_o).

20 pts.
2

5. Suppose you stand barefoot on a wet floor with a hand-held digital voltmeter (DVM) in one hand. You insert one probe of the DVM into the hot output of a 110 V outlet and touch the other probe with your free hand.

Hypothetical experiment—don't try this!

- a) Draw a circuit schematic of the situation. Use only circuit elements—sources and resistors—and their correct symbols. Do not draw pictures of elements. Assign reasonable values to all circuit components.

10 pts.
3

- b) Would you get hurt? Explain!

10 pts.
4

Password:
