

Question 1. True/False (5 Points)


Circle T for true and F for false below (0.5 points each):

- | | | |
|-----------------------------------------------------------------------------------------------------------------------------|------------------------------------|------------------------------------|
| (i) The set of prime implicants of a Boolean function are unique. | <input checked="" type="radio"/> T | F |
| (ii) A PAL is a device with a fully programmable AND plane. | <input checked="" type="radio"/> T | F |
| (iii) A $2^N:1$ Multiplexer can implement any function of N variables. | <input checked="" type="radio"/> T | F |
| (iv) The Sum of Products form of a Boolean function will always have fewer literals than its Products of Sums form. | T | <input checked="" type="radio"/> F |
| (v) All Boolean function implementations have hazards in them. | T | <input checked="" type="radio"/> F |
| (vi) Combinational logic determines its outputs as a function of the the current inputs and the history of the computation. | T | <input checked="" type="radio"/> F |
| (vii) A ROM is nothing more than a hardware truth table. | <input checked="" type="radio"/> T | F |
| (viii) A circuit with state is an example of combinational logic. | T | <input checked="" type="radio"/> F |
| (ix) PALs are typically faster than PLAs. | <input checked="" type="radio"/> T | F |
| (x) A selector and a multiplexer are essentially the same hardware. | <input checked="" type="radio"/> T | F |

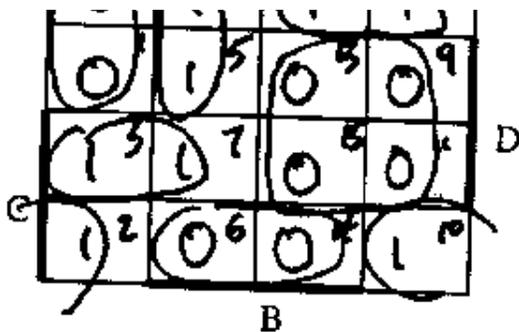Question 2. Canonical Forms (15 points)

Given the function $F(A,B,C,D)=(A+B+C)(B'+C'+D)(A'+C+D')(A'+B'+C')(A'+B+D')$, answer the following questions. Use the K-map below before your intermediate work.





- (i) Write F in *canonical* Product of Sums form using ΠM notation (3 points):

$$F(A, B, C, D) = \Pi M(0, 1, 5, 6, 9, 10, 11, 13, 14, 15)$$

- (ii) Write F in *canonical* Sum of Products form using Σm notation (2 points):

$$F(A, B, C, D) = \Sigma m(2, 3, 4, 5, 7, 8, 10, 12)$$

- (iii) Find the *minimum* literal count Product of Sums form of F (3 points):

$$F(A, B, C, D) = (A' + D')(B' + C' + D)(A + B + C)$$

- (iv) Find the *minimum* literal count Sum of Products form of F (3 points):

$$F(A, B, C, D) = AC'D' + A'BC' + A'CD + B'ED'$$

OR

$$AB'D' + BC'D' + A'BD + A'B'C$$

- (v) Find the *minimum* literal count Product of Sums form of F' (2 points):

$$F(A,B,C,D) = (A+C+D)(A+B'+C)(A+C'+D')(B+C'+D)$$

$$\text{OR } (A'+B+D)(B'+C+D)(A+B'+D')(A+B+C')$$

(vi) Find the minimum literal count Sum of Products form of F' (2 points):

$$F'(A,B,C,D) = AD + BCD' + A'BC'$$

Question 3. Minimization Over Multiple Functions (15 Points)

Given the following four minimized four-variable functions:

$$W(A,B,C,D) = AB^1 + B'C^2$$



$$X(A,B,C,D) = A'BC^3 + AB'C^4 + ABC^5$$



$$Y(A,B,C,D) = A'B^6 + A'C^7$$

$$Z(A,B,C,D) = A'BC^8 + A'B'C^8$$

How many unique product terms are there spanning these functions (1 points): 8

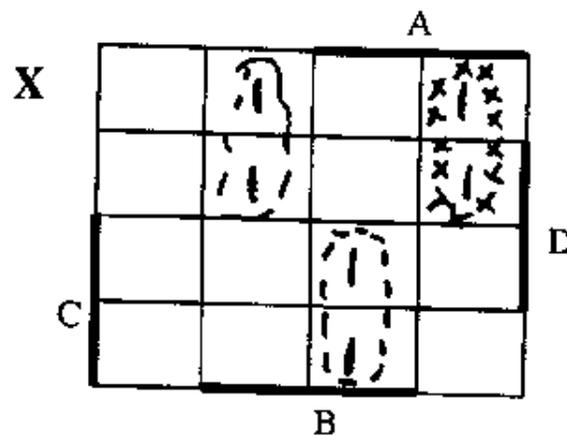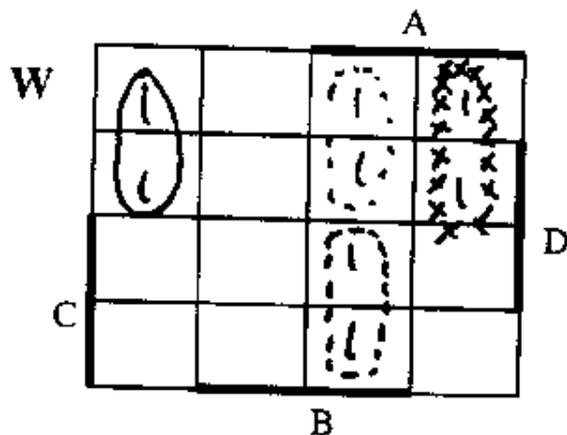Fill in the K-maps below and circle the implicants so as to yield the minimum number of unique product terms spanning the four functions (3 points per K-map and function):



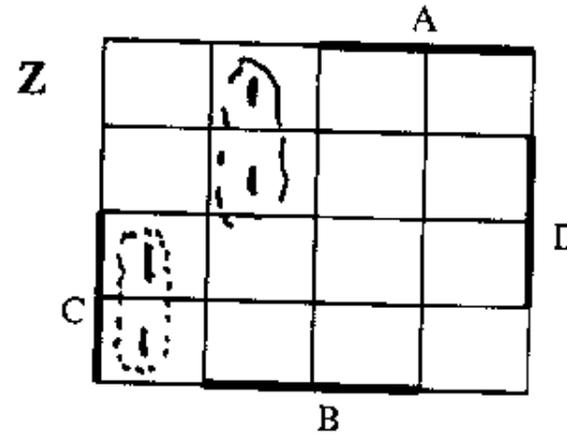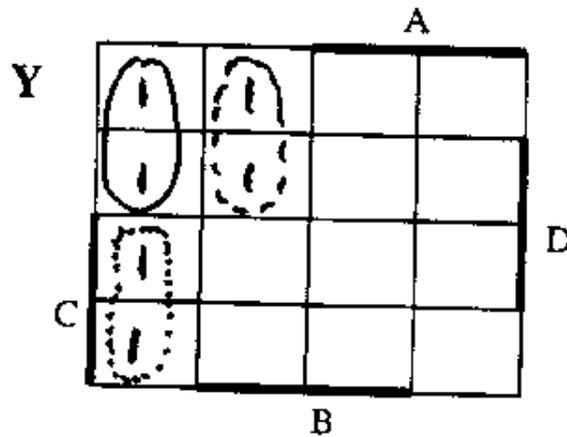

Write the revised expressions for W, X, Y, Z in the boxes below Array:

W = $A'B'C' + ABC' + ABC + AB'C'$

X = $A'BC' + ABC + AB'C'$



Y = $A'B'C' + A'BC' + A'BC'$

Z = $A'B'C' + A'BC'$

The number of unique product terms across all of the four functions is: 6 (2 points)

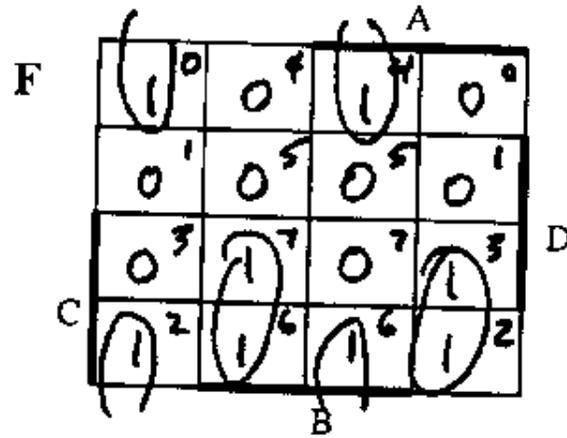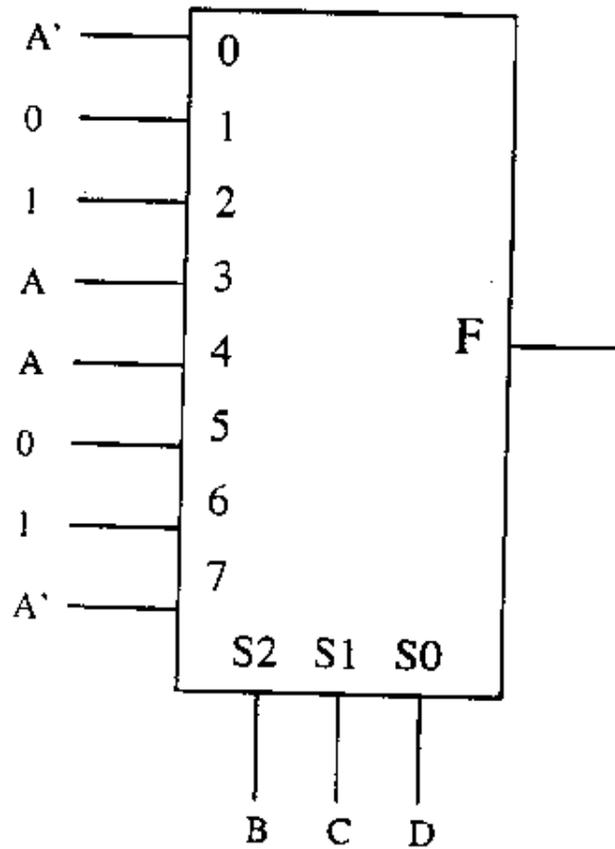Question 4. Multiplexer Implementation (15 Points)

The following implements the four variable function $F(A,B,C,D)$ using a multiplexer. Please note the choice of which variable is a data input and which are multiplexer control inputs:



Reverse engineer this function to write it down in minimized Sum of Products form (10 points):

F(A,B,C,D) = $A'B'D' + A'BC + ABD' + AB'C$

What is your literal count? 12


Assume that you can use XOR and XNOR operators as well AND, OR, and NOT operators. Rewrite the expression for the function F in a *multilevel form* that has an even further reduced literal count (5 points):

$$F(A,B,C,D) = (A \odot B)D' + (A \oplus B)C$$

What is your literal count? _____

6

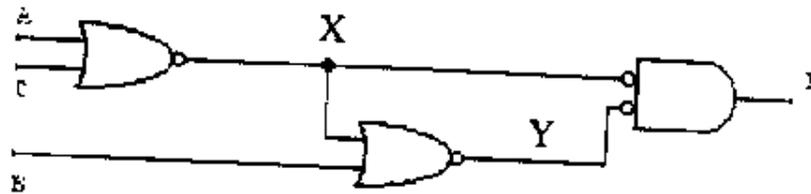Question 5. Circuit Timing and Waveform Diagrams (15 points)
Consider the following circuit schematic and timing waveform.



- (i) Write $F(A,B,C)$ as a multilevel function based on the above schematic (3 points):

$$F(A,B,C) = \overline{X} \overline{Y}$$

$$X = A + C$$

$$Y = X + B$$

- (ii) Write $F(A,B,C)$ in *minimized* literal count Sum of Products form (3 points):


$$F = (A+C)(X+B) = (A+C)(A'C'+B)$$

$$= AB + BC$$

(iii) Write $F(A,B,C)$ in *minimized* literal count Product of Sums form (3 points):

$$F = B(A+C)$$

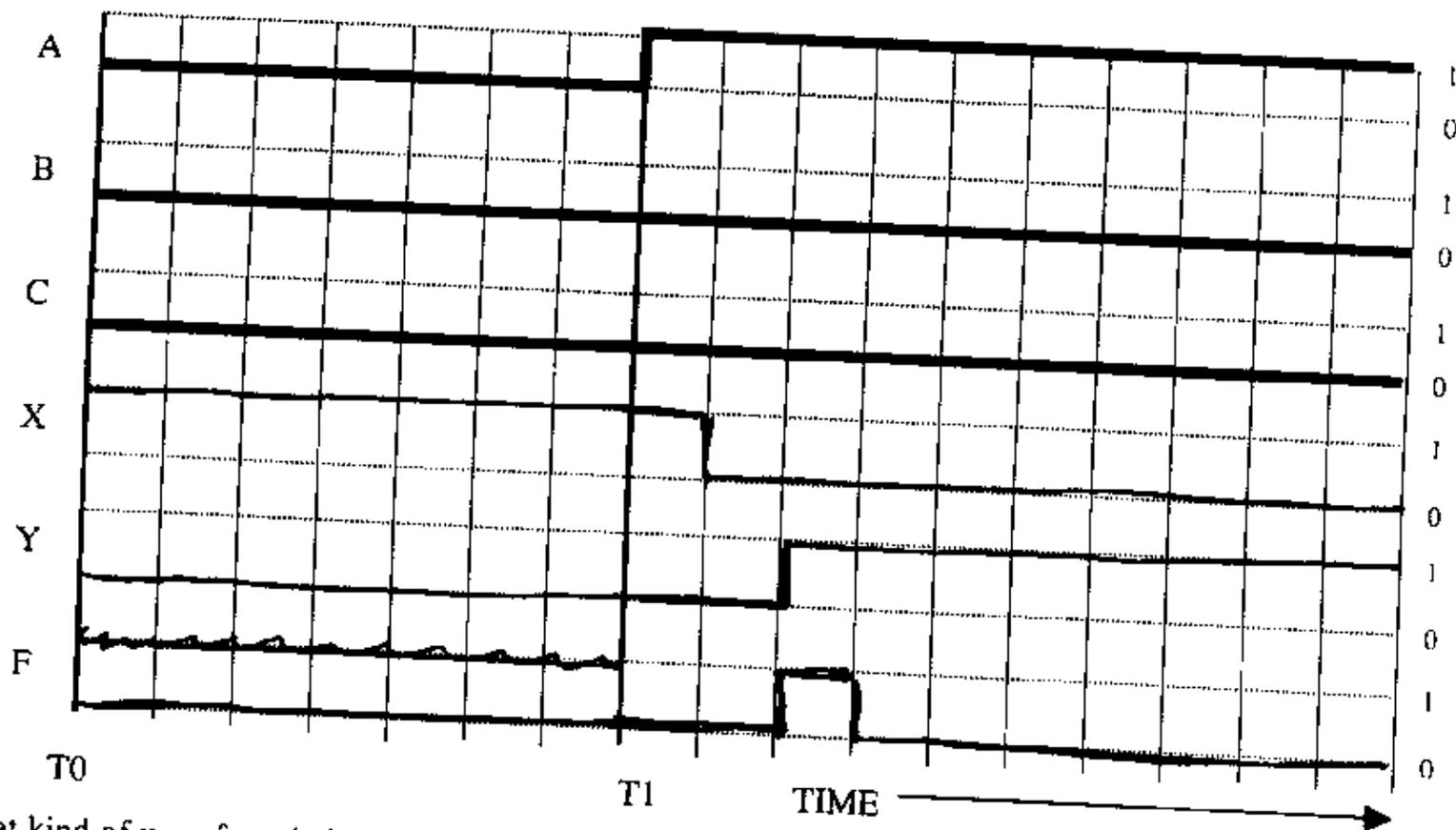(iv) All gates have identical gate delays. Each time division represents a gate delay. Complete the waveform diagram with the time behavior of output F and intermediate nodes X and Y , assuming that the inputs have not changed for quite some time before time T_0 (5 points):



(v) What kind of waveform behavior does F have? Briefly explain why it arises (1 point).

F has a glitch at the output. X and Y are complements, but due to asymmetric arrival times...

Hence the glitch can come about for one gate delay.
 Hence the glitch can come about for one gate delay.

CS 150 Midterm #1

Page 6


29 February 2004 2:00-3:30 PM

Question 6. Design Problem (15 Points)

Consider a subsystem that acts as a "tie detector". The function behaves as follows. If more of the inputs are true than false, the output **MoreOnes** is asserted. If more of the inputs are false than true, then the output **MoreZeros** is asserted. If number of ones and zeros at the inputs are the same, both **MoreOnes** and **MoreZeros** are false (that is, a tie has been detected).

Design a four-input tie detector subsystem.

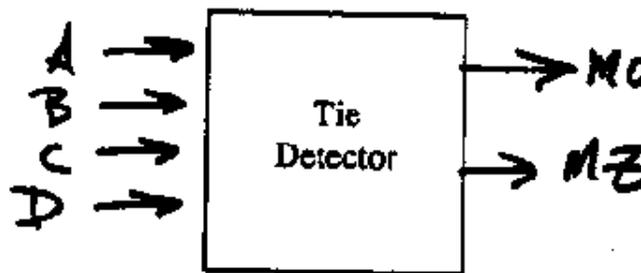(i) Identify your inputs and outputs. Draw a block diagram (2 points):



(ii) State your assumptions about the behavior of the circuit. Document your understanding of the function with a truth table (3 points):

A	B	C	D	MO	MZ
0	0	0	0	0	1
0	0	0	1	0	1
0	0	1	0	0	1
0	0	1	1	0	0
0	1	0	0	0	1
0	1	0	1	0	0
0	1	1	0	0	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	1	0
1	1	0	0	1	0
1	1	0	1	1	0
1	1	1	0	1	0
1	1	1	1	1	0

A	B	C	D	MO	MZ
1	0	0	0	0	1
1	0	0	1	0	0
1	0	1	0	0	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	1	0	0
1	1	1	0	1	0
1	1	1	1	1	0

15
14
10
12
13
55
9
69

