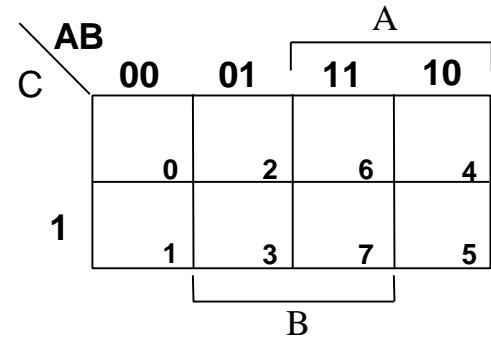


(ii) Implement F using a **single 4-input, 2-control-line multiplexer and a minimum number of two-input logic gates (AND, NAND, XOR, etc.) and inverters only. Show a Karnaugh map.**

2(b) (8pts)

(ii)



(c) **If F were to be implemented as a PLA:**

- (i) **Show the PLA table format for F. Indicate all don't-cares in the product terms (rows) with an asterisk (*) and use the minimum number of rows.**
- (ii) **Would your PLA contain any single-input static hazards, as shown? Why?**

2(c) (10pts)

(i)

(ii)

.....

.....

.....

.....

Additional space for Problem 2

Your Name: _____


(3) (a) Design a **clocked, sequential digital machine** that will output the following sequence of 2-bit values: **00, 01, 11, 10** and then **continuously repeat the sequence from 01** (i.e. never return to 00). **Show a state transition graph.**

(i) **Implement** the machine using **D flip-flops**.

3(a) (i) (10pts)

(ii) **Implement** the machine using **T flip-flops**.

3(a) (ii) (10pts)

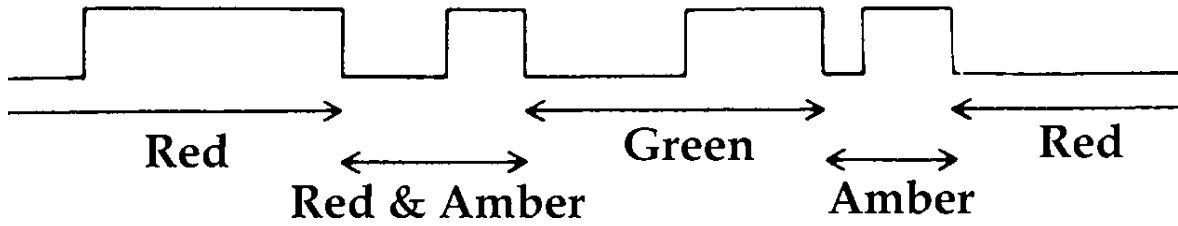

(b) Design a logic system to operate a set of traffic. The individual lights must be on in the following sequence: red, red & amber together, green, amber, red, etc. The lights change from one color (or color combination) whenever a 1→0 transition occurs in the input control signal, as shown above.

3(b) (10pts)

Additional space for Problem 3