

Your Name: _____

UNIVERSITY OF CALIFORNIA AT BERKELEY

BERKELEY • DAVIS • IRVINE • LOS ANGELES • RIVERSIDE • SAN DIEGO • SAN FRANCISCO

Department of Electrical Engineering
and Computer Sciences



SANTA BARBARA • SANTA CRUZ

CS 150 - Spring 1995
Prof. A. R. Newton

(1)	/18
(2)	/20
(3)	/20
(4)	/16
(5)	/26
TOTAL	/100

Final Examination

(Open Katz, asynchronous & test notes only, Calculators OK, 3 hours)

Include all final answers in locations indicated on these pages. Use space provided for all working. If necessary, attach additional sheets by staple at the end. BE SURE TO WRITE YOUR NAME ON EVERY SHEET.

(1) (18pts)

(a) Four chairs are placed in a row:



Each chair may be occupied ("1") or empty ("0"). Write a logic function $F(A,B,C,D)$ which is "1" iff there are **two (or more) adjacent chairs** that are **empty**. Express F:

- (i) As a **Karnaugh Map**.
- (ii) In **minimum Sum-of-Products form** using algebraic notation.
- (iii) In **Standard Sum-of-Products** (minterm) form.
- (iv) In **Standard Product of Sums** (maxterm) form.

1(a) 9pts

(i) $F(A,B,C,D)$ as a Karnaugh Map:

	AB			
	00	01	11	10
CD	00			
	01			
	11			
	10			

(ii) In minimum SoP form, $F(A,B,C,D) =$ _____

(iii) In Standard SoP form, $F(A,B,C,D) =$ _____

(iv) In Standard PoS form, $F(A,B,C,D) =$ _____

(b) How many different combinational logic functions of two variables (X and Y) are there?

1(b) 2pts

Total number. of switching functions: _____

(c) Given that:

$$F(A,B,C,D) = \Sigma m(1,4,5,6,7,9,13,15)$$

Using a Karnaugh Map:

(i) List all of the **essential prime implicants**.

(ii) How many **prime implicants** are there? List them.

(iii) How many **implicants** are there? Just give the number, don't list them.

(iv) Implement the function using a **single 8-to-1 MUX** and **two-input AND gates** only. Assume variables and their complements are available. Be sure to label your MUX inputs.

1(c) 7pts

	AB				
		00	01	11	10
CD	00				
	01				
	11				
	10				

(i) **Essential prime implicants:** _____


(ii) **Prime implicants:** _____

(iii) **Total number of implicants:** _____

(iv) **Implementation:**


Your Name: _____

 (2) (20pts) Consider the clocked J-K flip-flop with asynchronous preset and clear as shown below:



(a) **Complete the following timing diagram** for Q output of the flip-flop. Assume all internal delays are zero and that there are no setup or hold constraints.

2(a) (5pts)

 



(b) Derive the **characteristic equation for the flip-flop**, including the preset (P) and clear (C) inputs as well as J and K. Assume $P=C=0$ will never occur and treat P and C as synchronous inputs for this part of the problem.

2(b) (3pts)

$$Q_{n+1} = \underline{\hspace{10cm}}$$

(c) **Complete the timing diagram** for the circuit shown below. **Note that the CK (clock) inputs on the two flip-flops are different.** Assume all internal delays are zero and that there are no setup and hold constraints.

2(c) (12pts)

  


Additional space for Problem 2

Your Name: _____

(3) (20pts)

 (a) Construct a **state graph** for the circuit shown below (X is the input and Z is the output.)



3(a) (6pts)

Additional space for Problem 3

(b) A sequential network has only one input (X) and one output (Z). Draw a **Mealy state graph** for the case $Z=1$ iff the **total number of 1's received is divisible by 3**. (Note: 0, 3, 6, 9, 12,... are divisible by 3.)

3(b) (6pts)

(c) Draw the **Mealy state graph** for the network of (b) above if the total number of 1's received is divisible by 3 *and* the **total number of 0's received is an even number which is greater than zero**. (9 states are sufficient.)

3(c) (8pts)

Your Name: _____

(4) (16pts)

- (a) Draw the **schematic diagram for a minimal hazard-free realization** (gates + gate inputs) of the following function using **only 3-input NOR gates**. Assume variables and their complements are available.

$$F(A,B,C,D) = \Sigma m(0, 2, 6, 7, 8, 10, 13)$$

4(a) (6pts)



Additional space for Problem 4

(b) For the flow table shown below, **find a state assignment that avoids all critical races**. Additional states may be added as necessary, but use as few state variables as possible. Assign the all-0's combination to state A. If any additional states are needed to prevent critical races, **use your state assignment and adjacency map to explain why**.

		XY			
S_n		00	01	11	10
A		B	C	-	Ⓐ
B		Ⓑ	E	-	Ⓑ
C		F	Ⓒ	-	E
D		Ⓓ	F	-	B
E		D	Ⓔ	-	Ⓔ
F		Ⓕ	Ⓕ	-	A

S_{n+1}

4(b) (10pts)

State assignment:

Adjacency map:

Your Name: _____

(5) (26pts) This problem concerns a base-(-2) (base-(minus-two)) adder. In CS150, we only considered number systems with positive bases (in particular, the binary, or base-2, system). For example, in a base-3 system, the number $ABCD_3$ is equal to:

$$ABCD_3 = A \cdot 3^3 + B \cdot 3^2 + C \cdot 3^1 + D \cdot 3^0.$$

So for a base-(-2) system, $EFGH_2$ would be computed using:

$$EFGH_2 = E \cdot (-2)^3 + F \cdot (-2)^2 + G \cdot (-2)^1 + H \cdot (-2)^0$$

(a) Convert the following decimal numbers to base-(-2). Use as many bits as you need.

5(a) (8pts)

$5_{10} = \text{_____}_{-2}$

$6_{10} = \text{_____}_{-2}$

$-7_{10} = \text{_____}_{-2}$

$11_{10} = \text{_____}_{-2}$

(b) For the purpose of this problem, we define a number system as *contiguous* if, given any two integer values m and n which can be represented in the number system, there exists no integer value x , with $m < x < n$, that cannot be represented in the system. For example, a 1-bit decimal system is contiguous. It can represent the counting numbers 0-9, and there are no numbers in between 0 and 9 which cannot be represented using one decimal digit. The binary number system (base 2) is also contiguous.

(i) Is a four-bit base-(-2) system contiguous?

(ii) What are the maximum and minimum values (in decimal) that can be represented by a four-bit base-(-2) system?

(iii) Is an n -bit base-(-2) system contiguous, where n is any positive integer? Justify your answer.

5(b) (6pts)

(i) _____

(ii) **Maximum**₁₀ = _____ **Minimum**₁₀ = _____

(iii) _____

(c) Add the following numbers in base-(-2). Pay close attention to the carry-in and carry-out aspects because they are important in Part (d)

5(c) (2pts)

$$001110_{-2} + 001111_{-2} = \underline{\hspace{2cm}}_{-2}$$

(d) Draw a truth table for a one-bit bit slice of a base-(-2) adder. Assume one bit of carry-in. You must determine the specification for the carry-out.

5(d) (3pts)

(e) Repeat part (d) above but with two carry-in bits.

5(e) (3pts)

Your Name: _____

(f) Draw the block-diagram for a 4-bit base-(-2) adder, using your one-bit bit slice from 5(e) above.

5(f) (4pts)



Additional space for Problem 5

Additional Space for Working Problems