

NEATSELL THW'S

TO POST

Professor Oldham

Spring 2001

EECS 42 — MIDTERM #2

5 April 2001

Name: _____
Last, First

Student ID: _____



Signature: _____

Guidelines:


1. Closed book. A 3-page summary with formulas is provided at the end of the exam.
2. Show *all your work and reasoning on the exam* in order to receive credit.
3. **Warning:** Some problems will be graded with no partial credit, so check your answers.
4. You may use a calculator.
5. Do not unstaple the exam.
6. This exam contains 5 problems worth 20 points each, and corresponding worksheets plus the cover page and the 3-page summary with formulas.
7. **Please do not ask questions** except to point out possible errors or typographical mistakes.

Problem	Points Possible	Your Score
1	20	
2	20	
3	20	
4	20	
5	20	
Total	100	



Problem 1 Answer Sheet

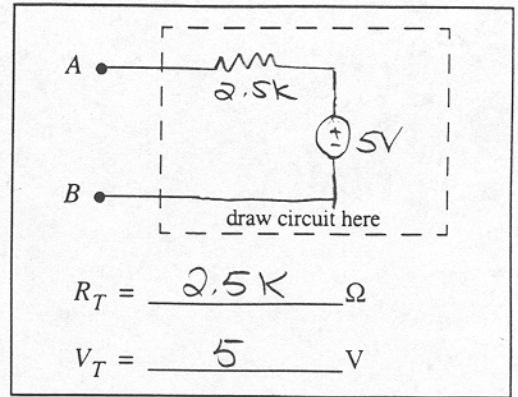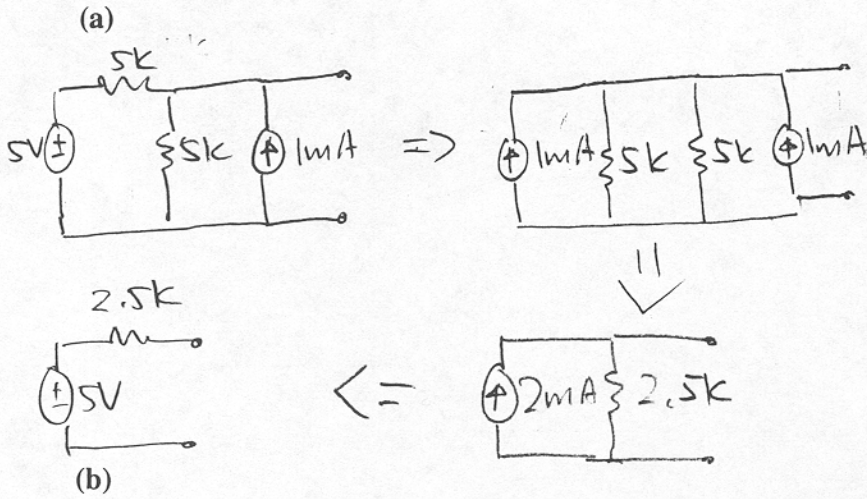

R_T : open 2mA short 2V

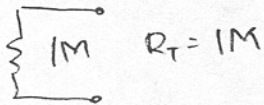


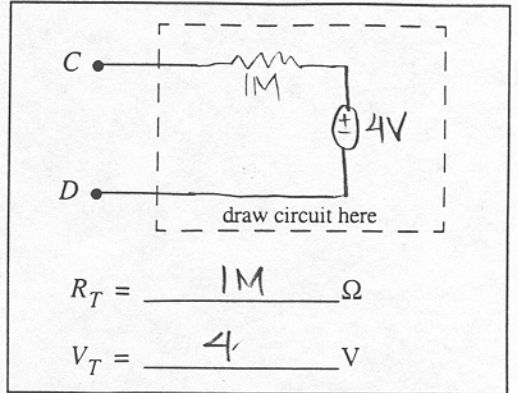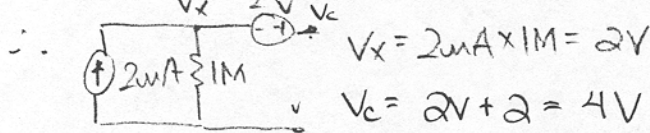$V_T = V_{oc}$: all of 2mA flows through 1M res.




(c)

R_T : open 1mA and short 2V

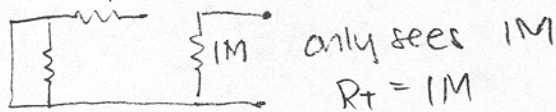


$V_T = V_{oc}$: all of 1mA flows through 1M

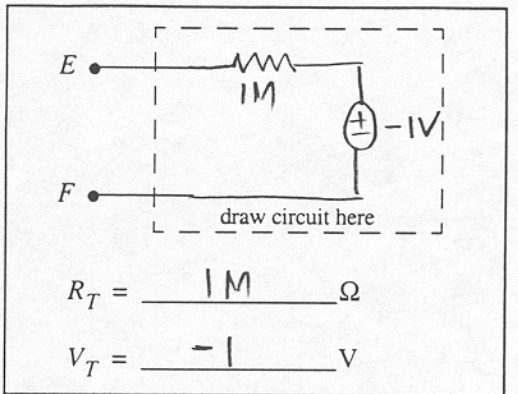$\therefore \frac{V_F - V_E}{1M} = 1mA \Rightarrow V_{EF} = -1mA \times 1M = -1V$





(d)

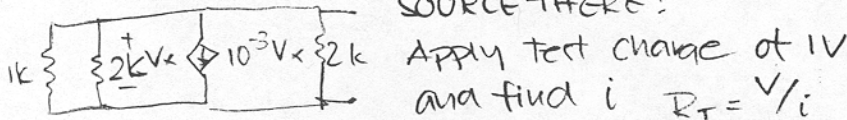R_T : open 2V KEEP DEPENDENT CURRENT SOURCE THERE!



$V_{test} = 1 \Rightarrow V_x = 1$

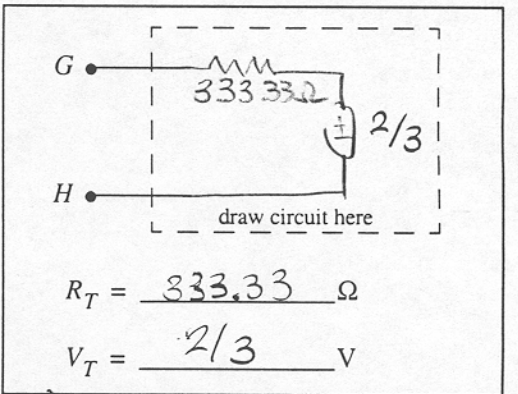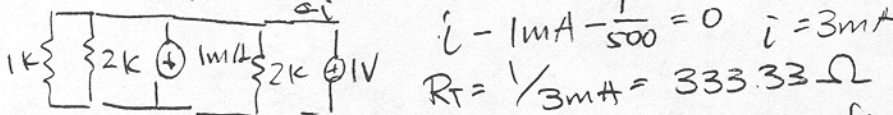






$V_T = V_{oc} = V_x$: write nodal equation to find V_x

$(2 - V_x)/1k + -V_x/2k - 10^{-3} V_x - V_x/2k = 0 \Rightarrow V_x = \frac{2}{3} V$

Problem 2 (20 points)

As you know, sometimes two quite different circuits are equivalent. Consider the five following circuits. Indicate by circling which circuits are equivalent to each other.

NOTE: Do not guess; you MUST actually demonstrate that the circuits are equivalent. If you do not show the basis for your assertions of equivalence, you cannot receive credit. (Please do not ask a question of how to demonstrate equivalence—you are responsible for knowing that.) The grading will reward for correct answers with appropriate basis for the choices and will subtract for wrong answers.

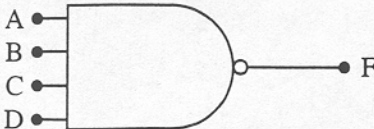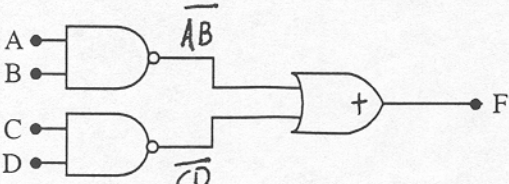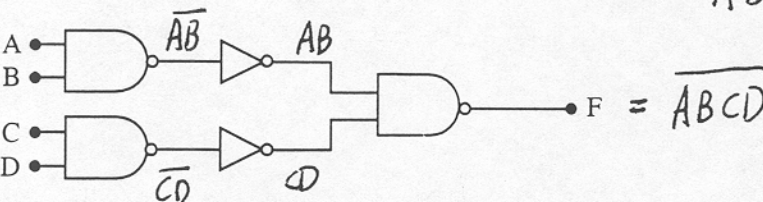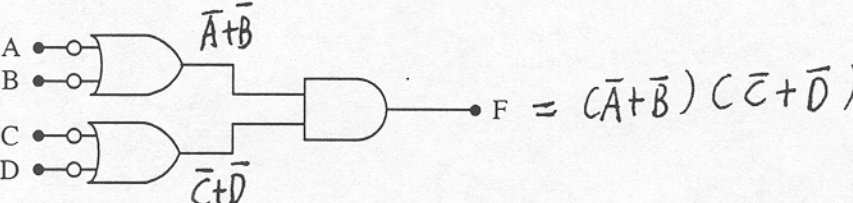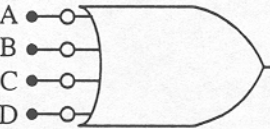- (a)  $F = \overline{ABCD}$
- (b)  $F = \overline{AB} + \overline{CD}$
 $= \overline{A+B} + \overline{C+D}$ DeMorgan's rule
 $= \overline{ABCD}$ DeMorgan's rule
- (c)  $F = \overline{ABCD}$
- (d)  $F = (\overline{A+B})(\overline{C+D})$
- (e)  $F = \overline{A+B+C+D}$
 $= \overline{ABCD}$ DeMorgan's rule

Problem 2 Worksheet

This problem ~~is~~ actually ~~has not~~ to be done by truth table. As shown, by applying DeMorgan's, we can find that a, b, c, e are equivalent. To test if d is equivalent

to the other four. We can try one (or two) test assignments (counterexamples).

A	B	C	D	\overline{ABCD}	$(\overline{A+B})(\overline{C+D})$
0	0	1	1	1	0

So, only a, b, c, e are equivalent

However, since most people used truth tables, I will also show full truth table comparison for d and other four.

A	B	C	D	(d) $(\overline{A+B})(\overline{C+D})$	(a,b,c,e) \overline{ABCD}
0	0	0	0	1	1
0	0	0	1	1	1
0	0	1	0	1	1
0	0	1	1	0	1
0	1	0	0	1	1
0	1	0	1	1	1
0	1	1	0	1	1
0	1	1	1	0	1
1	0	0	0	1	1
1	0	0	1	1	1
1	0	1	0	1	1
1	0	1	1	0	1
1	1	0	0	0	1
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	0	0

0 when A, B are both 1, or C, D are both 1.

only 0 when A, B, C, D are all 0.

Problem 3 Answer- and Worksheet

(a)

A	B	C	W	X	Y	Z	F
0	0	0	1	1	1	0	0
0	0	1	1	0	1	1	1
0	1	0	1	0	0	1	0
0	1	1	1	0	0	1	0
1	0	0	1	1	1	0	0
1	0	1	1	0	1	1	1
1	1	0	0	0	0	1	0
1	1	1	0	0	0	1	0

← $\bar{A}\bar{B}C$

← $A\bar{B}C$

SEE LECT 17 & 18 NOTES
OR TEXT BOOK
KEY IDEAS

(b)

FROM TRUTH TABLE:

$$F = \bar{A}\bar{B}C + A\bar{B}C$$


BUT $\bar{A}(\bar{B}C) + A(\bar{B}C) = (A + \bar{A})\bar{B}C$

↑
1


(c)

$$F = \bar{B}C$$


(d)

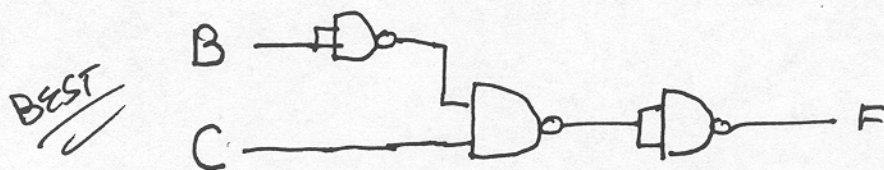

(OR)

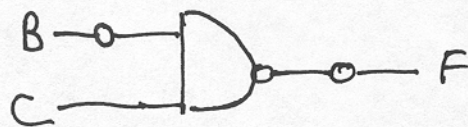


OR, IF UNSIMPLIFIED:

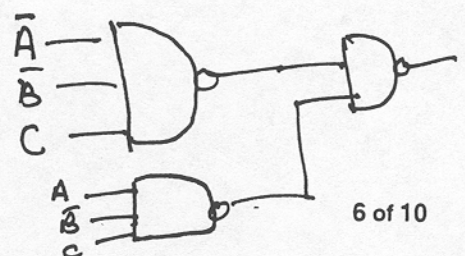

Problem 4 (20 points)

(a) Consider the circuit below:

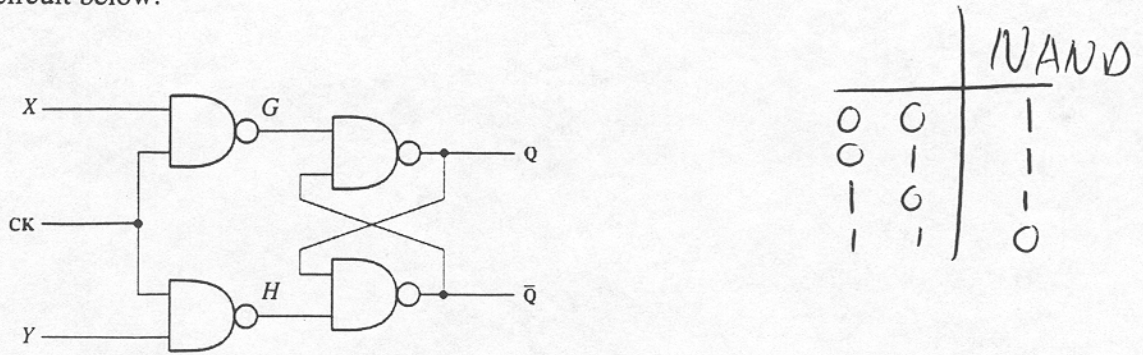


Fill in the value for Q in the timing diagram opposite. But to show your work, you must also show values for G and H . Note that the initial value of Q is 0, as shown by heavy dark line on the timing diagram. Ignore stage delay.

Find G by looking at X and CK , $G = X \text{ NAND } CK$

Find H by looking at Y and CK , $H = Y \text{ NAND } CK$

Find Q by analyzing the right two flip flops. It is similar to an SR Flip Flop

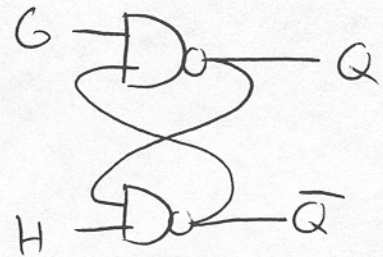(b) For the same circuit, fill in the table, opposite.




(not G) \setminus G = set

(not H) \setminus H = reset

$G = H = 1$; Hold

Problem 4 Answer Sheet

(a)

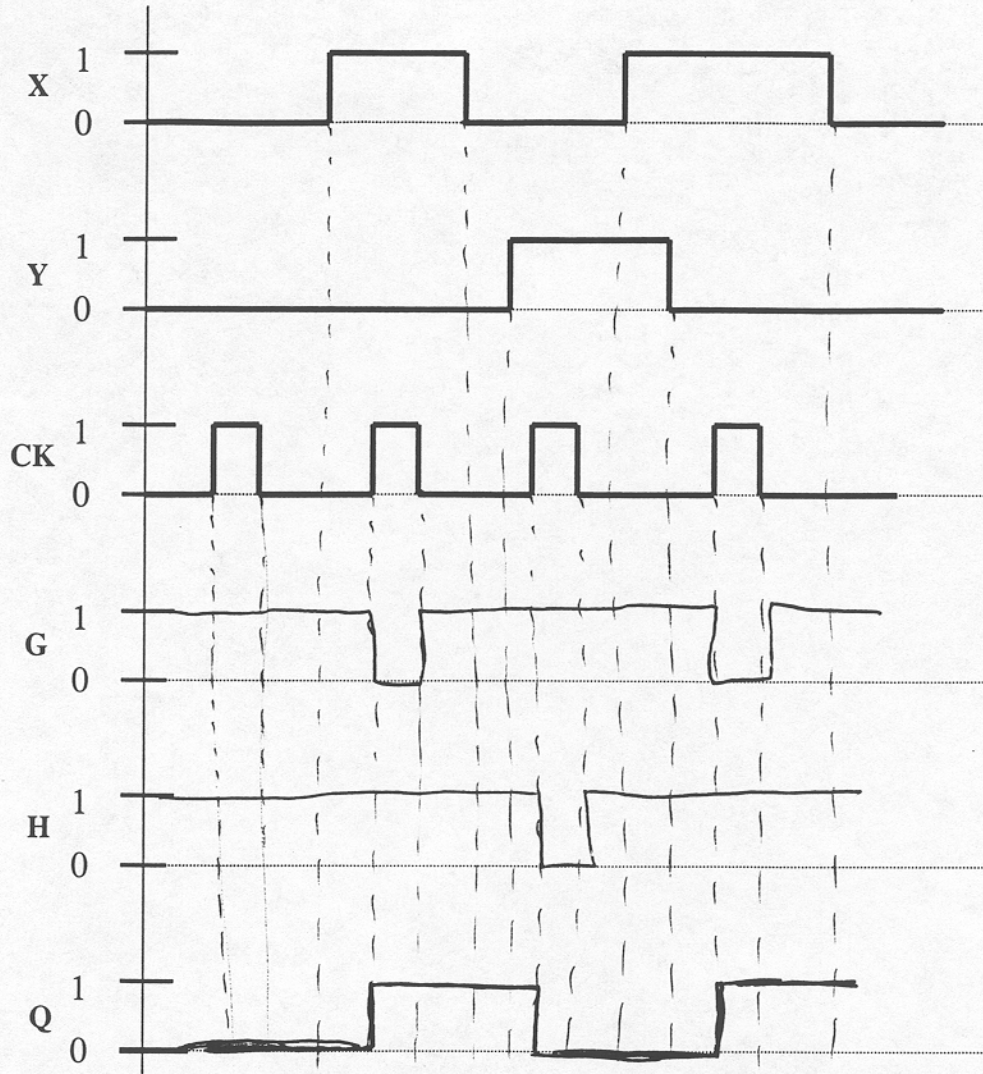


(b) The table below is intended to show the value of Q after CK goes high. Fill in the “Q” column with 0 or 1 or “ Q_{old} ”.

X	Y	Q (after CK=1)
0	0	Q_{old}
0	1	0
1	0	1

Problem 5 Worksheet and Answersheet

(a)

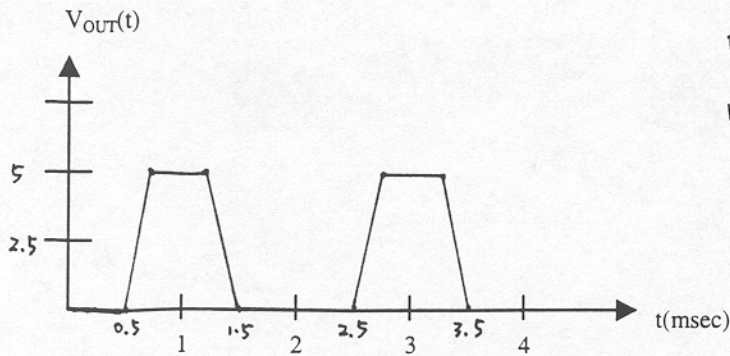

(a). In the linear Range, $V_{out} = 5 V_{in}$
 But high rail is 5V and Low rail is 0V. So for V_{out} ,

$$V_{out} = \begin{cases} 5V, & (5 V_{in} > 5) \\ 5 V_{in} & (0 < V_{in} < 1) \\ 0 & (V_{in} < 0) \end{cases}$$


(b). Since $V_{in}(t < 0)$ is not clearly specified. We give full credit for next two cases: either $V_{in} = 0$ for $t < 0$ or $V_{in} = 2$ for $t < 0$;

V_x follows V_{in} , but limited by the high/Low rail;

V_{out} will show transient because of the RC circuit.

$\tau = R \cdot C = 0.5 \mu\text{Sec}.$


(b)

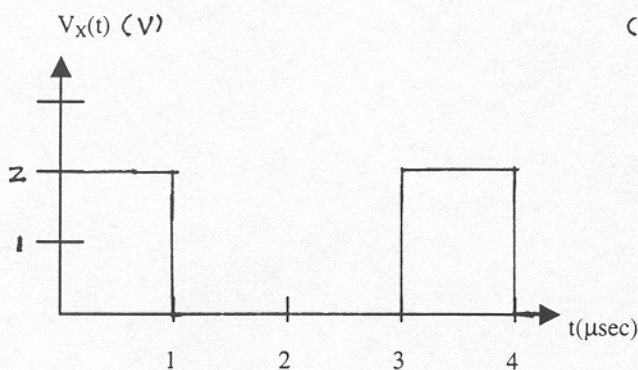

(i) $V_{in} = 2V$ for $t < 0$

(ii) $V_{in} = 0V$ for $t < 0$

(i)

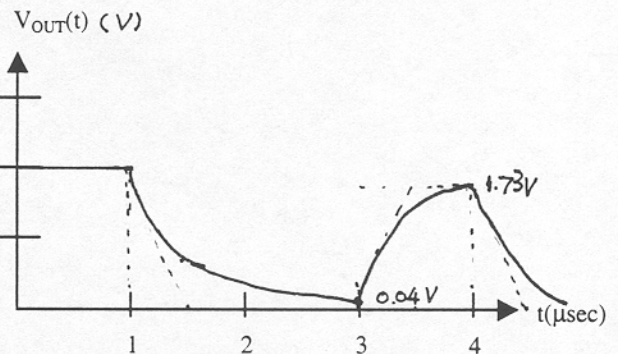

(ii)

