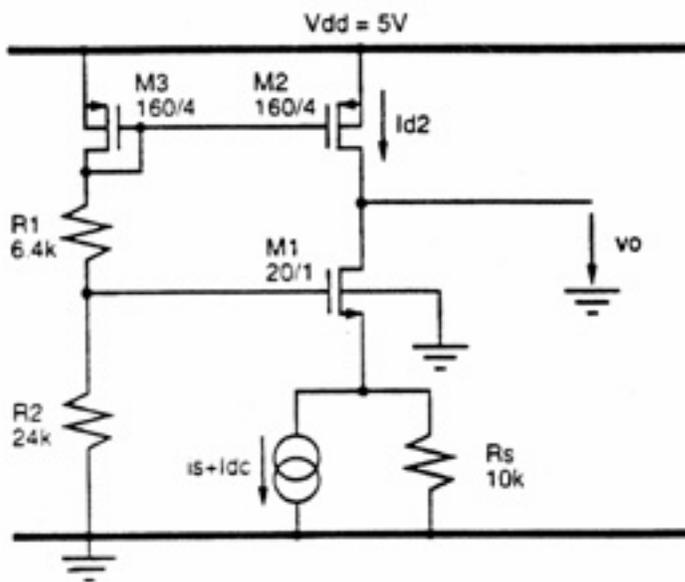


## EE 140, Spring 1995 Midterm 1 Prof. Boser

### Problem #1

In the amplifier shown below the dc bias  $I_{dc}$  is adjusted such that all devices operate in the forward active region.

- Find  $I_{d2}$ , the drain current in M2.
- Find the transresistance  $R_x = v_o/i_s$ . Don't neglect the body effect and beware that  $\lambda$  depends on channel length.
- What are the minimum and maximum output voltages that keep all devices in saturation?



### Problem #2

Assume that the all npn reference shown below has a stable operating point without startup problem and that all devices are in the forward active region. Neglect base currents and device output impedance.


(a) Find  $I_o$  at 300K.

Hint: find a loop around which all voltages sum to zero.

(b) Find the value of the fractional temperature coefficient(TCF) of  $I_o$ .

(c) What type of reference is this? (e.g. band-gap,  $V_t$ -referenced, etc).

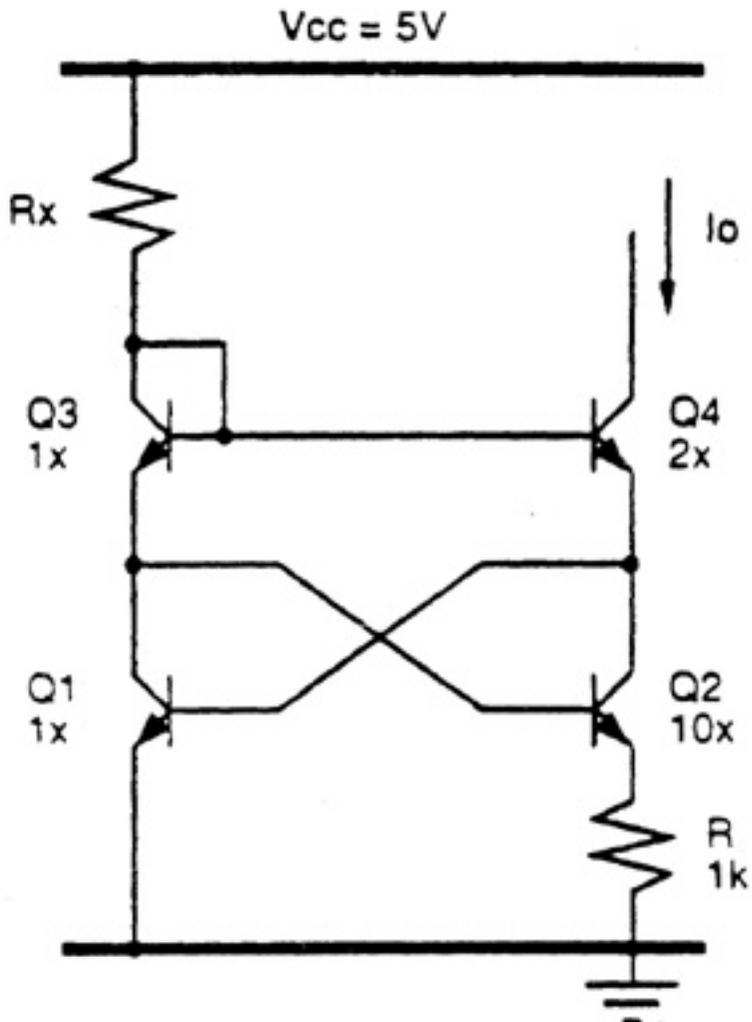
(d) What is the minimum voltage required at the output to keep Q4 forward active?



### Problem #3

Shown below is a simplified schematic of the input stage of an operational amplifier. Notice that Q1 and Q2 are not an emitter coupled pair.

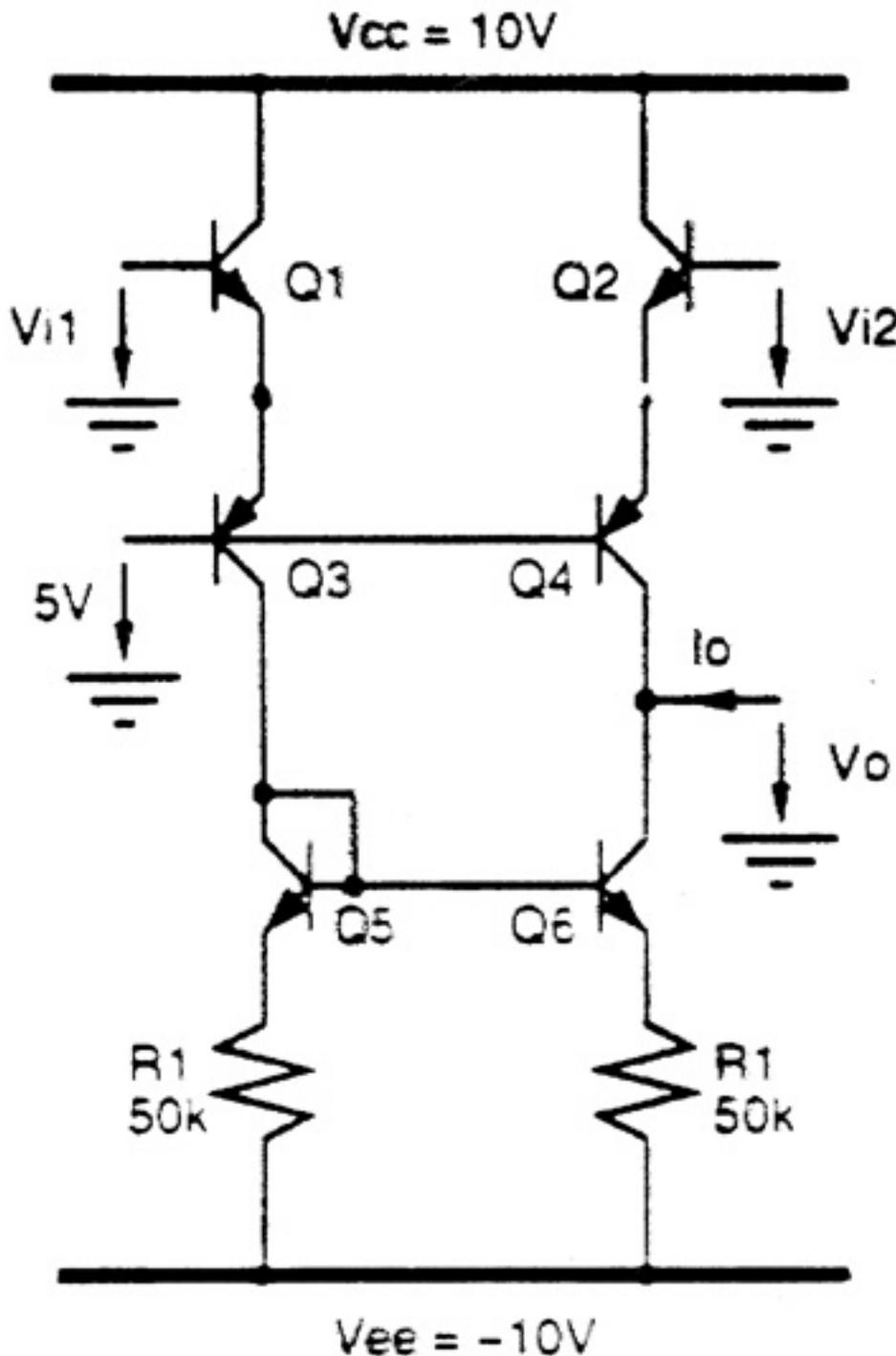- (a) Find the input common-mode voltage  $v_{ic} = (v_{i1} + v_{i2})/2$  for which  $I_{c1} = I_{c2} = 10$  microAmps. For this condition (i.e.  $I_{c1} = I_{c2} = 10$  microAmps),
- (b) Find the differential transconductance  $G_m = i_o/v_{id}$  ( $v_{id} = v_{i1} - v_{i2}$ ), output impedance  $R_o = v_o / i_o$ , and the differential voltage gain  $v_o/v_{id}$  of the circuit.
- (c) What are the minimum and maximum values of  $V_o$  for which all devices remain in the forward active region?



**Posted by HKN (Electrical Engineering and Computer Science Honor Society)  
University of California at Berkeley**

**If you have any questions about these online exams  
please contact <mailto:examfile@hkn.eecs.berkeley.edu>**