

EE 140, Spring 1994 Final Exam Professor ?

BJT Parameters

$$I_S = 1 \times 10^{-14} \text{ A}$$

$$C_\pi = 1 \text{ pf}$$

$$C_\mu = .1 \text{ pf}$$

$$C_{CS,nPn} = 1 \text{ pf}$$

$$C_{CS,pnP} = 0 \text{ pf}$$

$$V_{A,nPn} = V_{A,pnP} = 50 V_0$$

$$\beta_{nPn} = \beta_{pnP} = 100$$

$$V_{CE(SAT)} = .2$$

MOS

$$V_{T,n} = 1 V_0$$

$$V_{T,p} = -1 V_0$$

$$k'_n = k'_p = 50 \mu\text{A}/\text{V}^2$$

$$\lambda_n = \lambda_p = .05$$

$$\gamma_n = \gamma_p = .3$$


$$C_\pi = 1 \text{ pf}$$

$$C_\mu = .1 \text{ pf}$$

$$C_{SB} = 1 \text{ pf}$$


$$C_{DB} = 1 \text{ pf}$$

$$2\phi_f = .6 V_0$$

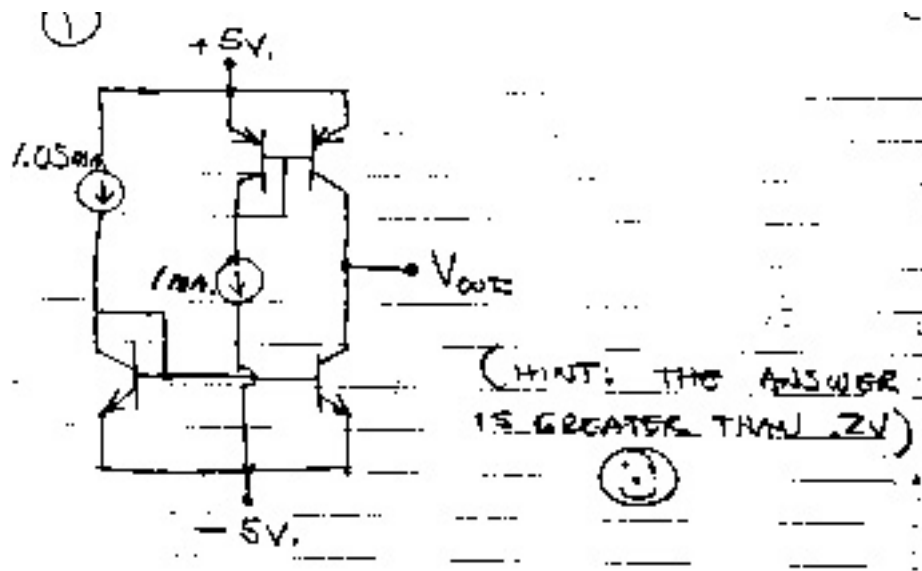


(1) What is the DC voltage at V_{OUT} ?

$V_{OUT} = \text{_____} V_0$

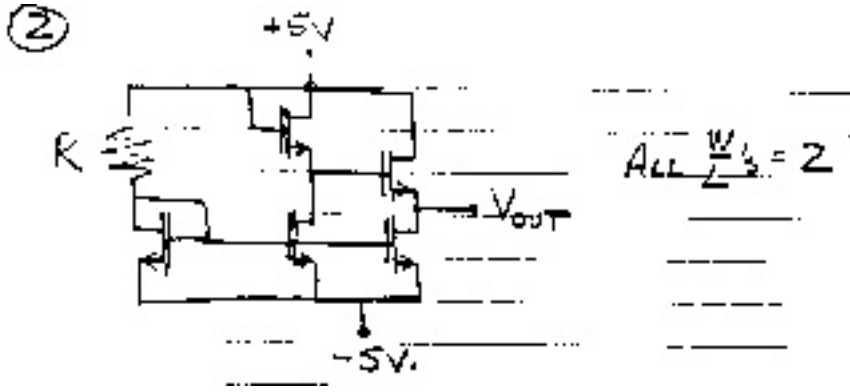


(2) What is the value of R so that $V_{OUT} = 1 V_0$?

$R = \text{_____} \Omega$

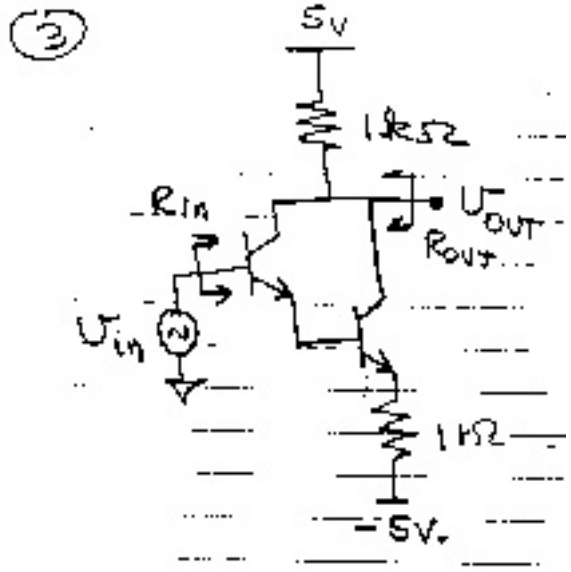


(3a) What is V_{OUT}/V_{IN} ? _____

(3b) What is R_{OUT} ? _____

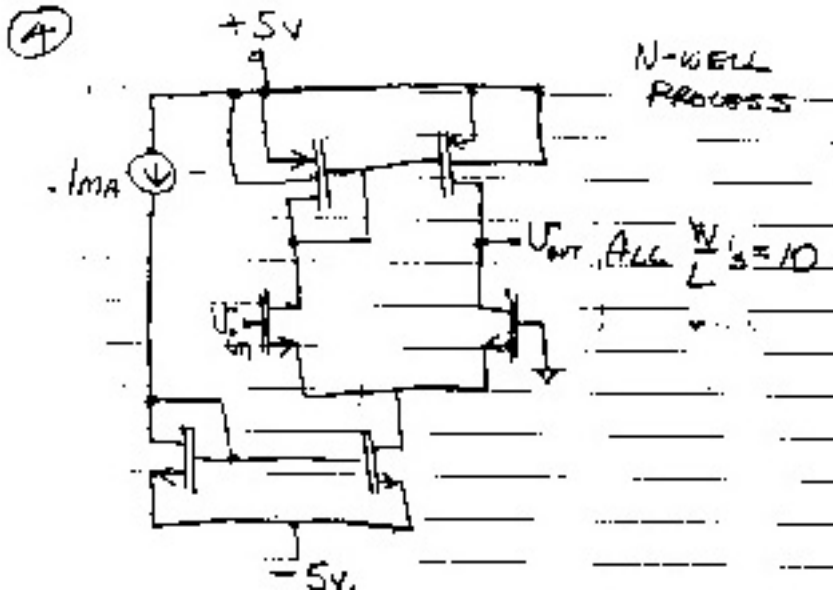


(4) What is V_{OUT}/V_{IN} ? _____

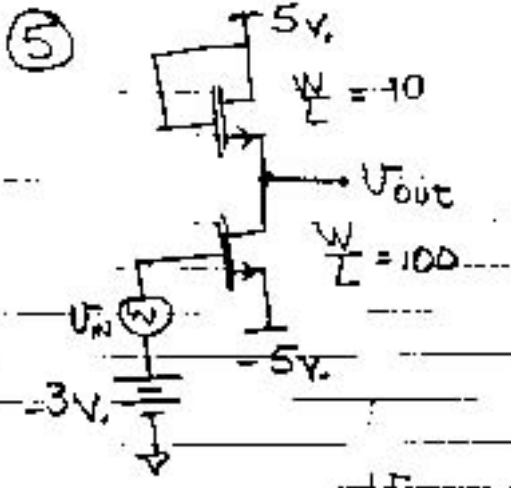


(5a) What is V_{OUT}/V_{IN} ? _____

(5b) What is the lowest frequency pole ω_{pi} _____ rad/sec

(6)

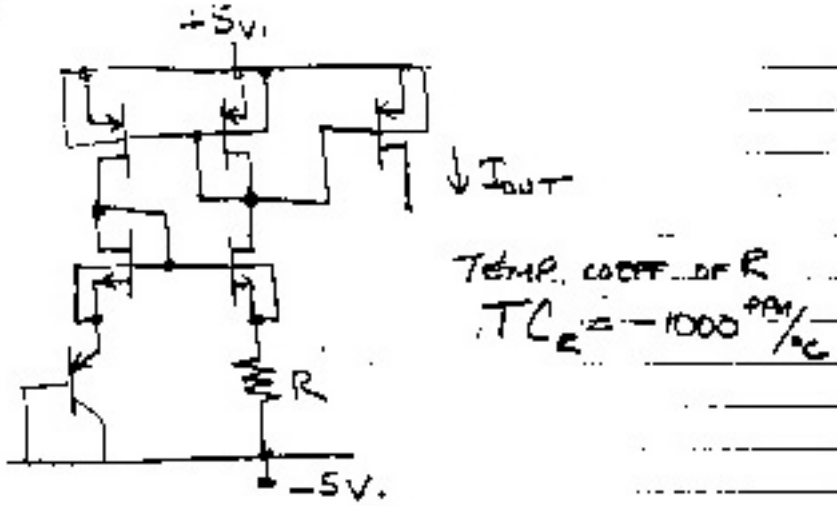

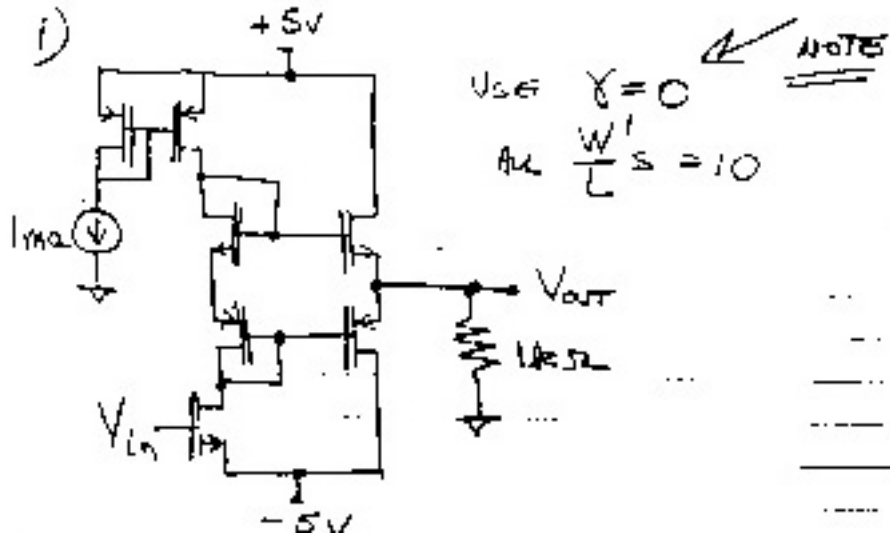(6a) What is the value of R for an output current of .1 mA? _____ Ω




(7a) If V_{IN} is set so that $V_{OUT} = 0 V_0$, what is the power dissipation of this circuit?


pwr = _____ mW

(7b) If $V_{OUT} = 3V_0$, what is the power dissipation for everything except the resistor? _____ mW

8)

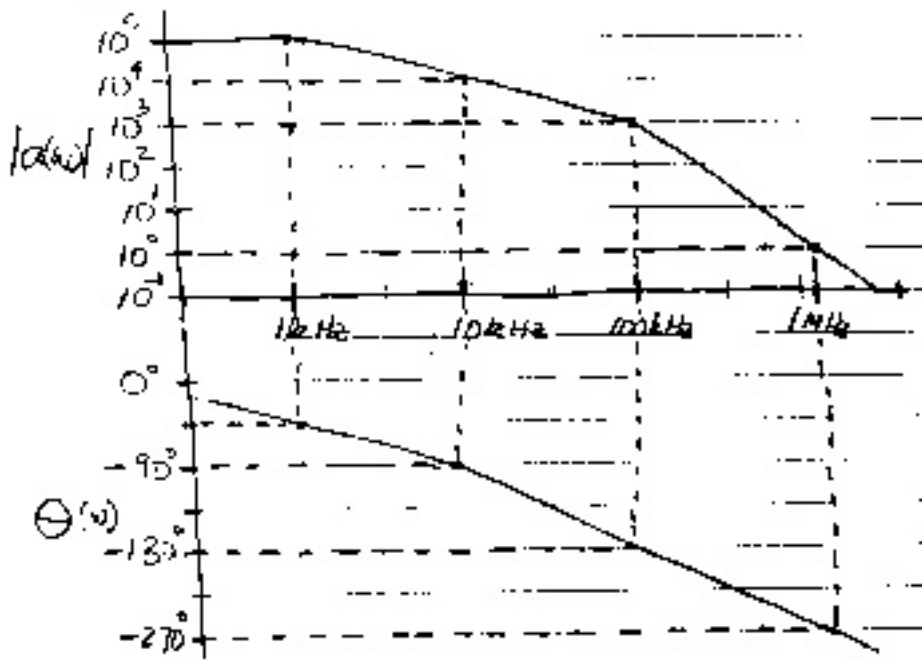

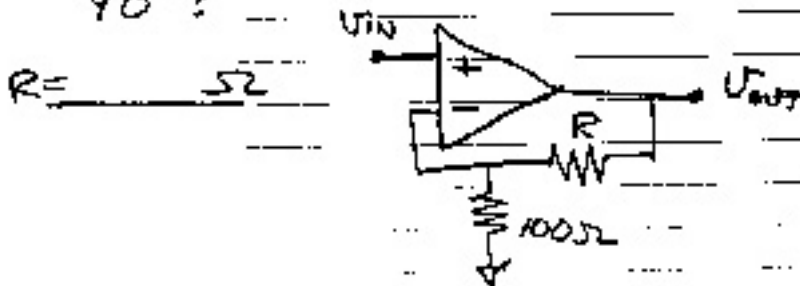
If the above Bode plots are for the op-amp in the following circuit, what is the value of R that will give a phase margin of 90° ?



(8) If the above Bode plots are for the op-amp in the following circuit, what is the value of R that will give a phase margin of 90° ?

$R = \underline{\hspace{2cm}} \Omega$


9)

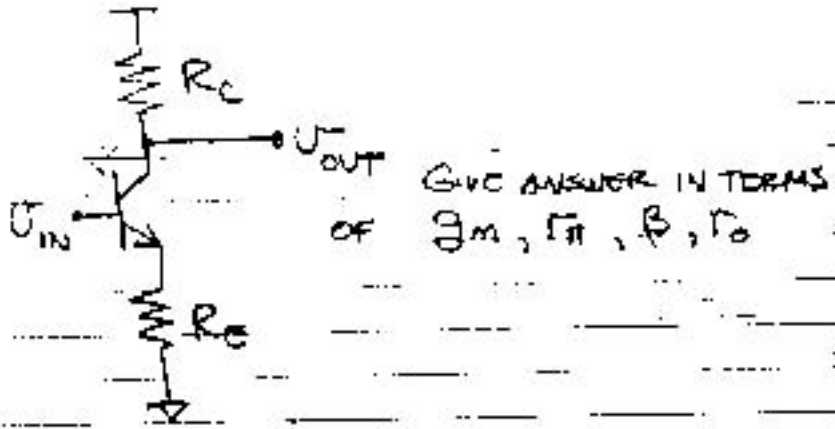

(9a) What kind of local feedback is being used in this circuit? _____


(9b) What is the loop gain, T , of this circuit? _____

10)

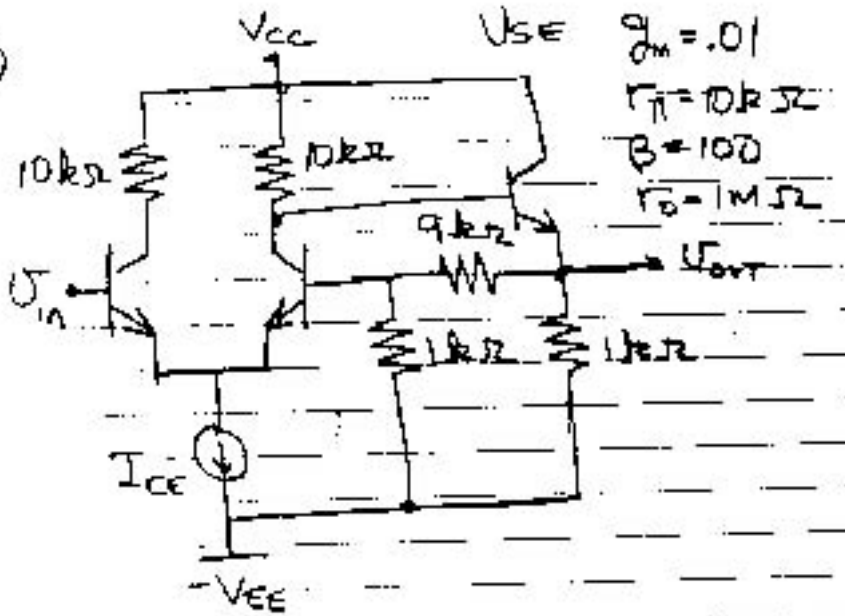

(10a) What is the loop gain of this circuit? $T =$ _____

(10b) What is V_{OUT}/V_{IN} ? _____

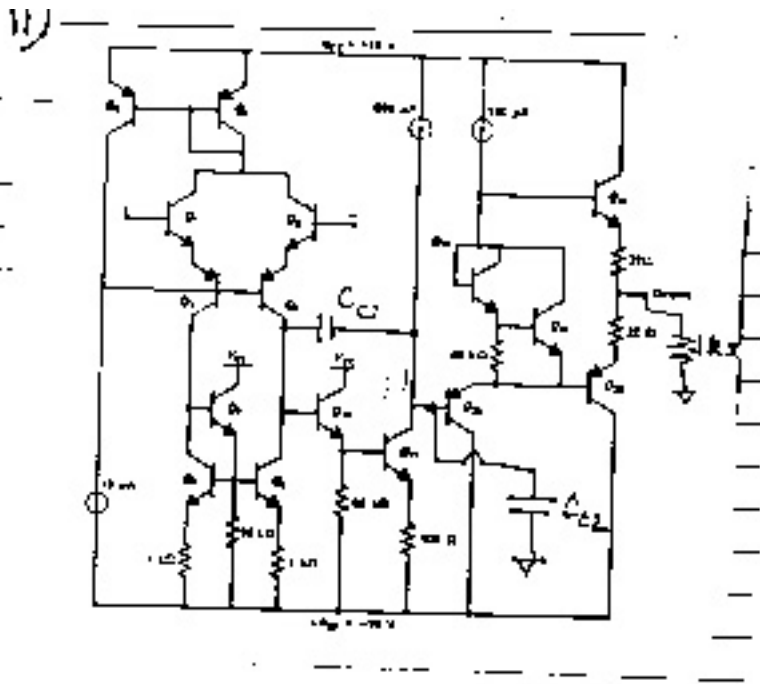

Assume the input is set so the output is at $-5V_0$

(11a) If $C_{C1} = 20$ pf and $C_{C2} = 0$ pf, what is the slew rate of this circuit? _____ V/ μ sec

(11b) At what frequency is the dominant pole if $C_{C1} = 20$ pf and $C_{C2} = 0$ pf? _____ rad/sec

(11c) For $C_{C1} = 10$ pf, what is the value of C_{C2} for 45° of phase margin if the poles and zeros of this circuit not associated with C_{C2} are at:

$$f_{p1} = 1 \text{ MHz}$$

$$f_{p2} = 1 \text{ MHz}$$

$$f_{p3} = 10 \text{ MHz}$$


$$f_{p4} = 100 \text{ MHz}$$

$$f_{z1} = 1.0 \text{ MHz}$$

$$f_{z2} = 50 \text{ MHz}$$

Assume that these poles do not move as the pole associated with C_{C2} is moved. Also assume the open loop gain, $A_0 = 10^5$.

(i.e. do not calculate the gain)

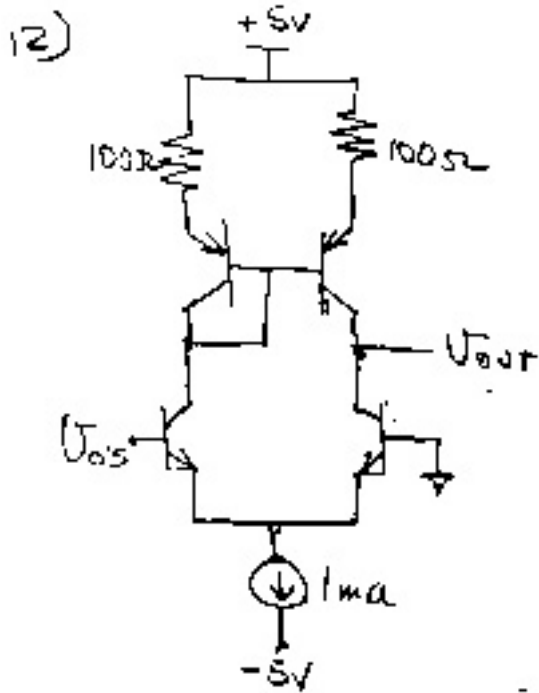

What is the input offset voltage, V_{OS} , that sets $V_{OUT} = 0V_0$

$V_{OS} = \underline{\hspace{2cm}} V$

**Posted by HKN (Electrical Engineering and Computer Science Honor Society)
University of California at Berkeley**
If you have any questions about these online exams
please contact <mailto:examfile@hkn.eecs.berkeley.edu>