

NAME SOLUTIONS

MIDTERM EECS 140

FALL, 1997

R.W. BRODERSEN

* WRITE ANSWERS BELOW

* USE APPROXIMATIONS SO YOUR ANSWER IS WITHIN $\pm 10\%$ OF THE EXACT SOLUTION

1 a) 5

b) 2.75V.

c) .6V.

2 a) 2M Ω


b) 5m Ω

3 a) 390k Ω

b) 7x10⁹ Ω

4 a) 6V.

b) ~~max~~ .04

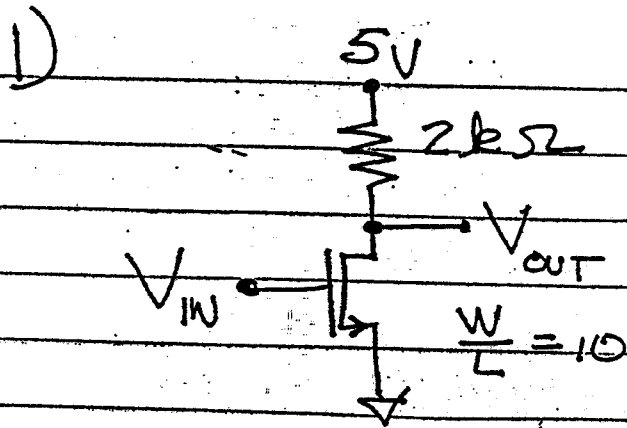

a) IF $V_{IN} = 0V$, WHAT IS V_{OUT} ?
 $V_{OUT} = 5V$

TRANSISTOR CUTOFF, $I_{DS} = 0$

b) IF $V_{IN} = 2.5V$, WHAT IS V_{OUT} ? $V_{OUT} = 2.75$
 (SATURATION)

$$I_{DS} = \frac{k}{2} \frac{W}{L} (V_{GS} - V_T)^2 = \frac{10}{2} \cdot 10 (1.5)^2$$

$$V_{OUT} = 5 - 2k\Omega \cdot I_{DS} = 5 - 2.25 = 2.75V$$


c) IF $V_{IN} = 5.0V$, $V_{OUT} = .56$
 (LINEAR)

$$I_{DS} = k' \frac{W}{L} (V_{GS} - V_T) V_{DS} = 10^{-3} (4.0) V_{OUT}$$

$$V_{OUT} = 5 - 2k I_{DS} = 5 - 8V_{OUT}$$

$$V_{OUT} = 5/9 \text{ VOLT} = .56V$$

2)

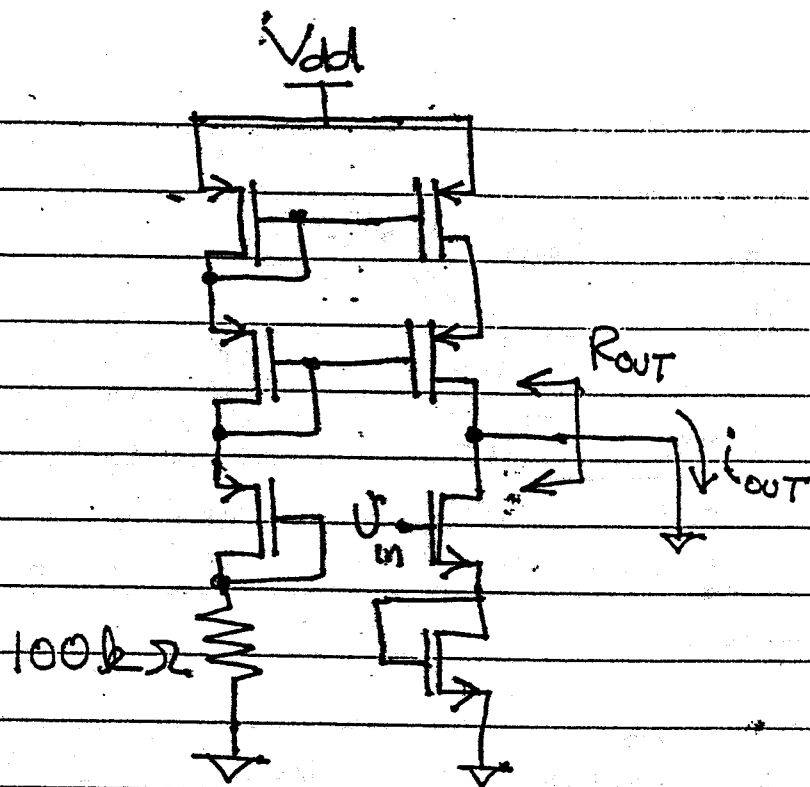

USE THESE SMALL
SIGNAL VALUES
FOR ALL THE
TRANSISTORS

↓

$$g_m = 10 \text{ mS}$$

$$r_o = 1 \text{ M}\Omega$$

$$g_{mb} = 0.25$$


a) WHAT IS R_{OUT} ? $R_{OUT} = 2 \text{ M}\Omega$

$$R_{OUT} = g_m r_o^2 \parallel r_o \left[1 + g_m \frac{1}{g_m} \right] \approx 2 r_o$$

b) WHAT IS $G_m (= \frac{i_{OUT}}{v_{in}}) = 5 \text{ mS}$

$$G_m = \frac{g_m}{1 + g_m \left(\frac{1}{g_m} \right)} = \frac{g_m}{2} = 5 \text{ mS}$$

3)

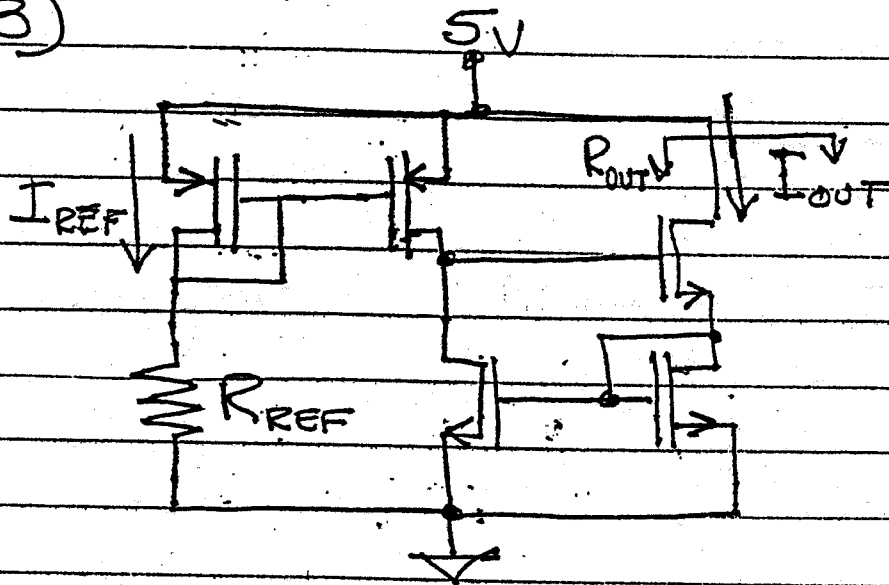

$A_{W/L} = 10$

$k'_n = k'_p = 100 \mu A/V^2$
 $\lambda_n = \lambda_p = .01$
 $V_{TN} = V_{TP} = 1V$
 $r_n = r_p = 0$

a) WHAT IS R_{REF} SO THAT $I_{OUT} = 10 \mu A$?
 $R_{REF} \quad \Omega$

$$R_{REF} = \frac{5 - V_T - V_{DSAT}}{I_{DS}} = \frac{5 - 1 - \left(\frac{2 I_{DS}}{k' W/L}\right)}{10^{-5}}$$

$$= \frac{5 - 1 - .14}{10^{-5}} = 390 k\Omega$$

b) WHAT IS R_{OUT} ? $\cdot 7 \times 10^9 \Omega$


$$R_{OUT} = \frac{g_m r_o^2}{2} = 7 \times 10^9 \Omega$$

$$g_m = \left(2 k' \frac{W}{L} I_{DS}\right)^{1/2} = \left(2 \times 10^{-3} \times 10^{-5}\right)^{1/2}$$

$$= .14 mS$$

$$r_o = \frac{1}{10 \cdot 10^{-5}} = 10 M\Omega$$

4)

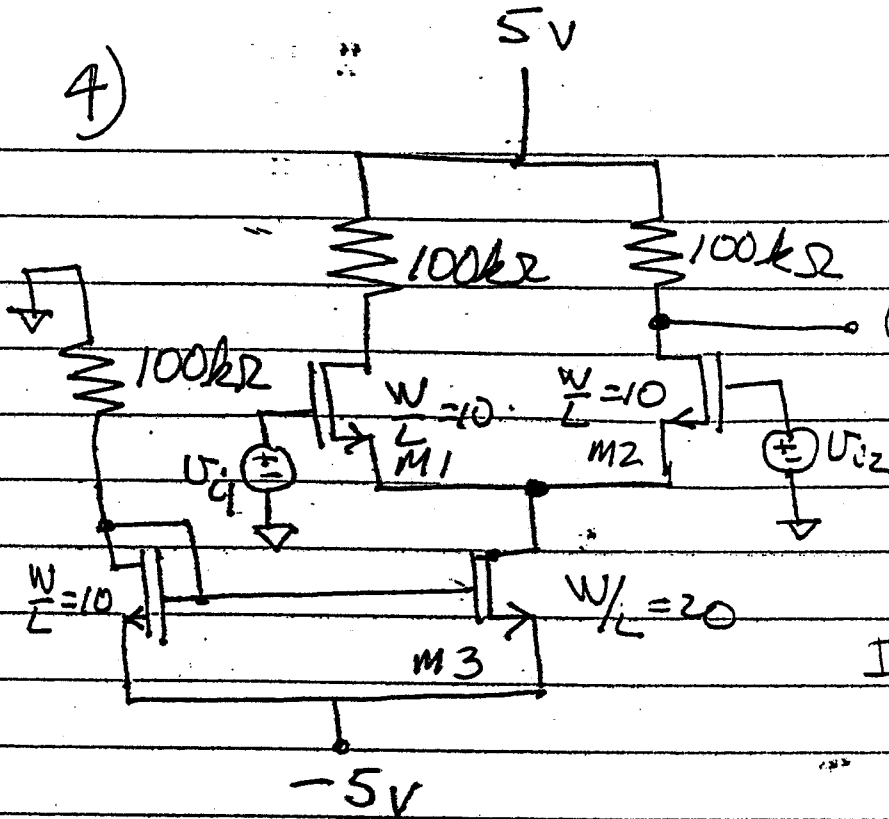

$$k' = 100 \frac{\mu A}{V^2}$$

$$\lambda = .01$$

$$V_T = 1V$$

$$\gamma = 0$$

$$I_{DS} \approx \frac{5 - 1}{10^5} = 40 \mu A$$

a) WHAT IS THE SIGNAL SWING AT U_{OUT} ($U_{max} - U_{min}$) 6V
 +5 IN THE POSITIVE DIRECTION
 - V_T IN THE NEGATIVE = -1V

b) WHAT IS $\frac{U_{OUT}}{U_{in}}$? MAXIMUM .04

$$g_m = \left(2k' \frac{W}{L} I_{DS} \right)^{1/2} = \left(2 \cdot 40 \times 10^{-6} \times 10 \times 10^{-4} \right)^{1/2}$$

$$= \left(8 \times 10^{-8} \right)^{1/2} = .28 mS$$

$$r_{o3} = \frac{1}{\lambda I_{DS}} = \frac{1}{(.01) 80 \times 10^{-6}} = 1.25 \times 10^6 \Omega$$

$$G_m = \frac{g_m}{1 + g_m r_{o3}} \approx \frac{1}{2r_{o3}}$$

$$R_{out} = r_{o2} (1 + g_m r_{o3}) \parallel 100k$$

$$\approx 100k$$

$$A_v = G_m R_{out} = .04$$