

Analog Integrated Circuits

Midterm 2

Thursday, April 6, 1995

EECS 140
SPRING 1995

B.E. BOSER

Name: ...

This exam has 3 problems with equal weights. Show how you arrived at each result to get credit. Please *mark results clearly with a box around them*. Write the answers directly on the exam sheets.

Device Parameters: (unless otherwise indicated)

$$I_s = 5 \times 10^{-15} \text{A}, \beta_F = 100, V_A = 100 \text{V}, V_{BE(on)} \approx 0.7 \text{V}, V_{CE}^{(sat)} = 0.2 \text{V},$$

NPN:

$$C_{je0} = 1 \text{pF}, \tau_f = 0.3 \text{ns}, C_\mu = 0.5 \text{pF}$$

$$I_s = 2 \times 10^{-15} \text{A}, \beta_F = 50, V_A = 50 \text{V}, V_{BE(on)} \approx -0.7 \text{V}, V_{CE}^{(sat)} = -0.2 \text{V},$$

PNP:

$$C_{je0} = 0.5 \text{pF}, \tau_f = 20 \text{ns}, C_\mu = 0.5 \text{pF}$$

$$\text{NMOS: } \mu_n C_{ox} = 50 \mu\text{A/V}^2, V_{th0} = +0.7 \text{V}, \lambda_n = 0.02 \text{V}^{-1} @ L = 4 \mu\text{m}, \gamma_n = 0.4 \sqrt{V}, 2\Phi_f = 0.6 \text{V}$$


$$\text{PMOS: } \mu_p C_{ox} = 25 \mu\text{A/V}^2, V_{th0} = -0.7 \text{V}, \lambda_p = 0.05 \text{V}^{-1} @ L = 4 \mu\text{m}, \gamma_p = 0.6 \sqrt{V}, |2\Phi_f| = 0.6 \text{V}$$

$$V_T \approx 26 \text{ mV (300 K)}$$

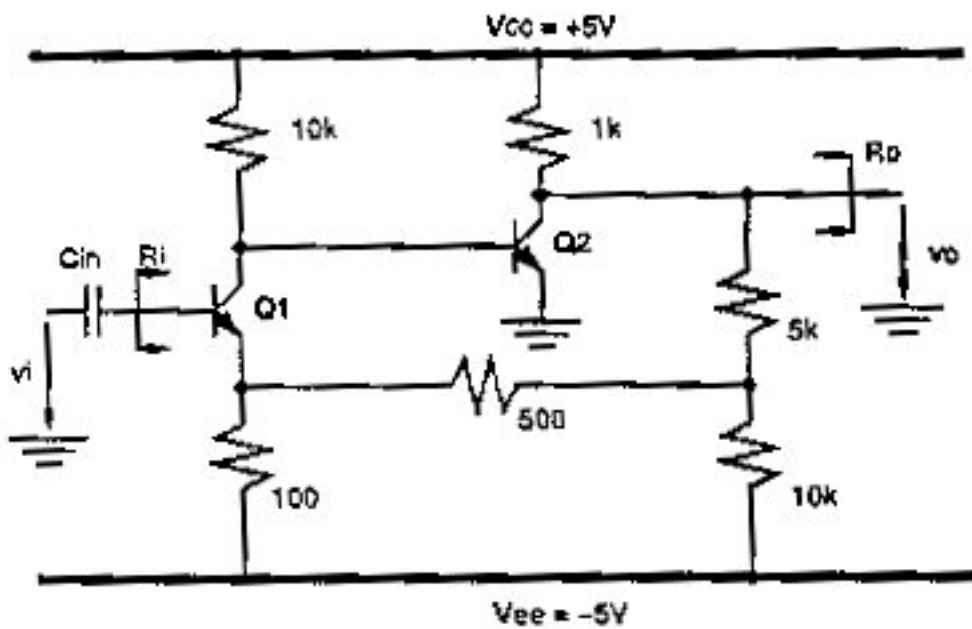Problem #1

In the amplifier shown below a dc biasing circuit (no shown) makes that the large signal output voltage is $V_o = 1 \text{V}$. C_i is a large coupling capacitor. Assume that the circuit is compensated to ensure stability.


- what is the type of feedback used?
- what is the feedback factor, f ?
- what is the loop gain, T , at low frequency?
- what is the low-frequency, small-signal voltage gain v_o/v_i of the circuit?
- what is the low frequency input resistance, R_i ?
- what is the low frequency output resistance, R_o ?



Problem #2

For the circuit below, find

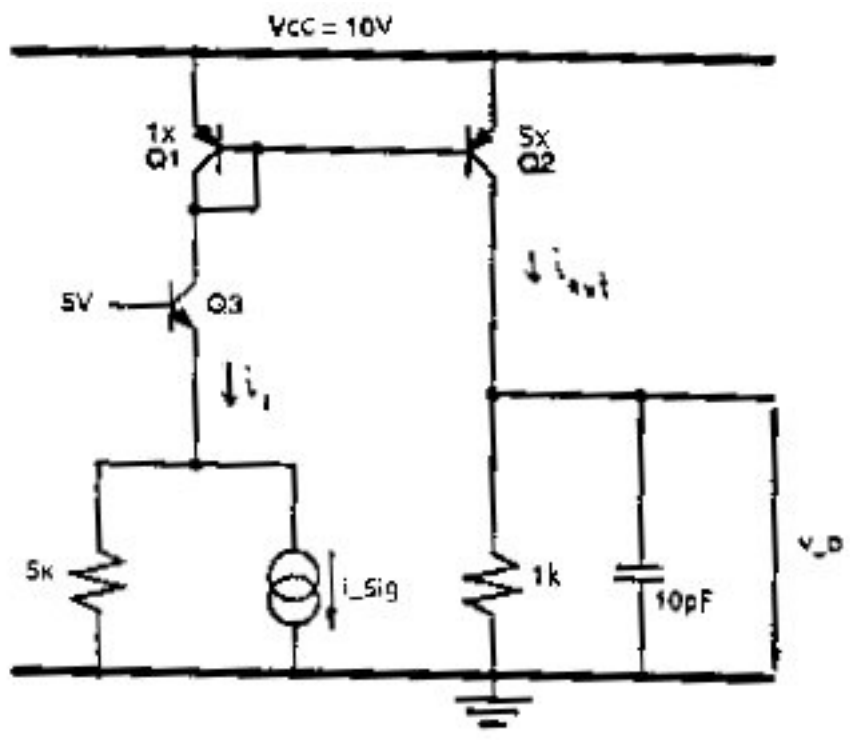
- (a) the low-frequency transresistance $R_x = v_o/i_{sig}$, and
- (b) the bandwidth f_{-3db} (use zero valued time constants).
- (c) write an expression for the frequency response $V_o(s)/I_{sig}(s)$ (polynomial in s). Include only the dominant pole and ignore zeroes.



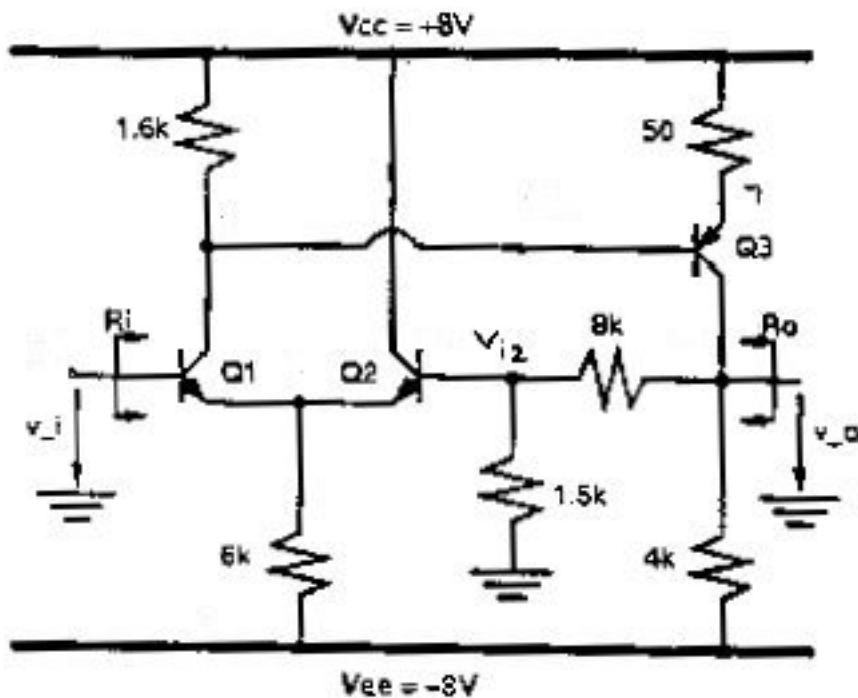Problem #3

In the amplifier below you may neglect base currents when determining dc conditions.

- What is the overall feedback used?
- Find the low-frequency loop-gain T_o .
- Determine the closed-loop voltage gain, v_o/v_i at low frequencies.
- Determine the closed-loop input and output resistances R_i and R_o .



Posted by HKN (Electrical Engineering and Computer Science Honor Society)
University of California at Berkeley

If you have any questions about these online exams please contact examfile@hkn.eecs.berkeley.edu.