

**EE 141, Spring 1994**  
**Midterm 2**  
**Professor J. M. Rabaey**

For all problems, you can assume the following transistor parameters:

**NMOS:**

$$V_{Tn} = 0.75V, k'n = 20\mu A/V^2, \lambda = 0.05, \gamma = 0.5 V^{1/2}, 2\Phi_F = -0.6V$$

**PMOS:**

$$V_{Tp} = -0.75V, k'p = 7\mu A/V^2, \lambda = 0.1, \gamma = 0.5 V^{1/2}, 2\Phi_F = -0.6V$$


**Bipolar NPN:**

$$\beta_F = 100, V_{BE(on)} = 0.7V, V_{BE(sat)} = 0.8V, V_{CE(sat)} = 0.1V$$

For all problems, you may assume that the transistor lengths indicated are the effective lengths ( $L_{eff}$ ) or, equivalently, that  $LD = 0$ .

 **Problem 1: Bipolar Gate**



A variant of an ECL gate is shown in FIG. 1.



- Determine  $R_E$  and  $R_C$  such that the logic swing at the output equals 0.8V, while the maximum static power consumption of the gate equals 50mW. You may assume that the input swings between 1.1V and 1.9V.
- Determine  $t_{pLH}$ . You may assume that **all internal capacitances can be ignored (including diffusion and junction capacitors)** and that  $C_L$  is the only capacitance of interest. Assume the following values:  $V_{swing} = 1V$ ,  $V_{in(low)} = 1V$ ,  $V_{in(high)} = 2V$ ,  $R_E = 800\Omega$ ,  $R_C = 1k\Omega$ .



FIG. 3 shows the NMOS pull-down network of a gate implemented in complimentary CMOS.

  

- Derive the logic function Z. NO NEED TO SIMPLIFY THE RESULT.
- Draw the schematics of the PMOS pull-up network. Hint: Use the Logic Graph approach introduced in Chapter 4.
- Determine the transistor sizes such that the identical worst case rise and fall times are obtained, while minimizing the area. The minimum size NMOS device which can be used equals (1.8/1.2) and is denoted with a ratio "1".

d. Assume that all internal capacitors can be lumped into a single load capacitance  $C_i$  and that this load capacitance is proportional to the transistor sizes. Assume that the available (dis)charge current for the minimum area solution derived above equals  $I_0$ . An external load capacitance  $C_L$  is connected to the output node. The input sources  $V_i$  can be assumed to be ideal voltage sources applying ideal step waveforms (between GND and  $V_{DD}$ ).

-> Derive a symbolic expression for the propagation delay of the gate.

-> Assume now that all transistors are scaled upwards with a factor  $S$ . Derive the minimum possible value of the propagation delay and the corresponding value of  $S$ .

---

**Posted by HKN (Electrical Engineering and Computer Science Honor Society)  
University of California at Berkeley**  
If you have any questions about these online exams  
please contact <mailto:examfile@hkn.eecs.berkeley.edu>