

EECS 141: Fall 2001
Midterm 1
Professor B. Nikolic

For all problems, you can assume the following transistor parameters (unless otherwise mentioned):

NMOS:


$$V_{tn} = 0.4, K'_n = 115 \text{ uA/V}^2, V_{dsat} = 0.6\text{V}, \lambda = 0, \gamma = 0.4\text{V}^{0.5}, 2\phi_f = -0.6\text{V}$$




PMOS:



$$V_{tp} = -0.4, K'_p = -30 \text{ uA/V}^2, V_{dsat} = -1\text{V}, \lambda = 0, \gamma = -0.4\text{V}^{0.5}, 2\phi_f = 0.6\text{V}$$


PROBLEM 1. MOS transistor as a switch

Find the final value of the voltage V_o . Assume $V_{tn} = |V_{tp}| = 0.5\text{V}$. Assume that the capacitor is initially discharged, and ignore subthreshold conduction and body effect.

 

   

  

 

PROBLEM 2. Equivalent RC models

In class we modeled the inverter delay by finding its equivalent resistance and capacitance. You are asked to find the equivalent resistance and input capacitance of a capacitively loaded symmetrically sized inverter.

a) Draw a schematic of how you would measure the equivalent resistance and briefly explain how you would do this.


b) Draw a schematic of how you would measure the equivalent input capacitance of this inverter. Explain the measurement procedure.

c) Does the input capacitance of this inverter depend on its loading? Explain your answer.


d) Does the input capacitance of this inverter depend on the type of transition (H-L or L-H transition)? If the answer is yes, which one is larger? Explain your answer.

 PROBLEM 3. Gate Delays

Consider a three-transistor circuit as shown in the figure below. $V_{dd} = 2.5V$ and input signal switches between 0 and V_{dd} with



 sharp rise and fall times.
 Use the transistor parameters indicated on the first page of the midterm.
 Ignore body effect. All transistors are minimum length, $L = 0.25\mu\text{m}$.
 Transistor widths:
 $W_2 = 2\mu\text{m}$, $W_1 = 1\mu\text{m}$.



a) Find the M_3 transistor width such that the switching point of the inverter (V_m) is placed in the middle of the V_x signal swing.

b) Find the t_{pLH} delay of this circuit. $C_{ox} = 6\text{fF}/\mu\text{m}^2$. Overlap capacitances are $C_o = 0.3\text{fF}/\mu\text{m}$. Bottom-plate PN junction capacitances are $2\text{fF}/\mu\text{m}$ (drain lengths are included). Ignore the sidewall capacitances. Ignore the impact of rise/fall times on propagation delay. $C_{out} = 10\text{fF}$.

PROBLEM 4. Wire Modeling

Consider an isolated 2mm long and 1 μ m wide M1 wire over a silicon substrate driven by an inverter with zero output resistance and capacitance.

a) If the wire width is doubled, the delay of this wire will be (circle one):

More than 2x shorter / Exactly 2x shorter / Shorter, but less than 2x /
Unchanged /
Less than doubled / Exactly doubled / More than doubled

Explanation:

b) If the wire width is halved, the delay of this wire will be (circle one):

More than 2x shorter / Exactly 2x shorter / Shorter, but less than 2x /
Unchanged /
Less than doubled / Exactly doubled / More than doubled

Explanation:

c) If the wire thickness is doubled, the delay of this wire will be (circle one):

More than 2x shorter / Exactly 2x shorter / Shorter, but less than 2x /
Unchanged /
Less than doubled / Exactly doubled / More than doubled

Explanation:

d) If the oxide thickness (between the wire and the substrate) is doubled, the wire delay will be (circle one):

More than 2x shorter / Exactly 2x shorter / Shorter, but less than 2x /
Unchanged /
Less than doubled / Exactly doubled / More than doubled

Explanation:

Posted by HKN (Electrical Engineering and Computer Science Honor Society)
University of California at Berkeley
If you have any questions about these online exams
please contact <mailto:examfile@hkn.eecs.berkeley.edu>