


EE141: Spring 1995 - Final Exam

Wednesday, May 17, 1995 Open Book, Open Notes, Write directly on this exam.

CMOS Parameters:

This exam is to be worked using the standard device models in the Rabaey for MOS(pp.50, 53, 66) and Bipolar(pp. 77, 83) devices unless otherwise specified in the problem.

I. (45 Points) Complementary CMOS

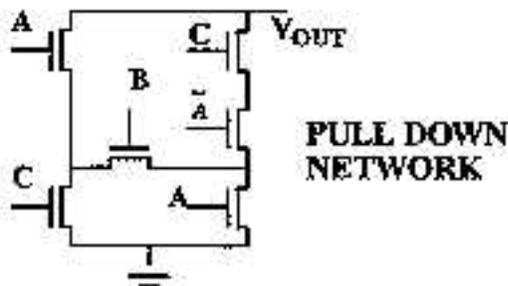


I.a.(20 Points) Pull Up Network

Draw the Pull Up Network to complete the complementary CMOS gate and give an Euler path if one exists.

I.b.(25 Points) Sticks Diagram of Layout

Create a Sticks Diagram using a **continuous diffusion** if possible. You may use more than one poly for each input and you may assume that both the input and its complement are available. Be sure to label all poly, diffusion, ground, V_{out} .

II.IIa(70 Points) Sequential Circuits and Logic Styles

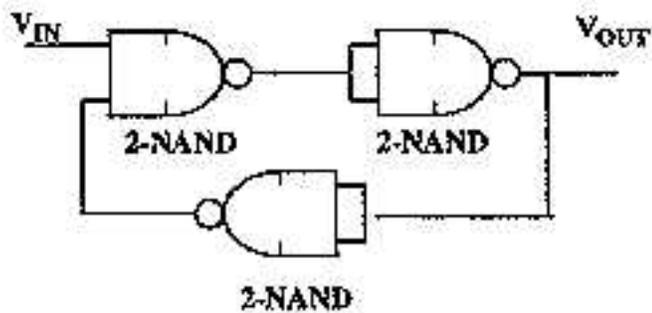**Operation**

At $t = 0$ V_{IN} goes from 0 to 1 and then remains at 1.

RC Model for Parts b), c) and d)

All minimum sized devices

$R_{NMOS} = 10 \text{ k}\Omega$, $R_{PMOS} = 30 \text{ k}\Omega$

$C_{GATE} = 4 \text{ fF}$

$C_{SOURCE} = C_{DRAIN} = 5 \text{ fF}$

II.a.(15 Points) Overall Circuit Function

Describe the output as a function of time based on less of loading have a delay of 0.5ns. Specify any delay, pulse widths, pulse sequences, etc.

II.b.(20 Points) Redesign

Assuming the 2-input NAND gates are Complementary CMOS with minimum sized devices. Use an RC switch level model to estimate the delay from the input at $t = 0$ to the 50% transition of the output.


II.c.(15 Points) Use of Extra Inputs

Specify a fixed voltage for the duplicate inputs for the second and third NAND gates such that the circuit will still function. Then use the RC switch level model to estimate the delay from the input to the 50% transition of the output.

II.d.(20 Points) Pseudo NMOS

The initial circuit is now to be implemented in psuedo-NMOS. Use the RC switch level model to estimate the delay from the input to the 50% transition of the output. Assume the pseudo-NMOS load has a $W/L = 1/4$ with $R_{on} = 4 \text{ R}_{pmos}$, $C_{gate} = 16 \text{ fF}$ and $C_{drain} = C_{source} = 5 \text{ fF}$.

III.(50 Points) Bipolar

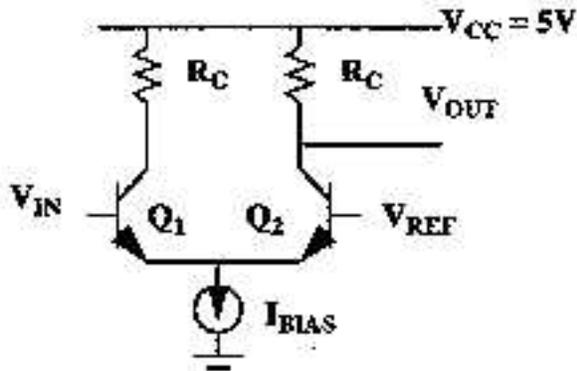

$V_{REF} = 4.2V$
 $\beta = 100$
 $V_{BE(on)} = 0.7V$
 $V_{CE(SAT)} = 0.1V$
 $\tau_{LIFE} = 1ns$
 Ignore all junction capacitance


III.a(20 Points) ECL Static Analysis

Design the bias current I_{BIAS} and load resistor R_C such that the power consumption is 1 mW and transistor Q_1 saturates at $V_{in} = 0.45V$.

III.b.(30 Points) Transient

Find the minority charge in the base of Q_1 when V_{in} is 4.2 V and all the current flows through Q_1 . Determine how long it takes for V_{out} of another gate to remove the minority charge. You may simplify the problem by assuming that V_{in} remains at 4.2 V.

(65 Points) Dynamic Logic and latches

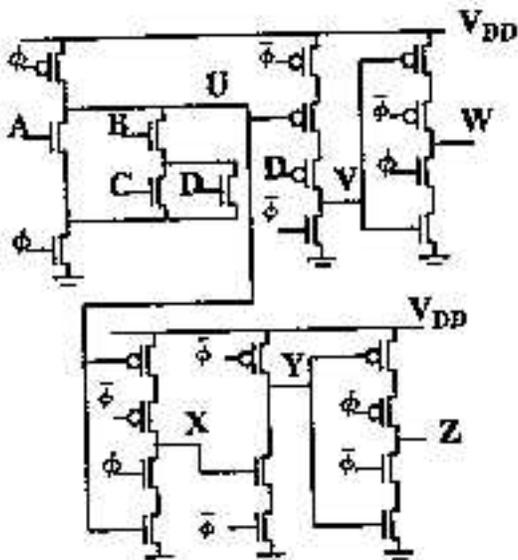

Conditions
 $A = 1, B = 1, C = 0, D = 0$
 ϕ low for long time
 $W = 1, X = 1$

Model
 All minimum sized devices
 $R_{NMOS} = 10k\Omega, R_{PMOS} = 30k\Omega$
 $C_{GATE} = 4fF$
 $C_{SOURCE} = C_{DRAIN} = 5fF$

IV.a.(15 Points) Intital Values


Determine the intial value of U, V, Y, and Z.


IV.b.(20 Points) Propagation Delay

Use the RC switch level model to determine the propagation delay from the rising edge of the clock to the 50% transition of V.

IV.c.(30 Points) Dynamic Operation

Neglecting rise and fall times, find W and Z as a function of time for two clock cycles. Note that input A changes during this time as well. (show results for intermediate signals for partial credit.)

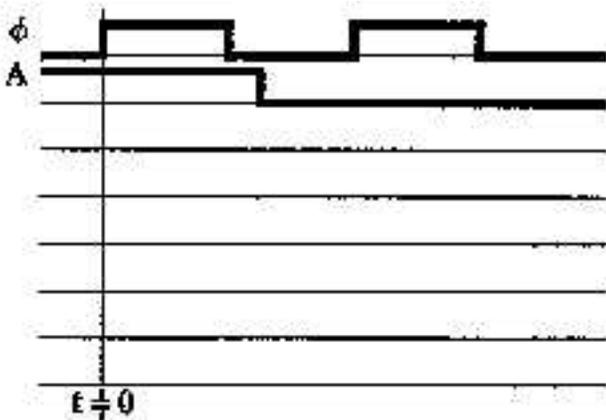**V.(70 Points) Memory**

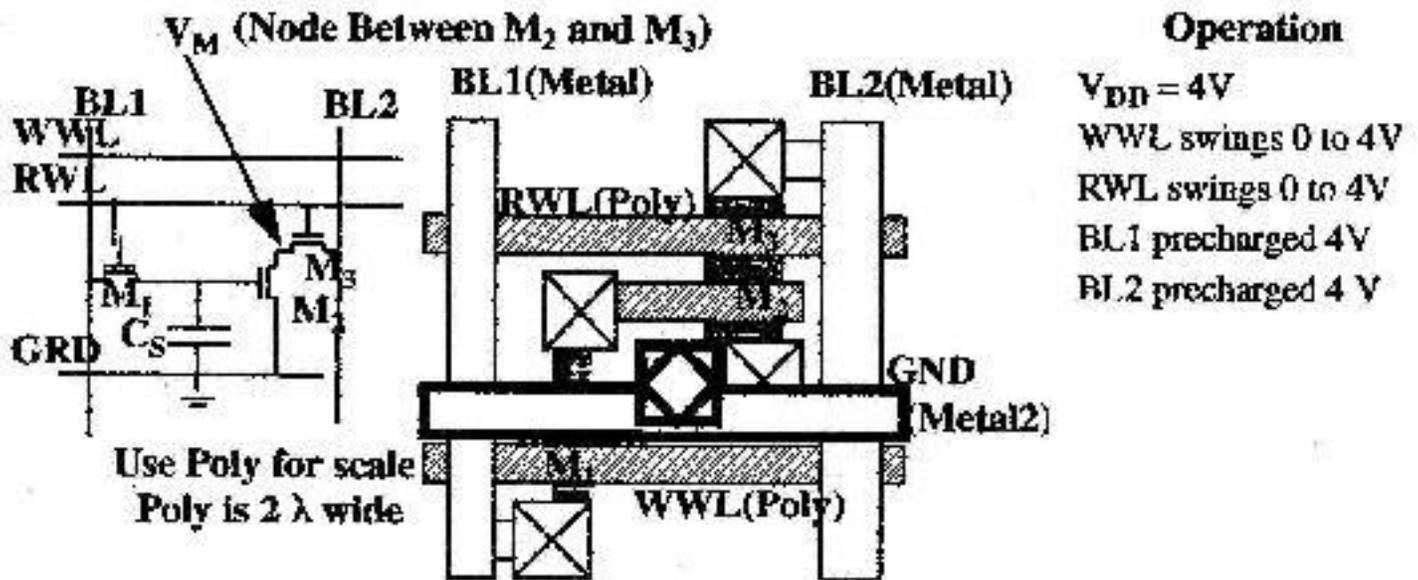

V.a.(15 Points) Circuit Drive and Bit Line Change

Assuming minimum sized devices and $V_M = 2V$, find the slew rate(volts/second) for **BL2** if it has a capacitance of 2 pF. Neglect Body Effect.

V.b.(25 Points) Sizing and Body Effect

Size M_2 such that V_M will be 2V. Be sure to include the **BODY EFFECT** on all devices.

V.c(15 Points) RC Delay and Layout

If the maximum read word line (RWL) delay is to be 1ns, find how many DRAM Cells could be placed in series. (Model poly as being either over field or gate and neglect inter conductor capacitances.)

V.d.(15 Points) Charge Sharing and Layout

If the read word line poly is floating during the charging of **BL2** from 0 to 4V by another circuit, what will be the voltage due to charge sharing on the read bit line? (Consider various sources of mutual capacitance.)

**Posted by HKN (Electrical Engineering and Computer Science Honor Society)
University of California at Berkeley**

**If you have any questions about these online exams
please contact <mailto:examfile@hkn.eecs.berkeley.edu>**