
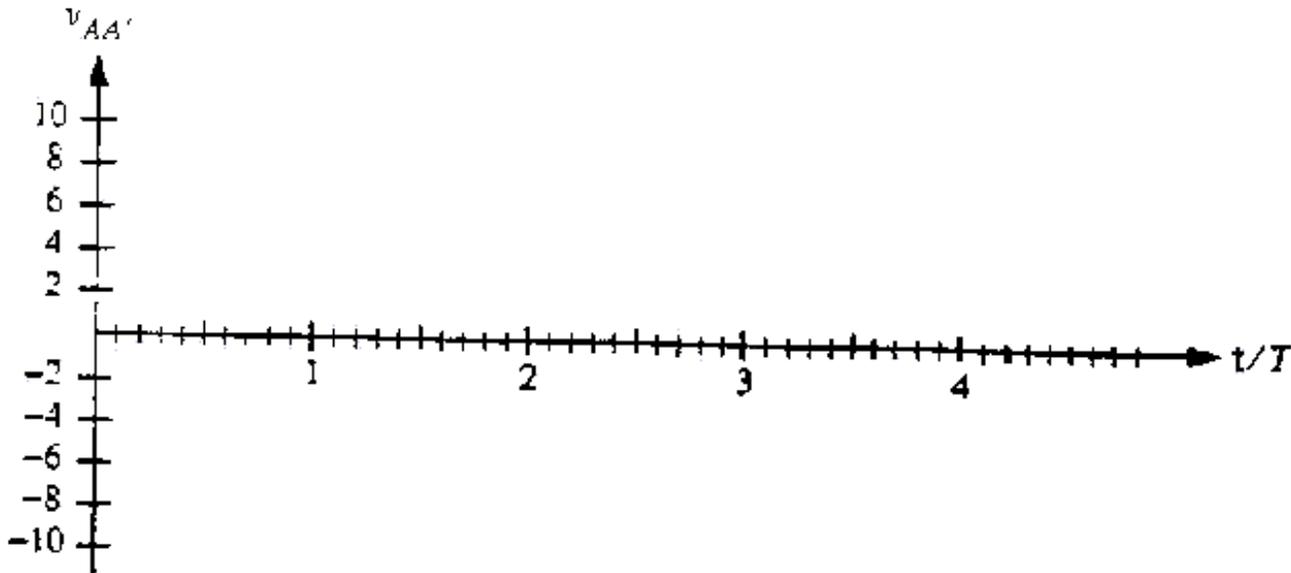


**EECS 117A, Fall 1998**  
**Midterm #1**  
**Professor S.E. Schwarz**

**Instructions:** You may use the textbook, a pocket calculator, and drafting instruments. Write answers in the space provided. Show your work on the Smith chart.

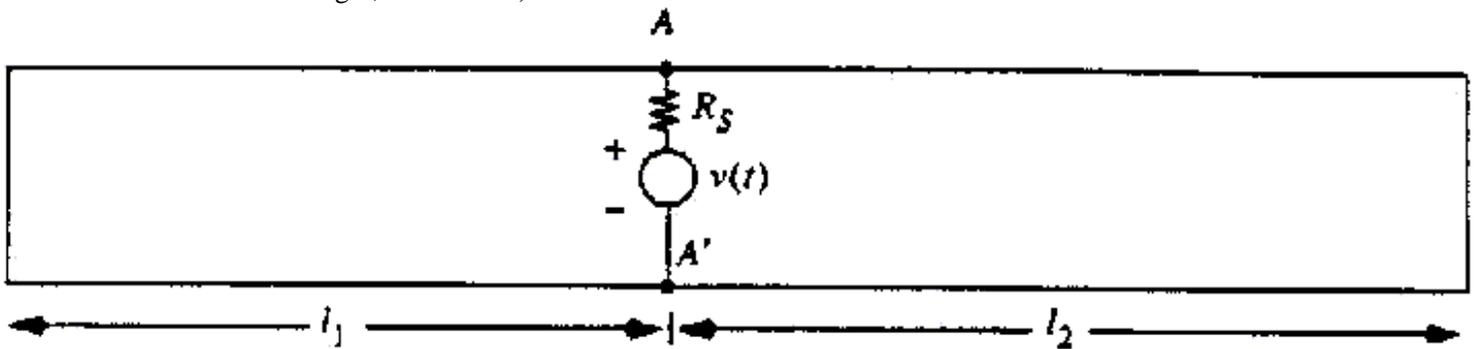**Problem #1 (30 points)**

The circuit below contains a Thevenin voltage source and two transmission lines of length  $l_1$  and  $l_2$ . Let  $T = l_1/U$  (where  $U$  is the phase velocity),  $l_2 = 1.25l_1$ ,  $R_s = Z_0/2$ . The voltage source  $v(t) = 10$  volts for  $0 \leq t \leq 0.2T$ , and zero for other times. Graph the voltage between terminals A and A' on the scales below, over the range  $0 < t < 4.8T$ . Show amplitudes of pulses clearly on the graph. (Note: The lines are not the same length,  $l_2 = 1.25l_1$ .)



**Problem #2 (35 points)**



In this problem the transmission line has a certain amount of loss, so that  $k = \beta - j\alpha$ .

(a) (10 pts.) Assume the voltage phasor representing the wave moving to the right at position AA' is  $v_+(A) = V_1$ . What is the phasor representing the reflected wave (moving toward the left) at position AA'?

Answer:  $v_-(A) = \underline{\hspace{2cm}}$


(b) (15 pts.) For the rest of this problem, let  $\beta l = \pi/2$ . Find the impedance seen looking into the line at position AA'.

(c) (10 pts.) Find the limit of your answer to (b) when  $\alpha$  becomes equal to zero, and explain why your answer is reasonable in this limit.

**Problem #3 (35 points)**


Show your work on the Smith chart.

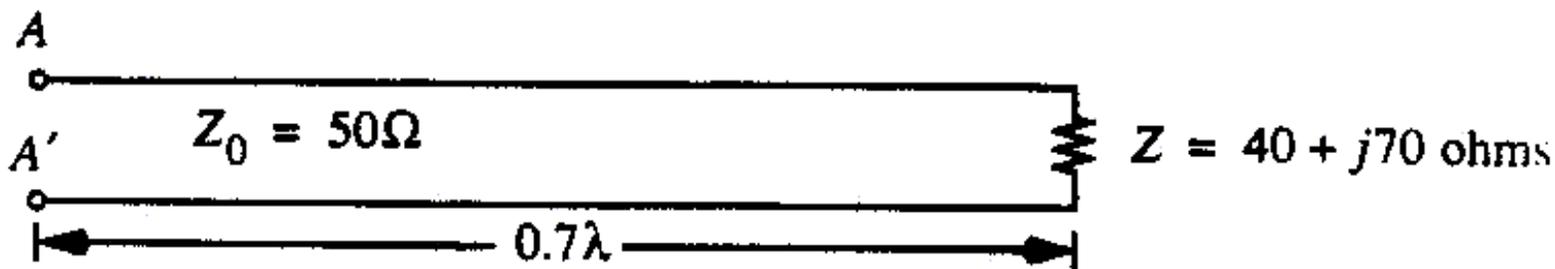(a) (10 pts.) Find the impedance seen looking to the right into terminals AA'.




Answer:  $Z_a = \underline{\hspace{2cm}}$  ohms

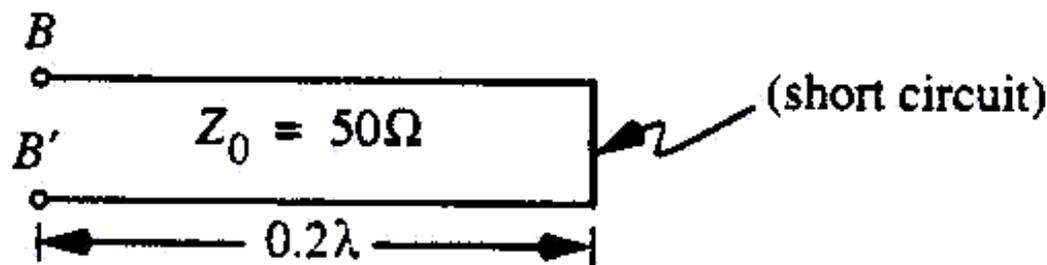(b) (10 pts.) Find the impedance seen looking into terminals BB'.




Answer:  $Z_b = \underline{\hspace{2cm}}$  ohms

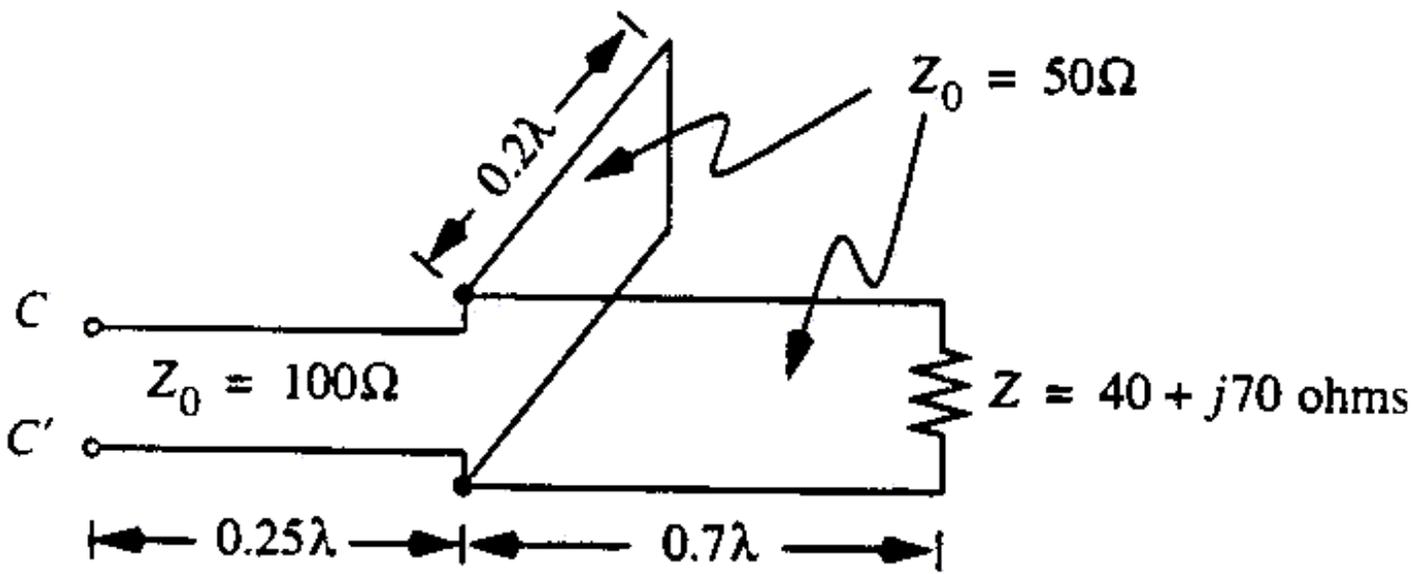(c) (15 pts.) Find the impedance looking into terminals CC'. (Note that one of three transmission lines has  $Z_0 = 100$  ohms).



Answer:  $Z_c =$  \_\_\_\_\_ ohms

Smith Chart:

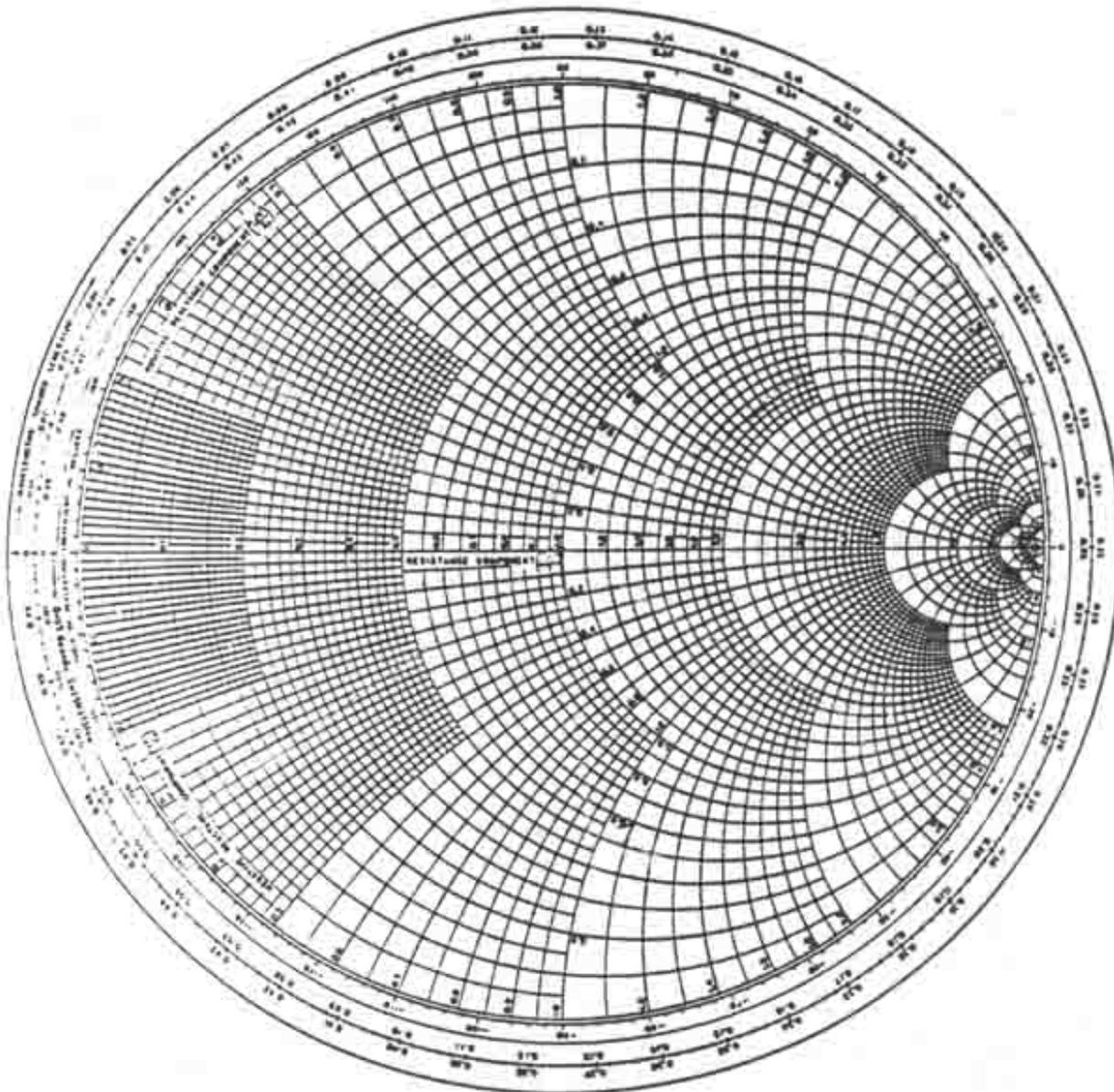



---

**Posted by HKN (Electrical Engineering and Computer Science Honor Society)  
University of California at Berkeley**  
If you have any questions about these online exams  
please contact <mailto:examfile@hkn.eecs.berkeley.edu>