

NAME (please print) \_\_\_\_\_

UNIVERSITY OF CALIFORNIA  
Electrical Engineering and Computer Sciences

EECS 145L Electronic Transducer Lab  
MIDTERM #2 (100 points maximum)

(closed book, equation sheet provided, calculators OK)

(You will not receive full credit if you do not show your work)

For the following problems, you may use any circuit components from the 145L lab.

**PROBLEM 1 (16 points)**

Sketch a circuit that uses a one-turn  $1\text{ k}\Omega$  circular resistor to convert a shaft angle ( $0^\circ$  to  $300^\circ$ ) into an output voltage ( $0.00\text{ V}$  to  $3.00\text{ V}$ ) that is proportional to the angle. The circuit must be able to drive a  $1\text{ k}\Omega$  load.

NAME (please print) \_\_\_\_\_

**PROBLEM 2 (16 points)**

Sketch a circuit that uses a PIN photodiode to convert light intensity (0 to  $6.24 \times 10^9$  photons per s) into an output voltage (0.0 V to 1.0 V) that is proportional to the intensity. (*Hint:*  $6.24 \times 10^9$  electrons per s = 1 nA) Assume that the photodiode converts photons into electron-hole pairs with 100% efficiency.

**PROBLEM 3 (16 points)**

Sketch a circuit that uses a resistive strain gauge to convert strain ( $-10^{-3} < \Delta L/L < 10^{-3}$ ) into an output voltage (-1.00 V to +1.00 V) that is proportional to the strain. The strain gauge has an unstrained resistance of 100  $\Omega$  and a gauge factor  $G_s$  of 2.00.

NAME (please print) \_\_\_\_\_

#### PROBLEM 4 (52 points)

You are designing a thermocouple-based system for measuring the temperature of a furnace ( $T_f$ ) over the temperature range from 25 °C to 500 °C with an absolute accuracy of 2 °C and do not want to provide ice to stabilize the temperature of the reference junction at 0 °C. Instead, you decide to leave the reference junction in the air of the room and measure the temperature of the room ( $T_r$ ) with a solid-state temperature sensor. The correction of the thermocouple output for room temperature will be done by a voltage-summing circuit.

Assume the following:

- The thermocouple sensitivity is 50  $\mu\text{V}/^\circ\text{C}$ .
  - The solid state temperature sensor produces 1  $\mu\text{A}$  per  $^\circ\text{K}$ . Note that 0 °C = 273 °K.
- a. (18 points) Sketch a circuit that uses a thermocouple to produce an output  $V_a = 0.25 \text{ V}$  when the temperature difference between the sensing and the reference junction is 25 °C and  $V_a = 5.00 \text{ V}$  when the temperature difference is 500 °C. Label all necessary analog circuit elements and signal lines. Include the thermocouple wires and furnace. (It is not necessary to include analog filtering).

NAME (please print) \_\_\_\_\_

- b. (18 points)** Sketch a circuit that converts the solid-state temperature sensor current into a voltage  $V_b$  that has the same sensitivity ( $V/^\circ\text{C}$ ) as the thermocouple circuit **a**. Draw a block diagram and label all necessary analog circuit elements and signal lines. Show where the solid-state temperature sensor is placed in the diagram of part **a**. above. (It is not necessary to include analog filtering)
- c. (16 points)** Sketch a circuit that combines the outputs of circuits **a**. and **b**. to provide a voltage  $V_c$  that is proportional to the furnace temperature (0.25 V at  $25^\circ\text{C}$  and 5.00 V at  $500^\circ\text{C}$ ) and does not depend on the room temperature.