



## **PROBLEM 2 (60 points)**

You have been given the assignment of designing an amplifier and filtering circuit that meets the following requirements:

- Differential input
- Operational temperature range  $10^{\circ}\text{C}$  to  $30^{\circ}\text{C}$
- Differential gain  $10^6$  between 1 Hz and 1000 Hz, with an accuracy of 30%
- Differential gain  $<1$  for frequencies  $>10,000$  Hz
- Common mode gain  $< 10^{-2}$  for all frequencies
- 


Assume the following

- Since you can't reliably get a differential gain  $>10^4$  from a single instrumentation amplifier, your circuit will need additional amplification.
- The input offset voltage of the first instrumentation amplifier varies by 1 mV over the range from  $10^{\circ}\text{C}$  to  $30^{\circ}\text{C}$ , but the direction and magnitude of variation cannot be predicted because it differs from part to part (assume all other offset voltages are much less important and can be neglected)
- It is not possible to measure the temperature of the circuit

### **Do the following:**

- a. (30 points) Draw a sketch of your circuit, showing all necessary components.

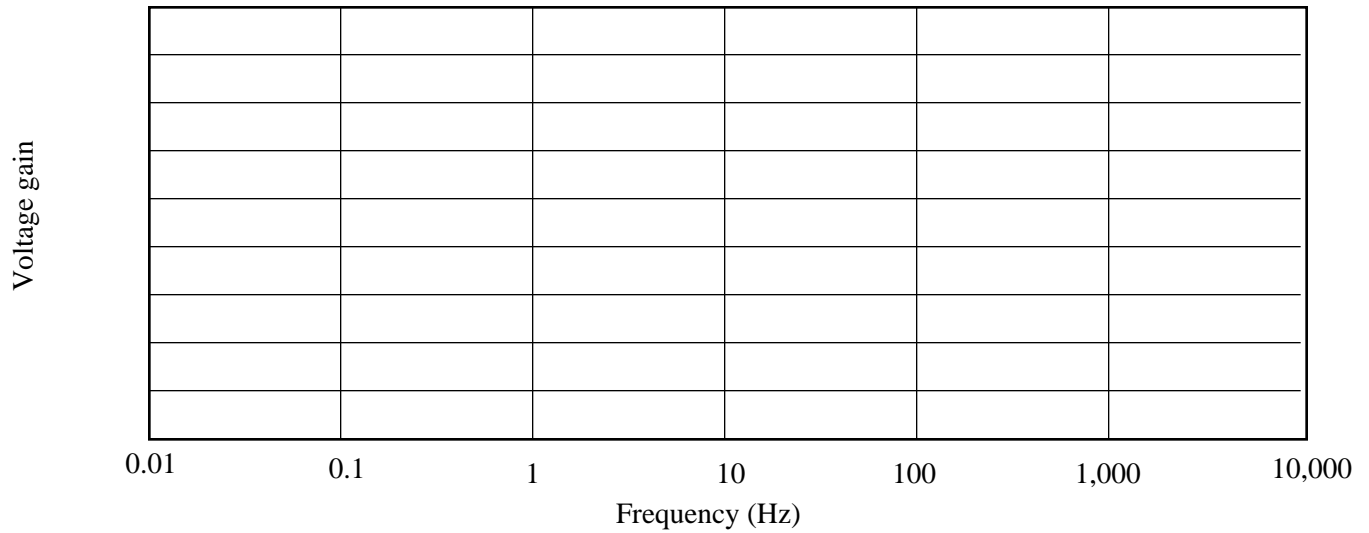- b. (15 points) Sketch the differential gain vs. frequency for your circuit from 0.01 Hz to 10 kHz in the figure below



- b. (5 points) What is the requirement for the common mode rejection ratio of the instrumentation amplifier in your circuit?

- c. (5 points) If a 1 k resistor is connected to one input and the other input is grounded, approximately how much Johnson noise does the resistor contribute to the output of the circuit?

- c. (5 points) If both inputs are connected to ground through 1 k resistors, approximately how much Johnson noise do the resistors contribute to the output of the circuit?

**Equations, some of which you may need:**

$$R(T) = R(T_0) \exp\left(\frac{1}{T} - \frac{1}{T_0}\right) \quad I = I_0 e^{-kLC} \quad V_{\text{rms}} = \sqrt{B[(D_1 G)^2 + (D_0)^2]}$$

$$V(t) = V_0 \sin(\omega t) \quad \omega = 2\pi f \quad V_0 = A(V_+ - V_-)$$

$$|G| = \frac{1}{\sqrt{1 + (f/f_c)^{2n}}} \quad \tan \frac{\phi}{n} = \frac{f}{f_c} \quad f_c = \frac{1}{2RC}$$

$$|G| = \frac{(f/f_c)^n}{\sqrt{1 + (f/f_c)^{2n}}}$$

$$x = e^{-\alpha t} [A \cos(\omega t) + B \sin(\omega t)] = Re^{-\alpha t} \cos(\omega t + \phi) \quad V = q/C$$

$$v = v_0 + at \quad x = x_0 + v_0 t + 0.5 at^2 \quad (\text{constant } a) \quad g = 10 \text{ m s}^{-2}$$

$$I_{\text{rms}} = \sqrt{2qI(F_2 - F_1)} \quad q = 1.60 \times 10^{-19} \text{ Coulombs}$$

$$V_{\text{rms}} = \sqrt{4kTR(F_2 - F_1)} \quad k = 1.38 \times 10^{-23} \text{ Volt}^2 \text{ sec ohm}^{-1} \text{ } ^\circ\text{K}^{-1}$$

$$R_T = R_3 \frac{V_b R_1 - V_0(R_1 + R_2)}{V_b R_2 + V_0(R_1 + R_2)} \quad V_0 = G_\pm(V_+ - V_-) + G_c(V_+ + V_-)$$

$$N(x) = N(0)e^{-x/\mu} \quad \text{“CMRR”} = \frac{G_\pm}{G_c} \quad \text{“CMR”} = 20 \log_{10} \frac{G_\pm}{G_c}$$

$$R = A/L \quad \frac{R}{R} = G_s \frac{L}{L} \quad V_0 = V_b G_s \frac{L}{L} \quad x = \frac{V}{dV/dx}$$

$$V_T = V_{\text{BE2}} - V_{\text{BE1}} = \frac{kT}{q} \ln \frac{I_1}{I_2} \quad k/q = 86.17 \mu\text{V/K}$$

$$P_R = AT^4 = 5.6696 \times 10^{-8} \text{ W m}^{-2} \text{ K}^4$$

$$E = hc/\lambda \quad hc = 1240 \text{ eV nm} \quad \lambda_{\text{max}} = (2.8978 \times 10^6 \text{ nm K})/T$$

$$= \frac{T_{n+2} - T_{n+1}}{T_{n+1} - T_n} \quad T_{\text{equ}} = T_{n+1} + \frac{T_{n+2} - T_{n+1}}{1 - \dots} \quad T = T_2 - (T_2 - T_1)e^{-t/\tau}$$

$$Q = I + I^2 R/2 + K_p(T_s - T_0) + K_a(T_a - T_0) \quad T_{\text{equ}} = \frac{I + I^2 R/2 + K_p T_s + K_a T_a}{K_p + K_a}$$

$$\mu \quad \bar{a} = \frac{1}{m} \sum_{i=1}^m a_i \quad \sigma_a = \frac{1}{m-1} \sum_{i=1}^m (a_i - \bar{a})^2 \quad \bar{a} = \frac{a}{\sqrt{m}}$$

$$f = \sqrt{\frac{f^2}{a_1^2} + \frac{f^2}{a_2^2} + \dots + \frac{f^2}{a_n^2}}$$

Johnson noise = 129  $\mu\text{V}$  for 1 MHz and 1 M

Iron+Constantan - 52.6  $\mu\text{V}/^\circ\text{C}$  W+W(Rh) - 16.0  $\mu\text{V}/^\circ\text{C}$