 


EE 105 Midterm I

Fall 2001

Prof. Roger T. Howe


1. Silicon-on-Insulator (SOI) Resistor [17 points]



1. *Starting material:* silicon-on-insulator substrate, which is a 500 μm -thick, heavily doped n-type silicon wafer, on which a 0.25 μm -thick "buried oxide" is grown, over which is grown (by a special process) a 0.25 μm -thick layer of n-type single crystal silicon. The 0.25 μm -thick silicon layer is doped with phosphorus at a concentration of $3 \times 10^{16} \text{ cm}^{-3}$
2. Implant boron with dose $Q_a = 5 \times 10^{13} \text{ cm}^{-2}$ and anneal so that the boron concentration is uniform through the 0.25 μm -thick silicon layer.
3. Pattern the 0.25 μm -thick silicon layer using the **Silicon Mask** (clear field).
4. Deposit 0.5 μm of CVD SiO_2 and pattern using **Contact Mask 1** (dark field).
5. Pattern the sandwich of the 0.25 μm -thick "buried oxide" and the 0.5 μm -thick CVD oxide using **Contact Mask 2** (dark field). *Note:* the resulting contact hole reaches to the underlying n-type silicon substrate.
6. Deposit 0.5 μm of aluminum and pattern using the **Metal Mask** (clear field).

Given: mobilities for this problem are $u_n = 1000 \text{ cm}^2/(\text{Vs})$ and $u_p = 400 \text{ cm}^2/(\text{Vs})$. Count the "dogbone" contact areas as 0.65 square each in finding the resistance. The permittivity of oxide is $\epsilon_{\text{ox}} = 3.45 \times 10^{-13} \text{ F/cm}$.

 
- a. [5 pts.] Sketch the cross section $A-A'$ on the graph below **after step 6**. Identify all layers clearly.



- b. [3 pts.] What is the sheet resistance R -square of the 0.25 μm -thick silicon layer?


- c. [3 pts.] What is the resistance R_{1-2} between terminals 1 and 2 in ohms? If you couldn't solve part (a), use R -square = 200 ohms (not a correct answer to (a)).

 - d. [4 pts.] Fill in the boxes in the circuit model below with the correct elements *and* their values. Your answer to part (c) should be helpful. You can assume that V_1 and V_2 are each greater than 2 V and that $V_3 = 0$ V.




- e. [2 pts.] Now if the voltages of terminals 1 and 2 are each lowered to approximately -0.25 V, with terminal 3 (the n-type substrate) being grounded, what is the effect on R_{1-2} compared to the case in part (d)? Justify your answer.

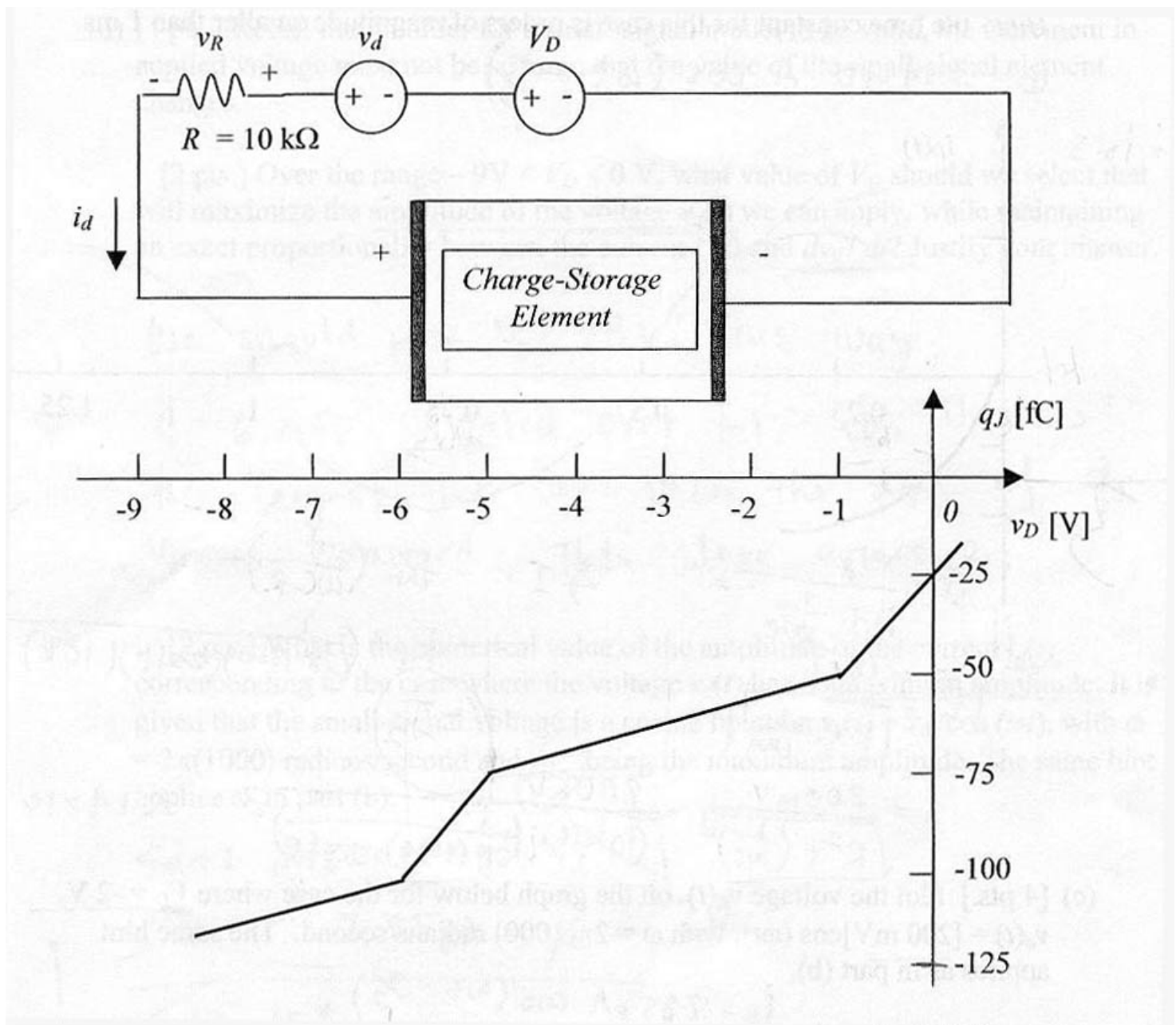2. Unusual junction charge-storage element [16 pts.]




a. [4 pts.] The plot is the internal stored charge q_J associated with the + terminal of the charge-storage element, as a function of the applied voltage v_D . The DC current I_D through the device is zero. Draw the small-signal equivalent circuit for the case where $V_D = -0.5\text{ V}$. *Hint*: your answer should have three circuit elements, two of which are the small-signal voltage source and the resistor.

 b. [4 pts.] For the case where $V_D = -0.5\text{ V}$ and $v_d(t) = [200\text{ mV}]\cos(\omega t)$, with $\omega = 2\pi(1000)$ radians/second, plot the current waveform $i_D(t)$ on the graph below. *Hint*: the time constant for this case is orders of magnitude smaller than 1 ms.



 
- c. [4 pts.] Plot the voltage $v_R(t)$ on the graph below for the case where $V_D = -2$ V, $v_d(t) = [200 \text{ mV}] \cos(\omega t)$, with $\omega = 2\pi(1000)$ radians/second. The same hint applies as in part (b).



- d. [4 pts.] Recall that in order for a small-signal model to be valid, the increment in applied voltage must not be so large that the value of the small-signal element changes.
- i. [2 pts.] Over the range $-9 \text{ V} < V_D < 0 \text{ V}$, what value of V_D should we select that will maximize the amplitude of the voltage $v_d(t)$ we can apply, while maintaining an exact proportionality between the current $i_d(t)$ and dv_d/dt ? Justify your answer.

- ii. [2 pts.] What is the numerical value of the amplitude of the current $i_d(t)$ corresponding to the case where the voltage $v_d(t)$ has its maximum amplitude. It is given that the small-signal voltage is a cosine function $v_d(t) = v_d^* \cos(\omega t)$, with $\omega = 2\pi(1000)$ radians/second and v_d^* being the maximum amplitude. The same hint applies as in part (b).

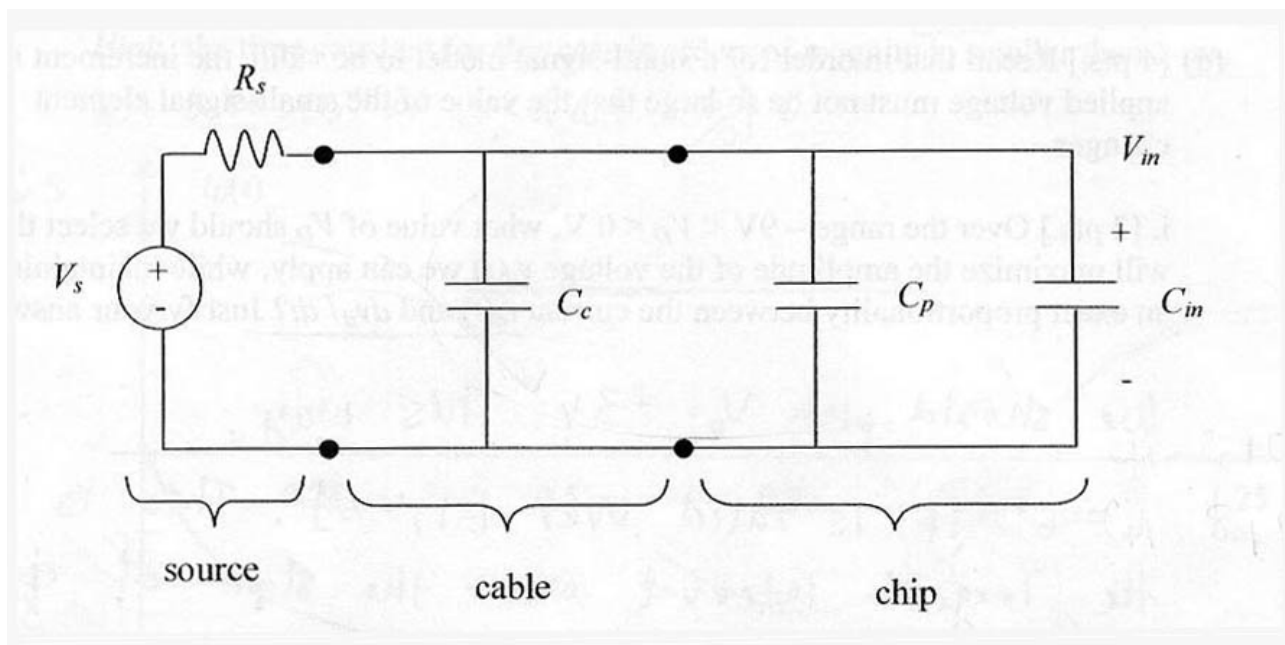3. Frequency response measurements [17 pts.]




The above circuit models a test set-up to measure the input impedance of an IC amplifier. The cable has a capacitance $C_c = 5$ pF, the chip has a pad and interconnect capacitance $C_p = 2$ pF, and the amplifier's input capacitance is $C_{in} = 1$ pF. The sinusoidal source has an amplitude of 100 mV and a source resistance $R_s = 50$ ohms.

a. [3 pts.] Find the transfer function V_{in} / V_s in the standard form of a low-pass filter.


b. [3 pts.] Find the amplitude of $v_{in}(t)$ when the source has a frequency $\omega = 2.5$ Grad/s.

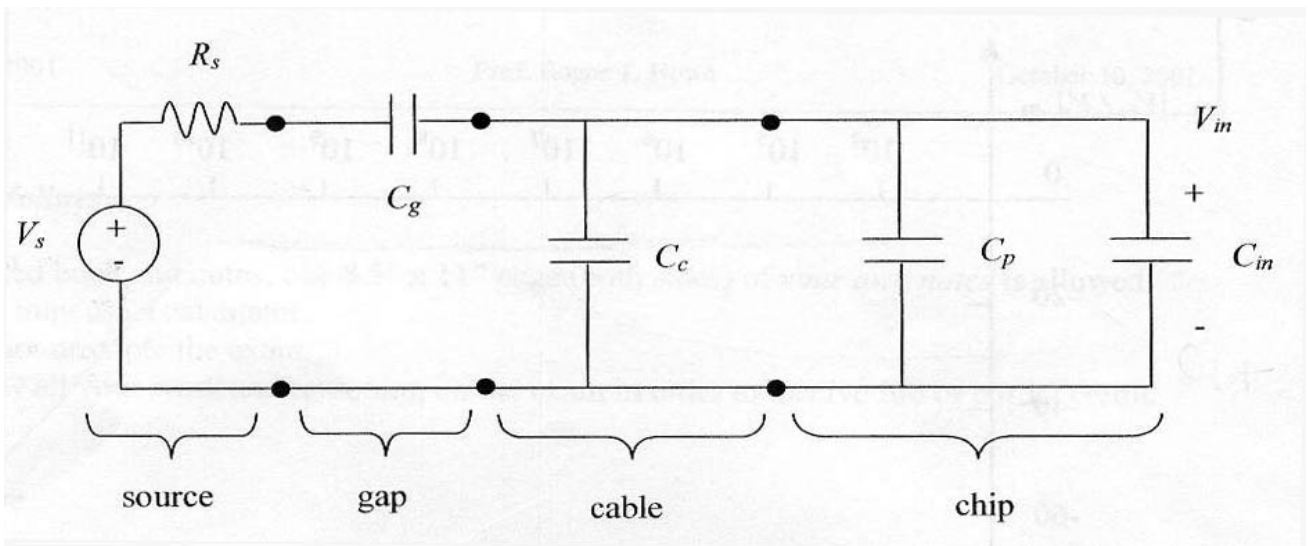c. [4 pts.] You notice that your measurements don't agree with the prediction from part (b), so you inspect your test setup. You discover that the cable connector wasn't fully inserted, so there's a small gap between it and the output of the source. This gap is modeled by a capacitor of value $C_g = 2$ pF, as shown in the schematic below.



Find the transfer function V_{in} / V_s . Hint: the denominator should be in the form of a low-pass filter.

 - d. [4 pts.] Sketch the magnitude of V_{in} / V_s in dB versus frequency on the plot below. Note that your low and high-frequency asymptotes should be accurate - use the "straight-line" approximation. If you couldn't solve part (c), you can assume that the low frequency magnitude is -20 dB (not the correct answer, of course).



- e. [3 pts.] For the circuit in part (c), find the phase of V_{in} for the case where the source frequency is $\omega = 2.5 \text{ Grad/s}$. *Hint:* your result in part (d) may be helpful.