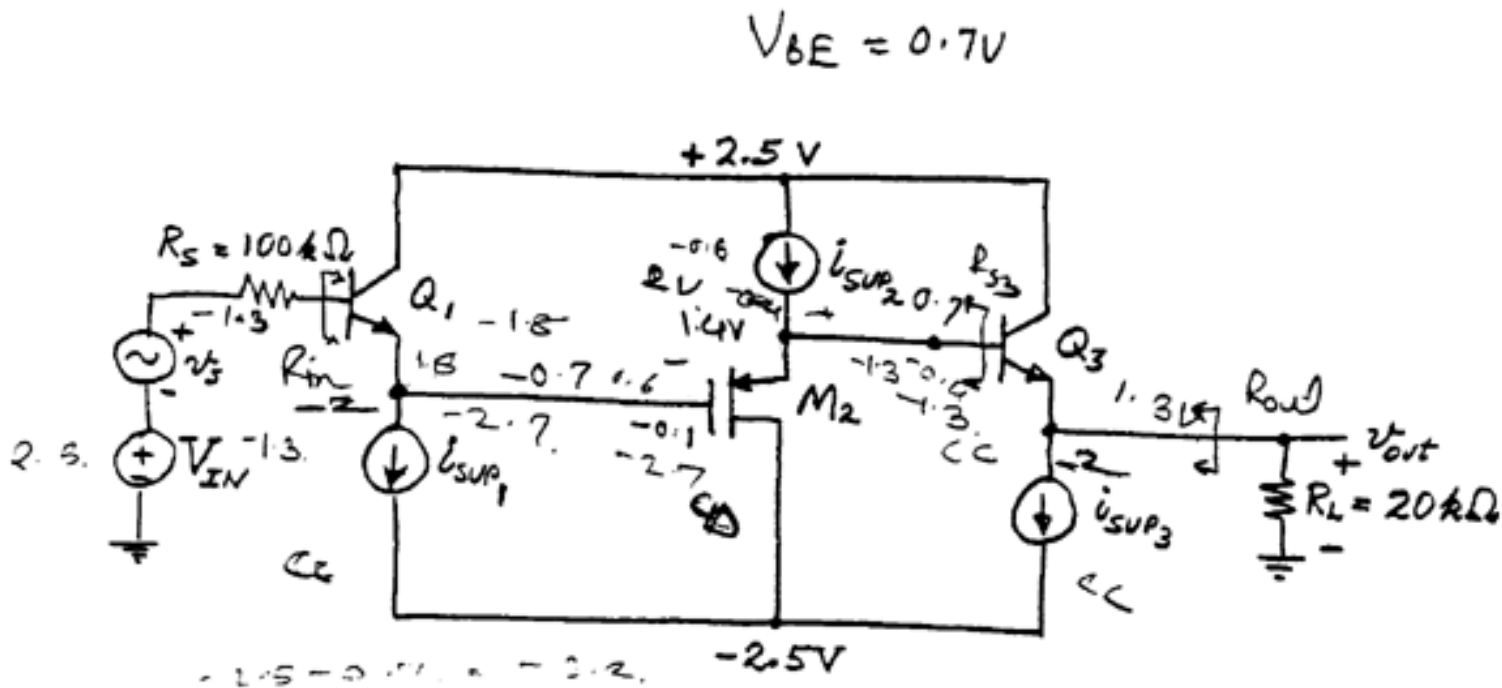


Ground Rules:

- Close book; one 8.5x11 crib sheet (both sides)
- Do all work on exam pages
- Default bipolar transistor parameters:
 - npn: $\beta_n=100, V_{An}=50 \text{ V}, V_{CE-sat}=0.2 \text{ V}$
 - pnp: $\beta_p=50, V_{Ap}=25 \text{ V}, V_{EC-sat}=0.2 \text{ V}$
- Default MOS transistor parameters: note LAMBDA depends on L!
 - NMOS: $\mu_n C_{ox}=100e-6 \text{ A/V}^2, \text{LAMBDA}_n=[0.1/L] \text{ V}^{-1}$ (L in micrometers) $V_{Tp}=1 \text{ V}$
 - PMOS: $\mu_p C_{ox}=50e-6 \text{ A/V}^2, \text{LAMBDA}_p=[0.1/L] \text{ V}^{-1}$ (L in micrometers) $V_{Tp}=-1 \text{ V}$

Problem #1: Small-Signal Amplifier [24 points]



GIVEN:

- | | |
|-----------------------|------------------------|
| $I_{SUP1} = 100\mu A$ | $r_{oc1} = 200k\Omega$ |
| $I_{SUP2} = 200\mu A$ | $r_{oc2} = 100k\Omega$ |
| $I_{SUP3} = 100\mu A$ | $r_{oc3} = 200k\Omega$ |

$V_{SUP(min)} = 0.5V$

a) [4 pts.] What is width of transistor M_2 such that the DC output voltage $V_{out}=0$ V for $V_{IN}=0$ V. Given: the length of M_2 is $L_2=2e-6$ m.

W=100 micrometers

b) [4 pts.] What is the numerical value of the input resistance R_{in} of this amplifier? Your answer should be correct to within +/- 5%.

If you couldn't solve (a) you can assume for this part that $W_2=25e-6$ m. Of course, this isn't the correct answer to part (a).

$R_{in}=14.31$ mega-ohms

c) [4 pts.] What is the numerical value of the output resistance R_{out} of this amplifier? Your answer should be correct to within +/- 5%.

If you couldn't solve (a) you can assume for this part that $W_2=25e-6$ m. Of course, this isn't the correct answer to part (a).

$R_{out}=260$ ohms


d) [6 pts.] What is the numerical value of the overall voltage gain v_{out}/v_s , with $R_s=100$ kilo-ohms and $R_L=20$ kilo-ohms? Your answer should be correct to within +/- 5%.

Again, If you couldn't solve (a) you can assume for this part that $W_2=25e-6$ m. Of course, this isn't the correct answer to part (a).


$A_{v-overall}=0.9804$

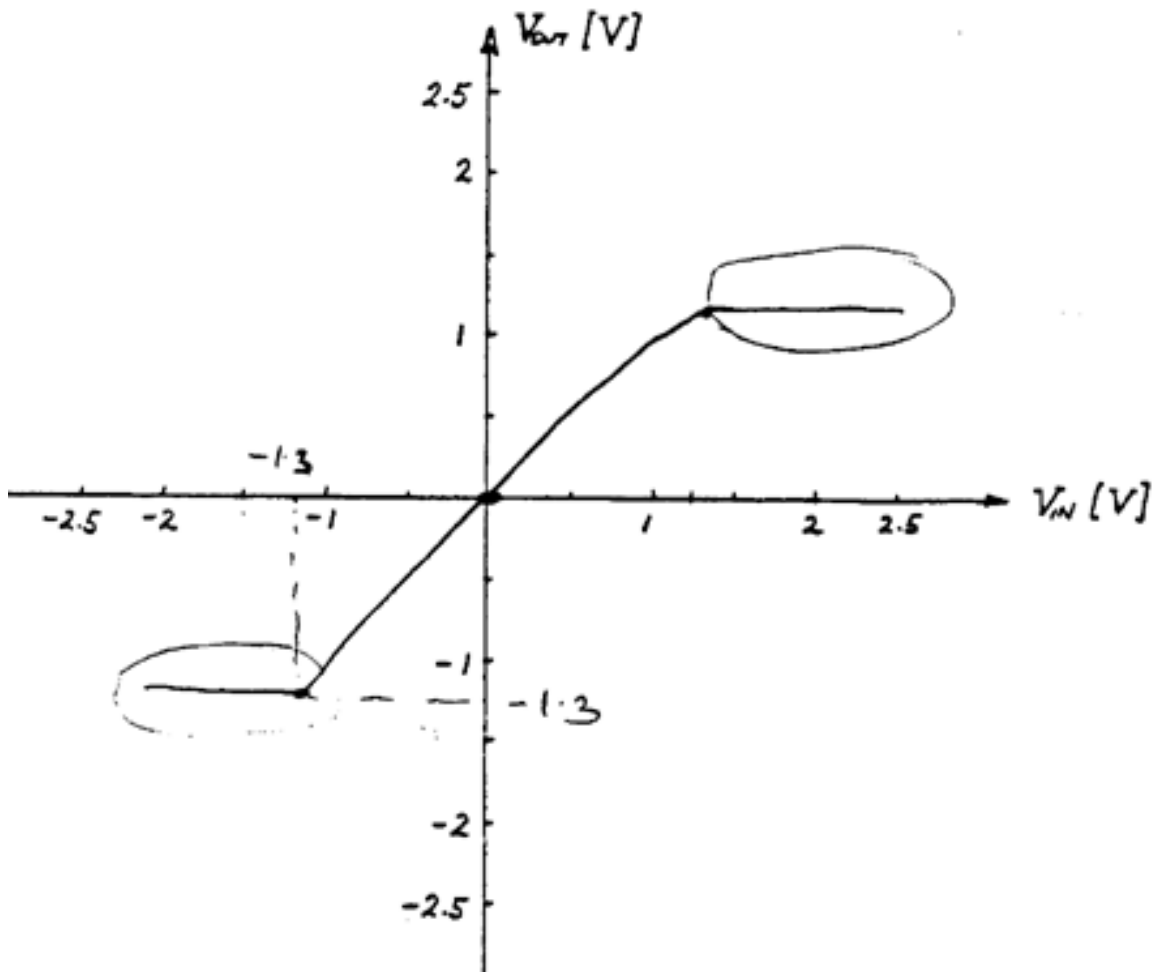e) [6 pts.] Sketch the transfer curve V_{OUT} versus V_{IN} for $-2.5 \leq V_{IN} \leq +2.5$ V on the graph below. For this part, R_L is infinity and $R_S=0$ V.

Hint: you should note that the current supplies each require at least $V_{SUP(min)}=0.5$ V in order to function.



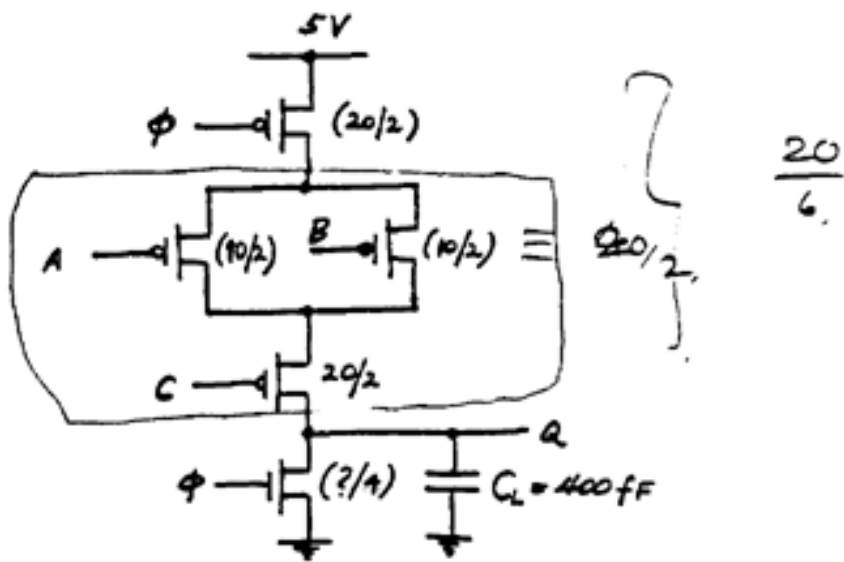
Problem #2: Digital Logic Gate [14 points]



a) [2 pts.] What is the logic operation performed by the above circuit? In other words, what is the logical expression for Q in terms of the three inputs A, B and C?

$Q = (\bar{A} + \bar{B}) \cdot \bar{C}$

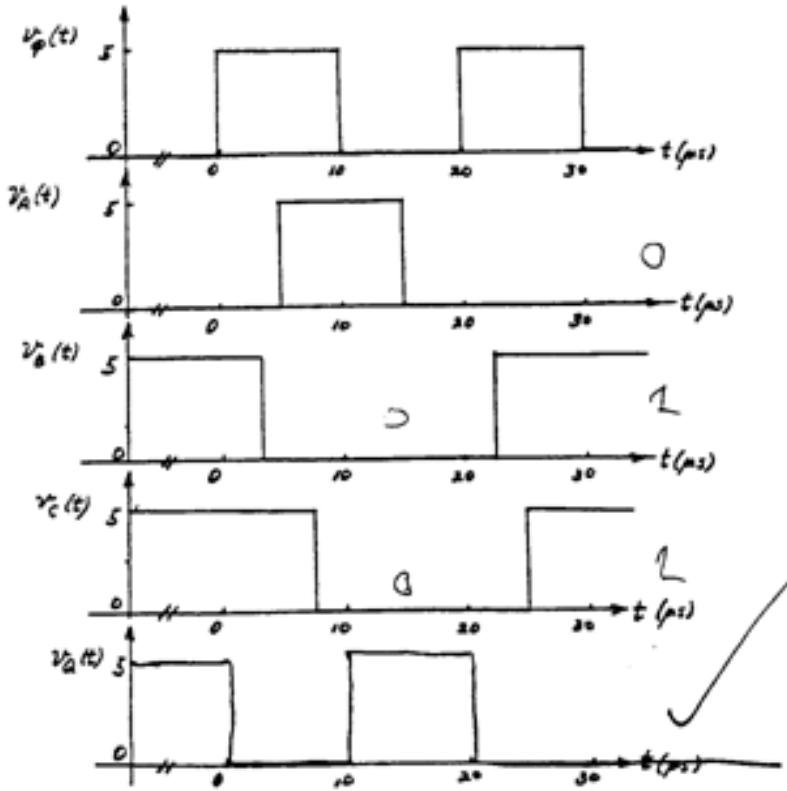b) [4 pts.] The graphs below plot the voltage waveforms over an interval of 35 microseconds. Fill in the output voltage waveform $v_Q(t)$ over $0 \Rightarrow 35 \mu\text{s}$. Note that the rise and fall times are essentially zero on this time scale.



c) [4 pts.] Find the numerical value of the **best case** low-to-high propagation delay (t_{PLH}) for this logic gate.


$t_{PLH} = 0.75 \text{ ns}$

d) [4 pts.] Find the width of the n-channel transistor such that the high-to-low propagation delay (t_{PLH}) is equal to your answer for part c). If you couldn't answer part c) you can assume for this part that $t_{PLH}(\text{best}) = 1 \text{ ns} = 10^{-9} \text{ s}$.

$W = 6.665 \text{ micrometers}$

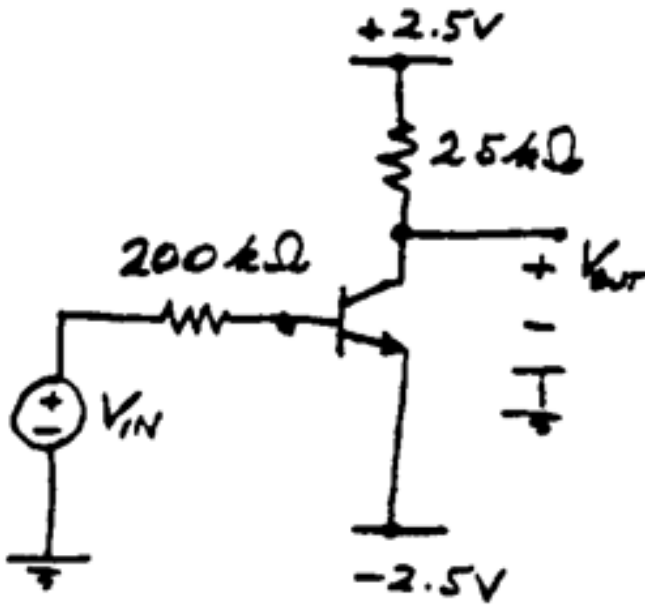Problem #3: Bipolar Transistor Physics [12 points]

NOTE: The default npn transistors do not apply for this problem!



GIVEN:


$$N_{dE} = 2 \times 10^{18} \text{ cm}^{-3}$$

$$N_{dB} = 10^{17} \text{ cm}^{-3}$$

$$N_{dC} = 10^{16} \text{ cm}^{-3}$$

The base and emitter widths are $W_B = W_E = 0.5$ micrometers. The electron diffusion coefficient in the base is $D_{nB} = 10 \text{ cm}^2/\text{s}$ and the hole diffusion coefficient in the emitter is $D_{pE} = 5 \text{ cm}^2/\text{s}$.

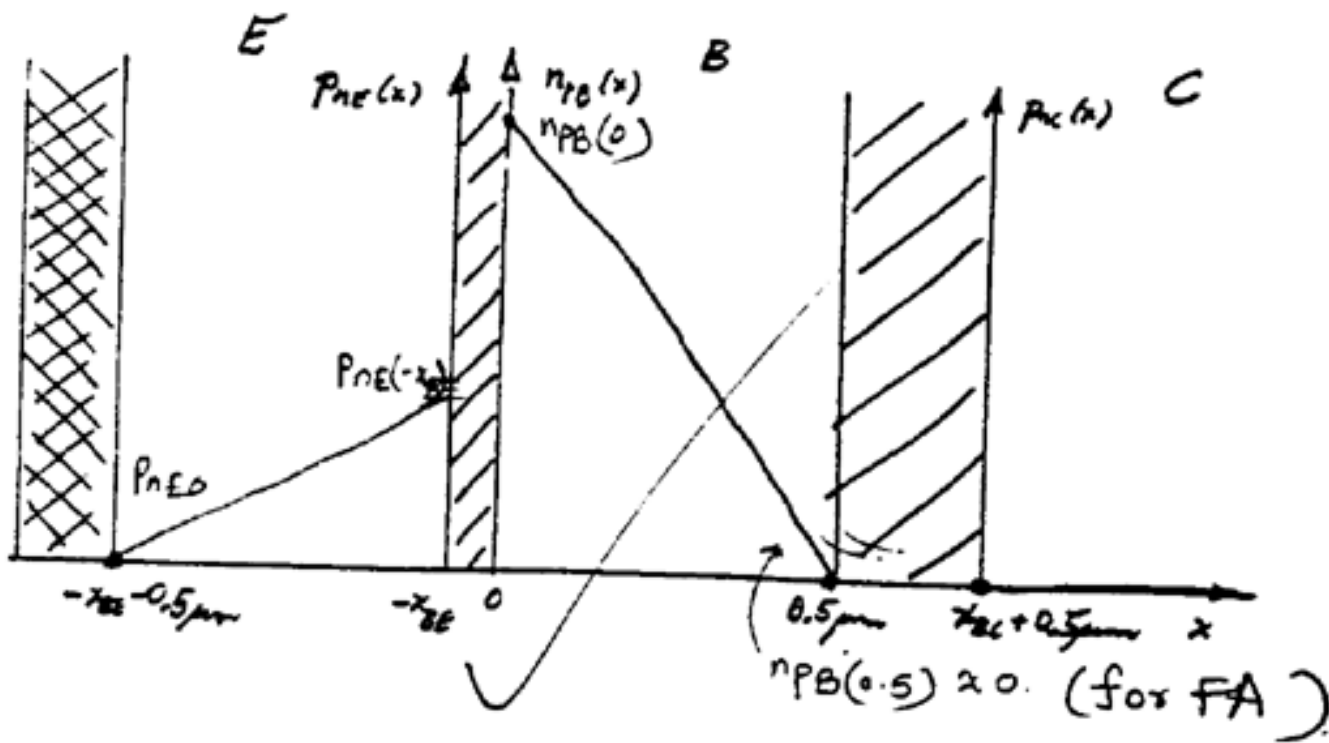a) [3 pts.] Qualitatively sketch the minority carrier concentrations in the emitter, base and collector on the graph below, assuming that the transistor is biased in the forward active region.



b) [3 pts.] For $V_{OUT}=0$ V what is the numerical value of the minority electron concentration at $x=0$, $n_{pB}(0)$? You can assume that the transistor is biased in the forward active region.

Not available

c) [3 pts.] What is the numerical value of the base current I_B for the bias condition in part b)? If you couldn't solve b) assume for this part that $n_{pB}(0) = 10^{15} \text{ cm}^{-3}$ -- not the correct answer to b), of course.

$I_B=2.5$ micro-amps

d) [3 pts.] What is the numerical value of V_{IN} in order that the transistor is biased in the forward active region with $V_{OUT}=0$ V?

Notes: You cannot assume that $V_{BE}=0.7$ V for this part. If you couldn't solve parts b) and c) you can assume that $n_{pB}(0)=10^{15} \text{ cm}^{-3}$ and that $I_B=4$ micro-amps. Neither of these answers are correct, of course.

$V_{IN}=3.277$ V

**Posted by HKN (Electrical Engineering and Computer Science Honor Society)
University of California at Berkeley
If you have any questions about these online exams
please contact <mailto:examfile@hkn.eecs.berkeley.edu>**