

EE 105, Fall 1992
Midterm #2
professor Howe

Closed book and notes; one formula sheet(both sides)

Do all work on exam pages

You have 50 min; use your time wisely

Problem #1

Bipolar Amplifier

Given: npn: $\beta_n=100$, Early voltage $V_{A_n}=100V$

pnp: $\beta_p=20$, Early voltage $V_{A_p}=50V$

The voltage V_{IN} is adjusted so that the DC output voltage level $V_{OUT}=0V$.

The resistances r_{oc} of the current sources are infinite. The various small-signal resistances referred to in parts(b)-(d) are defined on the schematic.

If you do not have time to find numerical values, leave the answer in symbolic form-be sure to include subscripts to identify which transistor the parameter is for.


(a) (3 pts) Find the DC values of V_{CE_1} , V_{EC_2} , and V_{CE_3} . You can neglect base currents.

(b) (3 pts) Find the numerical value of the input resistance R_i .

(c) (4 pts) Find the numerical value of the output resistance of the first stage, R_{o1} .


(d) (4 pts) Find the numerical value of the output resistance R_o . Given: the output resistance of the second stage is $R_{o2}=500K\Omega$.

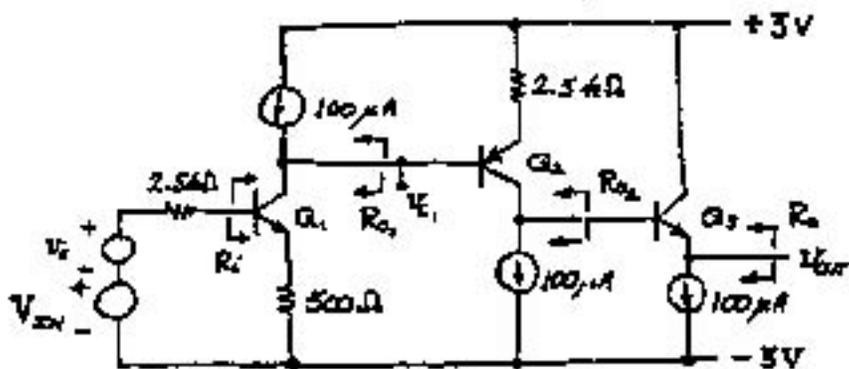(e) (4 pts) Find the numerical value of the small-signal voltage gain A_1 between the voltage source v_s and the collector of Q1: $A_1=v_{c1}/v_s$



Problem #2

(18 points) fancy MOS current source

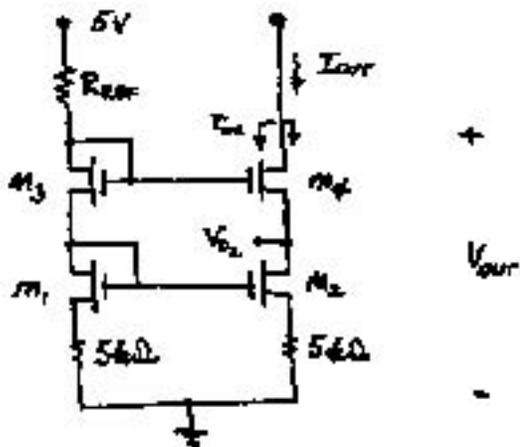

Given for all transistors: $(W/L)=32$, $\text{mobility} \cdot C_{ox}=100 \mu\text{A}/\text{V}^2$, $V_{Tn}=1\text{V}$, $\lambda_{\text{dan}}=0.01$.


- (a) (5 pts) Find the numerical value of $R(\text{REF})$ such that the output current is $I_{\text{OUT}}=100 \mu\text{A}$
- (b) (3 pts) Find the numerical value of the drain voltage of transistor M_2 , V_{D3} . If you could not solve part(a), assume that $R(\text{REF})=25\text{K}\Omega$, which is (of course) not the correct answer to part(a).
- (c) (5 pts) What is the minimum value of the output voltage V_{OUT} for which all transistors are saturated?
- (d) (5 pts) Find the numerical value of the output resistance r_{oc} of the current source. Given: $g_m \cdot r_o=800$ for all transistors.

Problem #3

Given: base-emitter junction is forward biased, base-collector junction is reverse biased, the base transport factor $\alpha(T)=1$ (meaning that no recombination occurs in the base).

Given: $D_n=20\text{cm}^2/\text{s}$, $D_p=10\text{cm}^2/\text{s}$. The area of the base-emitter junction is: $AE=10^{(-5)}\text{cm}^2$.

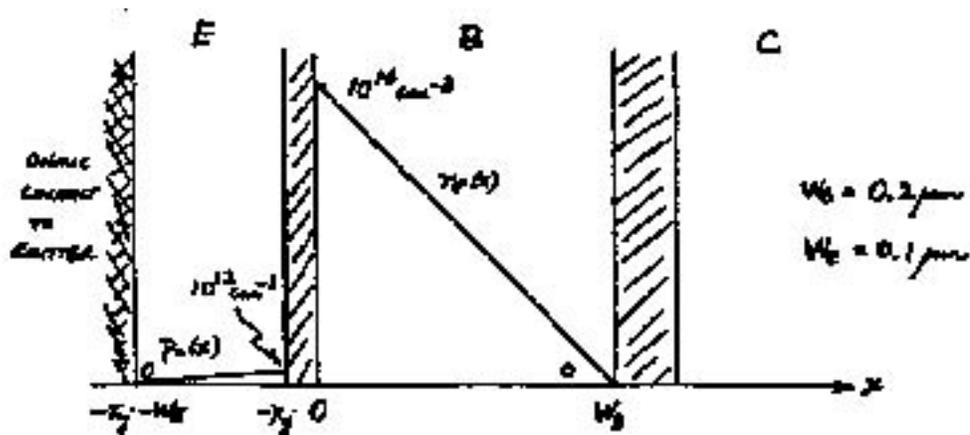- (a) (3 pts) What is the numerical value of the electron diffusion current density in the base (units: A/cm^2)
- (b) (3 pts) What is the numerical value of the hole diffusion current density in the emitter (units: A/cm^2)
- (c) (4 pts) What is the numerical value of the collector current I_C ?
- (d) (4 pts) What is the numerical value of the current gain?



Posted by HKN (Electrical Engineering and Computer Science Honor Society)
 University of California at Berkeley
 If you have any questions about these online exams
 please contact <mailto:examfile@hkn.eecs.berkeley.edu>