

**EE 105, Spring 1998**  
**Midterm #2**  
**Professor R.T. Howe**

(Note: Greek letters are in caps, "micro" is represented by a 'u'.)

Default bipolar transistor parameters:

*npn*:  $BETA_o = 100$ ,  $V_{An} = 50 \text{ V}$ ,  $V_{BE, oh} = 0.7 \text{ V}$ ,  $V_{CE, sat} = 0.2 \text{ V}$ ,  $V_{th} = 25 \text{ mV}$ .

Default MOS transistor parameters: note that LAMBDA depends on L!

*NMOS*:  $u_n C_{ox} = 50 \text{ uAV}^{-2}$ ,  $LAMBDA_n = [0.1/L] \text{ V}^{-1}$  ( $L$  in  $\text{um}$ ),  $V_{Tn} = 1 \text{ V}$ ,  $C_{ox} = 2 \text{ fF/um}^2$ ,  $C_{Jn} = 0.1 \text{ fF/um}^2$ ,  $C_{JSWn} = 0.5 \text{ fF/um}$ .

*PMOS*:  $u_p C_{ox} = 50 \text{ uAV}^{-2}$ ,  $LAMBDA_p = [0.1/L] \text{ V}^{-1}$  ( $L$  in  $\text{um}$ ),  $V_{Tp} = -1 \text{ V}$ ,  $C_{ox} = 2 \text{ fF/um}^2$ ,  $C_{Jp} = 0.1 \text{ fF/um}^2$ ,  $C_{JSWp} = 0.5 \text{ fF/um}$ .

**Problem #1 : Bipolar Transresistance Amplifier [20 points]**

Given:

$I_{SUP1} = 200 \text{ uA}$ ;  $R_{OC1} = 750 \text{ k}\Omega$


$V_{SUP1, min} = 0.15 \text{ V}, 0.45 \text{ V}$

$I_{SUP2} = 100 \text{ uA}$ ;  $R_{OC2} = 200 \text{ k}\Omega$

$V_{SUP2, min} = 0.3 \text{ V}$

$I_{BIAS} = -200 \text{ uA}$ ,  $V_{OUT} = 0 \text{ V}$

 - (a) [2 pts.] Identify the stages of this two-stage transresistance amplifier by labeling the two-ports below with "CE", "CB", or "CC" for common-emitter, common-base, or common-collector. Also, label node "X".



(b) [3 pts.] Find the numerical value of the small-signal input resistance of this amplifier,  $R_{in}$ .

*Your answer need only be correct to within (+/-)5% for full credit.*

(c) [3 pts.] Find the numerical value of the small-signal output resistance of this amplifier,  $R_{out}$ .

*Your answer need only be correct to within (+/-)5% for full credit.*


(d) [5 pts.] Find the numerical value of the "two-port" transresistance  $R_m$  of this amplifier (with  $R_s = \text{infinity}$  and  $R_L = \text{infinity}$ ). *Your answer need only be correct to within (+/-)5% for full credit.*

(e) [3 pts.] Find the numerical value of  $v_{out}/i_s$  for  $R_s = 500 \text{ OMEGA}$  and  $R_L = 10 \text{ kOMEGA}$ . If you couldn't solve parts (b)-(d), you can assume without loss of credit that  $R_{in} = 2.2 \text{ kOMEGA}$ ,  $R_{out} = 4 \text{ kOMEGA}$ ,  $R_m = -185 \text{ kOMEGA}$ . Needless to say, these are not the correct answers to (b)-(d).

(f) [2 pts.] Find the numerical value of the minimum output voltage  $V_{OUT, min}$  of this amplifier.


(g) [2 pts.] Find the numerical value of the maximum output  $V_{OUT, max}$  of this amplifier.

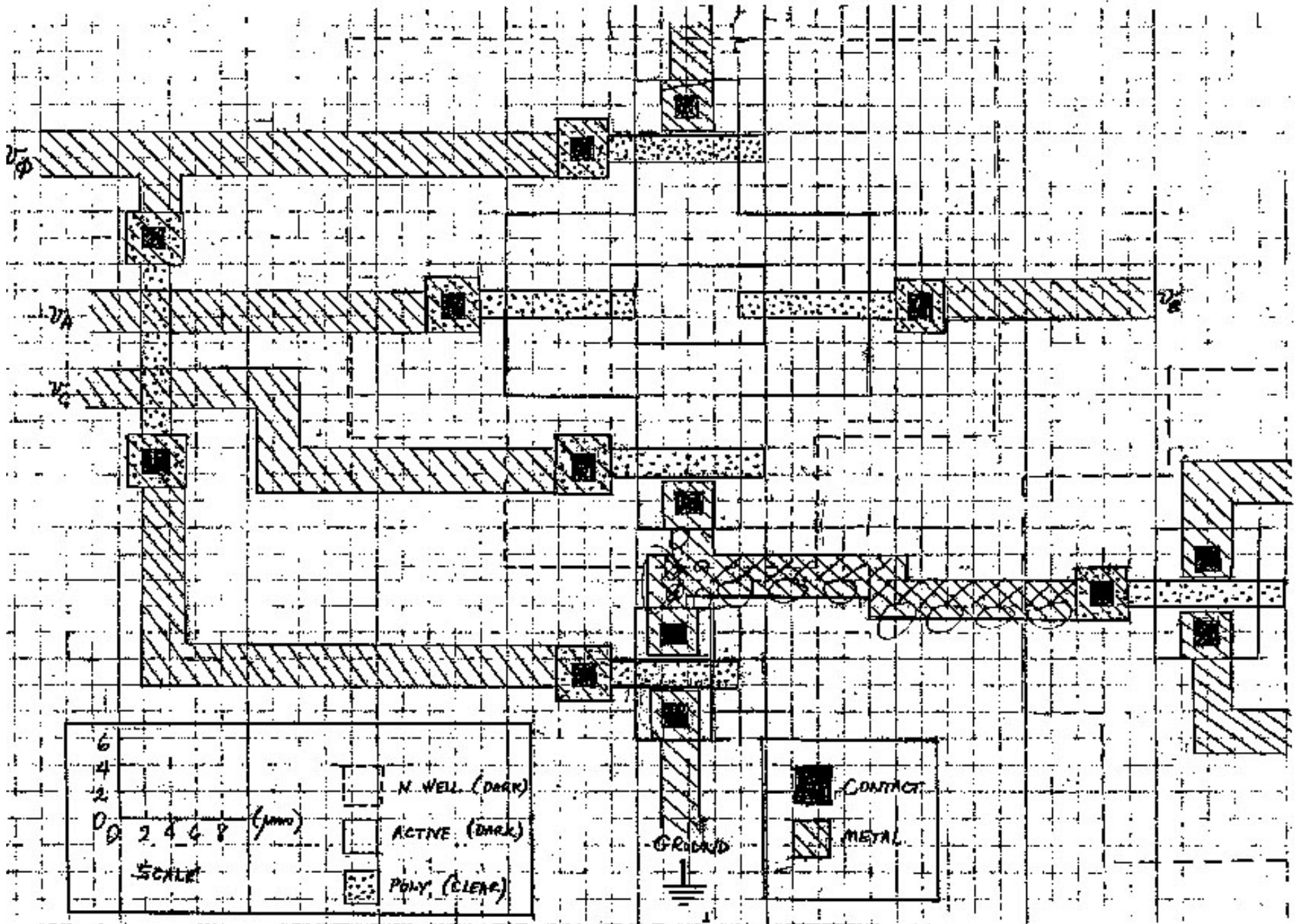**Problem #2 : CMOS Digital Logic Gate [20 pts.]**



(a) [5 pts.] Draw the schematic for this Logic gate, including the (W/L)'s of the transistors in ( $\mu\text{m}/\mu\text{m}$ ). Substrate and well contacts are omitted for this simplified layout; you can consider that the "select" mask is the same as the "n well" mask.

 (b) [2 pts.] Write the logic function implemented by this logic gate. If you couldn't do part (a), you can use the following circuit instead.



(c) [4 pts.] Find the numerical value of  $C_{db}$  for this logic gate in fF. You should identify clearly which areas on the layout contribute to  $C_{db}$ . Note that you don't need to have done part (a) in order to answer this part; useful device information is located on the cover page of the exam.


(d) [3 pts.] Find the numerical value of  $C_w$  for this logic gate in fF. Note that you don't need to have done part (a) in order to answer this part. The wiring capacitance per unit area is  $C_w = 0.1 \text{ fF}/\mu\text{m}^2$ .

(e) [2 pts.] Find the numerical value of  $C_g$  for this logic gate in fF. Note that you don't need to have done part (a) in order to answer this part.

(f) [2 pts.] What is the worst-case *charging* current for the load capacitance  $C_L$  for this amplifier in  $\mu\text{A}$ ? If you couldn't do part (a), you can use the substitute logic gate given in part (b).

(g) [2 pts.] What is the worst-case *discharging* current for  $C_L$  of this amplifier in  $\mu\text{A}$ ? If you couldn't do part (a), you can use the substitute logic gate given in part (b).
 
### Problem #3 : Current Sources [10 points]



- (a) [4 pts.] Using exactly 4 transistors, draw the circuit schematic of a CMOS current source that will implement  $i_{SUP}$  (sourcing current from the positive supply), using  $I_{REF}$  as a reference.
- (b) [3 pts.] Given:  $I_{REF} = 25 \mu\text{A}$  and  $I_{SUP} = 75 \mu\text{A}$ . If all except one of the transistors have widths  $W = 10 \mu\text{m}$  and all of the transistors have lengths  $L = 2 \mu\text{m}$ , find the width of the remaining transistor. There may be more than one correct answer to this part.
- (c) [3 pts.] Find the maximum voltage  $V_{OUT, max}$  for which this current supply will have all of its transistors in operating the constant-current region. If you were unable to solve (b), assume that the width of the PMOS current-source output transistor is  $W = 100 \mu\text{m}$ .

---

**Posted by HKN (Electrical Engineering and Computer Science Honor Society)**  
**University of California at Berkeley**  
 If you have any questions about these online exams  
 please contact <mailto:examfile@hkn.eecs.berkeley.edu>