

Electrical Engineering 40/40I/41I

Midterm 2 - Fall 1995

Professors S. Schwarz (40) and R.M. White (40I/41I)

Problem 1 [21%]: Phasors

(a) Put a cross (X) by each of the expressions below which could be a phasor voltage:

$$\underline{\quad} 3e^{j(\omega t + \phi)} \quad \underline{\quad} 3\cos(\omega t + 27^\circ) \quad \underline{\quad} 3\sin(\omega t + \pi) \quad \underline{\quad} 3 + j7$$

$$\underline{\quad} (3 + j7)\cos(\omega t + 27^\circ) \quad \underline{\quad} +3j \quad \underline{\quad} -3j \quad \underline{\quad} 3e^{j0.3} \quad \underline{\quad} (3 + j7) / (4 - j10)$$

(b) Write expressions for the real currents for each of the following, assuming that the frequency $f=60\text{kHz}$ and $I_0=10\text{mA}$, using the convention of the text. (Angles are in radians.)

$$I_0 e^{j3}$$

$$I_0 (3 + j4)$$

$$jI_0 e^{j\pi/2}$$

(c) Convert the following real expression to the corresponding phasors:


$$v(t) = 4 \sin(377t) \text{ mV}$$

$$v(t) = 12 \cos(377t - \pi/2) \text{ mV}$$


$$v(t) = \left(\sqrt{\frac{1}{2}} \right) \sin(377t - \pi/4) \text{ mV}$$

Problem 2 [21%]: Circuit Elements


- (a) [3%] List two passive circuit elements that store energy:
- (b) [9%] Suppose that in a portion of the circuit for an electronic door opener you need an impedance having a 10-ohm real part and a 30-ohm negative reactive part at a frequency of 60kHz. Show two circuits that provide this.
- (c) [9%] In this circuit I_0 is a sinusoidal ideal current source with amplitude 1mA, $C=1\ \mu\text{F}$, $R=1000\ \Omega$, $f=60\text{Hz}$. Find the amplitude of the sinusoid V .

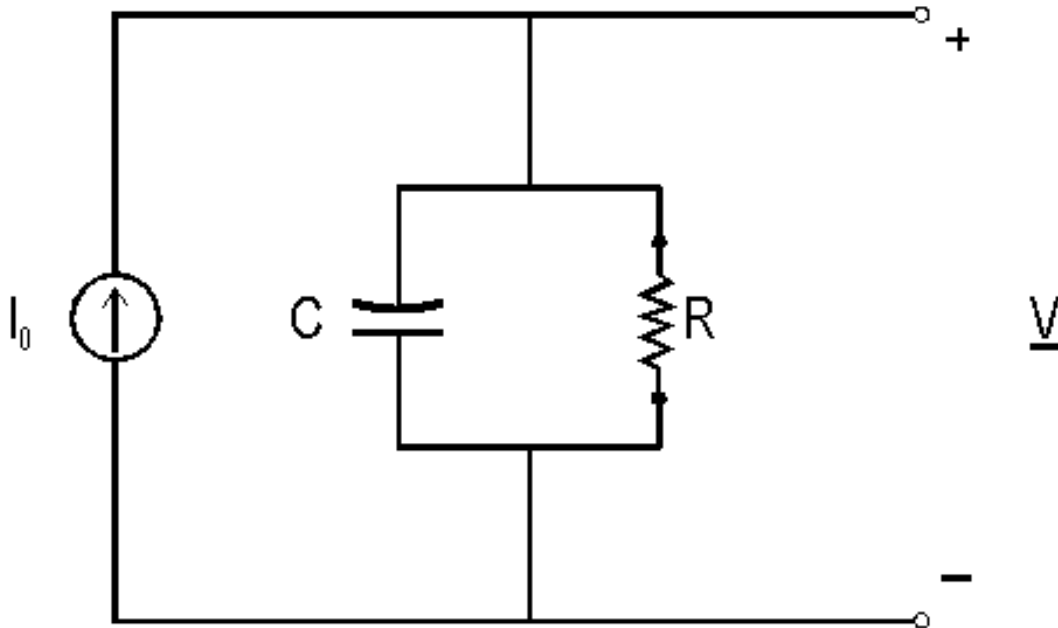

Page 2

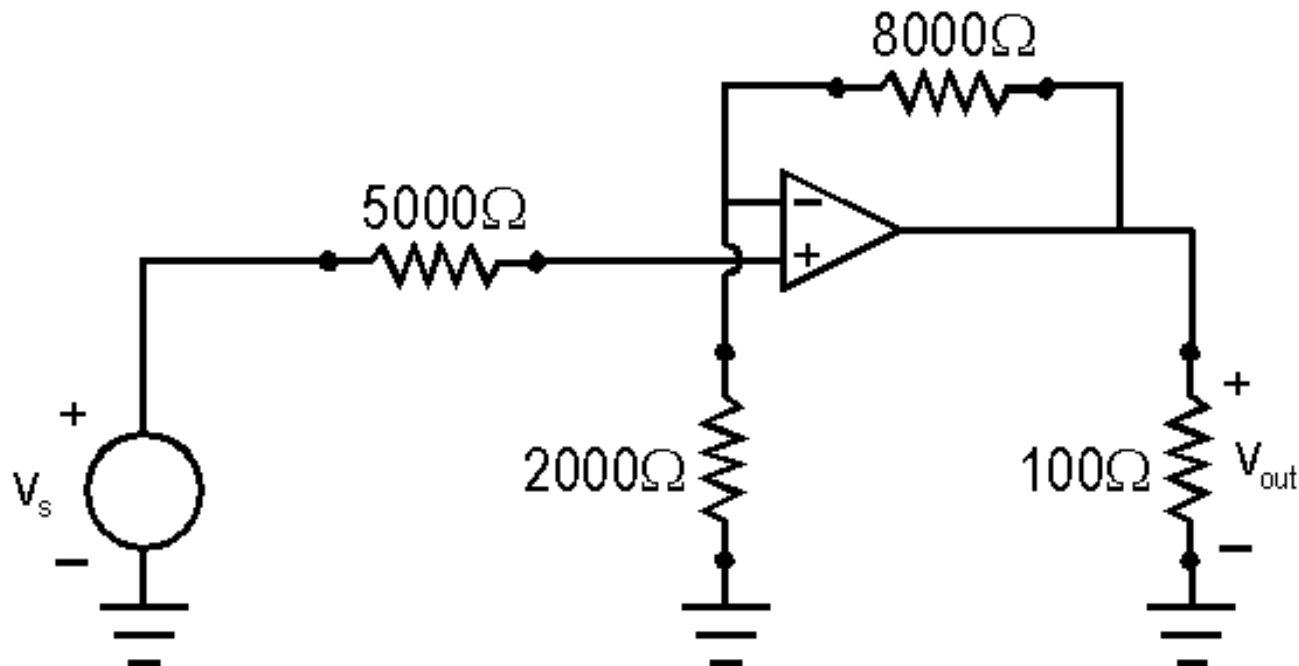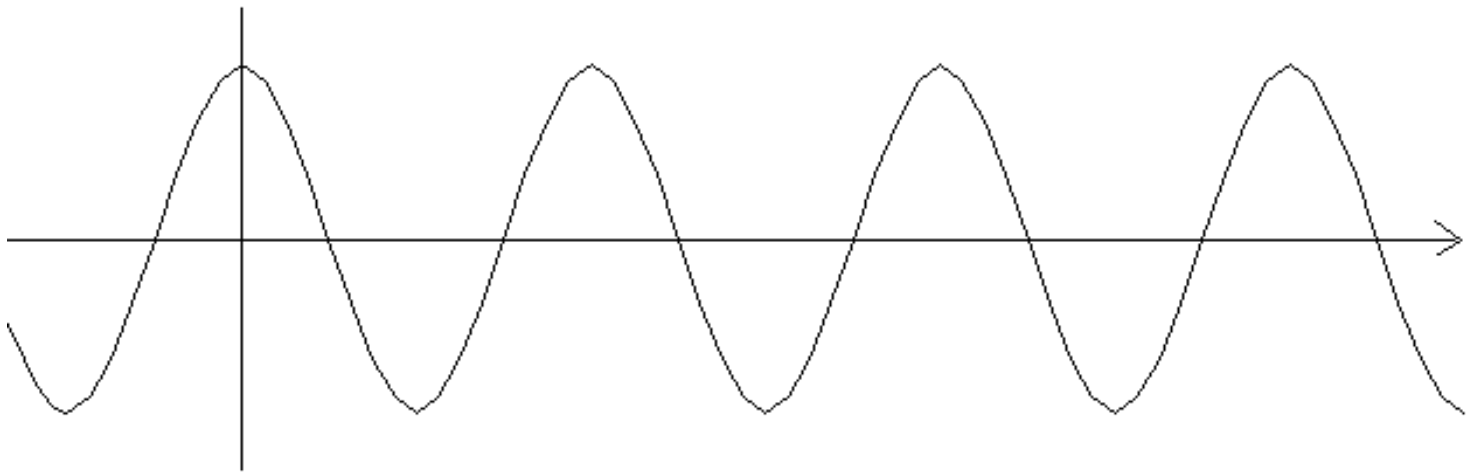Problem 3 [18%]: Op-Amps

The voltage $v_s(t)$ is an endless sinusoid with frequency 1MHz and amplitude 2V, as shown here:



(a) Assume the op-amp is completely ideal and its power-supply voltages are $\pm 15\text{V}$. Sketch v_{out} showing vertical scale and maximum values.



Page 3

(b) Same question as (a), except the op-amp has maximum output current of 50mA . Show the vertical scale and maximum values.




(c) Same question as (a); op-amp is completely ideal except that it has a finite gain-bandwidth product of $1\text{E}6\text{ 1/s}$. Show

the amplitude scale and maximum values.




Page 4


Problem 4 [20%]: Diodes

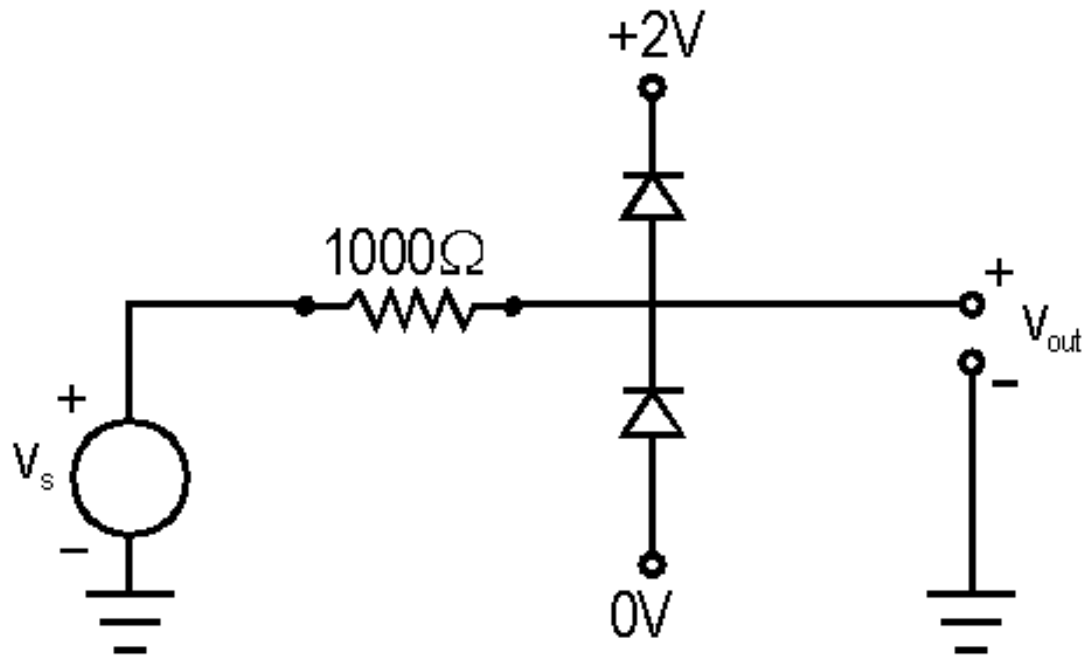

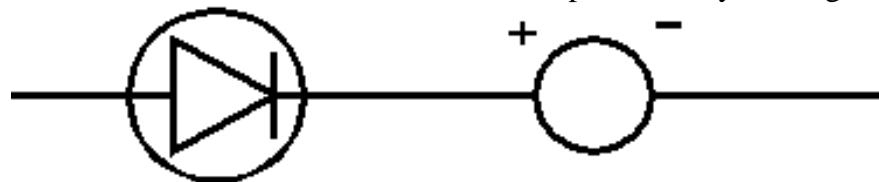In the above circuit, the diodes are to be represented by the large signal diode model, (the one that looks like this:)




(a) Suppose $v_s(t)$ is

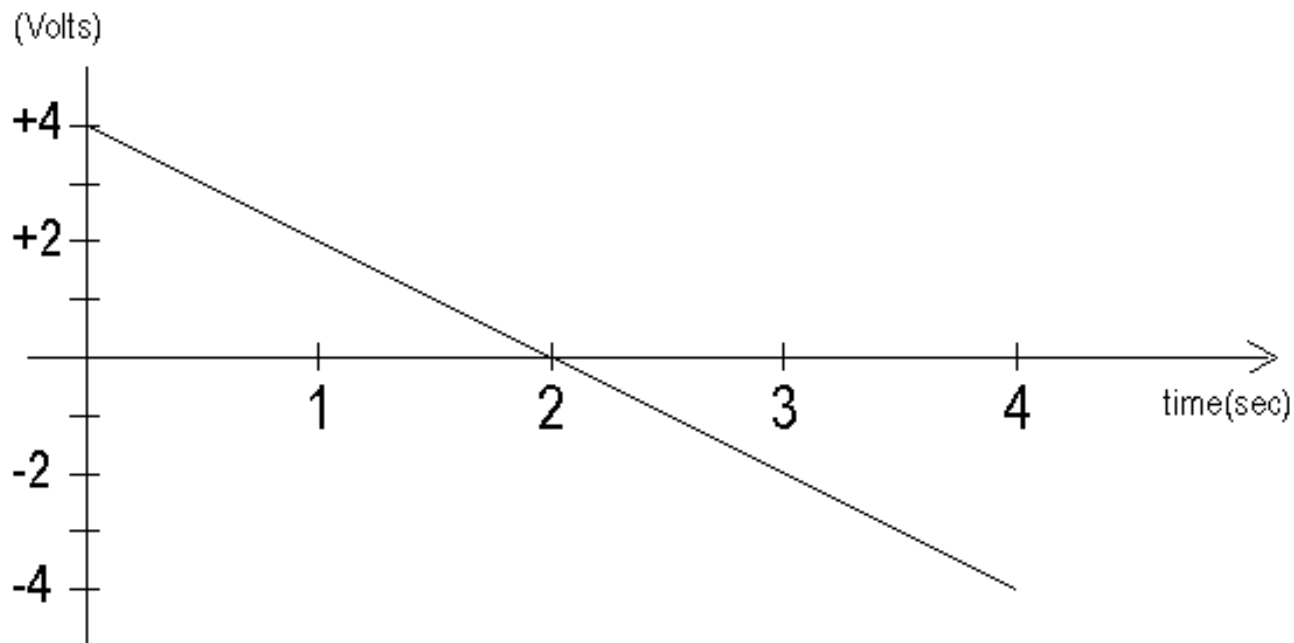

Graph $v_{out}(t)$ clearly on the same set of axes.

(b)

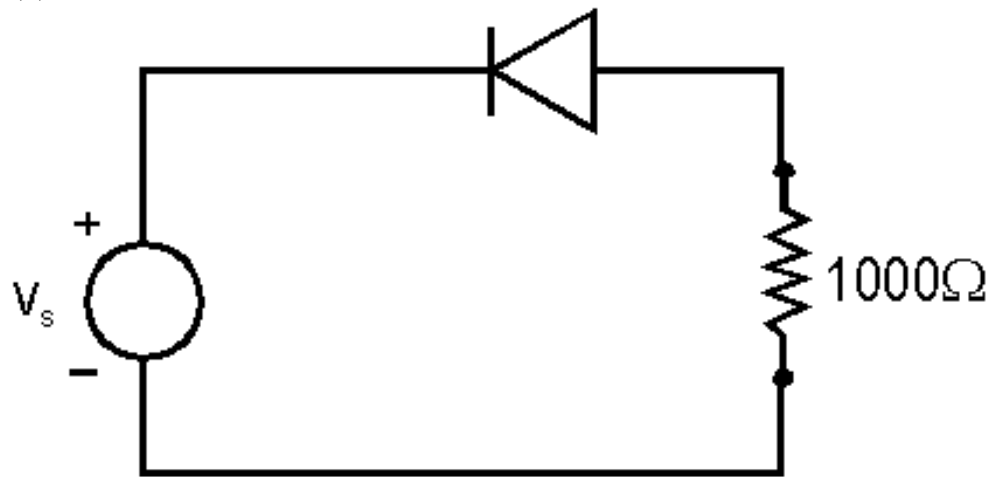

v_s and the diode are the same as in part (a). Find the time-averaged power dissipated in the diode, averaged over the 4-second period.


Page 5

Problem 5 [20%]: RC Circuits and Bode Plots

This problem relates to a probe often used with oscilloscopes to prevent them from adversely affecting circuits whose voltages they measure.

(a) The basic idea of the probe is shown here: The ideal oscilloscope would be connected at terminals C-D and the probe would be connected to the circuit under test at A-B. (Resistor R_p represents an actual resistor built into the probe, and resistor R_{in} represents the input resistance of the oscilloscope.)

Sketch the Bode plot in dB of $|v_{out}/v_{in}|$ for this circuit. Indicate slopes and break frequencies (if any).

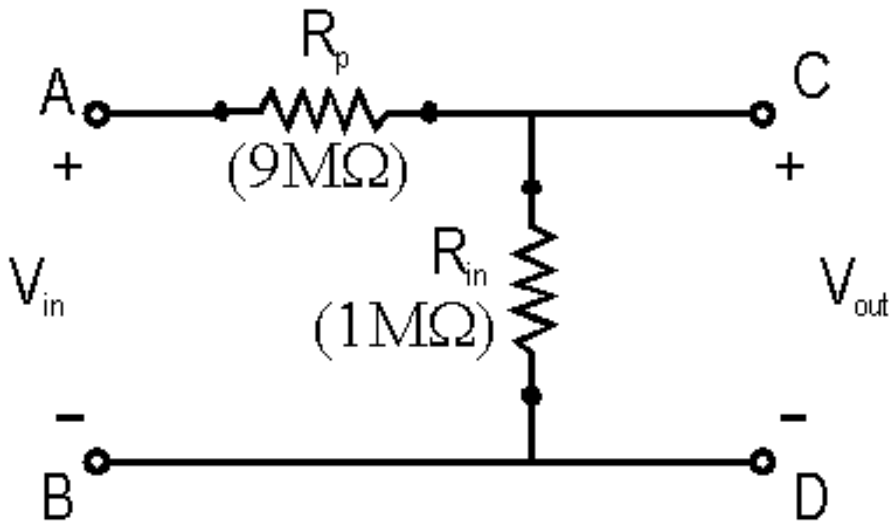

$$\left| \frac{v_{out}}{v_{in}} \right| (dB)$$



Page 6

(b) Sketch the Bode plot for another circuit in which

$$\left| \frac{v_{out}}{v_{in}} \right| = \frac{10^6 + 100\omega^2}{\omega \sqrt{\omega^4 + 10^{12}}}$$

Indicate slopes and break frequencies (if any).

$$\left| \frac{v_{out}}{v_{in}} \right| (dB)$$



Page 7



© 1995 by Schwarz and White
translated to HTML by Walter Hsiao
Eta Kappa Nu (November 1995)