

ECS 40, Fall 2008
Prof. Chang-Hasnain
Test #2
Version A

10:10 am – 11:00 am, Monday October 27, 2008

Total Time Allotted: 50 minutes

Total Points: 100

1. This is a closed book exam. However, you are allowed to bring one page (8.5" x 11"), double-sided notes.
2. No electronic devices, i.e. calculators, cell phones, computers, etc.
3. SHOW all the steps on the exam. Answers without steps will be given only a small percentage of credits. Partial credits will be given if you have proper steps but no final answers.
4. **Remember to put down units. Points will be taken off for missed unit.**

Last (Family) Name: _____


First Name: _____

Student ID: _____ Discussion Session: _____

Signature: _____

Score:	
Problem 1 (40 pts)	
Problem 2 (24 pts)	
Problem 3 (16 pts)	
Problem 4 (20 pts)	
Total	

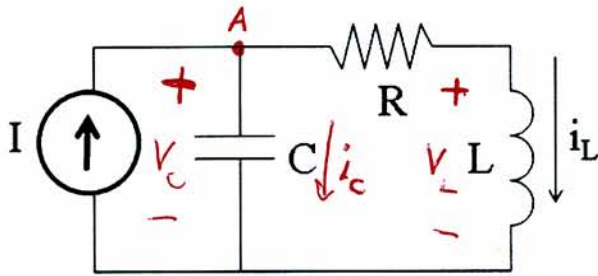Problem 1: Transient Response of RLC circuits (40 pts)
 Consider the circuit shown below



a) Derive the differential equation for $i_L(t)$ (20 pts)

$$\text{KVL: } V_c = R i_L + V_L = R i_L + L \frac{d i_L}{d t} \quad (1)$$

$$\text{KCL@A: } I - i_L = i_c = C \frac{d V_c}{d t} \quad (2)$$

Differentiate (1)

$$\frac{d V_c}{d t} = R \frac{d i_L}{d t} + L \frac{d^2 i_L}{d t^2} \quad (3)$$

Plug (3) \rightarrow (2)

$$I - i_L = C R \frac{d i_L}{d t} + L C \frac{d^2 i_L}{d t^2}$$

Rearranging

$$\frac{d^2 i_L}{d t^2} + \frac{R}{L} \frac{d i_L}{d t} + \frac{1}{L C} i_L = \frac{I}{L C}$$

Solution: $\frac{d^2 i_L}{d t^2} + \frac{R}{L} \frac{d i_L}{d t} + \frac{1}{L C} i_L = \frac{I}{L C}$

- b) Let $L = 1$ H, $C = 1/3$ F, $R = 4$ Ω , $I = 2$ A. What is the undamped resonant frequency ω_0 ?
It is ok to express your answer as a square root. (5 pts)

$$\omega_0^2 = \frac{1}{LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(1)(1/3)}}$$

$$\omega_0 = \sqrt{3} \frac{\text{rad}}{\text{sec}}$$

$$\omega_0 = \sqrt{3} \frac{\text{rad}}{\text{sec}}$$

- c) What is the damping ratio ζ ? Is this system over-, critically, or under-damped?
Again, it is ok to have square roots in your answer. (10 pts)

$$2\zeta\omega_0 = \frac{R}{L}$$

$$\zeta = \frac{R}{2L\omega_0} = \frac{4}{2(1)(\sqrt{3})} = \frac{2}{\sqrt{3}}$$

$$\zeta = \frac{2}{\sqrt{3}}$$

$$\zeta = \frac{2}{\sqrt{3}} > 1 \Rightarrow \text{overdamped}$$

- overdamped
 critically damped
 underdamped

- d) Write down the general form of the solution. Give numerical values for the forced response. You don't need to solve for any other constant (K_1 , K_2 , $s_{1,2}$ etc.) (5 pts)

Solution for overdamped case:


$$i_L(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t} + f(t)$$

@ steady-state $\frac{d^2 i_L}{dt^2} = \frac{d i_L}{dt} = 0 \Rightarrow \frac{1}{LC} i_L = \frac{1}{LC} I \Rightarrow i_L(t) = I = 2$ [A]

$$i_L(t) = K_1 e^{s_1 t} + K_2 e^{s_2 t} + 2 \text{ [A]}$$

Problem 2: 2nd-Order Circuit (24 points)

Consider the circuit shown below

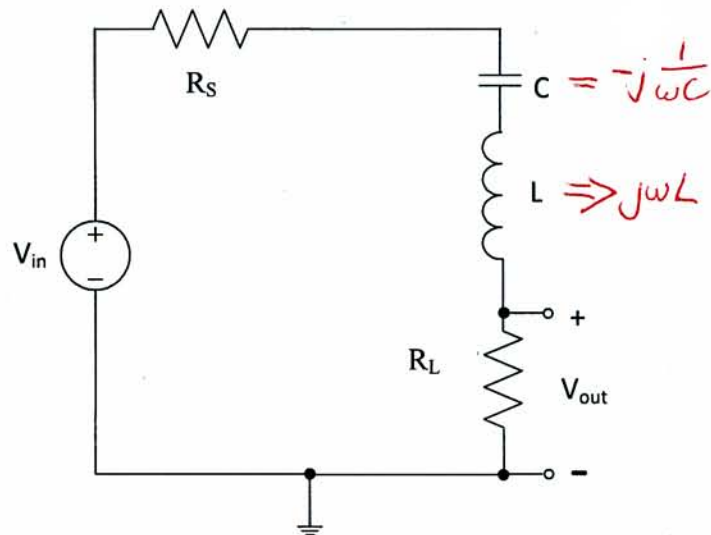

- (a) Using complex impedances, derive the transfer function $H(\omega) = V_{out}/V_{in}$ as a function of R_s , C , L and R_L . (12 pts)

Bring your answer into one of the standard forms known from lecture (high-pass, low-pass band-pass, band-reject (notch) filter)

$$H(\omega) = \frac{R_L}{R_L + R_s + j\left(\omega L - \frac{1}{\omega C}\right)}$$

Series RLC $\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$

$$H(\omega) = \frac{R_L}{R_L + R_s + j\left(\frac{\omega L \frac{1}{\sqrt{LC}}}{\frac{1}{\sqrt{LC}}} - \frac{1}{\omega \frac{1}{\sqrt{LC}}}\right)} = \frac{R_L}{R_L + R_s + j\left(\frac{\omega \sqrt{L/C}}{\frac{1}{\sqrt{LC}}} - \frac{1}{\omega \sqrt{L/C}}\right)}$$

$$H(\omega) = \frac{R_L}{R_L + R_s + j\sqrt{\frac{L}{C}}\left(\frac{\omega}{\frac{1}{\sqrt{LC}}} - \frac{1}{\omega}\right)} = \frac{\frac{R_L}{R_L + R_s}}{1 + j\frac{1}{R_L + R_s}\sqrt{\frac{L}{C}}\left(\frac{\omega}{\frac{1}{\sqrt{LC}}} - \frac{1}{\omega}\right)}$$

$$H(\omega) = \frac{K}{1 + jQ\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)}$$

$$H(\omega) = \frac{\frac{R_L}{R_L + R_s}}{1 + j\frac{1}{R_L + R_s}\sqrt{\frac{L}{C}}\left(\frac{\omega}{\frac{1}{\sqrt{LC}}} - \frac{1}{\omega}\right)}$$

(b) What type of filter does this circuit implement? (3 pts)

- | | |
|--|---|
| <input type="radio"/> Low-pass | <input type="radio"/> High-pass |
| <input checked="" type="radio"/> Band-pass | <input type="radio"/> Band-reject (Notch) |

(c) Depending on your answer in part b), answer one of the following 3 questions ((i) – (iii)) (9 pts)

(i) If your answer in part b) is either high- or low-pass filter:

Write down the break frequency ω_B , the slope of $|H(\omega)^2|$ in dB/decade for very small and very high frequencies respectively as well as the order of the filter.

$\omega_B =$
slope =
order =

(ii) If your answer in part b) is band-pass filter:

Write down the resonance frequency ω_0 , the quality factor Q of the filter as well as the slope of $|H(\omega)^2|$ in dB/decade for very small and very high frequencies.

$$\begin{aligned}\omega_0 &= \frac{1}{\sqrt{LC}} \\ Q &= \frac{1}{R_L + R_S} \sqrt{\frac{L}{C}} \\ \text{slope } (\omega \ll) &= 20 \frac{\text{dB}}{\text{dec}} \\ \text{slope } (\omega \gg) &= -20 \frac{\text{dB}}{\text{dec}}\end{aligned}$$


(iii) If your answer in part b) is band-reject (notch) filter:

Write down the resonance frequency ω_0 , the quality factor Q of the filter as well as the values of $|H(\omega)^2|$ in dB for very small and very high frequencies.

$$\begin{aligned}\omega_0 &= \\ Q &= \\ |H(\omega \ll)| &= \\ |H(\omega \gg)| &= \end{aligned}$$

Problem 3: 1st Order Bode Plots (16 pts)

Consider the circuit shown below

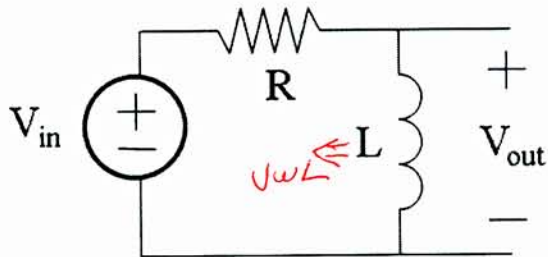

- a) Using complex impedances, derive the transfer function $H(\omega) = V_{out}/V_{in}$ as a function of R and L (6 pts)

$$H(\omega) = \frac{j\omega L}{R + j\omega L} = \frac{1}{\frac{R}{j\omega L} + 1} = \frac{1}{1 - j\frac{R}{\omega L}}$$

$$H(\omega) = \frac{1}{1 - j\frac{R}{\omega L}}$$

- b) What is ω_B or ω_0 (depending on the transfer function you came up with in a)) of the system? (Give your answer again as a function of R and L) (2 pts)

$$\frac{\omega_0}{\omega} = \frac{R}{\omega L}$$
$$\omega_0 = \frac{R}{L}$$


$$\omega_B \text{ OR } \omega_0 = \frac{R}{L}$$

c) What type of filter does this circuit implement? (2 pts)

<input type="radio"/> Low-pass	<input checked="" type="radio"/> High-pass
<input type="radio"/> Band-pass	<input type="radio"/> Band-reject (Notch)

d) Sketch the magnitude Bode plot on the graph below. Make sure you mark all important characteristics of your graph (important values of ω , slopes, pass-band value). (6 pts)

Be aware of the fact that the frequency axis is logarithmic

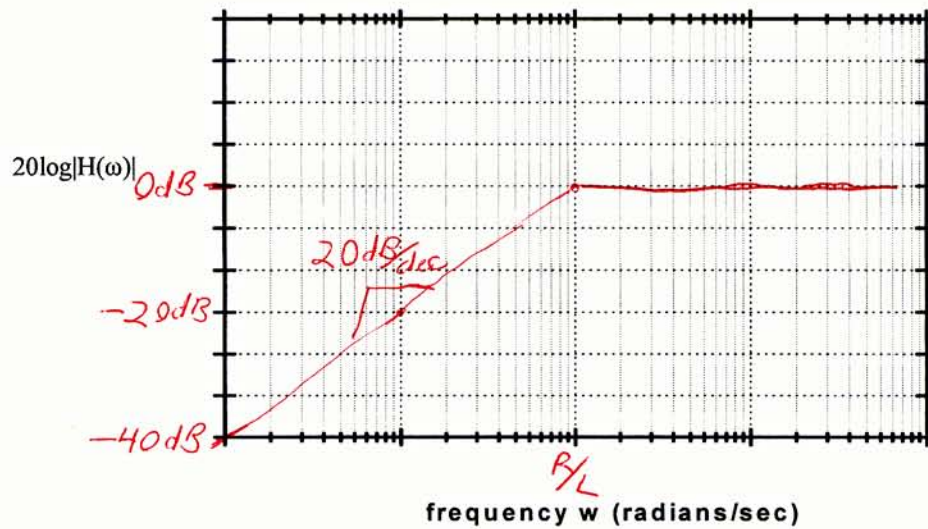

Problem 4: Bode Plots (20 pts)

Given is the following transfer function:

$$H(\omega) = \frac{K}{1 + jX\left(\frac{\omega}{Y} - \frac{Y}{\omega}\right)}$$

where $K = 0.5$ and $Y = 100$

In the graphs below sketch the amplitude and phase transfer functions for the two cases where $X = 1$ and $X = 10$. Make sure you clearly mark important characteristics (any slopes of magnitude response as well as magnitude and phase at $\omega=Y$) in your graphs and you clearly indicate any differences between the two cases.

Be aware of the fact that the frequency axis is logarithmic.

