

University of California at Berkeley
College of Engineering
Dept. of Electrical Engineering and Computer Sciences

EECS 40 Midterm II

Fall 1998

Prof. Roger T. Howe

November 19, 1998


Name: _____**Student ID:** _____**Guidelines**

1. Closed Book and notes; one 8.5" x 11" page (both sides) of your own notes is allowed.
2. You may use a Calculator
3. Do not unstaple the exam.
4. Show all your work and reasoning on the exam in order to receive full or partial credit.

Score

Problem	Possible Points	Score
1	24	
2	18	
3	8	
Total	50	

 1. Integrated Circuit Structure [24 points]



Process Sequence:

1. Starting Material: boron-doped silicon, concentration $5 \times 10^{16} \text{ cm}^{-3}$
2. Deposit 250 nm of silicon dioxide and pattern using the **oxide mask** (dark field)
3. Implant phosphorus and anneal (depth 500 nm and concentration $1.25 \times 10^{17} \text{ cm}^{-3}$)
4. Deposit 250 nm of silicon dioxide and then etch 250 nm of oxide using the **via mask** (dark field).
5. Deposit 250 nm of arsenic-doped polysilicon and pattern using the **polymask** (clear field). The arsenic concentration is $5 \times 10^{18} \text{ cm}^{-3}$
6. Deposit 250 nm of silicon dioxide and then etch 500 nm of oxide using the **contact mask** (dark field).
7. Deposit 500 nm of aluminum and pattern using the **metal mask** (clear field).

Given :	single crystal silicon:	$\mu_n = 1000 \text{ cm}^2 / (\text{Vs})$	$\mu_p = 400 \text{ cm}^2 / (\text{Vs})$
	polysilicon:	$\mu_n = 100 \text{ cm}^2 / (\text{Vs})$	$\mu_p = 50 \text{ cm}^2 / (\text{Vs})$

(a) [8 pts.] Sketch the cross section **A-A'** on the graph below. Identify all layers clearly.


(b) [8 pts.] Sketch the cross section **B-B'** on the graph below. Identify all layers clearly.

(c) [2 pts] What is the sheet resistance $R_{\text{square, poly}}$ of the polysilicon layer in ohms/square? Given : the magnitude of the hole or electron charge is $1.6 \times 10^{-19} \text{ C}$.

(d) [2 pts.] What is the sheet resistance $R_{\text{square, implant}}$ of the phosphorus-implanted layer [ohm/square]?

(e) [4pts] What is the numerical value of the resistance between terminals 1 and 2? You can neglect the "end squares" at connections between the conducting layers. If you have no answers for parts (c) and (d), you can use $R_{\text{square, poly}} = 250$ ohms/square for the polysilicon layer and that $R_{\text{square, implant}} = 150$ ohms/square for the phosphorus implanted layer for this part.

2. CMOS inverter pair [18 points]

 

Gate capacitance:

$$C_{ox} = 2 \text{ fF}/\mu\text{m}^2$$

PMOS:

$$\text{Width} = W_p = 3 \mu\text{m}$$

$$\text{Length} = L_p = 0.5 \mu\text{m}$$

$$\text{"on" resistance} = R_p = 200 \Omega$$

NMOS:


$$\text{Width} = W_n = 2 \mu\text{m}$$

$$\text{Length} = L_n = 0.5 \mu\text{m}$$

$$\text{"on" resistance} = R_n = 150 \Omega$$

 (a) [4pts.] This inverter pair has been "at rest" for some time with its input "high." The wave for $v_{in1}(t)$ is sketched

below. Draw the switch-model circuit for finding the output voltage $v_{out1}(t)$ of inverter 1 for $t > 0$. Provide some numerical values for the circuit elements. You can neglect the drain-bulk capacitances and any wire capacitance.



(b) [4 pts.] Determine the wave form $v_{out1}(t)$ for $t > 0$.


(c) [4pts.] Due to contamination of the gate oxide furnace, you discover that the gate oxide is not a perfect insulator, but instead is modeled by a resistance $R_G = 1 \text{ k}\Omega$ in parallel with the gate-source capacitance (C_{Gn} for the NMOS, C_{Gp} for the PMOS). Repeat part (a) using these "leaky" NMOS and PMOS transistors for both inverters.

(d) [3pts] What is the value of $v_{out1}(t)$ ($t < 0$) for the circuit in part (c), assuming the input wave form $v_{in1}(t)$ that is given in

part (a). Note that the inverter has had a "high" input for a long time before its input transitions at $t = 0$.

(e) [3pts.] What is the value of $v_{out1}(t)$ (t approaches infinity) for the circuit in part (c), assuming the input waveform $v_{in1}(t)$ that is given in part (a). Hint: consider superposition.

3. Bond wire inductance [8 points]

 

(a) [5pts] The bond wire can be modeled by a 1 nH inductor. Given the wave form for the supply current $i_s(t)$, plot the voltage drop across the bondwire $v_{bw}(t)$ on the graph below.

(b) [3pts] A particular circuit can tolerate at most $|v_{bw}(t)| = 250$ micro - V for a critical application. How many bondwires are needed to meet this requirement, given the $i_s(t)$ waveform? Hint: consider whether series or parallel bond wires will help.

**Posted by HKN (Electrical Engineering and Computer Science Honor Society
University of California at Berkeley
If you have any questions about these online exams
please contact <mailto:examfile@hkn.eecs.berkeley.edu>**