





Electrical Engineering 40/40I/41I

Midterm 1 - Fall 1995

Professors S. Schwarz (40) and R.M. White (40I/41I)

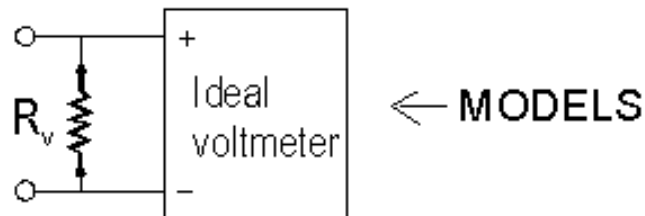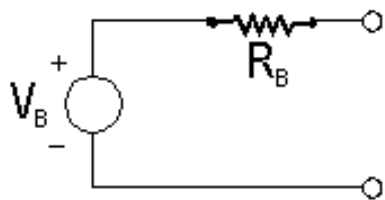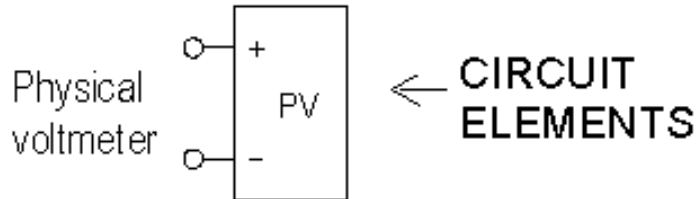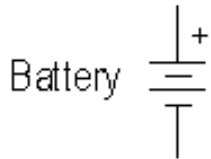
Problem 1: [25%]

Circuit models for a battery and a physical voltmeter are shown below:




$$R_v = 1\text{M}\Omega \quad (10^6 \text{ ohms})$$

A circuit is constructed as shown below:

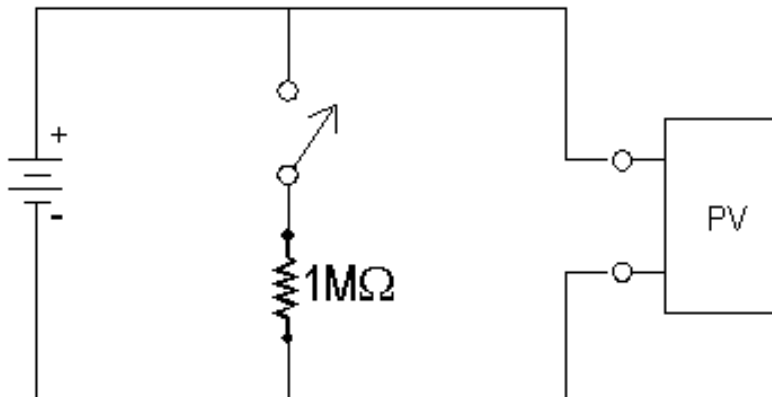

When the switch is open (not connected) the physical voltmeter reads 8 volts. When the switch is closed (connected) the physical voltmeter reads 6 volts. Find R_B and V_B .

$R_B =$ _____ ohms $V_B =$ _____ volts


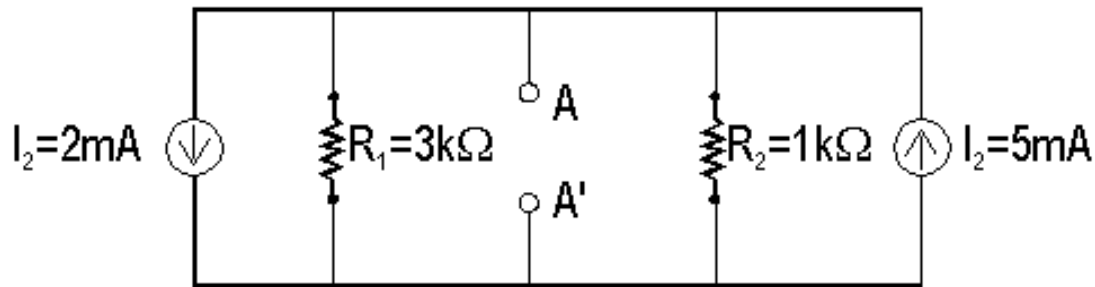
Problem 2: [25%]

A two-terminal subcircuit is shown with terminals A and A'. Find its Thévenin equivalent, making your method clear. (Label the terminals AA' in your equivalent circuit)

$R_{TH} =$ _____ ohms
$V_{TH} =$ _____ volts

Problem 3: [25%]

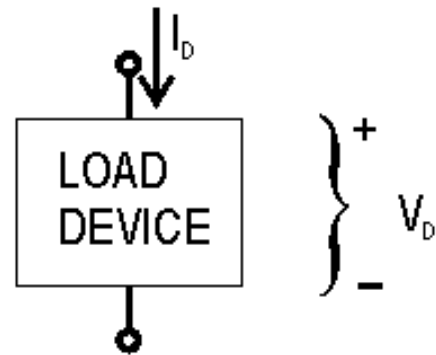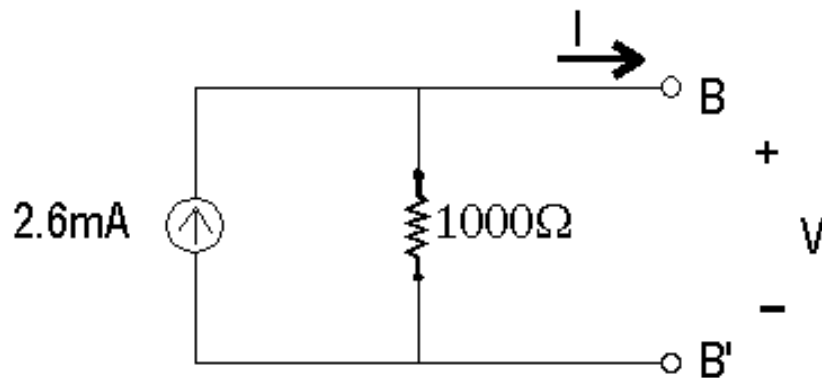
(a) Plot the I-V characteristic of the Norton equivalent circuit having terminals B-B' on the axes below:




(b) The I-V characteristic of a load device is also plotted on these axes. If the load device is connected to terminals B-B', what current, I_D , flows and what voltage, V_D , appears across the load device?

$I_D =$ _____ mA
$V_D =$ _____ V

(c) Under the conditions of part (b), find the power delivered to the load device.

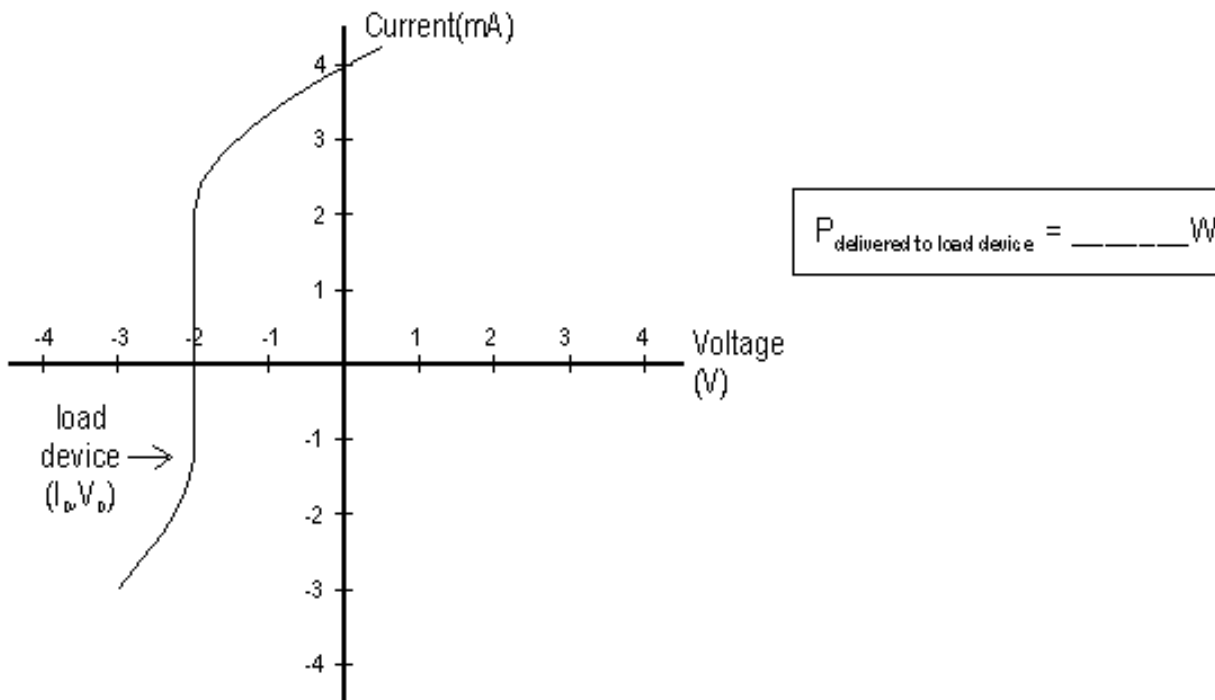

Problem 4: [25%]

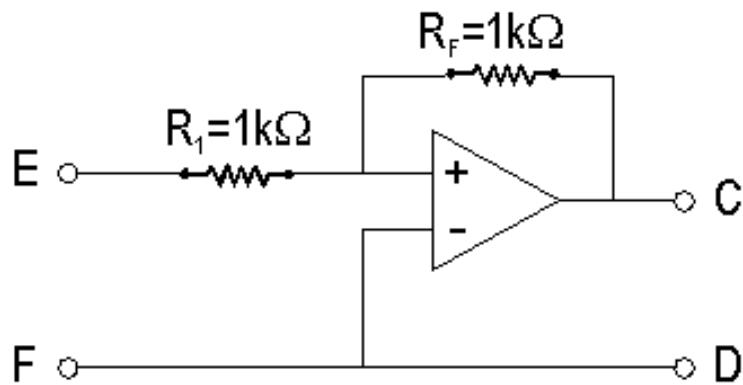

In the above circuit the op-amp has an abnormally low voltage amplification; in fact, $A=5$. Its input resistance $R_i=1M\Omega$ and $R_o=0$. Output terminals C, D, are open-circuited.

- (a) Re-draw the circuit with the full op-amp equivalent circuit inserted. (Do NOT use the ideal op-amp technique.)
- (b) Find the input resistance looking into terminals E, F. Use the full op-amp model. (Do NOT use the ideal op-amp technique.) Output terminals C, D are open-circuited.



© 1995 by Schwarz and White
translated to HTML by Walter Hsiao
Eta Kappa Nu (November 1995)