

University of California at Berkeley
College of Engineering
Dept. of Electrical Engineering and Computer Sciences

EECS 40 Final Examination

Fall 1998

Prof. Roger T. Howe

December 14, 1998

Name: _____
Last, first

Student ID _____


Guidelines

1. Closed book and notes; 3, 8.5" x 11" page (both sides) of your own notes are allowed.
2. You may use a calculator.
3. Do not unstaple the exam.
4. Show *all your work and reasoning on the exam* in order to receive full or partial credit.

Score

Problem	Points Possible	Score
1	25	
2	20	
3	20	
4	20	
5	15	
Total	100	

1. Digital Logic Gate [24 points]

 


Process Sequence:


Starting material: phosphorus-doped silicon, concentration $5 \times 10^{17} \text{ cm}^{-3}$

 1. Deposit 500 nm of silicon dioxide and pattern using the **oxide mask** (dark field)
2. Grow 5 nm of thermal silicon dioxide.
3. Deposit 500 nm of boron-doped polysilicon and pattern using the **poly mask** (clear field).
4. Implant boron and anneal (depth 250 nm and concentration = $1.25 \times 10^{18} \text{ cm}^{-3}$.)
5. Deposit 500 nm of silicon dioxide and etch 505 nm of oxide using the **contact mask** (dark field).
6. Deposit 500 nm of aluminum and pattern using the **metal mask** (clear field).


Given: polysilicon sheet resistance: $R = 25 \Omega/$, $\epsilon_{ox} = 3.45 \times 10^{-13} \text{ F/cm}$,
 $R_{on} = 150 \Omega$ (on resistance for MOSFET)



 (a) [6 pts.] Sketch the cross section A-A' on the graph below. Identify all layers clearly.



 (b) [6 pts.] Sketch the cross section ***B-B'*** on the graph below. Identify all layers clearly.



(c) [5 pts.] Given: metal lines 1-5 on the layout are connected as listed:


1. v_{IN1}
2. v_{IN2}
3. $V_{DD} = 2.5 \text{ V}$
4. v_{OUT}
5. Ground.

First, draw the circuit model for the physical structures between nodes 1, 2, 3, and 4 using the correct MOSFET symbol. Second, redraw the circuit model using the “switch model” for the transistors. Give numerical values for any resistors or capacitors; you can neglect the drain-to-bulk capacitors.

(d) [4 pts] Draw the circuit model for the physical structures between nodes 4 and 5 *only*. Given: for finding the resistance, there are 70 squares of polysilicon between nodes 4 and 5. Hint: it is *not* necessary to use multiple lumps here.

(f) [4 pts.] What is the maximum value of the output voltage in Volts?

2. CMOS digital circuit [20 points]

 

“Regular” PMOS:
 Gate capacitance: $C_{ox} = 2 \text{ fF}/\mu\text{m}^2$
 Width = $W_p = 3 \mu\text{m}$
 Length = $L_p = 0.5 \mu\text{m}$
 “on” resistance = $R_p = 300 \Omega$

“Regular” NMOS:
 Gate capacitance: $C_{ox} = 2 \text{ fF}/\mu\text{m}^2$
 Width = $W_n = 2 \mu\text{m}$
 Length = $L_n = 0.5 \mu\text{m}$
 “on” resistance = $R_n = 200 \Omega$

$V_{Th} = 1.9 \text{ V}$, $V_{Tl} = 0.6 \text{ V}$




Interconnect:
 $C_{int} = 0.2 \text{ fF}/\mu\text{m}$
 $R_{int} = 0.1 \Omega/\mu\text{m}$
 $L = 800 \mu\text{m}$

“Pad Driver” PMOS:
 Gate capacitance: $C_{ox} = 2 \text{ fF}/\mu\text{m}^2$
 Width = $W_p = 150 \mu\text{m}$
 Length = $L_p = 0.5 \mu\text{m}$
 “on” resistance = $R_p = 15 \Omega$

“Pad Driver” NMOS:
 Gate capacitance: $C_{ox} = 2 \text{ fF}/\mu\text{m}^2$
 Width = $W_n = 100 \mu\text{m}$
 Length = $L_n = 0.5 \mu\text{m}$
 “on” resistance = $R_n = 10 \Omega$

$V_{Th} = 1.4 \text{ V}$, $V_{Tl} = 1.1 \text{ V}$

   The waveforms for $v_A(t)$, $v_B(t)$, and $v_C(t)$ are:




(a) [2 pts.] The input voltages to this circuit have been constant for a long time for $t < 0$. What are the numerical values of the voltages v_{OUT1} and v_{OUT2} for $t < 0$?

(b) [4 pts.] Find the waveform $v_{OUT1}(t)$ for the time interval $0 < t < 0.4$ ns.


(c) [4 pts.] Find the waveform $v_{OUT2}(t)$ for the time interval $0 < t < 0.4$ ns.

(d) [4 pts.] Find the waveform $v_{OUT1}(t)$ for the time interval $0.4 < t < 0.8$ ns. If you couldn't solve part (b), you can assume for this part that $v_{OUT1}(0.8 \text{ ns}) = 2.5 \text{ V}$.

 (e) [6 pts.] Sketch the waveforms $v_{OUT1}(t)$ and $v_{OUT2}(t)$ on the graphs below over the interval $0 < t < 1.8$ ns. Note that the logic thresholds for the pad driver are different from those of the regular CMOS logic gate. Your sketch should be consistent with your answers for (a) – (d).



3. Linear circuit analysis [20 points]

 


- (a) [8 pts.] What is the numerical value of the Norton equivalent current I_N for this two-terminal linear network?

(b) [8 pts.] What is the numerical value of the Thevenin equivalent resistance R_{Th} for this two-terminal linear network?

(c) [4 pts.] What is the numerical value of the maximum power that can be extracted from this two-terminal network in Watts? What is the numerical value of the load resistance R_L required for this case? If you couldn't solve parts (a) and (b), you can assume for this part that $I_N = 20$ mA and $R_{Th} = 8$ k Ω .

 4. Inductor-resistor circuit analysis [20 points]





(a) [4 pts.] What is the numerical value of the inductor current $i_L(0)$ when $t = 0$.

(b) [4 pts.] Find the numerical value of the final inductor current, $i_L(t \rightarrow \infty)$.

(c) [6 pts.] Find the inductor current $i_L(t)$ for $0 \leq t \leq 10 \text{ ps}$.

(d) [6 pts.] Find the inductor current $i_L(t)$ for $t \geq 10 \text{ ps}$.

5. Capacitive coupling [15 points]

  

Inverters A and B: $R_n = R_p = 100 \Omega$ $V_{DD} = 2.5 \text{ V}$
 $C_{Gn} + C_{Gp} = 25 \text{ fF}$

The interconnect (line 1) between inverters A and B runs close by lines 2 and 3, as shown in the cross section, for a distance of $200 \mu\text{m}$. The interconnects are surrounded by SiO_2 . Lines 2 and 3 are floating (not connected to anything at either end).

- (a) [5 pts.] Draw the circuit model for the pull-up transition of inverter A. Include the numerical values of the capacitors between lines 1, 2, and 3 (and between them and the grounded substrate); you can neglect the interconnect resistance.
 Given: $\epsilon_{ox} = 3.45 \times 10^{-13} \text{ F/cm}$.

(b) [5 pts.] Find the peak voltage $v_{2,\max}$ on line 2 after the pull-up transition of inverter A .

(c) [5 pts.] Find the peak voltage $v_{3,\max}$ on line 3 after the pull-up transition of inverter A .