

**EE 40, Spring 1998**  
**Midterm 2**  
**Professor S. Schwarz, Professor R. M. White**


**Problem #1 (25 Points)**

The phasor representing the sinusoid  $v(t)$  is  $\mathbf{v} = (1+2j)/1-3j$ . The angular frequency  $\omega$  is 100 radians/sec.

[8 pts.] a) Find the amplitude of the sinusoid.

[8 pts.] b) Find the phase angle of the sinusoid.

[9 pts.] c) Find the first time after  $t = 0$  at which  $v$  has its maximum value.

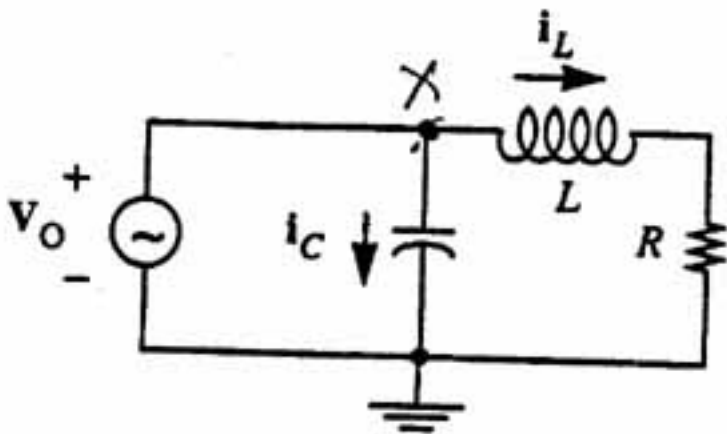**Problem #2 (25 Points)**

In the above circuit,  $\mathbf{V}_0 = 10$  V (real,  $C = 10^{-8}$  F,  $L = 2 \times 10^{-4}$  H,  $R = 100$  ohms,  $\omega = 10^6$  radians/sec.


[5 pts.] a) Find the numerical value of the phasor  $\mathbf{i}_C$ . Express answer in simplest rectangular form  $A + jB$ .

[10 pts.] b) Find the numerical value of the phasor  $\mathbf{i}_L$ . Express answer in simplest rectangular form  $A + jB$ .

[10 pts.] c) Find the time-averaged power produced by the voltage source. (That is, find the power that comes out of the voltage source and goes into the rest of the circuit.)

**Problem #3 (25 Points)**


For a certain circuit block, the ratio  $|V_{out}|/|V_{in}|$  is represented by the following:

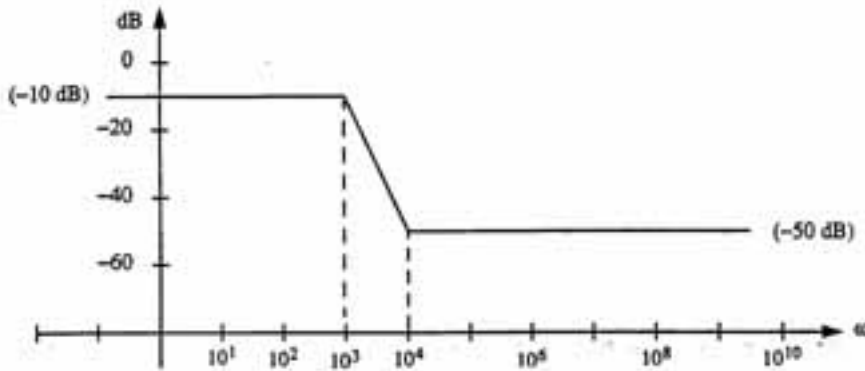

The general expression for this transfer function is

$$\frac{|V_{out}|}{|V_{in}|} = \frac{(1 + A\omega)^M}{(B + C\omega)^N}$$

Find A, B, C, M and N. Note: 0 dB corresponds to  $|V_{out}|/|V_{in}| = 1$ .

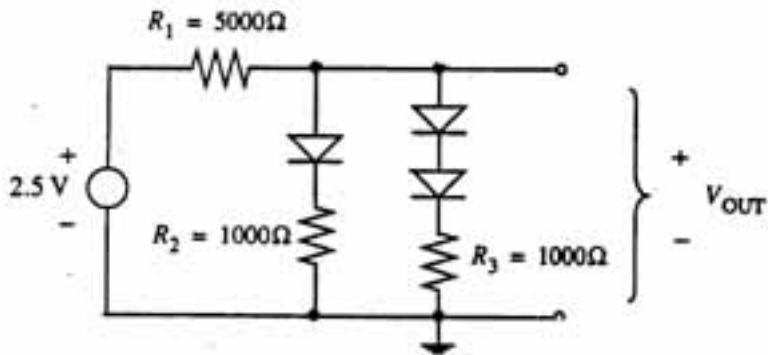**Problem #4 (25 Points)**

Find  $V_{out}$  in the above circuit. The diodes are to be represented by the large-signal diode model (including the 0.7 V drop across a forward-biased diode.) **Make sure your answer is reasonable and consistent.** Explain your reasoning.

**If you have any questions about these online exams  
please contact <mailto:examfile@hkn.eecs.berkeley.edu>**