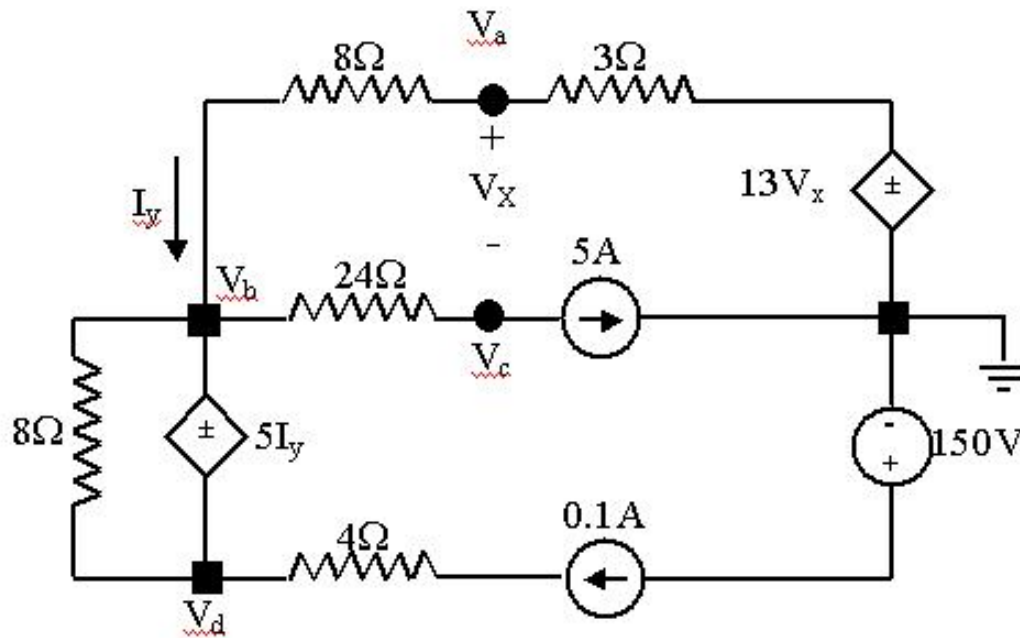


EE 40, Summer 1999
Midterm #1
Professor Dennis M. Sylvester

Problem #1

Node Voltages V_a through V_d are labeled on the above circuit diagram. Note the location of ground.

- Circle all supernodes
- Write V_x and I_y in terms of variables V_a through V_d .

$$V_x = \underline{\hspace{2cm}}$$

$$I_y = \underline{\hspace{2cm}}$$

- Perform nodal analysis for the entire circuit. You should get four simultaneous equations and four unknowns. The unknowns are V_a , V_b , V_c , and V_d . Simplify these equations and fill in the blanks below. Do not solve these equations.

Eq 1 $\underline{\hspace{1cm}} V_a + \underline{\hspace{1cm}} V_b + \underline{\hspace{1cm}} V_c + \underline{\hspace{1cm}} V_d = \underline{\hspace{1cm}}$

Eq 2 $\underline{\hspace{1cm}} V_a + \underline{\hspace{1cm}} V_b + \underline{\hspace{1cm}} V_c + \underline{\hspace{1cm}} V_d = \underline{\hspace{1cm}}$


Eq 3 $\underline{\hspace{1cm}} V_a + \underline{\hspace{1cm}} V_b + \underline{\hspace{1cm}} V_c + \underline{\hspace{1cm}} V_d = \underline{\hspace{1cm}}$

Eq 4 $\underline{\hspace{1cm}} V_a + \underline{\hspace{1cm}} V_b + \underline{\hspace{1cm}} V_c + \underline{\hspace{1cm}} V_d = \underline{\hspace{1cm}}$

d. Find the power that the 150V voltage source releases into the circuit.

$$P = \underline{\hspace{1cm}}$$

Problem #2

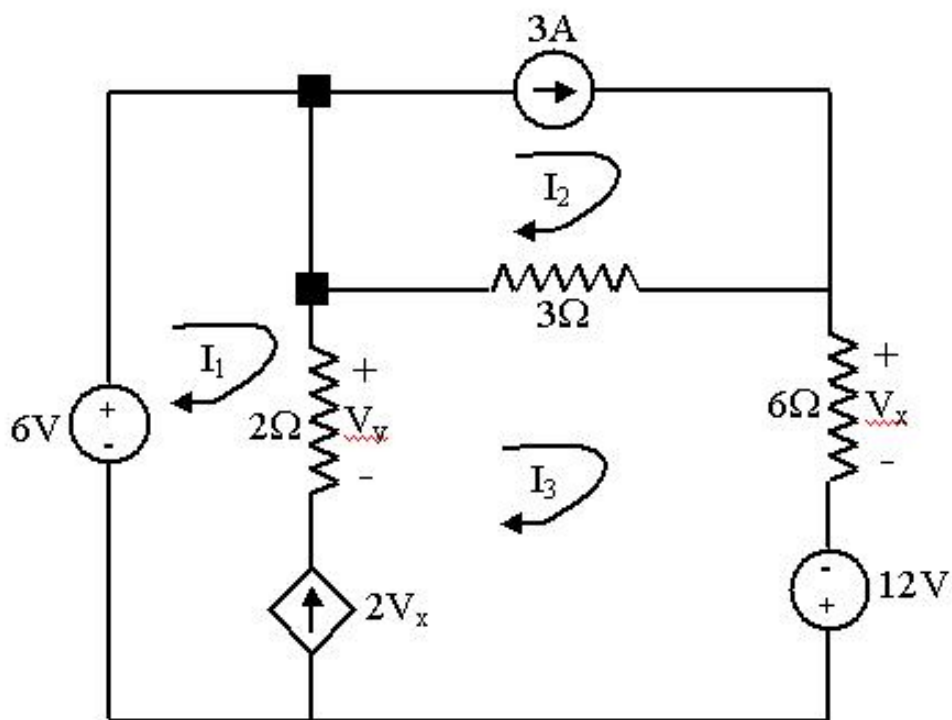

a. Solve for the mesh currents I_1 , I_2 , and I_3 . (Hint: Use the dependent sources to find the relationship between I_1 and I_3)

$$I_1 = \underline{\hspace{1cm}}$$

$$I_2 = \underline{\hspace{1cm}}$$

$$I_3 = \underline{\hspace{1cm}}$$

- b. Using your results in part (a), find V_y .


$$V_y = \underline{\hspace{2cm}}$$

- c. Determine the power that the voltage/current source is releasing into the circuit or absorbing from the circuit:

Circle one

- i. The 6V voltage source is [releasing / absorbing] _____ W.
 ii. The 12V voltage source is [releasing / absorbing] _____ W.

Problem #3

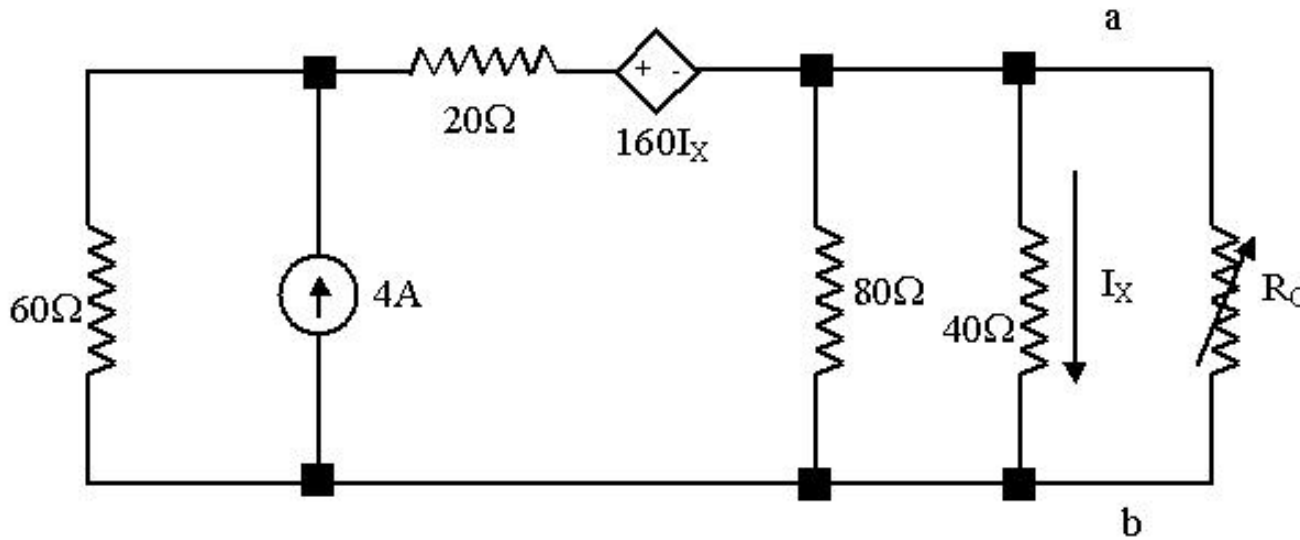

The variable resistor (R_0) in the circuit has its resistance adjusted until the resistor absorbs maximum power from the circuit.

- a. Find V_{ab} if the variable resistor is replaced with an open circuit.

$$V_{ab} = \underline{\hspace{2cm}}$$

- b. Find the Thevenin resistance R_{TH} for the entire circuit left of nodes a and b without finding I_{sc} (short-circuit current).


$$R_{TH} = \underline{\hspace{2cm}}$$

- c. Draw a Norton equivalent circuit for the entire circuit left of nodes a and b.

- d. Find the maximum power delivered to the variable resistor.

P_{MAX} = _____

Problem #4

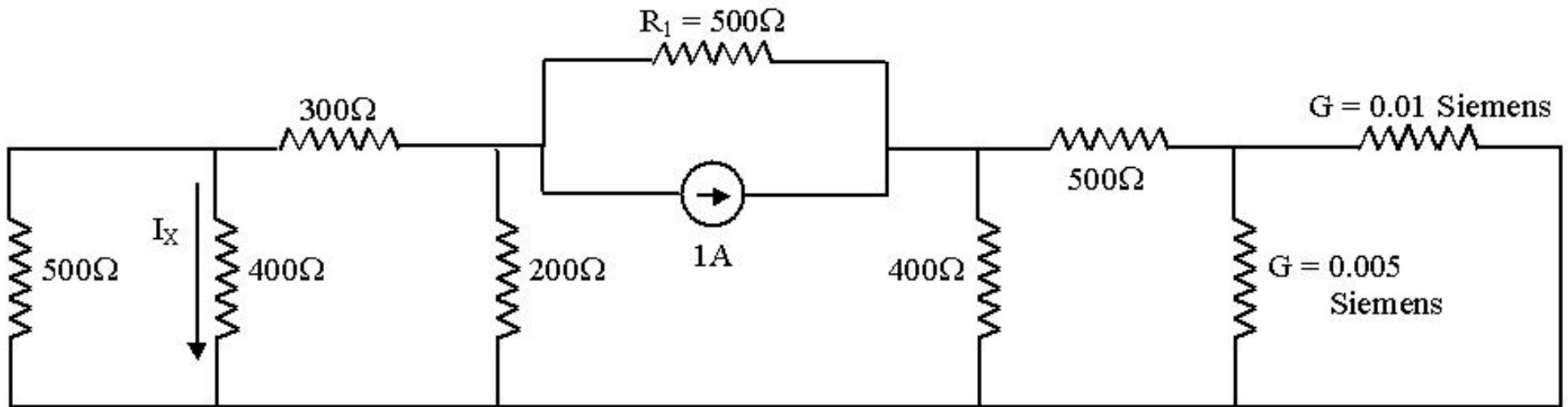

- a. Find the power supplied by or absorbed by the current source.

Circle one

The current source is [supplying / absorbing] _____ W.



- b. Find the power absorbed by R₁.

Power absorbed = _____

- c. Find I_x (remember sign convention).

I_x = _____

Problem #5

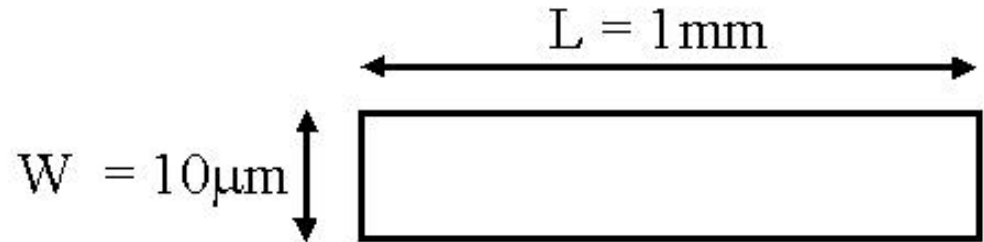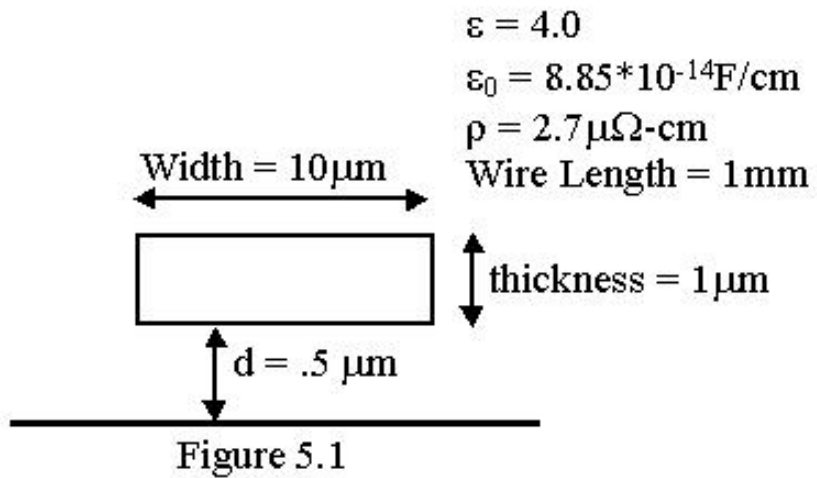

The figure 5.1 shows the cross section of a wire surrounded by silicon dioxide (SiO_2). The wire is $.5 \mu\text{m}$ above another layer of conducting material. Figure 5.2 shows the wire viewed from above.


- a. Find the sheet resistance and the total resistance of the wire.

$$R = \underline{\hspace{2cm}} \quad R_{\text{Wire}} = \underline{\hspace{2cm}}$$

- b. Calculate the total capacitance (parallel plate only).


$$C_{\text{wire}} = \underline{\hspace{2cm}}$$

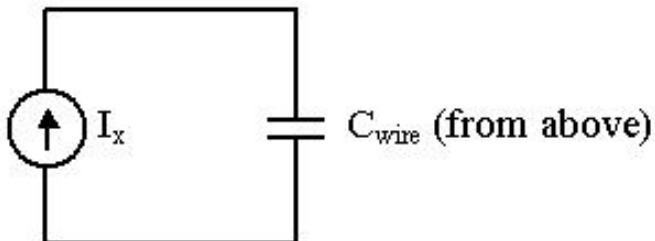- c. Current source I_x charges C_{wire} to a voltage of 5V in 100ps. The capacitor's initial voltage is zero. Find I_x . For this part of the problem, we are ignoring the wire resistance R_{Wire} . If you were unable to find C_{wire} in part (c), use $C_{\text{wire}} = 1 \text{ pF}$.



$I_X =$ _____

- d. C_{wire} is charged to 5V before t_0 . At time t_0+ , what is the current through C_{wire}? If you were unable to find R_{wire} in part (b), use R_{wire} = 5 ohms.

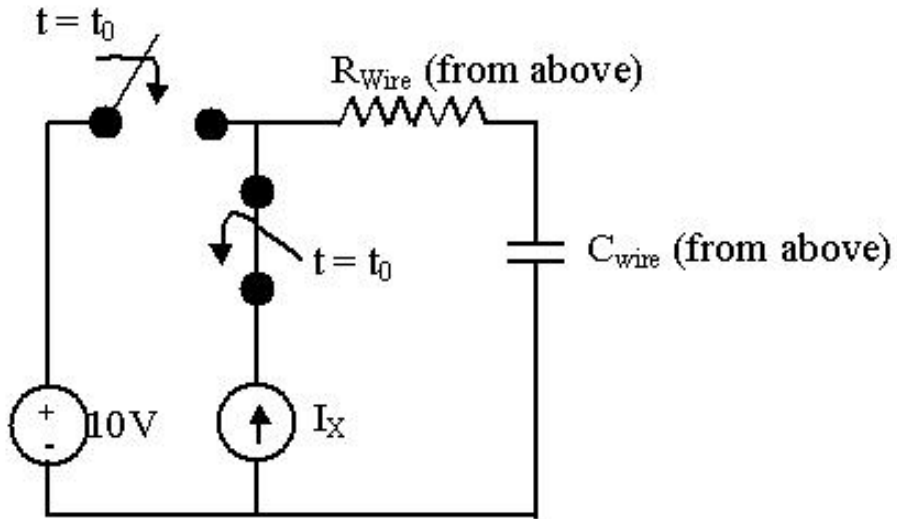
 $I =$ _____

Posted by HKN (Electrical Engineering and Computer Science Honor Society)

University of California at Berkeley

If you have any questions about these online exams
please contact <mailto:examfile@hkn.eecs.berkeley.edu>