

Midterm 1 Solution for EE40 Sp 2006

(Prepared by Josh Hug, jhug@eecs.berkeley.edu)

1. Resistive Circuits and Capacitors

- a. This is most easily solved by using the current divider rule:

$$I_7 = I_s/8$$

- b. If we treat the two resistances R in parallel as a $\frac{1}{2}R$ ohm resistor, we can use the voltage divider rule:

$$V_1 = V_s * \frac{1/2}{(1/2 + 1)} * V_s = 1/3 V_s$$

- c. At the node of interest, we have $2I$ current coming in from the right, and I current leaving from the bottom, so we know that there must be I current leaving through the top. Thus, by Ohm's law, we know that $V_1 = 10 + I * 5$. Furthermore, we also know by Ohm's law that $V_1 = 10I$. Using these two equations, we can find that $V_1 = 20$ Volts.


Another way to solve this problem is to use KCL at the V_1 node:

$$\frac{V_1 - 10}{5} + \frac{V_1}{10} - \frac{2V_1}{10} = 0$$

$$2V_1 - 20 + V_1 - 2V_1 = 0$$

$$V_1 = 20 \text{ Volts}$$

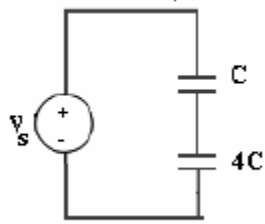- d. We know that for two capacitors in series, the charges are equal, and for two capacitors in parallel, the voltages are equal. If we treat the pair of $2C$ capacitors in parallel as a single $4C$ capacitor. Then we have the following equivalent circuit:



We know that $Q_C = Q_{4C}$, and $V_C + V_{4C} = V_s$, $Q_C = C * V_C$, and $Q_{4C} = 4C * V_{4C}$.


From $Q_C = C * V_C$, $Q_{4C} = 4C * V_{4C}$, and $Q_C = Q_{4C}$, we know that $V_C = 4V_{4C}$

Thus $4V_{4C} + V_{4C} = V_s$, so $V_{4C} = 1/5 * V_s$, and $V_C = 4/5 * V_s$

$$Q_C = Q_{4C} = 4C/5 * V_s$$

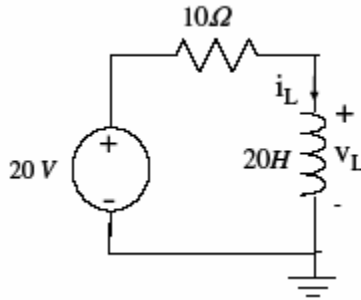2. One solution is to use the trick from homework 4.

For $0 < t < 2$ sec, we have the following circuit:



First we note that $i_L(0^-) = i_L(0^+) = 0$, and $i_L(\infty) = 20/10 = 2$ Amps


Next, we find the Thevenin resistance that the inductor sees, which is trivially 10 Ohms. This gives us the time constant $L/R = 20/10 = 2$ seconds

Now that we know the initial current (0 Amps), the steady state voltage (2 Amps), and the time constant (2 seconds), we use the shortcut from Homework 4 and get:

$$I_L(t) = I_f - (I_f - I_i)e^{-t/\tau}$$

$$= 2 - 2e^{-t/2\text{sec}} \text{ Amps}$$

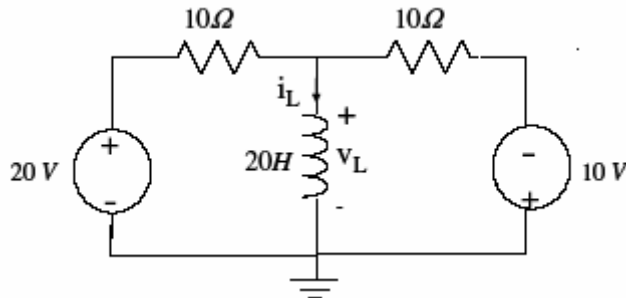For $t > 2$ sec, we have the following circuit:



First we note that $i_L(2^-) = i_L(2^+) = 2 - 2e^{-2/2} = 2 - 2e^{-1} = 1.26$ Amps

To find $i_L(\infty)$, we can use superposition. From the 20 volt source, $i_L(\infty)$ is increased by 2 Amps. From the 10 volt source, $i_L(\infty)$ is decreased by 1 amp. Thus, $i_L(\infty) = 2 - 1 = 1$ Amp.

Next, we find the Thevenin resistance that the inductor sees by zeroing out the independent sources, yielding the following circuit:

This is just a 10 ohm resistor in parallel with another 10 ohm resistor, which means that the resistance the inductor sees is 5 ohms.

Thus our time constant is $20/5 = 4$ seconds.

So, again using the trick from homework 4, we have

$$\begin{aligned} I_L(t) &= I_f - (I_f - I_i)e^{-(t-2)/\tau} \\ &= 1 - (1 - 1.26)e^{-(t-2)/4} \\ &= 1 + 0.26e^{-(t-2\text{sec})/4\text{sec}} \text{ Amps} \end{aligned}$$

Another possible solution is to write the differential equations in both cases and solve.

For the first case, we can use KVL to find that:

$$\begin{aligned} 10 - 10I_L - 20I_L' &= 0 \\ 2 - I_L - 2I_L' &= 0 \\ I_L + 2I_L' &= 2 \end{aligned}$$

We first find the complementary solution $I_C(t) = Ke^{-t/\tau}$. Since we have our equation in the form $I_L + \mathcal{D}I_L = f(t)$, we know that $I_C(t) = Ke^{-t/2\text{sec}}$ Amps.

Next we can find the particular solution by guessing that our solution is of the form $I_P(t) = A * f(t) + B * f'(t) = A$. Plugging this into our differential equation above, we get that $A+0=2$, or $A=2$.

Finally, we know that $I(0)=0$, so we find $I(0) = I_C(0) + I_P(0) = K + 2 = 0$, or $K=-2$. Thus, our final solution for $0 < t < 2$ is $I(t) = 2 - 2e^{-t/2\text{sec}}$ Amps.

For the second part of the problem, we write a new differential equation using KCL at our node of interest. (We could also write two KVL equations and add them).

Doing this, we obtain:

$$\begin{aligned} \frac{V_L - 20}{10} + \frac{V_L + 10}{10} + \int \frac{V_L}{20} &= 0 \\ V_L &= LI_L' \\ \frac{20I_L' - 20}{10} + \frac{20I_L' + 10}{10} + \frac{20I_L}{20} &= 0 \\ 2I_L' - 2 + 2I_L' + 1 + I_L &= 0 \\ 4I_L' - 1 + I_L &= 0 \\ 4I_L' + I_L &= 1 \end{aligned}$$

Since our equation is in the form $I_L + \tau I_L' = f(t)$, we know that our complementary solution is of the form $I_{Lc}(t) = Ke^{-(t-2\text{sec})/4\text{sec}}$ Amps.

Next we find the particular solution. As above, we assume that $I_{Lp}(t) = A$, and plug this into our differential equation, finding that $A=1$.

Now we add our particular and complementary solution and have that $I_L = Ke^{-(t-2)/4} + 1$. To find K , we know that $I_L(2) = 2 - 2e^{-1} = 1.26A$, so $I_L(2) = Ke^{-(2-2)/4} + 1 = K + 1 = 1.26A$, and therefore $K=0.26A$.

Thus our final solution is $I_L(t) = 1 + 0.26e^{-(t-2\text{sec})/4\text{sec}}$ Amps

There are many more possible solutions, such as using separation of variables, etc,

3.

- a. For $t < 0$, the circuit has been closed for a long time, and since we have a DC source, we can perform DC steady state analysis. We treat the capacitor as an open circuit, and the inductor like a short. Thus, we find that $I_L = 5/500,000 = 10^{-5}$ Amps, and since the inductor acts like a short, $V_C = 0$ Volts.
- b. One method is to write KCL at the node, take the derivative of both sides, and reorganize the terms, as shown below:

$$\frac{V_L - \cos(t)}{R} + CV_L' + \int \frac{V_L}{L} = 0$$

$$\frac{V_L' + \sin(t)}{R} + CV_L'' + \frac{V_L}{L} = 0$$

$$\frac{V_L'}{RC} + V_L'' + \frac{V_L}{LC} = -\frac{\sin(t)}{RC}$$

$$V_L'' + 2V_L' + V_L = -2\sin(t)$$

- c. Since, our equation is in the form

$$\frac{d^2x(t)}{dt^2} + 2\alpha \frac{dx(t)}{dt} + \omega_0^2 x(t) = f(t)$$

, we know that

$$\alpha = 1, \omega_0 = 1, \zeta = \frac{\alpha}{\omega_0} = \frac{1}{1} = 1$$

Therefore, the complementary/transient solution is:

$$V_C(t) = K_1 e^{-\alpha t} + K_2 t e^{-\alpha t} \text{ Volts}$$

- d. Critically damped
 e. We assume a solution of the form $V_p(t) = A \cos(t) + B \sin(t)$

$$V_p(t) = A \cos(t) + B \sin(t)$$

$$V_p'(t) = -A \sin(t) + B \cos(t)$$

$$V_p''(t) = -A \cos(t) - B \sin(t)$$

Then we plug them into our equation from part b, and get:

$$-A \cos(t) - B \sin(t) - 2A \sin(t) + 2B \cos(t) + A \cos(t) + B \sin(t) = -2 \sin(t)$$

By collecting sine and cosine terms, we find the following:

$$-A + 2B + A = 0$$

$$-B - 2A + B = -2$$

From the first equation we find that $B=0$.

Plugging $B=0$ into the second equation, we get $-2A=-2$, or $A=1$.

Thus our particular solution $V_p(t) = \cos(t)$

- f. We obtain the complete solution by adding the particular solution and the complementary solution, so we have:

$$V(t) = K_1 e^{-t} + K_2 t e^{-t} + \cos(t)$$

To find the constants, we can first use the initial condition $v(0)=0$, and obtain:

$$V(0) = K_1 e^0 + K_2 0 e^0 + \cos(0) = 0$$

$$K_1 + 1 = 0$$

$$K_1 = -1$$

To find K_2 , we know that $i_L(0^-) = i_L(0^+) = 10^{-5} \text{ Amps}$. However, to use this information directly, we'd need an equation for $I_L(t)$.

Instead, it's easier to find $i_C(0^+)$. Note: $i_C(0^+) \neq i_C(0^-)$!! At time 0^+ , we can write KCL at node V_L , which gives us:

$$\frac{V_L(0^+) - \cos(0)}{500000} + I_C(0^+) + I_L(0^+) = 0$$

We also know the following facts:

$$V_L(0^+) = V_C(0^+) = V_C(0^-) = 0$$

$$I_L(0^+) = I_L(0^-) = 10^{-5} \text{ Amps}$$

So our above KCL equation becomes:

$$\frac{-10^{-5}}{5} + I_C(0^+) + 10^{-5} \text{ Amps} = 0$$

This gives us:

$$I_C(0^+) = -4/5 * 10^{-5} \text{ amps}$$

Next, we find $I_C(t) = CV_C'(t) = 10^{-6}(e^{-t} + K_2e^{-t} - K_2te^{-t} - \sin(t))$, and thus :

$$I_C(0) = 10^{-6}(1 + K_2) = -4/5 * 10^{-5}$$

$$(1 + K_2) = -40/5$$

$$(1 + K_2) = -8$$

$$K_2 = -9$$

Thus, we have our final solution:

$$V_L(t) = -e^{-t/\text{sec}} - 9te^{-t/\text{sec}} + \cos(t) \text{ Volts}$$