

UNIVERSITY OF CALIFORNIA, BERKELEY
College of Engineering
Department of Electrical Engineering and Computer Sciences

EE 105: Microelectronic Devices and Circuits

Fall 2010

MIDTERM EXAMINATION #2

Time allotted: 60 minutes

NAME: _____ *Solution* _____

STUDENT ID#: _____

INSTRUCTIONS:

- 1. SHOW YOUR WORK. (Make your methods clear to the grader!)**
Specially, while using chart, make sure that you indicate how you have got your numbers. For example, if reading off mobility, clearly write down what doping density that corresponds to.
- 2. Clearly mark (underline or box) your answers.**
- 3. Specify the units on answers whenever appropriate.**

SCORE: 1 _____ / 16

2 _____ / 14


3 _____ / 10

Total _____ / 40

For all questions, if not explicitly mentioned, ignore the BJT capacitances.

Prob 1. [16 pts]

Consider the following amplifier:

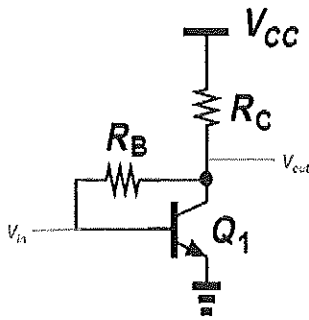

(a) [5 pts] Explain how this amplifier is robust against variation in R_B and R_C .


$$V_{BE} = V_{CC} - (I_C + I_B) R_C - I_B R_B$$

$$= V_{CC} - \frac{\beta + 1}{\beta} I_C R_C - \frac{I_C R_B}{\beta}$$

$$V_{BE} = V_{CC} - I_C \left[\frac{(\beta + 1) R_C + R_B}{\beta} \right]$$

Thus I_C is linearly dependent on V_{BE} rather than being exponentially dependent.

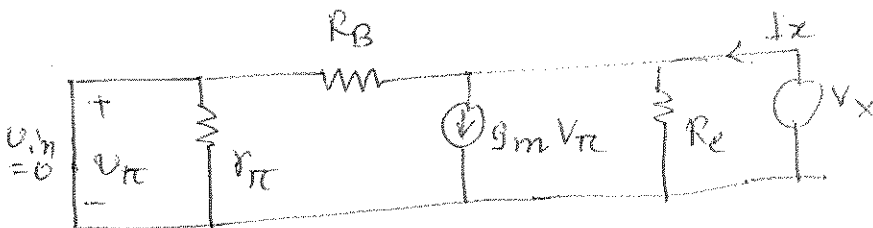
(c) [5 pts] Find out the small signal output resistance. You may ignore the early effect.



v_{π} is shorted out
 $g_m v_{\pi}$ is open.

$$\therefore R_{out} = R_B \parallel R_e$$

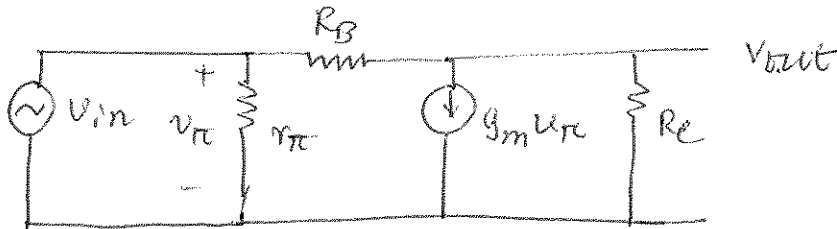(d) [6 pts] Find out the small signal voltage gain. You may ignore the early effect.



$$v_{\pi} = v_{in}$$

$$v_{in} - v_{out} = R_B \left[g_m v_{\pi} + \frac{v_{out}}{R_e} \right]$$

$$\therefore \frac{v_{in} - v_{out}}{R_B} = g_m v_{in} + \frac{v_{out}}{R_e}$$

$$v_{in} \left[\frac{1 - g_m R_B}{R_B} \right] = v_{out} \left[\frac{1}{R_B} + \frac{1}{R_e} \right]$$


$$\boxed{\frac{v_{out}}{v_{in}} = - \left(\frac{g_m R_B - 1}{R_B} \right) \left(\frac{R_B R_e}{R_B + R_e} \right) = - (g_m R_B - 1) \frac{R_e}{R_B + R_e}}$$

if, $g_m R_B \gg 1$

$$\boxed{A_v = -g_m (R_B \parallel R_e)}$$

Prob 2 [14 pts].

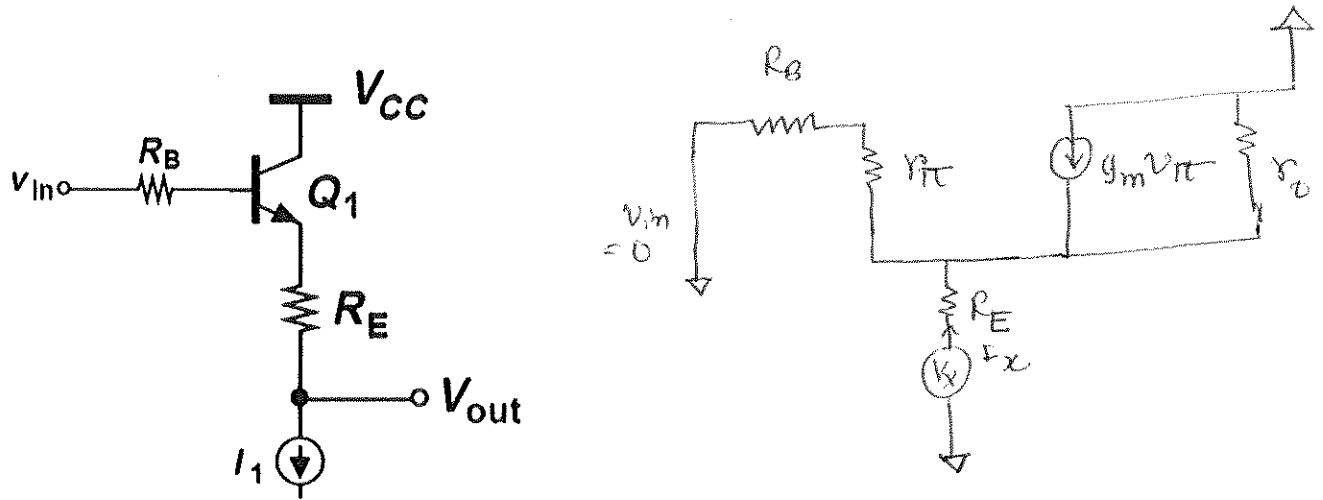(a) [6 pts] For the following amplifier, derive an expression for small signal input resistance starting from the small signal model including the early effect.



KCL

$$i_x + \frac{v_{\pi}}{r_{\pi}} + g_m v_{\pi} = \frac{v_x - i_x R_E}{r_o} \quad \text{--- (1)}$$

KVL


$$v_x - i_x R_E + v_{\pi} + \frac{v_{\pi}}{r_{\pi}} R_B = 0 \quad \text{--- (2)}$$

$$\begin{aligned} \therefore v_x &= i_x R_E - \frac{v_{\pi}}{r_{\pi}} (r_{\pi} + R_B) \\ &= i_x R_E - \frac{v_x / r_o - i_x (1 + R_E / r_o)}{\beta + 1} (r_{\pi} + R_B) \end{aligned}$$

$$\begin{aligned} v_x \left[1 + \frac{r_{\pi} + R_B}{\beta + 1} - \frac{1}{r_o} \right] &= i_x \left[R_E + \frac{R_E + r_o}{r_o} \cdot \frac{r_{\pi} + R_B}{\beta + 1} \right] \\ &= i_x R_E \left[1 + \frac{r_{\pi} + R_B}{\beta + 1} \cdot \frac{1}{r_o} \right] + i_x \frac{r_{\pi} + R_B}{\beta + 1} \end{aligned}$$

$$\therefore Z_{out} = \frac{v_x}{i_x} = R_E + \frac{\frac{r_{\pi} + R_B}{\beta + 1} \times r_o}{r_o + \frac{r_{\pi} + R_B}{\beta + 1}} = R_E + (r_o \parallel \frac{r_{\pi} + R_B}{\beta + 1})_4$$

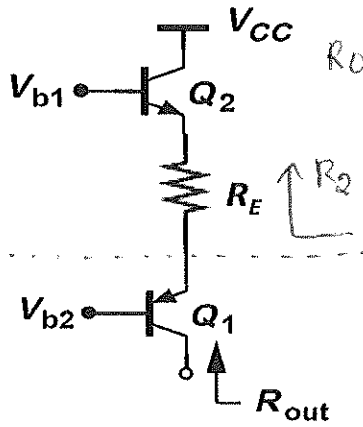(b) [4 pts] Is the following a good cascode? Why or Why not? Assume that $g_m R_E \gg 1$.



$$R_{out} = r_{o1} + (1 + g_{m1} r_{o1}) (R_E \parallel Y_{\pi1})$$

From prob (a)

$$R_2 = R_E + \left(r_{o1} \parallel \frac{Y_{\pi1}}{\beta + 1} \right)$$

$$\approx R_E + \frac{1}{g_{m2}} \approx R_E \quad [\because g_m R_E \gg 1]$$


Assuming both transistors have similar

$$g_m = g_{m1} = g_{m2}$$

$$\therefore R_{out} \approx g_{m1} r_{o1} (R_E \parallel Y_{\pi1})$$

Hence it is a good cascode.

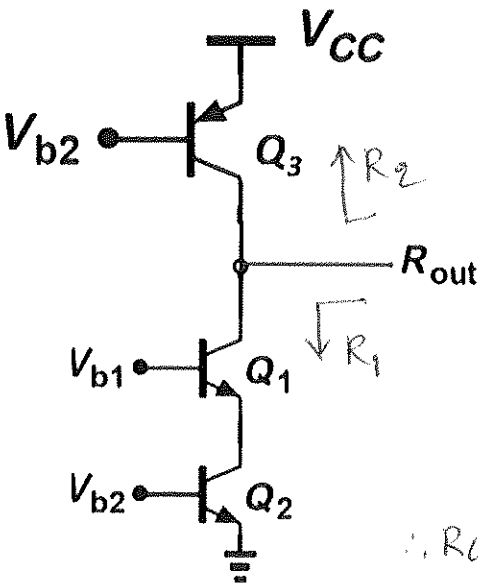(c) [4 pts] Find out the output resistance of the following cascode. Is it a good cascode? Why or why not? Assume that parameters for all transistors are identical.



$$R_{out} = R_1 \parallel R_2$$

$$R_1 = r_{o1} + (1 + g_{m1} r_{o1}) (r_{o2} \parallel Y_{\pi1})$$

$$\approx g_{m1} r_{o1} (r_{o2} \parallel Y_{\pi1})$$

$$R_2 = r_{o3}$$

$$\therefore R_{out} = \left(g_{m1} r_{o1} (r_{o2} \parallel Y_{\pi1}) \right) \parallel r_{o3}$$

since all transistors are identical


$$R_o = \left\{ g_m r_o (r_o \parallel \beta/g_m) \right\} \parallel r_o$$

$$\therefore \boxed{R_o = r_o}_{max}$$

hence not a good cascode.

Prob 3 [10 pts]:

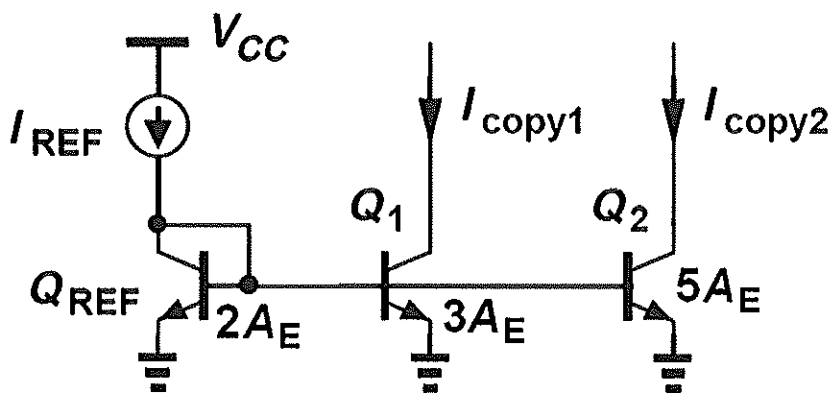(a) [6 pts] For the following configuration, what is I_{copy1} accounting for the base currents?



$$I_{ref} = \frac{I_{copy1}}{\beta} + \frac{I_{copy2}}{\beta} + \frac{I_{ref}}{\beta} + I_{ref} \quad \text{--- ①}$$

$$I_{ref} = I_{copy1} \times \frac{2}{3} \quad ; \quad I_{ref} = \frac{2}{5} I_{copy2}$$

$$\therefore I_{copy2} = \frac{5}{2} \times \frac{2}{3} I_{copy1}$$

$$\therefore \text{From ①} \rightarrow I_{ref} = \frac{I_{copy1}}{\beta} + \frac{5}{3\beta} I_{copy1} + \frac{2}{3\beta} I_{copy1} + \frac{2}{3} I_{copy1}$$


$$I_{ref} = I_{copy_1} \left[\frac{1}{\beta} + \frac{5}{3\beta} + \frac{2}{3\beta} + \frac{2}{3} \right]$$

$$= I_{copy_1} \left(\frac{10 + 2\beta}{3\beta} \right)$$

$$\therefore I_{copy_1} = I_{ref} \left(\frac{3\beta}{10 + 2\beta} \right)$$

$$I_{copy_1} = I_{ref} \left(\frac{3}{10/\beta + 2} \right)$$

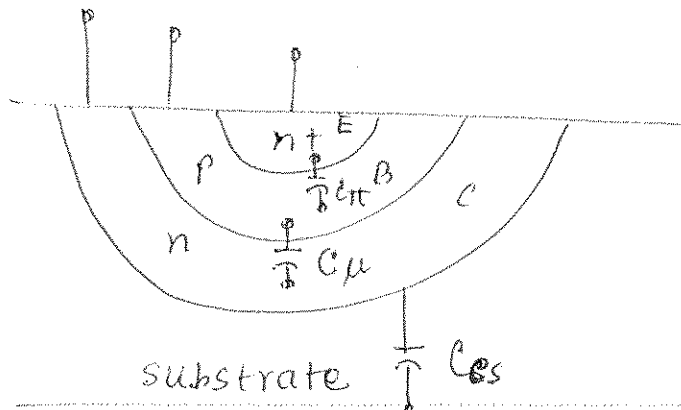(b)[4 pts] For a bipolar junction transistor, draw all the relevance capacitances. Also mention their physical origin.



Emitter junction: Depletion capacitance

+ Diffusion capacitance = C_{TC}

collector junction: Depletion capacitance = C_{μ}

Due to substrate ground plane = C_{es}