

UNIVERSITY OF CALIFORNIA  
 Department of Electrical Engineering and Computer Sciences  
 EE42/100 Fall 2011


Prof. Subramanian

**Test 2**

***FOR ALL QUESTIONS, ASSUME OP-AMPS ARE IDEAL UNLESS OTHERWISE STATED***

1) Consider the circuit below.

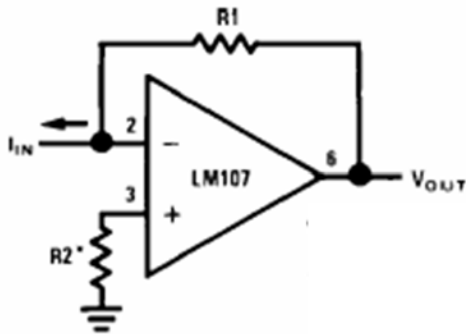a) Derive an equation for the output voltage as a function of the input current.




b) Suppose R2 was replaced by a short circuit, would your answer above change? Give reasons as appropriate.

c) Now, suppose the input of the op-amp is no longer ideal, and in fact, there is an input resistance  $R_{in}$  between the non-inverting and inverting inputs. Derive an equation for  $V_{out}$  as a function of  $I_{in}$  in this case.

- d)  $R_{in}$  is typically not a well-controlled parameter in operation amplifiers. What value would you pick for  $R_2$  above to ensure that variations in  $R_{in}$  do not significantly impact the circuit performance? Give reasons as appropriate.

2) Consider the circuit below.

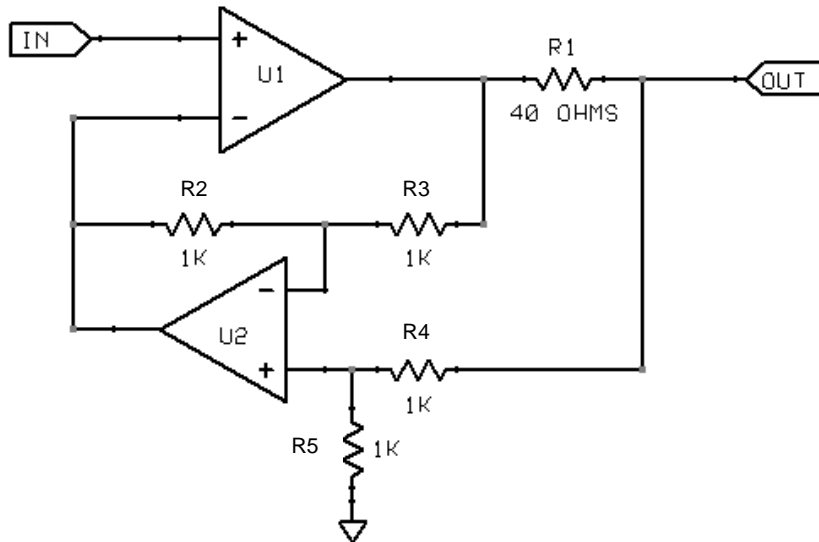

a) Derive equations for  $V_{out}$

b) Suppose a load resistor  $R_L$  is connected from the output to ground. Derive an equation for  $I_{out}$ , i.e., the current through  $R_L$ .

3) Consider Operational Amplifiers as used in modern circuits

- a) Why do we use high-gain op-amps and then use negative feedback to reduce the gain? Why not just use an op-amp with the desired gain?
  
- b) Suppose I designed a voltage amplifier with a gain of 100, and used a  $V_{DD}$  and  $V_{SS}$  of +15V and -15V respectively. What is the maximum input signal sinusoid amplitude that could be used without clipping?
  
- c) Why do clipped waveforms sound distorted to the human ear? Given a mathematical justification (no need to write any equations; just explain the concept).
  
- d) For the amplifier in part (b), what is the gain in dB?

4) For the following circuit, derive  $V_{out} / V_{in}$  as a function of “a”. “R” is a fixed value of resistance.

