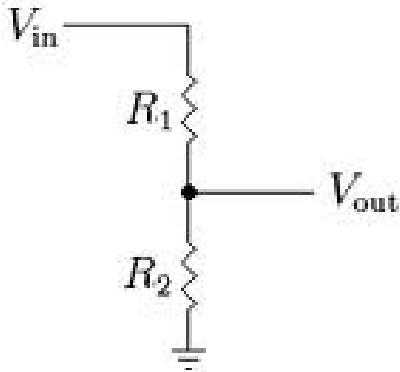


UNIVERSITY OF CALIFORNIA  
Department of Electrical Engineering and Computer Sciences  
EE42/100 Fall 2011

Prof. Subramanian


**Test 1**

- 1) The circuit below is known as a resistive voltage divider




- a) Assuming  $V_{in}$  is an ideal voltage source, derive an equation for  $V_{out}$
- b) Suppose I wanted to measure the voltage at  $V_{out}$  with a voltmeter.
- Would I want the voltmeter to have a low or high resistance? Why?
  - Redraw the circuit above to include the resistance of the voltmeter, and derive an equation for  $V_{out}$  as a function of the resistance of the voltmeter.

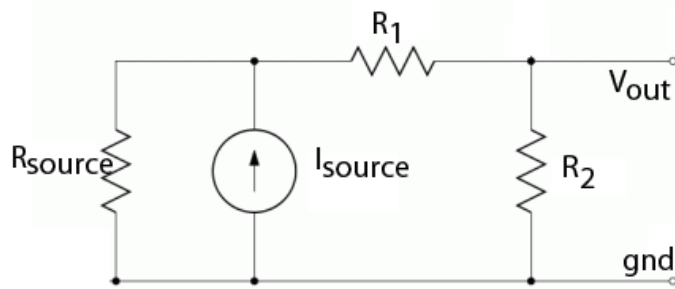- c) In the above analysis, you have assumed that  $V_{in}$  is an ideal voltage source. Suppose, instead of the voltage source, I use a Norton current source to drive the voltage divider as follows:




Derive an equation for  $V_{out}$  as a function of the various component values above.


- 2) Consider the following circuit:

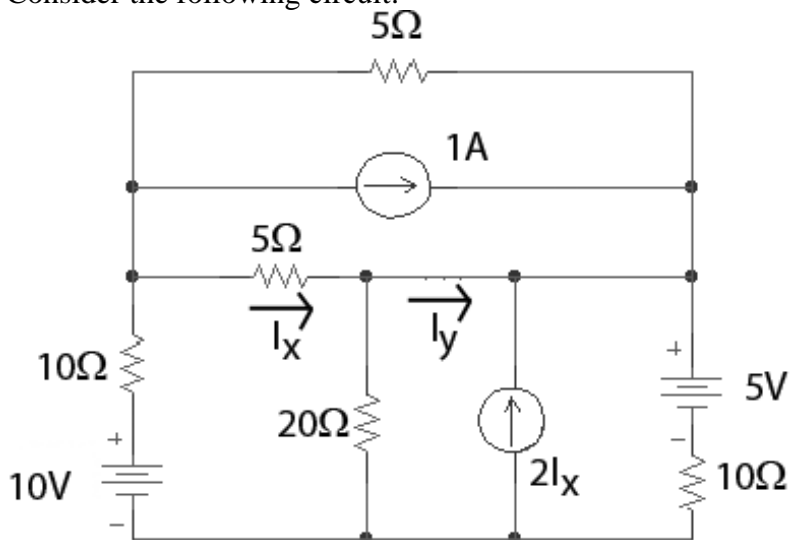

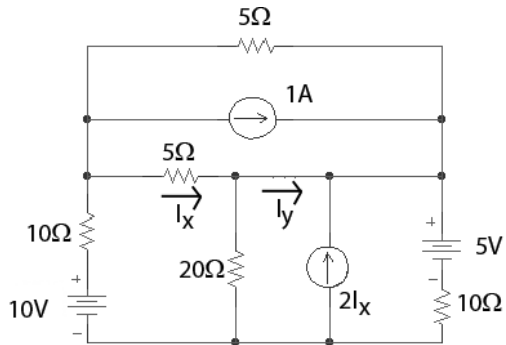- a) Calculate current  $I_y$  using nodal analysis (you can leave your answer in a simplified set of equations ; no need to find a final answer).




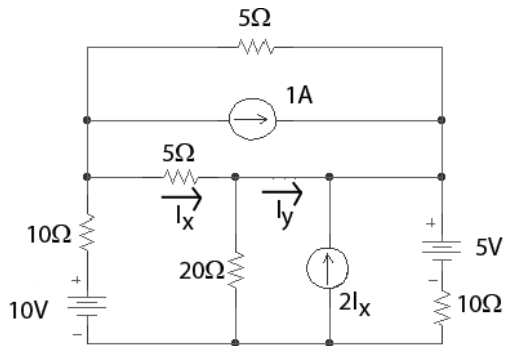- b) Similarly, calculate current  $I_y$  using mesh analysis (just set up the equations; no need to calculate the final solution).



- c) Ignoring your personal preference, would you recommend nodal or mesh analysis for the analysis of this circuit? Why?

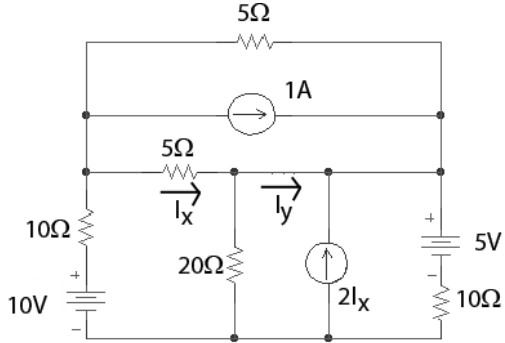- d) Analyze the circuit above to find  $I_y$  using superposition (again, just show the equations; no need to calculate a final solution).



- e) Replace the dependent current source with a  $2\text{A}$  constant current source. Derive the matrix equation to be solved if this circuit were to be solved by inspection.

