

Fall 2011

EE 40

Midterm 2

NAME:           *Solution*          

SSID: \_\_\_\_\_

*Instructions*

Read all of the instructions and all of the questions before beginning the exam.

There are 4 problems in this exam. The total score is 100 points. Points are given next to each problem to help you allocate time. Do not spend all your time on one problem.

Unless otherwise noted on a particular problem, you must show your work in the space provided, on the back of the exam pages or in the extra pages provided at the back of the exam. Simply providing answers will only result in partial credit, even if the answers are correct.

Draw a **BOX** or a **CIRCLE** around your answers to each problem.  
Be sure to provide units where necessary.

GOOD LUCK!

<b>PROBLEM</b>	<b>POINTS</b>	<b>MAX</b>
<b>1</b>		<b>15</b>
<b>2</b>		<b>25</b>
<b>3</b>		<b>40</b>
<b>4</b>		<b>20</b>


"Pessimism is just an ugly word for pattern recognition."

-Anonymous

Problem 1 Quickie

(12.5 points)

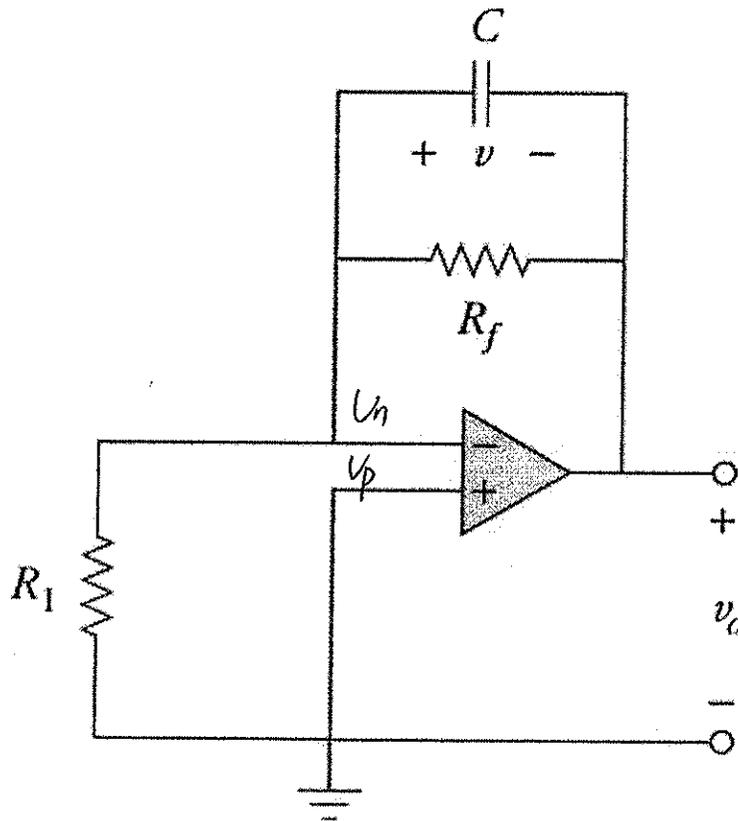a) In the box below, provide a symbolic expression for  $v_o$  for  $t > 0$  if  $v(0) = 4$  V.



$$V_o = -V(0) e^{-\frac{t}{R_f C}} \quad (V) \quad t > 0$$

Ideal Op :  $v_n = v_p = 0$  .  $\therefore$  No current goes into  $R_1$ .

$$\therefore \tau = C \cdot R_f.$$

$$V_o(\infty) = 0, \quad V_o(0) = -V(0)$$

$$\therefore V_o(t) = -V(0) e^{-\frac{t}{R_f C}} \quad (V)$$

b) If  $R_f = 40 \text{ k}\Omega$ ,  $R_1 = 10 \text{ k}\Omega$ ,  $C = 10 \text{ }\mu\text{F}$ , and  $v(0) = 4 \text{ V}$ , write the expression for  $v_o$  for  $t > 0$  in the **BOX BELOW**. (2.5 points)

$$V_o(t) = -4 e^{-\frac{t}{0.4}} \quad (\text{V}) \quad t > 0$$

$$R_f \cdot C = 40 \text{ k} \cdot 10 \text{ }\mu\text{F} = 0.4$$


"If a person offends you... do not resort to extremes,  
simply watch your chance and hit him with a brick."

- Mark Twain

**Problem 2 First order circuits**

(25 points)

Consider the circuit below.

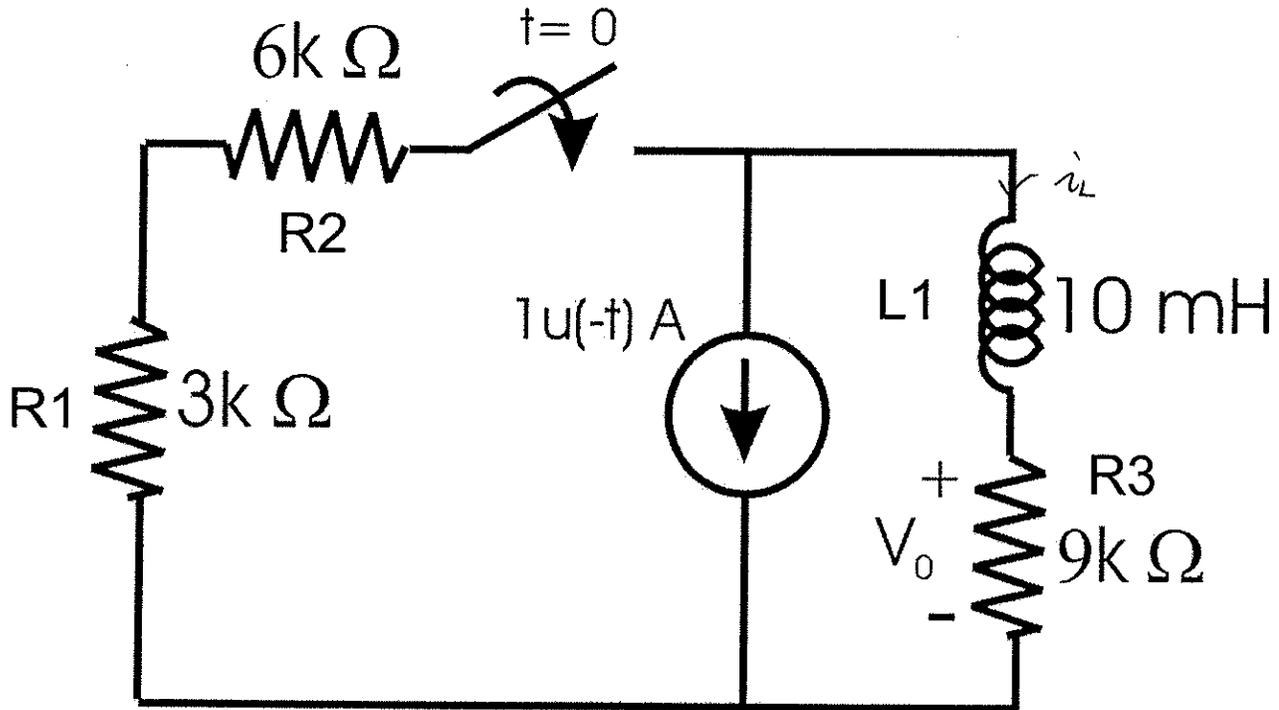

a) What is the value of  $V_0$  at  $t = 0^+$ ? Write It in the BOX BELOW. (5 points)

$$V_0(0^+) = -9000 \text{ V.}$$

$$i_L(0^-) = -1 \text{ A} \Rightarrow i_L(0^+) = -1 \text{ A.}$$

$$V_0(0^+) = i_L(0^+) \cdot R_3 = -9000 \text{ V.}$$

b) Using whatever method you like (yes, anything, don't raise your hand to ask if you can use ~~XXX~~), provide a symbolic expression for the voltage  $V_0(t)$  for  $t > 0$  in the **BOX BELOW**. (17.5 points)

$$V_0(t) = -R_3 e^{-\frac{(R_1+R_2+R_3)t}{L_1}} \quad (V) \quad t > 0.$$

$$\tau = \frac{L}{R_{eq}} = \frac{L_1}{R_1 + R_2 + R_3}$$

$$V(0^+) = -R_3$$

$$V(\infty) = 0.$$

$$V(t) = -R_3 e^{-\frac{t}{\tau}}$$

c) Using the values provided in the figure, provide an expression for the voltage  $V_0(t)$  for  $t > 0$  in the **BOX BELOW**. (2.5 points)

$$V_0(t) = -9000 e^{-1.8 \times 10^6 t} \quad (V) \quad t > 0.$$

$$R_3 = 9000.$$


$$\frac{L_1}{R_1 + R_2 + R_3} = \frac{10 \text{ mH}}{3\text{k} + 6\text{k} + 9\text{k}} = \frac{5}{9} \times 10^{-6}$$

"Accept that some days you are the pigeon, and some days you are the statue."  
 -David Brent, The Office

**Problem 3 Second order circuits**

(40 points)

Consider the circuit below.

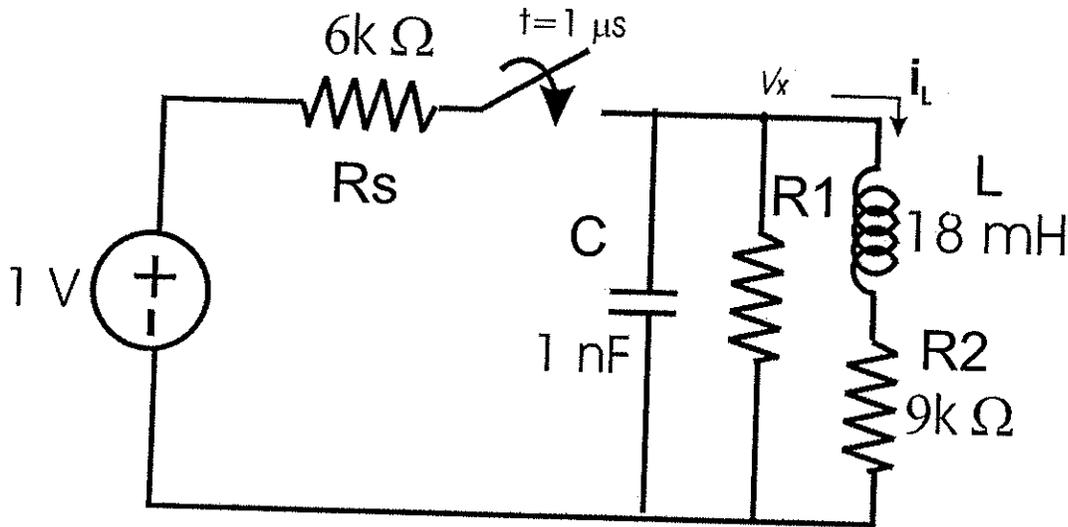

a) Find the second order **differential equation** for the variable  $i_L$  that describes the circuit behavior for  $t > 1 \mu s$ . Write into the box below. (15 points)

$$\frac{d^2 i_L}{dt^2} + \left( \frac{1}{R_5 C} + \frac{1}{R_1 C} + \frac{R_2}{L} \right) \frac{d i_L}{dt} + \frac{1}{LC} \left( \frac{R_2}{R_5} + \frac{R_2}{R_1} + 1 \right) i_L = \frac{1}{LC R_5}$$

KCL @  $V_x$        $\frac{V_x - 1}{R_5} + C \frac{dV_x}{dt} + \frac{V_x}{R_1} + i_L = 0$       ①

$V_x = L \frac{d i_L}{dt} + i_L R_2$       ②

② → ①       $\frac{L}{R_5} \frac{d i_L}{dt} - \frac{1}{R_5} + \frac{R_2}{R_5} i_L + CL \frac{d^2 i_L}{dt^2} + CR_2 \frac{d i_L}{dt} + \frac{L}{R_1} \frac{d i_L}{dt} + \frac{R_2}{R_1} i_L + i_L = 0$

⇒  $CL \frac{d^2 i_L}{dt^2} + \left( \frac{L}{R_5} + CR_2 + \frac{L}{R_1} \right) \frac{d i_L}{dt} + \left( \frac{R_2}{R_5} + \frac{R_2}{R_1} + 1 \right) i_L = \frac{1}{R_5}$

⇒  $\frac{d^2 i_L}{dt^2} + \left( \frac{1}{R_5 C} + \frac{R_2}{L} + \frac{1}{R_1 C} \right) \frac{d i_L}{dt} + \frac{1}{LC} \left( \frac{R_2}{R_5} + \frac{R_2}{R_1} + 1 \right) i_L = \frac{1}{LC R_5}$

b) Is there a value for  $R_1$  such that the resonant circuit can be *critically damped* for  $t > 1 \mu\text{s}$ ? (5 points)

Please show your equations clearly.

If YES, write the value here:

If NO, provide an expression that shows why not here:

$R_1 = -3 + 3\sqrt{2} \text{ k}\Omega$	
--	--

$$\alpha = \frac{1}{2} \left( \frac{R_2}{L} + \frac{1}{CR_5} + \frac{1}{CR_1} \right) = \frac{1}{2} \left( \frac{9\text{k}}{18\text{mH}} + \frac{1}{1\text{nF} \times 6\text{k}} + \frac{1}{1\text{nF} \times R_1} \right) = \left( \frac{1}{3} + \frac{1}{2R_1} \right) \times 10^6$$

$$\omega_0 = \sqrt{\frac{1}{LC} \left( \frac{R_2}{R_5} + \frac{R_2}{R_1} + 1 \right)} = \sqrt{\frac{1}{1\text{nF} \times 18\text{mH}} \left( \frac{9}{6} + \frac{9}{R_1} + 1 \right)} = \sqrt{\frac{1}{2R_1} + \frac{5}{36}} \times 10^6$$

Critical damped  $\alpha = \omega_0$

$$\therefore \left( \frac{1}{3} + \frac{1}{2R_1} \right) \times 10^6 = \sqrt{\frac{1}{2R_1} + \frac{5}{36}} \times 10^6$$

$$\Rightarrow \frac{1}{9} + \frac{1}{3R_1} + \frac{1}{4R_1^2} = \frac{1}{2R_1} + \frac{5}{36}$$

$$\Rightarrow 4R^2 + 12R_1 + 9 = 18R_1 + 5R_1^2$$

$$\Rightarrow R_1^2 + 6R_1 - 9 = 0$$

$$\Rightarrow R_1 = \frac{-6 + \sqrt{36 + 36}}{2} = -3 + 3\sqrt{2} \text{ k}\Omega$$

c) Determine the **two relevant** initial conditions of the circuit

(5 points)

Condition 1:

$$i_L(1\text{ms}^+) = 0$$

Condition 2:

$$i_L'(1\text{ms}^+) = 0$$

$$i_L(1\text{ms}^-) = 0 \quad \Rightarrow \quad i_L(1\text{ms}^+) = 0$$

$$V_C(1\text{ms}^-) = 0 \quad \Rightarrow \quad V_C(1\text{ms}^+) = 0$$

$$L i_L'(1\text{ms}^+) + i_L(1\text{ms}^+) \cdot R_2 = V_C(1\text{ms}^+)$$

$$\Rightarrow i_L'(1\text{ms}^+) = 0$$

d) Assuming  $R_1 = 9000 \Omega$ , provide a complete expression for  $i_L(t)$  for  $t > 1 \mu s$ .

(15 points)

$$i_L(t) = \frac{1}{21} + e^{-\frac{7}{18} \times 10^6 (t-1\mu s)} \left[ \frac{-1}{21} \cos\left(\frac{\sqrt{14}}{18} \times 10^6 (t-1\mu s)\right) - \frac{1}{3\sqrt{14}} \sin\left(\frac{\sqrt{14}}{18} \times 10^6 (t-1\mu s)\right) \right] \text{ mA}$$

From b.

$$\alpha = \left(\frac{1}{3} + \frac{1}{2R_1}\right) \times 10^6 = \frac{7}{18} \times 10^6$$

$$\omega_0 = \sqrt{\frac{5}{36} + \frac{1}{2R_1}} \times 10^6 = \sqrt{\frac{7}{36}} \times 10^6$$

$$\alpha^2 - \omega_0^2 = \left[\frac{7 \times 7}{18 \times 18} - \frac{7 \times 9}{36 \times 4}\right] \times 10^{12} < 0 \quad \therefore \alpha < \omega_0$$

Underdamped.

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{\frac{(63-49)}{18 \times 18}} \times 10^{12} = \frac{\sqrt{14}}{18} \times 10^6$$

$$i_L(\infty) = \frac{1}{2} \cdot \frac{1}{6k + (9k/19k)} = \frac{1}{21k} = \frac{1}{21} \text{ mA}$$

$$i_L(t) = i_L(\infty) + e^{-\alpha(t-1\mu)} \left[ B_1 \cos \omega_d(t-1\mu) + B_2 \sin \omega_d(t-1\mu) \right]$$

$$B_1 = -i_L(\infty) = \frac{-1}{21} \times 10^{-3}$$

$$B_2 = \frac{i_L'(0) + \alpha [i_L(0) - i_L(\infty)]}{\omega_d} = \frac{-\frac{7}{18} \times 10^6 \times \frac{1}{3 \times 21} \times 10^{-3}}{\frac{\sqrt{14}}{18} \times 10^6} = \frac{-1}{3\sqrt{14}} \times 10^{-3}$$


"I know they were just kids...but man we beat the f\$%! out of them!"

- Dogma

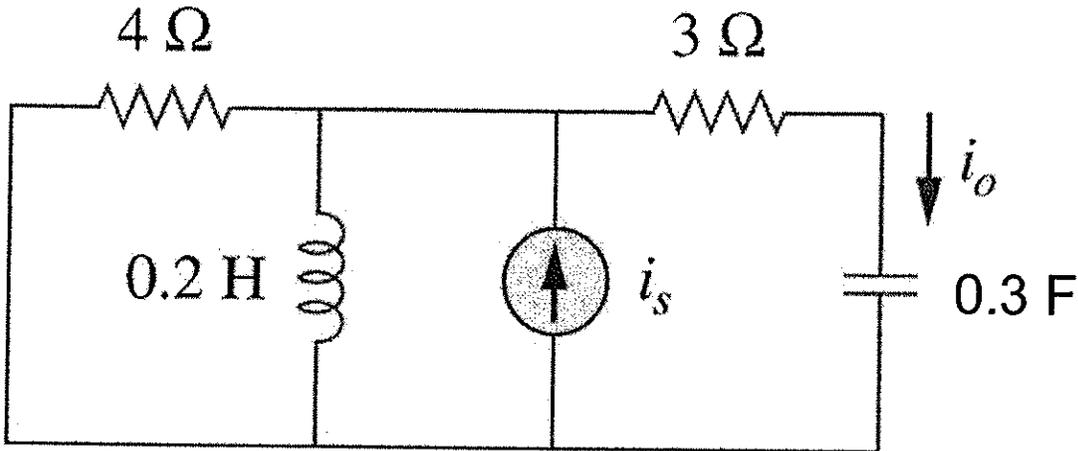Problem 4 Phasors


(20 points)

If  $i_s = 5 \cos(10t + 40^\circ)$  A in the circuit below, find  $i_o$



$$i_o(t) = \frac{30\sqrt{2}}{19} \cos(10t + 85^\circ) \text{ A}$$

$$I_s = 5 e^{j40^\circ}$$

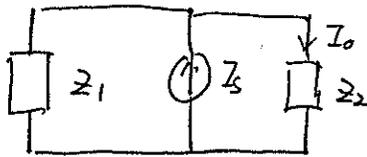

$$Z_1 = 4 \parallel 2j = \frac{8j}{4+2j}$$

$$Z_2 = 3 + \frac{1}{3j}$$

$$I_o = \frac{Z_1}{Z_1 + Z_2} \cdot I_s$$

$$\begin{aligned}
 I_o &= \frac{\frac{8j}{4+2j}}{\frac{8j}{4+2j} + 3 + \frac{1}{3j}} \cdot 5 e^{j40^\circ} = \frac{8j \times 5 e^{j40^\circ}}{8j + 12 + 6j + \frac{4}{3}j + \frac{2}{3}} = \frac{40 e^{j130^\circ}}{\frac{38}{3} + \frac{38}{3}j} \\
 &= \frac{40}{\frac{38}{3}\sqrt{2}} \cdot \frac{e^{j130^\circ}}{e^{j45^\circ}} = \frac{30}{19}\sqrt{2} e^{j85^\circ}
 \end{aligned}$$

Page for extra work

x	atan(x) radians	atan(x) degrees
0	0	0
0.1	0.099668652	5.710593137
0.2	0.19739556	11.30993247
0.3	0.291456794	16.69924423
0.4	0.380506377	21.80140949
0.5	0.463647609	26.56505118
1	0.785398163	45
1.5	0.982793723	56.30993247
2	1.107148718	63.43494882
3	1.249045772	71.56505118
4	1.325817664	75.96375653
5	1.373400767	78.69006753
6	1.405647649	80.53767779
100	1.56079666	89.4270613