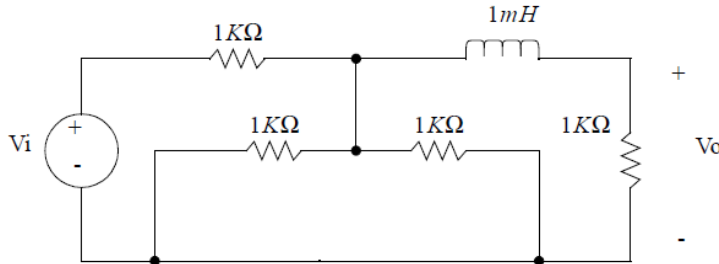


UNIVERSITY OF CALIFORNIA
Department of Electrical Engineering and Computer Sciences
EE42/100 Fall 2011

Prof. Subramanian

Test 3 Solutions**FOR ALL QUESTIONS, ASSUME OP-AMPS ARE IDEAL UNLESS OTHERWISE STATED**

1) Consider the circuit below:



- a) Derive an equation for the transfer function. Your answer should be in the form of a single equation (i.e., solve any simultaneous equations that you establish; this problem is easy enough to solve without a calculator).

3 pts

$$\sum I_{V_a} = \frac{V_a - V_i}{1K\Omega} + \frac{V_a}{1K\Omega} + \frac{V_a}{1K\Omega} + \frac{V_a - V_o}{0.001D} = 0$$

$$V_a \left(\frac{3}{1K\Omega} + \frac{1}{0.001D} \right) + V_i \left(\frac{-1}{1K\Omega} \right) = V_o \left(\frac{1}{0.001D} \right) \quad (1)$$

$$\sum I_{V_o} = \frac{V_o - V_a}{0.001D} + \frac{V_o}{1K\Omega} = 0$$

$$V_o \left(\frac{1}{0.001D} + \frac{1}{1K\Omega} \right) = V_a \left(\frac{1}{0.001D} \right)$$

$$V_o \left(\frac{0.001D + 1K\Omega}{1K\Omega} \right) = V_a \quad (2)$$

substitute (2) into (1)

$$V_o \left(\frac{0.001D + 1K\Omega}{1K\Omega} \right) \left(\frac{3}{1K\Omega} + \frac{1}{0.001D} \right) + V_i \left(\frac{-1}{1K\Omega} \right) = V_o \left(\frac{1}{0.001D} \right)$$

$$\frac{V_o}{V_i} = \frac{\frac{1}{1K\Omega}}{\left(\frac{0.001D + 1K\Omega}{1K\Omega} \right) \left(\frac{3}{1K\Omega} + \frac{1}{0.001D} \right) - \left(\frac{1}{0.001D} \right)}$$

- b) If $V_i = 10\sin(1E6*t)$, determine V_o . Please simplify as much as you can without a calculator; you should certainly be able to get the answer into the form of a single complex number.

for the given input of $V_i(t) = 10\sin(1,000,000 t)$,

$$\frac{V_o}{10 + 0j} = \frac{\frac{1}{1K\Omega}}{\left(\frac{0.001j10^6 + 1K\Omega}{1K\Omega} \right) \left(\frac{3}{1K\Omega} + \frac{1}{0.001(j10^6)} \right) - \left(\frac{1}{0.001(j10^6)} \right)}$$

$$\frac{V_o}{10 + 0j} = \frac{10^{-3}}{(j+1)(3 \times 10^{-3} - j10^{-3}) + j(10^{-3})}$$

$$\frac{V_o}{10 + 0j} = \frac{1}{(j+1)(3-j) + j}$$


$$\frac{V_o}{10 + 0j} = \left(\frac{1}{4+3j} \right) \left(\frac{4-3j}{4-3j} \right)$$

$$V_o = 10 \left(\frac{4-3j}{25} \right) = 2 \angle -0.644$$

$$V_o(t) = 2.00 \sin(10^6 t - 0.644) V$$

2 pts

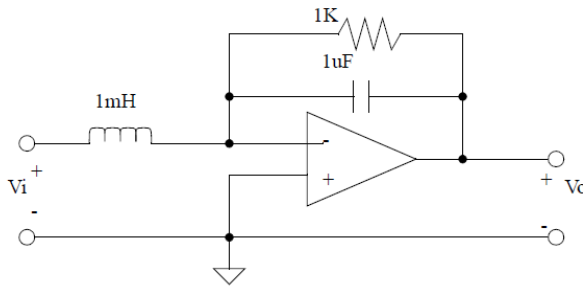2) Derive the transfer function for the following circuit:




4 pts

$$\frac{V_{out}}{V_{in}} = \frac{-R \parallel Z_c}{Z_L} = \frac{-R}{(1 + j\omega RC)j\omega L} = \frac{-10^6}{j\omega(1 + j\omega 10^{-3})}$$

3) Consider the following filter circuits:

3 pts

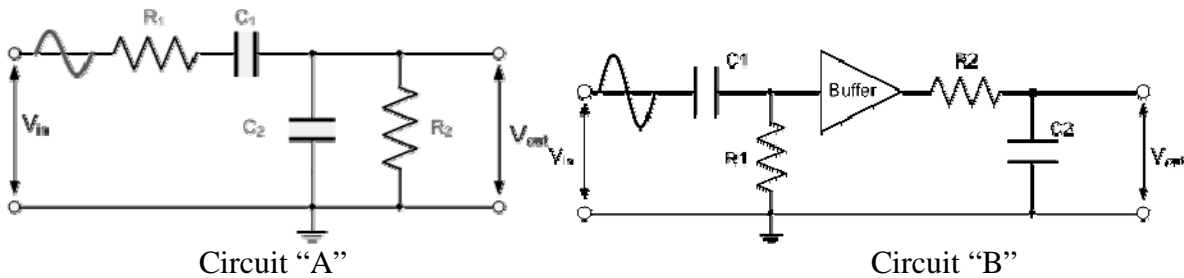

a) What type of filter is circuit "A"? Give reasons for your answer.

This is probably a band-pass filter, since $R1C1$ passes high frequency, while $R2C2$ rejects high frequencies. Assuming $R1C1 < R2C2$, this will be bandpass

b) Circuit "B" is supposed to be an improvement on circuit "A". How does the buffer improve the circuit operation?

The buffer separates the individual 1st order elements so they don't load each other.

c) Usually, for audio applications, we often find that LC filters are difficult / expensive to use. Why?

For audio applications, due to the low frequencies, the size of the L's and C's are large; large L values are typically expensive to build.

- 4) Sketch a bode plot for the magnitude and phase of the following transfer function. Please make sure you label everything properly.

8 pts

$$G(s) = \frac{10s^2 \left(1 + \frac{s}{10^2}\right) \left(1 + \frac{s}{10^6}\right)^2}{\left(1 + \frac{s}{10}\right)^2 \left(1 + \frac{s}{10^3}\right) \left(1 + \frac{s}{10^5}\right)^4}$$

where $s = j\omega$
and G is the gain of the system in V/V.

