

Name Rubrik SID _____

EE42/100 Midterm 1
 -1 for missing/wrong units
 -3 for gross calculation error

NO CALCULATORS, CELL PHONES, or other electronics allowed. Show your work, and put final answers in the boxes provided. Use proper units in all answers.

1. [5] You have a copper trace on a Printed Circuit Board that is 10cm long and 1mm wide. The thickness of the copper is 0.1mm. The resistivity of copper is 1.7×10^{-8} Ohm-m. Calculate the resistance of the wire.

$$\rho \frac{L}{A} = 1.7 \times 10^{-8} \frac{10^{-1}}{10^{-3} \cdot 10^{-4}} = 1.7 \times 10^{-2} \Omega$$

$R = 17 m\Omega$

2. [10] An electric car has a rechargeable battery with a capacity of 60kWh. A standard J1772 charger supplies 30A at 200V. What is the power output of the charger (use the correct units)? If the battery is completely empty, how long does it take to fully charge it from the J1772 charger?

$$P = IV = (30A)(200V) = 6kW$$


$$T = \frac{E}{P} = \frac{60kWh}{6kW} = 10h$$

$P = 6kW$

$T = 10h$

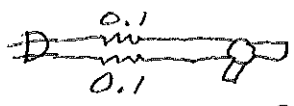3. [10] You have a hair dryer that is rated at 1,200W. You plug it into a 3-wire extension cord. Each wire in the extension cord has a resistance of 0.1 Ohms. You plug the extension cord into an ideal 120V outlet. Estimate the current in the hair dryer, and the power dissipated in the extension cord.

$$I = \frac{P}{V} = \frac{1200}{120} = 10A$$




$I = 10A$

$P = 20W$

10W - 2
30W - 2


$$P_{cord} = 2(10A)^2(0.1\Omega) = 20W$$

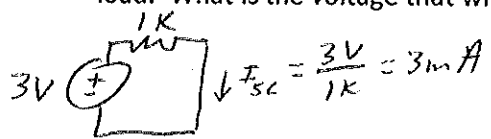4. [10] A lithium coin cell battery has a Thevenin equivalent circuit model with $V_{eq} = 3V$ and $R_{eq} = 1k\Omega$. What is the current that will flow if you short-circuit the battery? You connect the battery to a $4k\Omega$ resistive load. What is the voltage that will appear across the load?




$I = 3mA$


$V = 2.4V$

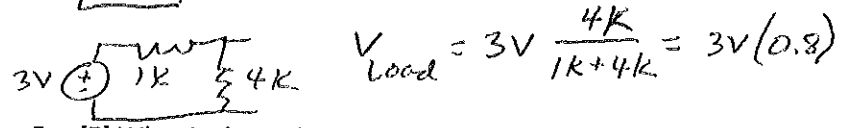

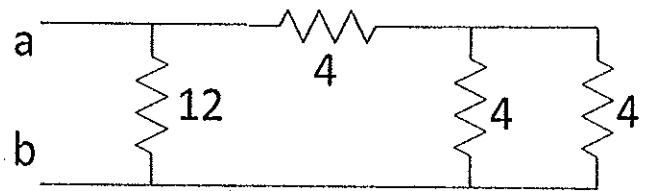
5. [5] What is the resistance between nodes a and b in the figure below?



$R = 4\Omega$

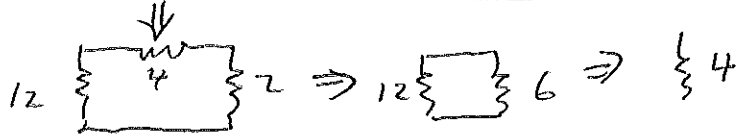

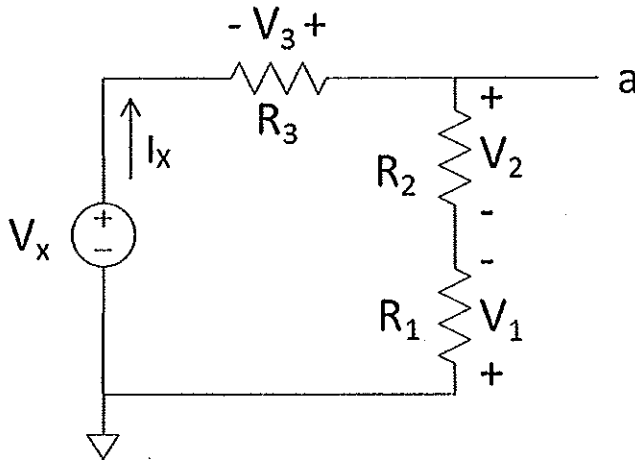6. [20] For the figure below, write an expression for the voltage at node a in terms of V_1 and V_2 only. Write an expression for the voltage at node a in terms of V_x and V_3 only. Write an expression for V_1 in terms of I_x and R_1 only. Write an expression for V_2 in terms of I_x and R_2 only.



$V_a(V_1, V_2) = -V_1 + V_2$ signs 4




$V_a(V_x, V_3) = V_x + V_3$ signs 4

$V_1(I_x, R_1) = -I_x R_1$ signs 4

$V_2(I_x, R_2) = I_x R_2$ signs 4

* If relationship wrong no credit

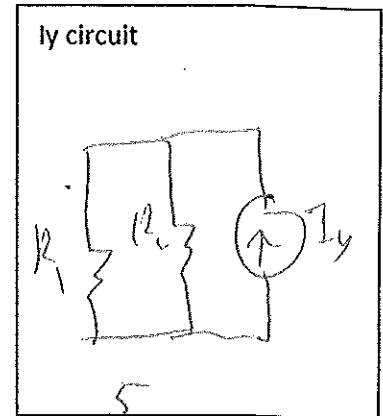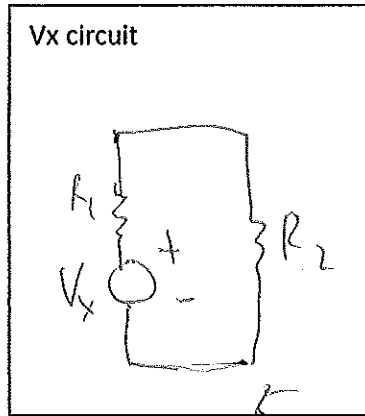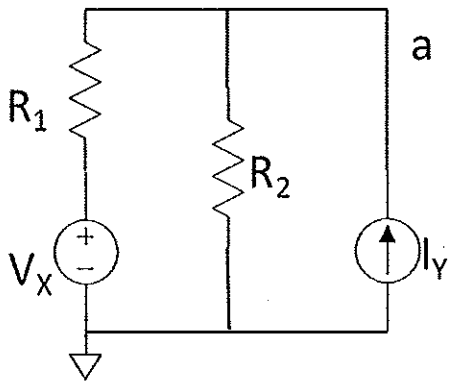7. [20] Use superposition to calculate the voltage at node a in the figure below by
- drawing the two simplified circuits corresponding to the individual independent sources
 - solving for the effect of each source and writing the equation for the output as a function of the independent sources




$V_a(V_x, I_y) = I_y \frac{R_1 R_2}{R_1 + R_2} + V_x \frac{R_2}{R_1 + R_2}$

If unit wrong, 0, If unit right, 1/2.

8. [25] You measure the performance of several identical diodes and find that they each pass 0.1mA of current at a forward bias of 0.6V.

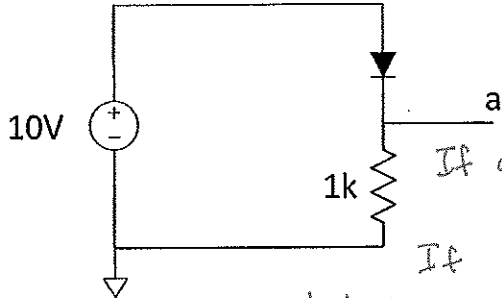- a. Estimate the bias necessary to get a diode to pass 1mA of current.
- b. Estimate the voltage at node a in the circuit below to within 10mV.



i) wrote down


$I_D = I_S 10^{V_d/60mV}$; $I_d = \frac{10 - V_d}{1k}$ (+1)

If assumed 1mA $\rightarrow V_d = 0.66V$
 $V_a = 9.34$ (+2)
 If $V_a = 1mA(1k)$ or $1mA(1k)$ (+0)

$V_d(1mA) = 660mV = 0.66V$ (+5)
 All or nothing unless off by obvious factor of 10. (+2)


$V_a = 9.28V$ (+5)

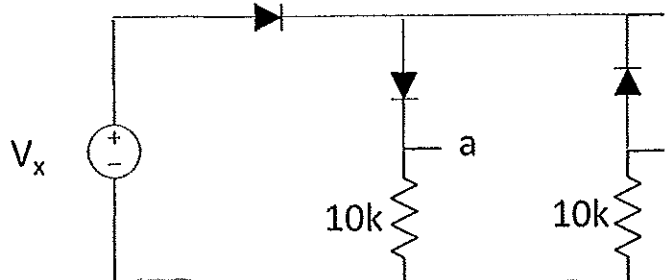- c. Given that the voltage at node a in the circuit below is 1V, estimate the voltage at nodes b and c, and the value of V_x .



All or nothing \rightarrow $V_b = 0$ or $10^{-14} \cdot 1 \times 10^4 = 10^{-10}$ (+5)
 $V_c = 1.6V$ (+5)
 $V_x = 2.2V$ (+5)
 If got $V_c = 1 + V_d$ and $V_x = 1 + 2V_d$ but used wrong V_0 : (+5) total
 if used $V_0 = 0.66V$ (+7) Total

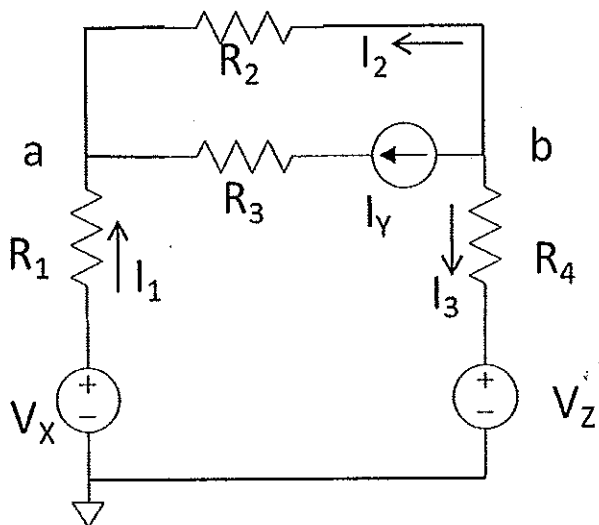9. [30] For the figure below, use nodal analysis and write the node voltage equations for the two extraordinary nodes. Equations should contain node voltages, resistors, and independent sources.



$I_1 + I_y + I_2 = 0$

node a $\frac{V_x - V_a}{R_1} + I_y + \frac{V_b - V_a}{R_2} = 0$

$I_2 + I_y + I_3 = 0$


node b $\frac{V_b - V_a}{R_2} + I_y + \frac{V_b - V_z}{R_4} = 0$

5pts per term
 -1 if no = sign
 -2 for wrong sign

Name Rubik

SID _____

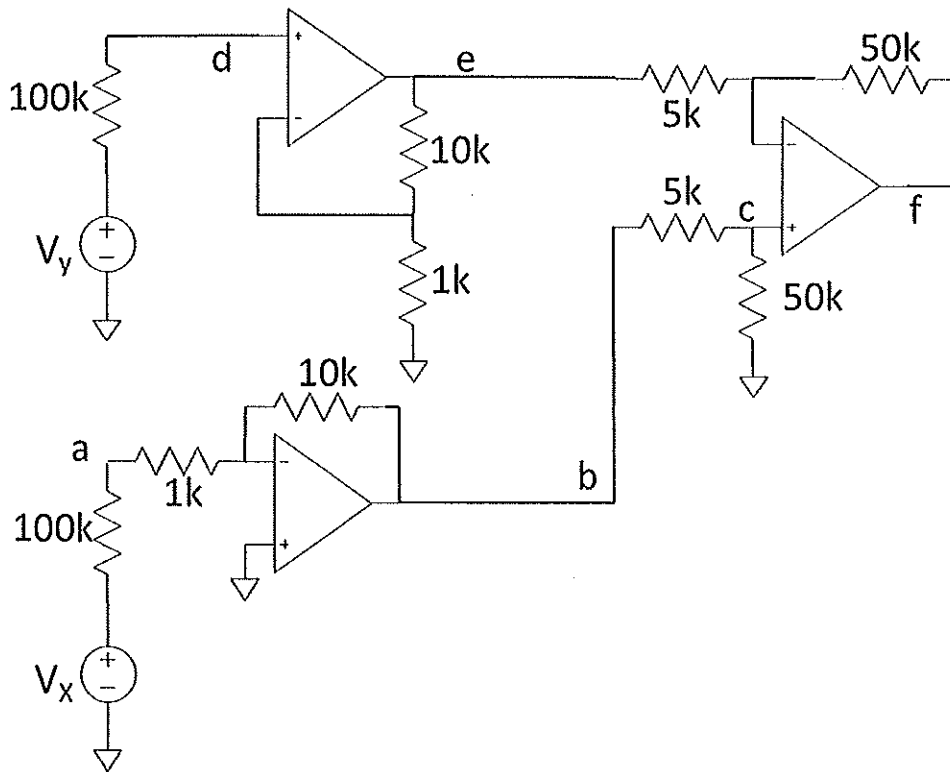10. [35] In the op-amp circuit below, find the gain from V_x to a, from a to b, from b to c, and so on.



Gain from V_x to a (= V_a / V_x) (this might be the hardest one)	$\frac{1k}{101k}$ 100k	$\frac{1}{100}$ -1 $\frac{100}{701}$ -3
Gain from Va to Vb (= V_b / V_a)	$-\frac{10k}{1k} = -10$	10 -2
Gain from Vb to Vc (= V_c / V_b)	$\frac{50k}{55k} = \frac{50}{55} = \frac{10}{11}$	$\frac{11}{10}$ -2 $\frac{1}{11}$ -3
Gain from Vc to Vf (= V_f / V_c)	$\frac{55k}{5k} = 11$	10 -2
Gain from Vy to Vd (= V_d / V_y)	1	
Gain from Vd to Ve (= V_e / V_d)	$\frac{11k}{1k} = 11$	-11 -2 10 -3
Gain from Ve to Vf (= V_f / V_e)	$-\frac{50k}{5k} = -10$	-11 -2 10 -2

+ other terms e.g. $\frac{V_b}{V_e} = -2$