

Name \_\_\_\_\_

SID \_\_\_\_\_

## EE42/100 Midterm 1

NO CALCULATORS, CELL PHONES, or other electronics allowed. Show your work, and put final answers in the boxes provided. Use proper units in all answers.

1. [5] You have a copper trace on a Printed Circuit Board that is 10cm long and 1mm wide. The thickness of the copper is 0.1mm. The resistivity of copper is  $1.7 \times 10^{-8}$  Ohm-m. Calculate the resistance of the wire.

2. [10] An electric car has a rechargeable battery with a capacity of 60kWh. A standard J1772 charger supplies 30A at 200V. What is the power output of the charger (use the correct units)? If the battery is completely empty, how long does it take to fully charge it from the J1772 charger?




3. [10] You have a hair dryer that is rated at 1,200W. You plug it into a 3-wire extension cord. Each wire in the extension cord has a resistance of 0.1 Ohms. You plug the extension cord into an ideal 120V outlet. Estimate the current in the hair dryer, and the power dissipated in the extension cord.




4. [10] A lithium coin cell battery has a Thevenin equivalent circuit model with  $V_{eq}=3V$  and  $R_{eq}=1k\Omega$ . What is the current that will flow if you short-circuit the battery? You connect the battery to a  $4k\Omega$  resistive load. What is the voltage that will appear across the load?



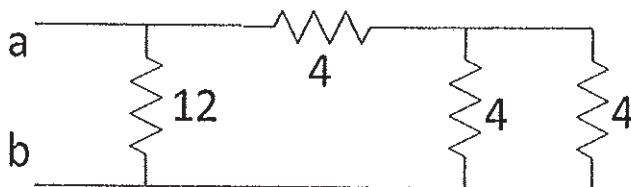5. [5] What is the resistance between nodes a and b in the figure below?



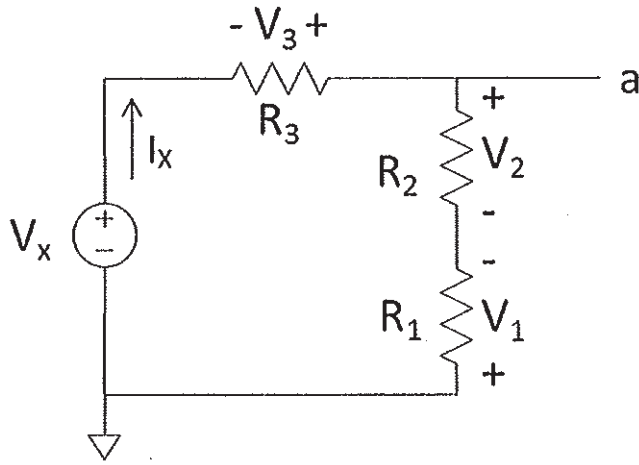6. [20] For the figure below, write an expression for the voltage at node a in terms of  $V_1$  and  $V_2$  only. Write an expression for the voltage at node a in terms of  $V_x$  and  $V_3$  only. Write an expression for  $V_1$  in terms of  $I_x$  and  $R_1$  only. Write an expression for  $V_2$  in terms of  $I_x$  and  $R_2$  only.






$V_a(V_1, V_2) =$

$V_a(V_x, V_3) =$

$V_1(I_x, R_1) =$

$V_2(I_x, R_2) =$

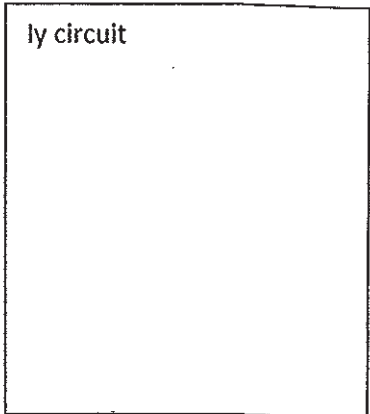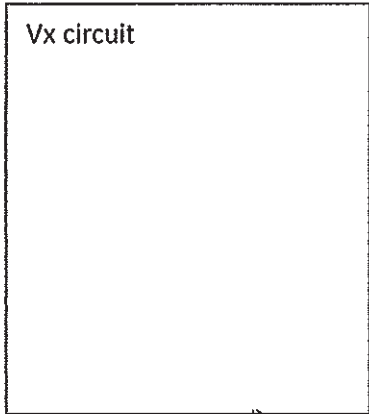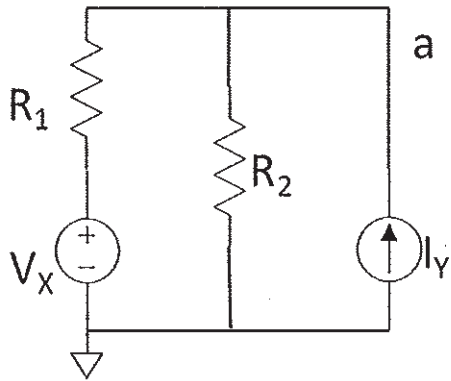7. [20] Use superposition to calculate the voltage at node a in the figure below by
- drawing the two simplified circuits corresponding to the individual independent sources
  - solving for the effect of each source and writing the equation for the output as a function of the independent sources




$V_a(V_x, I_y) =$

8. [25] You measure the performance of several identical diodes and find that they each pass 0.1mA of current at a forward bias of 0.6V.


$V_d(1mA) =$

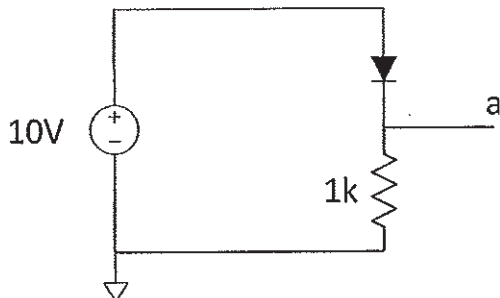- a. Estimate the bias necessary to get a diode to pass 1mA of current.
- b. Estimate the voltage at node a in the circuit below to within 10mV.



$V_a =$

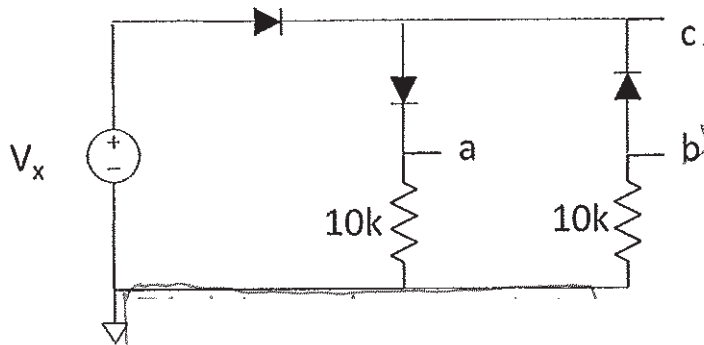- c. Given that the voltage at node a in the circuit below is 1V, estimate the voltage at nodes b and c, and the value of  $V_x$ .




$V_b =$

$V_c =$

$V_x =$

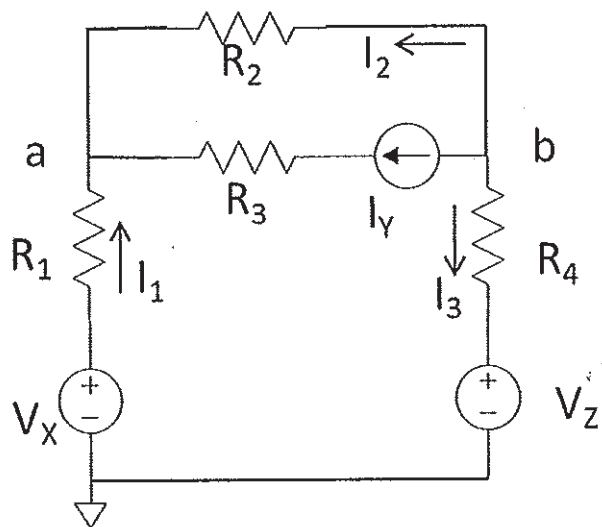9. [30] For the figure below, use nodal analysis and write the node voltage equations for the two extraordinary nodes. Equations should contain node voltages, resistors, and independent sources.




node a

node b

Name \_\_\_\_\_

SID \_\_\_\_\_

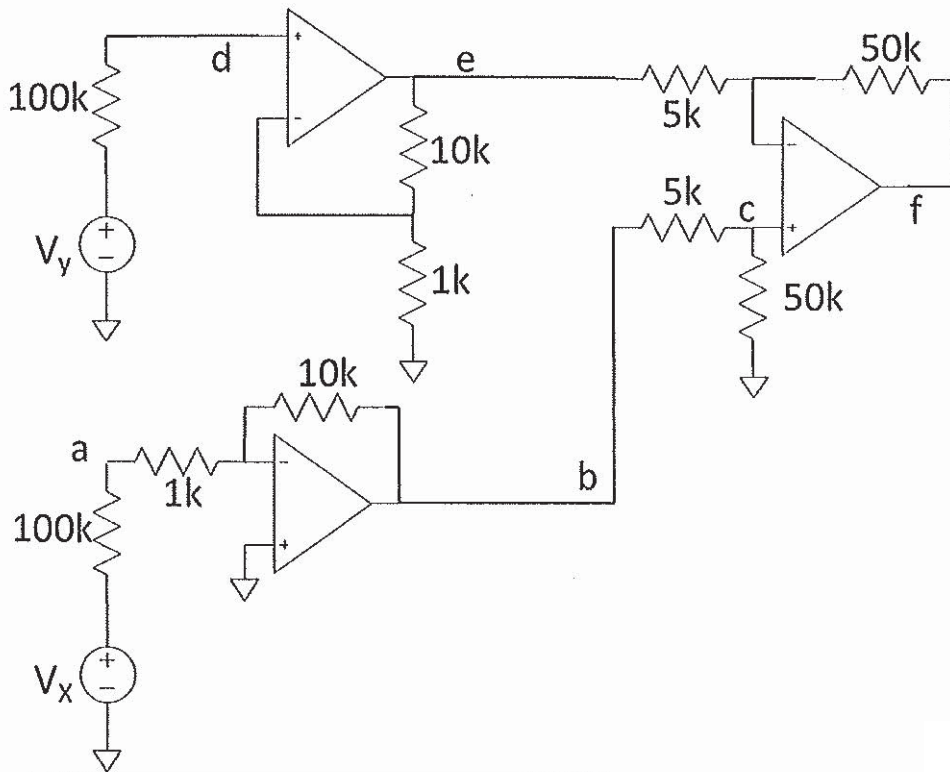10. [35] In the op-amp circuit below, find the gain from  $V_x$  to a, from a to b, from b to c, and so on.



Gain from $V_x$ to a ( $= V_a / V_x$ ) (this might be the hardest one)	
Gain from Va to Vb ( $= V_b / V_a$ )	
Gain from Vb to Vc ( $= V_c / V_b$ )	
Gain from Vc to Vf ( $= V_f / V_c$ )	
Gain from Vy to Vd ( $= V_d / V_y$ )	
Gain from Vd to Ve ( $= V_e / V_d$ )	
Gain from Ve to Vf ( $= V_f / V_e$ )	