

Name Early Rey SID _____

EE42/100 Midterm 2

NO CALCULATORS, CELL PHONES, or other electronics allowed. Show your work, and put final answers in the boxes provided. Use proper units in all answers.

15)

1. [5] Express the following power ratios in dB

P/Pref	P/Pref [dB]
20	13
50	17
2×10^{-10}	-97
$1/4$	-6
2.5×10^8	74

1 pt, no partial credit
no units necessary (dB) on top

no credit for answers that include log of anything.

2. [5] Express the following voltage ratios in dB

V/Vref	V/Vref [dB]
Sqrt(2)	3
$1/2$	-6
0.04	-28
1	0
2×10^{-3}	-24

$$2^2 \cdot 10^{-2} \Rightarrow 2 \cdot 6 = 2 \cdot 20$$

3. [8] You measure an AC voltage across a $1\text{k}\Omega$ resistor. The digital voltmeter that you use measures in RMS (like all voltmeters), and reports that the voltage is 1 V. *use units*

- a. What is the zero-to-peak voltage?

$$\cancel{V_{ZP}} = \sqrt{2} \cdot 1\text{V} = 1.4$$

$$\sqrt{2} \text{ OK}$$

$$V_{0\text{-p}} = 1.4\text{V}$$

- b. What is the peak-to-peak voltage

$$V_{P\text{-p}} = 2.8\text{V}$$

- c. What is the max power dissipated in the resistor?

$$\frac{(1.4)^2}{1\text{K}} = \frac{2\text{V}^2}{1\text{K}}$$

$$P_{\text{max}} = 2\text{mW}$$

- d. What is the average power dissipated in the resistor?

$$P_{\text{avg}} = 1\text{mW}$$

-1 missing unit


-2 all missing units

-1 right formula, wrong calc

Name _____

SID _____

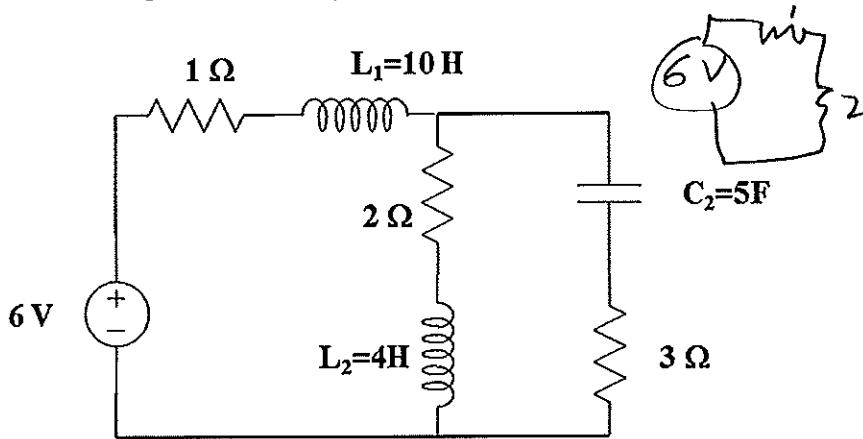4. [10] For the circuit below, calculate the steady state values for the current in the two inductors, the voltage across the capacitor, the energy stored in L_1 , and the energy stored in C_2 .



I_{L1}	2 A
I_{L2}	2 A
V_{C2}	4 V
W_{L1}	20 J
W_{C2}	40 J

OK if R
consistent w/ wrong answer above

$$\frac{1}{2} L_1 I^2 = \frac{1}{2} (10 \text{ H}) (2 \text{ A})^2 = 20$$

$$\frac{1}{2} C V^2 = \frac{1}{2} (5 \text{ F}) (4 \text{ V})^2 = 40$$

5. [10] Two capacitors, each $2\mu\text{F}$, are charged in parallel from a single AA battery with a voltage of 1.5V, and then discharged in series into a $1\text{k}\Omega$ load. The battery has a source resistance of 1Ω .

a. What is the equivalent capacitance seen by the battery during charging?

$$C_{\text{charge}} = 4 \mu\text{F}$$

b. What is the time constant during charging?

$$\tau_{\text{charge}} = 4 \mu\text{s}$$

c. What is the equivalent capacitance of the series combination driving the load?

$$C_{\text{series}} = 1 \mu\text{F}$$


d. What is the time constant during discharging?

$$\tau_{\text{discharge}} = 1 \text{ ms}$$

e. How long does it take for the output voltage to drop 5% after the phi2 switches are closed?

$$(5\%) (1 \text{ ms}) =$$

$$t_{5\%} = 50 \mu\text{s}$$

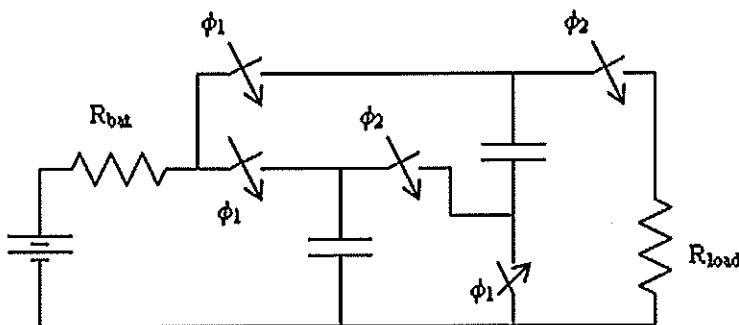


also accept $-0.001 \ln(0.95)$
-1 right formula wrong calc

Name _____

SID _____


1:58

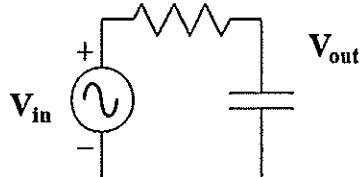6. [10] In the RC circuit below assume V_{in} is a voltage step from 0 to 10V at $t=0$. If $R=1$ and $C=1nF$, sketch the response of the circuit on the three different time scales provided.



$$\tau = RL = 10^{-9} \text{ s}$$
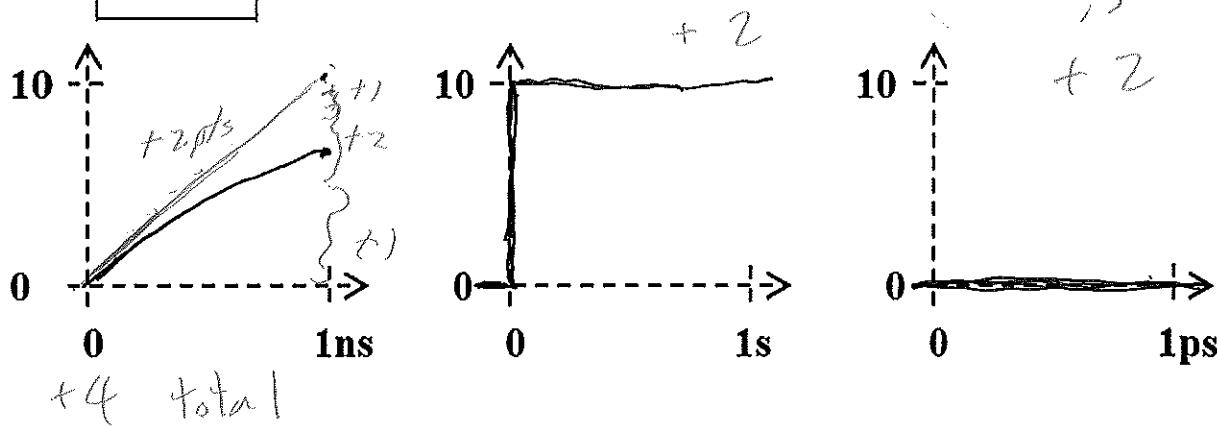
$$H(s) = \frac{1}{1 + j\omega/\omega_p}, \quad \omega_p = 10^9 \text{ rad/sec.}$$



7. [8] The RC circuit above is driven by an input signal $v_{in}(t) = \sin(100t) + \cos(10^9t)$. What is $V_{out}(t)$ in steady state?


$$V_{out}(t) = \cancel{100} \sin(100t) + \frac{1}{\sqrt{2}} \cos(10^9t - 45^\circ)$$

↑ 2 pts each
0V ↑ 1 each
 $\sin(100t - 10^\circ)$ ↑ 1 each

-3 pts total max

dB OK

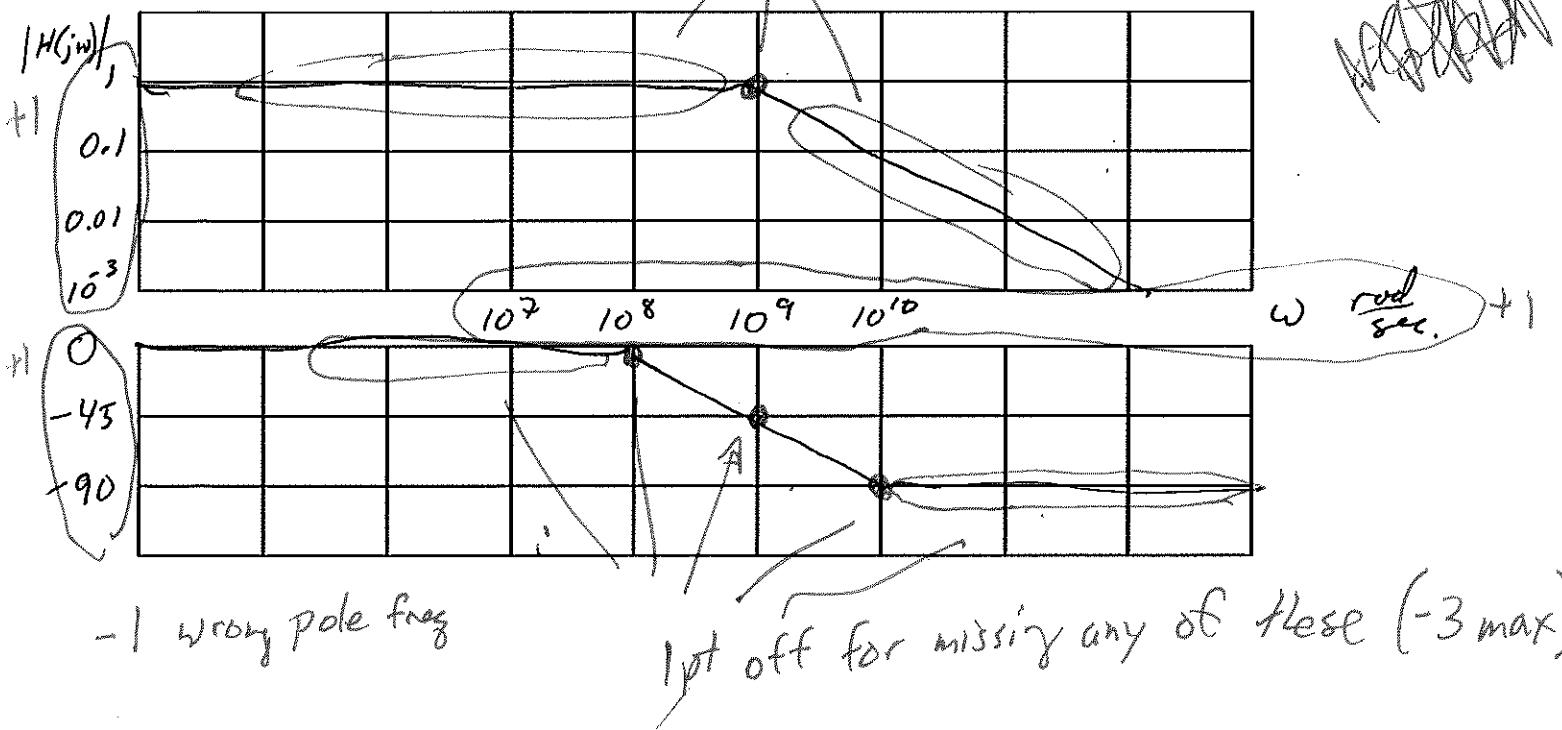8. [8] Sketch a Bode plot of the transfer function of the RC circuit above. Label each axis!



Name _____ SID _____

$$L = 10^{-4} \quad 10^7 = \frac{1}{\sqrt{10^{-4}C}} \quad 10^{14} = \frac{1}{10^{-4}L} \quad C = 10^{-10}$$

9. [18 total] You want to build an AM radio with an LC tank at a resonant frequency of 10^7 rad/sec. Your inductor is 100uH and has a series resistance of 20Ω .

a. [2] How big should your capacitor be?

$$C = 100 pF$$

b. [6] Sketch the magnitude of the inductor impedance (including series resistor) and capacitor impedance on the axes below. Label each axis!

c. [2] Assuming an ideal capacitor, what will the Q of your LC tank be?

$$\frac{\omega_p L}{R} = \frac{10^7 \cdot 10^{-4}}{20} = \frac{1000}{20} = 50$$

$$Q = 50$$

d. [2] What is the magnitude of the tank impedance at 1 rad/sec?

$$Z(j1) = 20$$

e. [2] What is the magnitude of the tank impedance at 10^6 rad/sec?

$$Z(j10^6) = 100$$


f. [2] What is the magnitude of the tank impedance at the resonant frequency?

$$Q = \omega_p L$$

$$Z(j\omega_p) = 50K$$

g. [2] What is the magnitude of the tank impedance at 10^9 rad/sec?

$$Z(j10^9) = 10$$

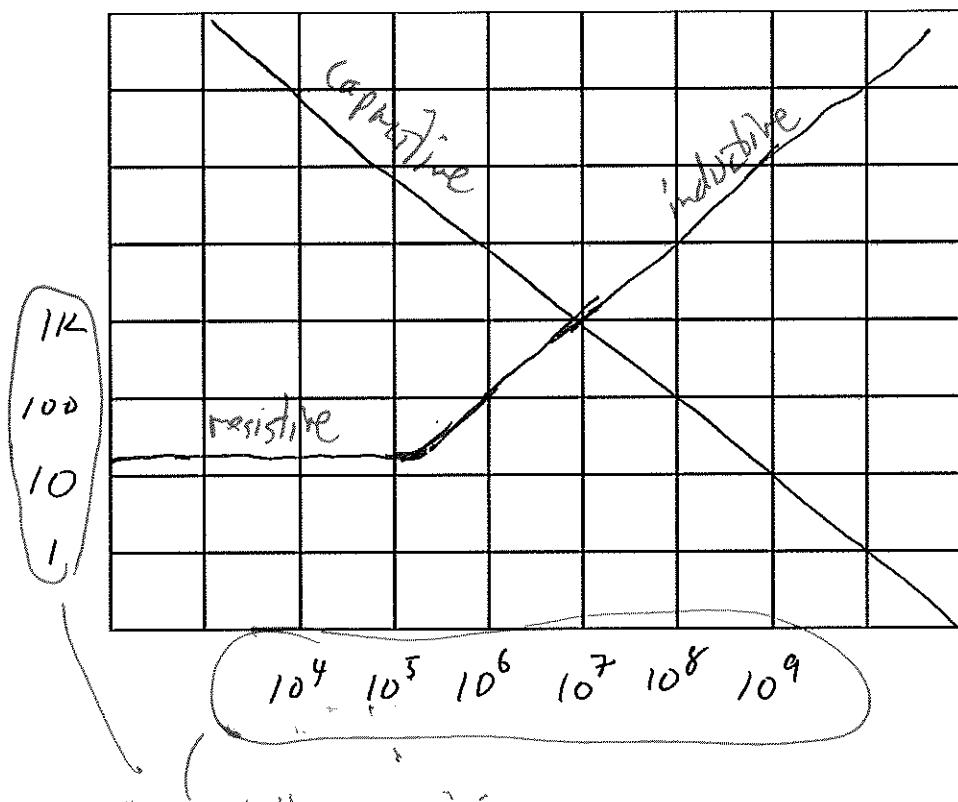

-1 total if either or both are missing

2 pts each for Resistive/Inductive, Capacitive pts { 1 pt shape
1 pt correct value.

Rubric:

- Off by 00M but wrote formula (Wrong no work $\ominus 2$). $\ominus 1$

only punished once on the problem for wrong units.

- (b) Missing axis (one or both) $\ominus 1$

- 1 pt. each for crossings
◦ 1 pt. each for shape

- $\ominus 1$ wrong units. $\ominus 1$

No units = ok.

- only Swiggle $\frac{1}{2}$ credit

Wrong L value $\ominus 1$

- $\ominus 1$ additionally if resistor and inductor not added correctly.

-
- $\ominus 1$ the formulas for Q (wrong answer)

$\ominus 1$

- $\ominus 1$ no axes labels.

- No simplification

$\ominus 1$

→

-
- 120Ω

$\ominus 1$ → wrong answer

- $\ominus 1$ 20Ω instead of 10Ω (didn't use C value)
→ used R instead)

full credit.

Find this paper:

- $\ominus 1$ did not multiply by Q

$\ominus 1$

- 120Ω versus 100Ω
- read off correctly from their graph: no punishment, ok.
- propagated wrong L value. ok. no punishment.

• inverted Q $\textcircled{-1}$

• just expression left but evaluates to correct answer $\textcircled{1}$

• symbolic expression $\textcircled{-2}$

} C is right
graph is wrong

$\textcircled{-2}$

answer is wrong, but taken from graph

• add Q instead
of multiply
by Q.

