

P1

V_{o_1} = output 1
(left op amp)

$$\text{KCL's: } -\frac{V_{in}}{R_1} - \alpha V_x - \frac{V_{o_1}}{R_2} = 0 \quad (1)$$

ideal op amps:

$$V_{n_1} = V_{p_1} = 0$$

$$\frac{V_{o_1} - V_{out}}{R_4} + \frac{V_{o_1}}{R_3} = 0 \quad (2)$$

$$V_{o_1} = V_{p_2} = V_{n_2}$$

(no current through
 R_5)

$$(2) \rightarrow V_{o_1} = V_{out} \frac{1}{R_4} \left(\frac{1}{1/R_4 + 1/R_3} \right)$$

$$V_x = V_{out} - V_{o_1}$$

$$(2) \rightarrow (1): 0 = -\frac{V_{in}}{R_1} - \alpha V_{out} + V_{o_1} \left(\alpha - \frac{1}{R_2} \right)$$

$$0 = -\frac{V_{in}}{R_1} - \alpha V_{out} + \frac{V_{out}}{R_4} \frac{1}{1/R_4 + 1/R_3} \left(\alpha - \frac{1}{R_2} \right)$$

$$\rightarrow \frac{V_{out}}{V_{in}} = \frac{1}{R_1} \left[-\alpha + \frac{1}{1/R_4 + 1/R_3} \left(\alpha - \frac{1}{R_2} \right) \right]^{-1}$$


$$\therefore \boxed{\text{gain} = \frac{1}{R_1} \left[-\alpha + \frac{R_3}{R_3 + R_4} \left(\alpha - \frac{1}{R_2} \right) \right]^{-1}}$$

or simplify

$$\boxed{\text{gain} = -\frac{R_2(R_3 + R_4)}{R_1 R_3 + \alpha R_1 R_2 R_4}}$$

P2

(a)

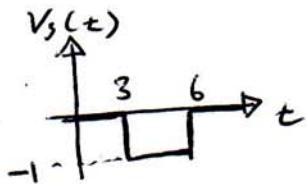

$$-\infty < t < 3 : \quad V_c(t) = 0$$

$$3 < t < 6 : \quad V_c(3) = 0 \quad V_c(\infty) = -1$$

$$V_c(t) = e^{-(t-3)/R_1 C} - 1$$


$$6 < t : \quad V(6) = e^{-3/R_1 C} - 1$$

$$V_c(t) = V_c(6) e^{-(t-6)/R_1 C} = (e^{-3/R_1 C} - 1) e^{-(t-6)/R_1 C}$$

$$\therefore V_c(t) = \begin{cases} 0 & t < 3 \\ e^{-(t-3)/R_1 C} - 1 & \text{for } 3 < t < 6 \\ (e^{-3/R_1 C} - 1) e^{-(t-6)/R_1 C} & t > 6 \end{cases}$$

(b)
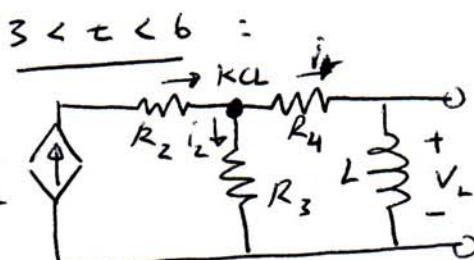
$$-\infty < t < 3 : \quad V_L(t) = 0 \quad V_L = L \frac{di_L}{dt}$$



$$\begin{aligned} \beta V_c &= i_L + i_2 = i_L + \frac{(i_L R_3 + L \frac{di_L}{dt})}{R_3} \\ &= i_L \left(\frac{R_3 + R_4}{R_3} \right) + \frac{L}{R_3} \frac{di_L}{dt} \end{aligned}$$

$$\rightarrow i_L \left(\frac{R_3 + R_4}{L} \right) + \frac{di_L}{dt} = \frac{R_3}{L} \beta V_c$$

for $3 < t < 6$,

$$\therefore i_L \underbrace{\left(\frac{R_3 + R_4}{L} \right)}_k + \frac{di_L}{dt} = \underbrace{\frac{R_3}{L} \beta}_{kA} \left[e^{-(t-3)/R_1 C} - 1 \right]$$

$$\rightarrow i_L = \frac{R_3 \beta}{R_3 + R_4 - \frac{L}{R_1 C}} \left[e^{-(t-3)/R_1 C} - 1 \right]$$

$$V_L = L \frac{di_L}{dt} = \frac{R_3 L \beta}{R_3 + R_4 - L/R_1 C} \left(-\frac{1}{R_1 C} \right) e^{-(t-3)/R_1 C}$$

$$V_L(t) = \frac{-R_3 L \beta}{R_1 C (R_3 + R_4) - L} e^{-(t-3)/R_1 C}$$

$t < t$:

$$i_L \underbrace{\left(\frac{R_3 + R_4}{L} \right)}_k + \frac{di_L}{dt} = \underbrace{\frac{R_3}{L} \beta (e^{-3/R_1 C} - 1)}_{kA} e^{-(t-6)/R_1 C}$$

$$\rightarrow i_L = \frac{R_3 \beta (e^{-3/R_1 C} - 1)}{R_3 + R_4 - L/R_1 C} e^{-(t-6)/R_1 C}$$


$$V_L(t) = \frac{L R_3 \beta (e^{-3/R_1 C} - 1)}{R_3 + R_4 - L/R_1 C} \left(-\frac{1}{R_1 C} \right) e^{-(t-6)/R_1 C}$$

$$= - \frac{L R_3 \beta (e^{-3/R_1 C} - 1)}{R_1 C (R_3 + R_4) - L} e^{-(t-6)/R_1 C}$$

$$\therefore V_L(t) = \begin{cases} 0 & t < 3 \\ - \frac{R_3 L \beta}{R_1 C (R_3 + R_4) - L} e^{-(t-3)/R_1 C} & 3 < t < 6 \\ - \frac{R_3 L \beta (e^{-3/R_1 C} - 1)}{R_1 C (R_3 + R_4) - L} e^{-(t-6)/R_1 C} & t > 6 \end{cases}$$

P3

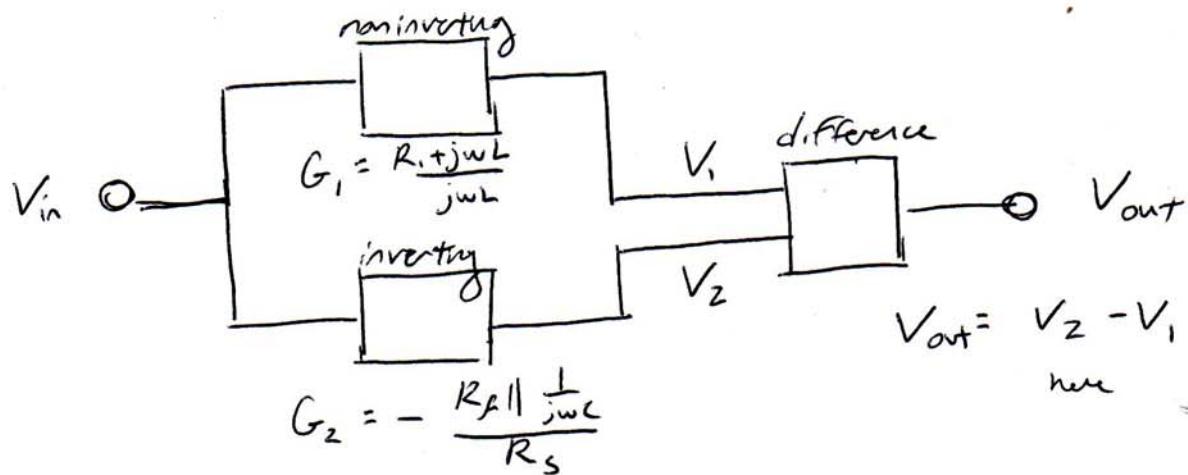Interpret as a network of transfer functions:



$$\therefore V_{out} = V_2 - V_i = \left(-\frac{R_f}{R_s} \frac{1}{(1+j\omega R_f C_f)} - \frac{R_i + j\omega L}{j\omega L} \right) V_{in}$$

$$H(\omega) = \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_s} \frac{1}{(1+j\omega R_f C_f)} - \frac{R_i}{j\omega L} - 1$$

P4


4x RC LPF
4x RL LPF
2x LC LPF

(a) multiple implementations


exist... here's one:

$$\omega_c = \frac{1}{RC}$$

$$N=4 \rightarrow$$

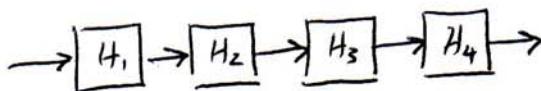

4 cascaded RC low-pass filters

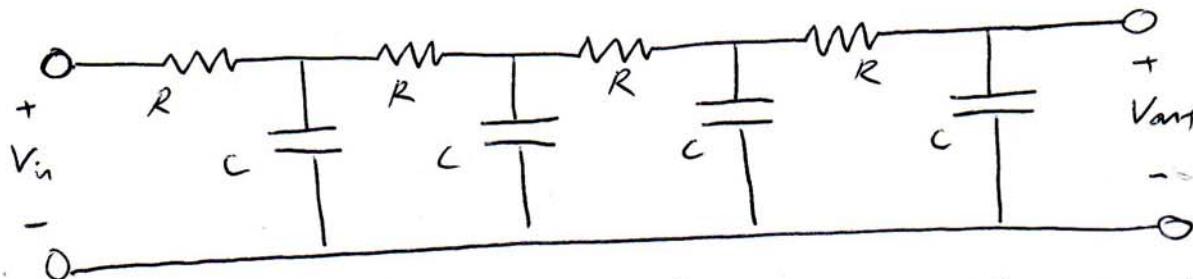

(b) $|H(\omega)| = \frac{1}{4} \rightarrow \boxed{-12 \text{ dB}}$

(c) $\phi = 0 - \tan^{-1}(1) = -45^\circ$


$$N=4 \rightarrow \boxed{\phi = -180^\circ}$$

or

$$\boxed{\phi = -\pi}$$

P5

non-ideal

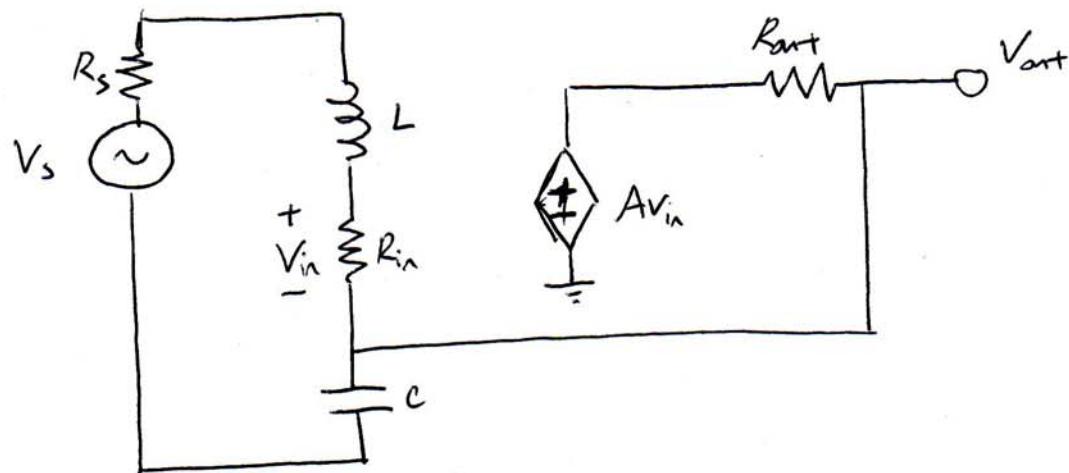

V_{out} follows phase of $A V_{in}$ since R_{out} is purely real.

phasor domain:

$$V_{in} = V_s \frac{R_{in}}{R_s + R_{in} + j\omega L + \frac{1}{j\omega C}}$$

no phase shift b/w $V_s \rightarrow V_{in} \rightarrow V_{out}$

if no imaginary components.

$$\therefore j\omega L + \frac{1}{j\omega C} = 0 \rightarrow \boxed{\omega = \frac{1}{\sqrt{LC}}}$$

$V_s(t)$ is a sinusoidal function with this frequency.

Note: This is the resonance of an RLC circuit!