

PHYSICS 8B, FALL 2014

Lecture 1, Midterm 1


C. Bordel

Wednesday, October 8th, 7pm-9pm

Make sure you show all your work and justify your answers in order to get full credit.

Problem 1 – Semicircular charged ring (25pts)


Calculate the electric field created at the center O of a *uniformly* charged semicircular ring of radius R . The linear charge density λ is positive. Remember to give both the magnitude and direction of the electric field.

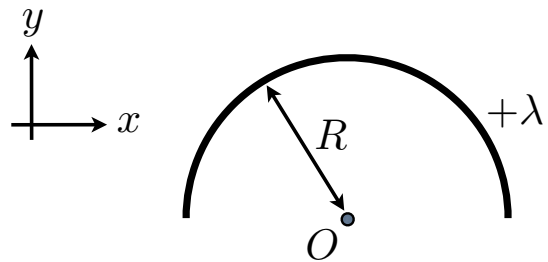

Problem 2 – Parallel plate capacitor (25pts)

A capacitor is made of two parallel *square* plates of lateral size L , separated by a distance d , and carrying the charges $+Q$ and $-Q$ respectively. The space between the plates *initially* contains a vacuum.


- Specify under which conditions those plates could be considered as uniformly charged infinite sheets, and determine the electric field inside and outside the capacitor.
- Express the voltage across the capacitors plates.
- Derive the capacitance C_0 of the parallel plate capacitor.
- Determine the capacitance C of the new capacitor if the gap between the plates is filled with an insulator of dielectric constant κ over the entire thickness d , length L and width $w < L$.
Hint: You may view this as a combination of capacitors.

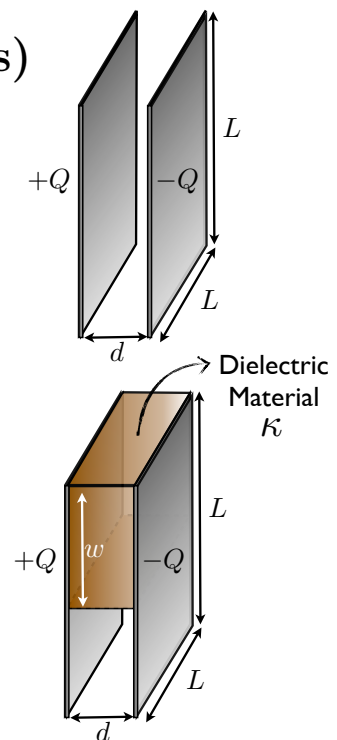

(Problem 2.d.)

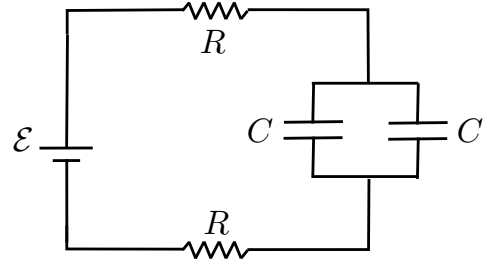Problem 3 – RC circuit (25pts)

In the right figure R and C are respectively a resistance and a capacitance, and \mathcal{E} is the voltage sourced by the battery.



- Draw a simplified version of that electrical circuit using only one resistor of equivalent resistance R_{eq} and one capacitor of equivalent capacitance C_{eq} . Express R_{eq} and C_{eq} as a function of R and C .
- Before the battery is connected to the circuit, the capacitors are uncharged. Establish the differential equation satisfied by the charge Q accumulating on the equivalent capacitors plates, using R_{eq} and C_{eq} . *Hint: You don't need to solve the equation, the solution is provided on the equation sheet.*
 - Determine the current I going through the equivalent circuit immediately after the battery is connected to the circuit. *You may consider using the mathematical form of $I(t)$ if you cannot think of any other way to answer the question.*
 - Sketch a qualitative plot of the current as a function of time.
- What is the maximal electric potential energy that can be stored by the equivalent capacitor, in terms of R_{eq} and C_{eq} ?

Problem 4 – Resistivity and current (Conceptual questions) (25pts)

- A typical value of the magnitude of the drift velocity in a Cu wire is on the order of 0.1 mm/s, while the random speed is on the order of 10^6 m/s. Explain what causes the drift velocity to be so small.
- Based on the drift velocity reported in (a), it would take several hours for an electron to travel 1 m! Explain why the light goes on almost instantaneously when you flip a light switch. *Hint: remember what causes the electron motion.*
- If you stretch a wire of initial length ℓ_0 and cross-sectional area A_0 such that the length is doubled, how does the final resistance R compare to the initial resistance R_0 , assuming that the resistivity ρ is unchanged in this process? Give a *qualitative* explanation for the *quantitative* result you got.
- For a given voltage sourced by a battery, how does the power consumption change across the resistor if the resistance is doubled?
 - The resistor converts the electrical energy provided by the battery into another form of energy. Which form of energy is this?

Midterm 1 Equation Sheet

- $\vec{F} = \frac{1}{4\pi\epsilon_0} \frac{Q_1 Q_2}{r^2} \hat{r}$
- $\vec{F} = Q\vec{E}$
- $\vec{E} = \frac{1}{4\pi\epsilon_0} \int \frac{dQ}{r^2} \hat{r}$
- $\lambda = \frac{dQ}{d\ell}$
- $\sigma = \frac{dQ}{dA}$
- $\rho = \frac{dQ}{dV}$
- $\Phi_E = \int_A \vec{E} \cdot d\vec{A}$
- $\oint_A \vec{E} \cdot d\vec{A} = \frac{Q_{enc}}{\epsilon_0}$
- $\vec{p} = Q\vec{d}$
- $\vec{\tau} = \vec{p} \times \vec{E}$
- $U = -\vec{p} \cdot \vec{E}$
- $\Delta U = Q\Delta V$
- $dV = -\vec{E} \cdot d\vec{\ell}$
- $V = \frac{1}{4\pi\epsilon_0} \int \frac{dQ}{r}$
 $= k \int \frac{dQ}{r}$
- $Q = CV$
- $C_{eq} = C_1 + C_2$ (in parallel)
- $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$ (in series)
- $\epsilon = \kappa\epsilon_0$
- $U = \frac{Q^2}{2C}$
- $I = \frac{dQ}{dt}$
- $V = IR$
- $R = \rho \frac{\ell}{A}$
- $P = IV$
- $I = \int_A \vec{j} \cdot d\vec{A}$
- $\vec{j} = nq\vec{v}_d = \frac{\vec{E}}{\rho}$
- $R_{eq} = R_1 + R_2$
(in series)
- $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$
(in parallel)
- $\sum_{\text{junction}} I = 0$
- $\sum_{\text{loop}} V = 0$
- $Q(t) = C\mathcal{E} \left(1 - e^{-t/(RC)}\right)$
(RC Circuit, charging)
- $Q(t) = C\mathcal{E}e^{-t/(RC)}$
(RC Circuit, discharging)
- $\int x^m dx = \frac{x^{m+1}}{m+1}$ for $m \neq -1$
- $\int \frac{1}{x} dx = \ln x$
- In the following, a is a constant:
- $\int \frac{dx}{\sqrt{x^2 + a^2}} = \ln \left(x + \sqrt{x^2 + a^2}\right)$
- $\int \frac{1}{x^2 + a^2} dx = \frac{1}{a} \tan^{-1} \left(\frac{x}{a}\right)$
- $\int \frac{1}{(x^2 + a^2)^{3/2}} dx = \frac{x}{a^2 \sqrt{x^2 + a^2}}$
- $\int \frac{x}{(x^2 + a^2)^{3/2}} dx = -\frac{1}{\sqrt{x^2 + a^2}}$
- $\int \sin x dx = -\cos x$
- $\int \cos x dx = \sin x$
- $\cos 0 = -\cos \pi = 1$
- $\sin \left(\frac{\pi}{2}\right) = -\sin \left(\frac{3\pi}{2}\right) = 1$
- $\cos \left(\frac{\pi}{2}\right) = \sin 0 = \sin \pi = 0$