

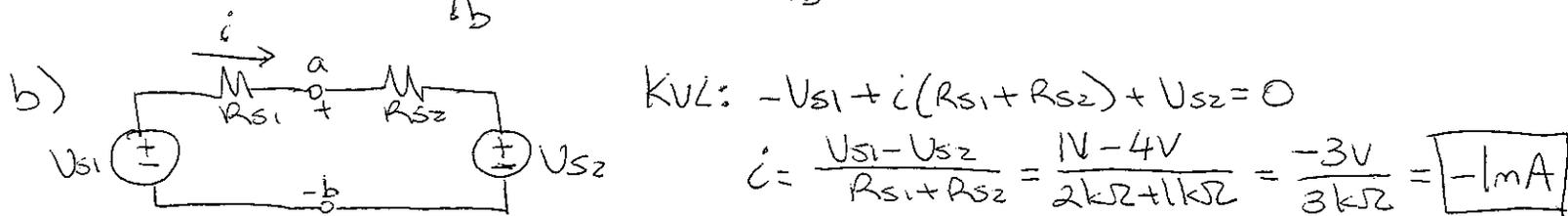
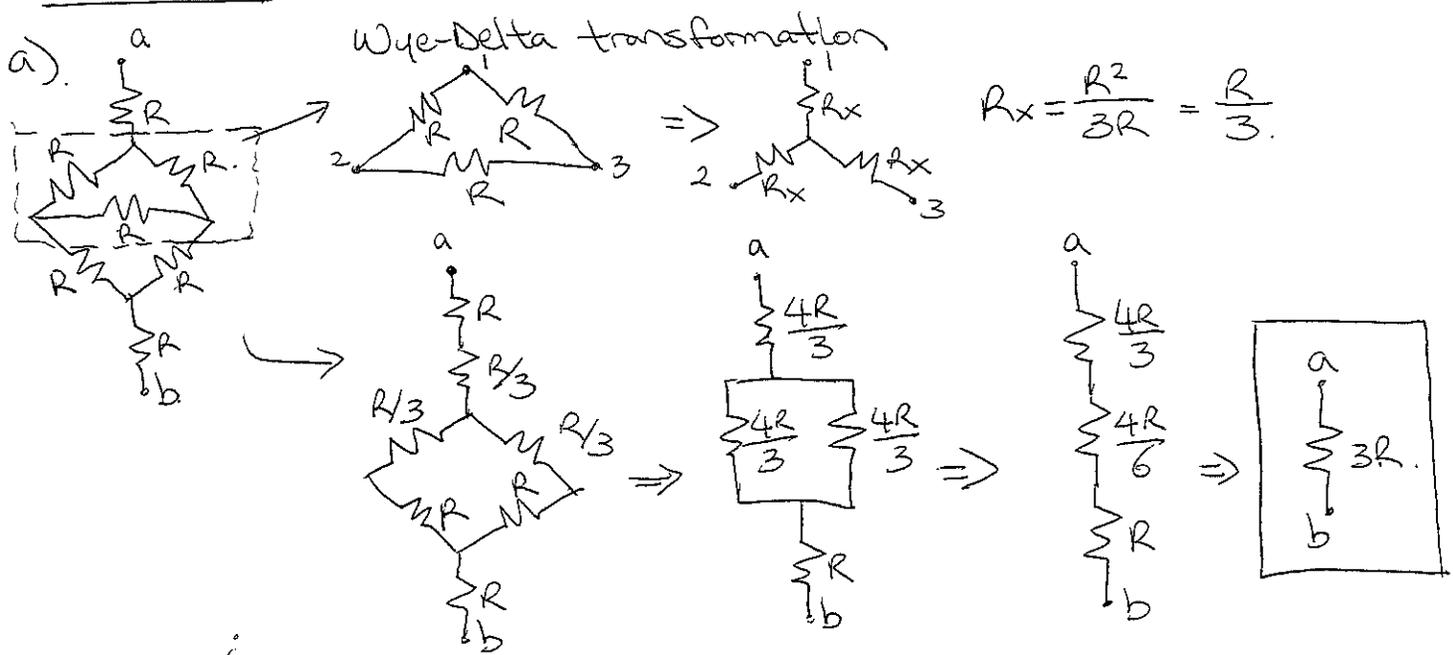


Problem 1

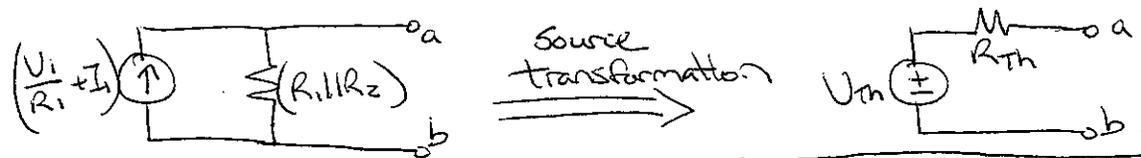


KVL w/ U_{AB} : $-V_{S1} + iR_{S1} + U_{AB} = 0$

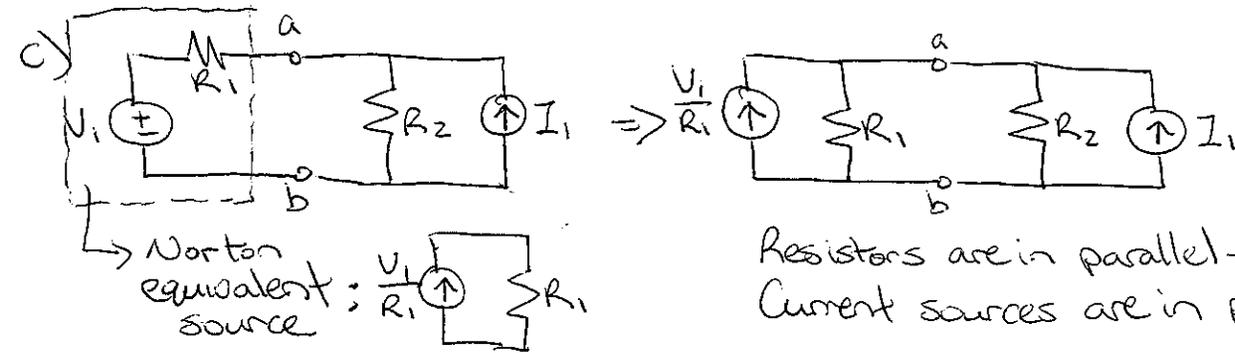$U_{AB} = V_{S1} - iR_{S1} = 1V - (-1mA)(2k\Omega) = 1V + 2V = \boxed{3V}$




$U_{Th} = \left(\frac{V_1}{R_1} + I_1\right)(R_1 || R_2) \Rightarrow U_{Th} = \left(\frac{V_1}{R_1} + I_1\right)\left(\frac{R_1 R_2}{R_1 + R_2}\right)$

$R_{Th} = R_1 || R_2 \Rightarrow R_{Th} = \frac{R_1 R_2}{R_1 + R_2}$

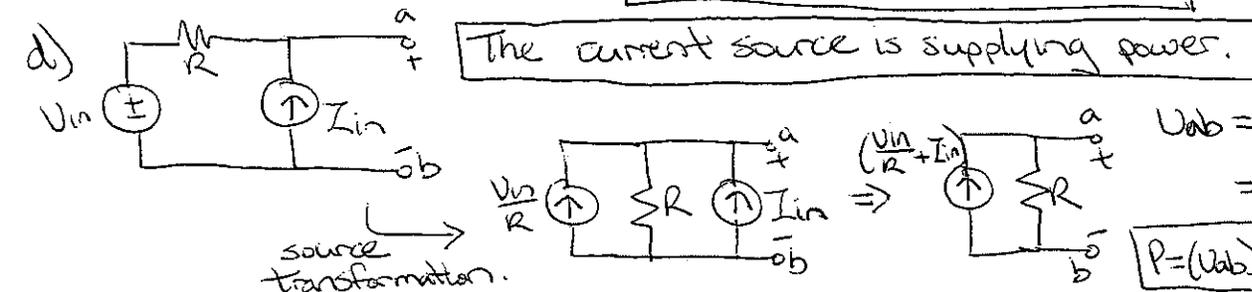

Problem 2

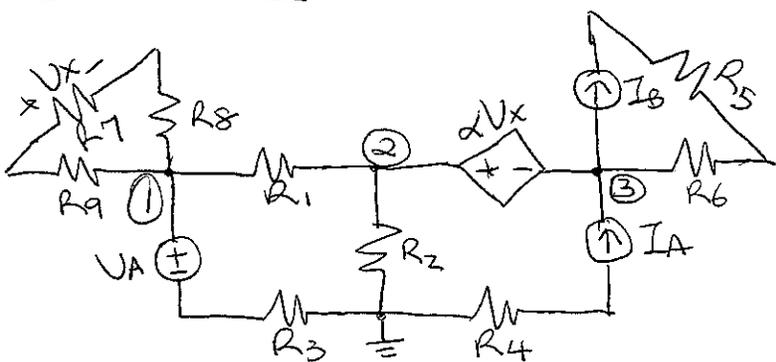

a) Node 1:

- KVL shows no current flows in the triangle

$$I R_7 + I R_8 + I R_9 = 0$$

$$I(R_7 + R_8 + R_9) = 0 \Rightarrow I = 0$$

- KCL:

$$\frac{V_1 - V_A}{R_3} + \frac{V_1 - V_2}{R_1} = 0 \Rightarrow \underline{\underline{EQ1}}$$

b) Node 2 & 3:

- Nodes 2 & 3 form a supernode b/c only a voltage source is between

- KCL:

$$\frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} + I_B - I_B - I_A = 0 \Rightarrow \underline{\underline{EQ2}}$$


System of equations:

$$EQ1: \frac{V_1 - V_A}{R_3} + \frac{V_1 - V_2}{R_1} = 0 \Rightarrow \left(\frac{1}{R_1} + \frac{1}{R_3}\right)V_1 + \left(\frac{-1}{R_1}\right)V_2 = \frac{V_A}{R_3}$$

$$EQ2: \frac{V_2 - V_1}{R_1} + \frac{V_2}{R_2} - I_A = 0 \Rightarrow \left(\frac{-1}{R_1}\right)V_1 + \left(\frac{1}{R_1} + \frac{1}{R_2}\right)V_2 = I_A$$

Current through \$R_7\$ is 0, so \$U_x = 0\$, so \$\alpha U_x = 0\$, so $\boxed{U_3 = U_2}$

• Q3

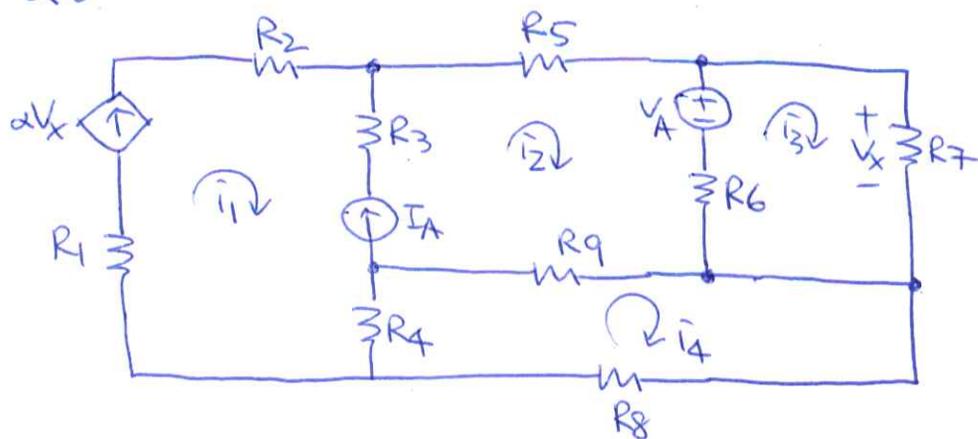

$$\hat{i}_1 = \alpha V_x$$

$$I_A = \hat{i}_2 - \hat{i}_1$$

$$(\hat{i}_4 - \hat{i}_1)R_4 + (\hat{i}_4 - \hat{i}_2)R_9 + \hat{i}_4 R_8 = 0$$

$$-V_A + \hat{i}_3 R_7 + (\hat{i}_3 - \hat{i}_2)R_6 = 0$$

$$V_x = \hat{i}_3 R_7$$

total 5 unknowns: $\hat{i}_1, V_x, \hat{i}_2, \hat{i}_3, \hat{i}_4$

total 5 equations.

\therefore fulfills requirement


$$\hat{i}_1 = \alpha V_x$$

$$-\hat{i}_1 + \hat{i}_2 = I_A$$








$$-R_4 \hat{i}_1 - R_9 \hat{i}_2 + (R_4 + R_8 + R_9) \hat{i}_4 = 0$$

$$-R_6 \hat{i}_2 + (R_6 + R_7) \hat{i}_3 = V_A$$


$$R_7 \hat{i}_3 = V_x$$

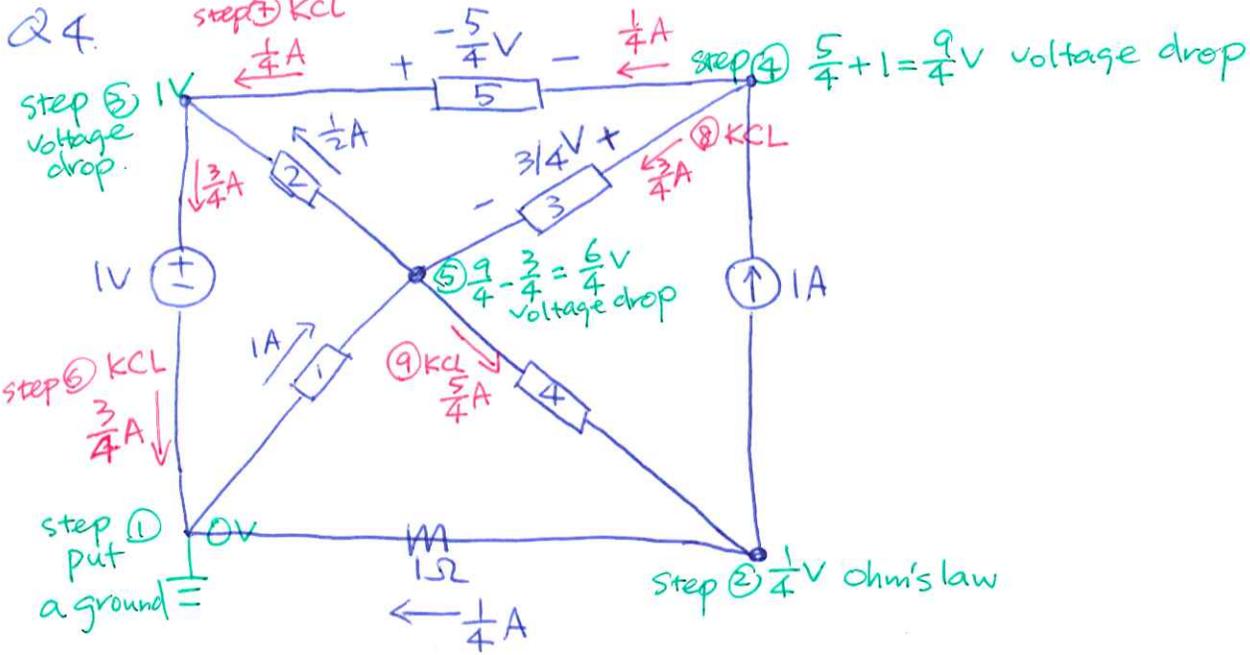

Unknown element	Symbol	Power Mag. (W)	consuming or providing
1	$\oplus \frac{3}{2}V$ or $\oplus 1A$	$ 1 \cdot (0 - \frac{6}{4}) = \frac{3}{2}$	providing
2	$\frac{1\Omega}{\text{---}}$	$\frac{1}{2} \cdot \frac{1}{2} = \frac{1}{4}$	Consuming
3	$\frac{1\Omega}{\text{---}}$	$\frac{3}{4} \cdot \frac{3}{4} = \frac{9}{16}$	Consuming
4	$\frac{1\Omega}{\text{---}}$	$\frac{5}{4} \cdot \frac{5}{4} = \frac{25}{16}$	consuming
5	$\frac{5\Omega}{\text{---}}$	$\frac{1}{4} \cdot \frac{5}{4} = \frac{5}{16}$	Consuming

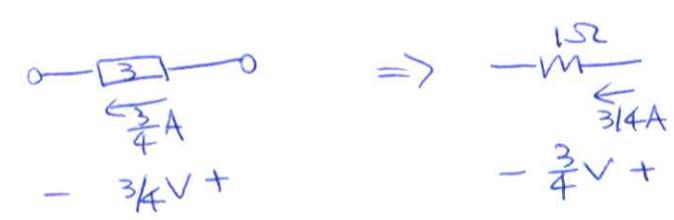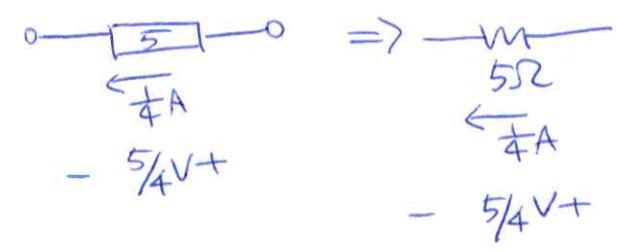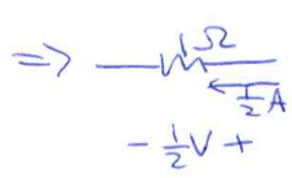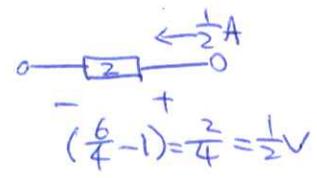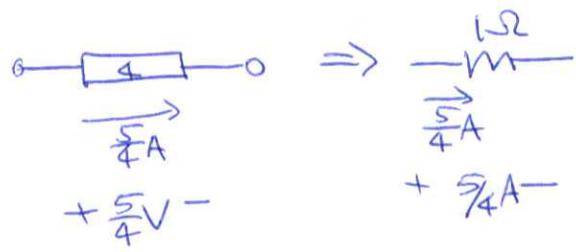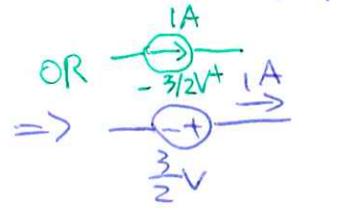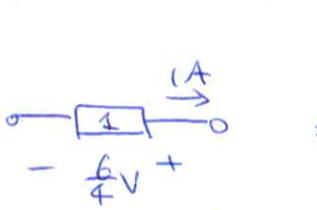

Q4 rubric

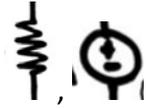

Each correct symbol, e.g.  ,  worth 2 points. In total there should be 5 symbols.

Each correct symbol value with correct unit, e.g., 1.5V, 1 ohm , worth 1 point. In total there should be 5 values with correct unit.

Each correct power magnitude worth 1 point. In total there should be 5 power magnitudes.

Each correct consuming or providing power, worth 1 point. In total there should be 4 consuming and 1 providing.