
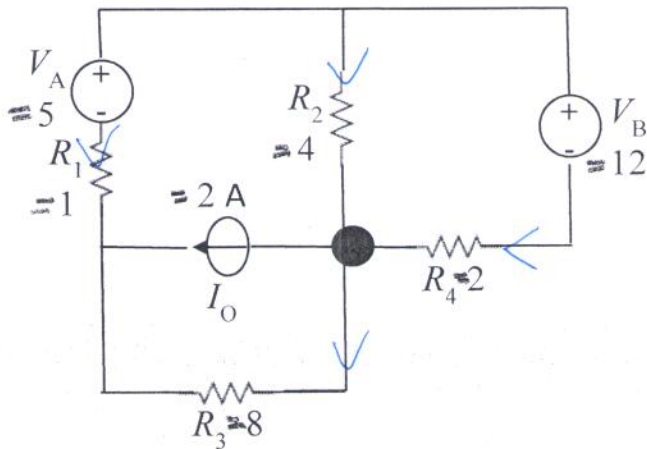


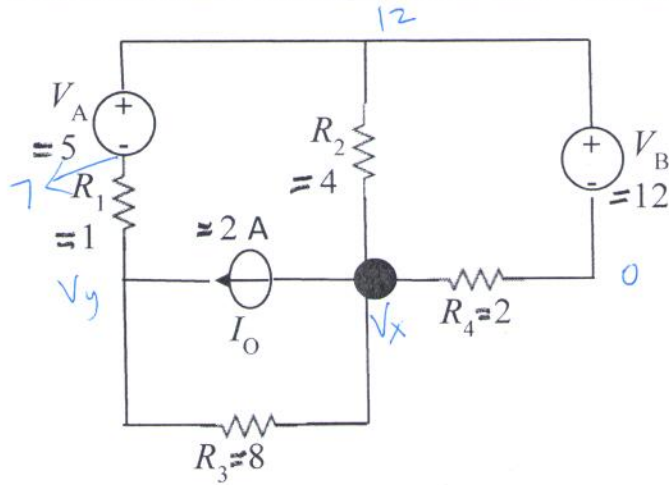1. **Circuit Analysis (14 points)** Find the current in each element. Show each step in your solution to receive full credit. Two copies of the same schematic are shown in case you need more than one.



$$\begin{cases} 7 - V_y + 2 + \frac{V_x - V_y}{8} = 0 \\ \frac{12 - V_x}{4} - \frac{V_x}{2} + \frac{V_y - V_x}{8} = 2 \end{cases}$$

①: $56 - 8V_y + 16 + V_x - V_y = 0$
 $V_x - 9V_y = -72$

②: $24 - 2V_x - 4V_x + V_y - V_x = 16$
 $-7V_x + V_y = -8$

$$-62V_x = -144$$


$$V_x = \frac{72}{31} = 2.32$$

$$V_y = 8.26$$

Element	Current (A)
---------	-------------

I_{R1}	$7 - V_y = -1.26 \text{ A}$
I_{R2}	$\frac{12 - V_x}{4} = 2.42 \text{ A}$
I_{R3}	$\frac{V_x - V_y}{8} = -0.74 \text{ A}$
I_{R4}	$-\frac{V_x}{2} = -1.16 \text{ A}$
I_{V_A}	$= I_{R1}$
I_{V_B}	$= I_{R4}$
I_{I_0}	2 A

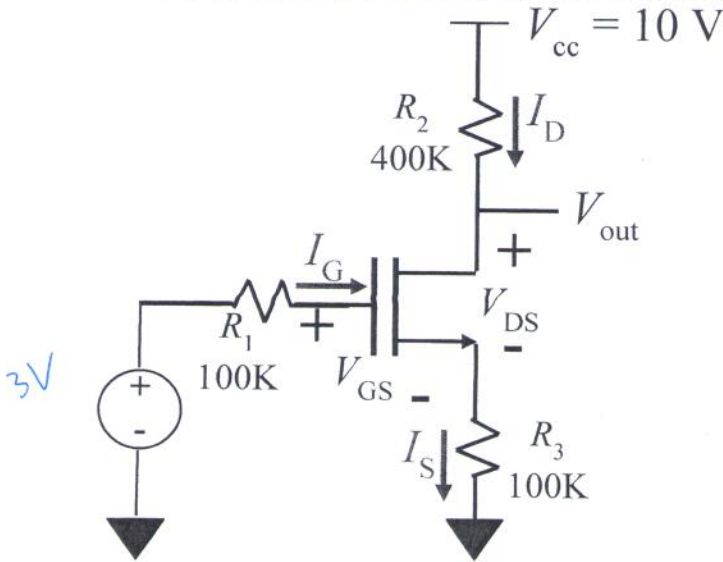2. **MOSFET DC Bias (18 points).** For the circuit below find the DC values of I_G , I_D , V_G , V_S , V_D and V_{out} . Assume $V_{TN} = 1.0$ V and $K_n = 40 \mu\text{A}/\text{V}^2$.



Assume in saturation:

$$I_D = I_S = \frac{K_n}{2} (V_{GS} - V_{th})^2$$

$$= 20 \cdot 10^{-6} (3 - V_S - 1)^2$$

$$I_S \cdot 100k = V_S$$

$$V_S \cdot 10^5 = 20 \cdot 10^{-6} \cdot 2 (2 - V_S)^2$$

$$V_S = 2(4 - 4V_S + V_S^2)$$

$$2V_S^2 - 9V_S + 8 = 0$$

$$V_S = \frac{9 \pm \sqrt{17}}{4} = \begin{cases} 1.22 \text{ V} \\ 3.28 \text{ V} \end{cases} \quad \times$$

$$V_S = 1.22 \text{ V} \quad I_S = 12.2 \mu\text{A}$$

$$V_{GS} = 1.78 \text{ V}$$

$$V_D = 10 \text{ V} - 400k \cdot 12.2 \mu\text{A}$$

$$= 5.12 \text{ V} \quad V_{DS} = 3.9 \text{ V}$$

$$> V_{GS} - V_{th}$$

\therefore in saturation

Parameter	Value (w / units)
-----------	-------------------

I_G 0

I_D 12.2 μA


V_G 3V

V_S 1.22V

V_D 5.12V


V_{out} 5.12V

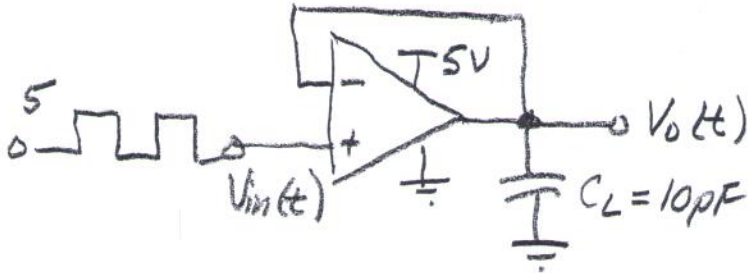3. **Time-Domain Analysis [15 points].** An opamp with rail-to-rail output voltage swing is connected to a 5 V supply. The opamp can supply or sink a maximum of 1 mA of current at its output terminal. It is driving a 10 pF load capacitor as shown. The input is driven with an ideal square wave, $V_{in}(t)$, that goes from 0 to 5V at a frequency of 10MHz. Plot the output voltage waveform, $V_o(t)$.




$$V_o(t) = \frac{I \cdot \Delta t}{C_L} = \frac{1\text{mA}}{10\text{pF}} \Delta t = 10^8 \Delta t$$

$$\frac{5\text{V}}{10^8} = 50\text{ns}$$

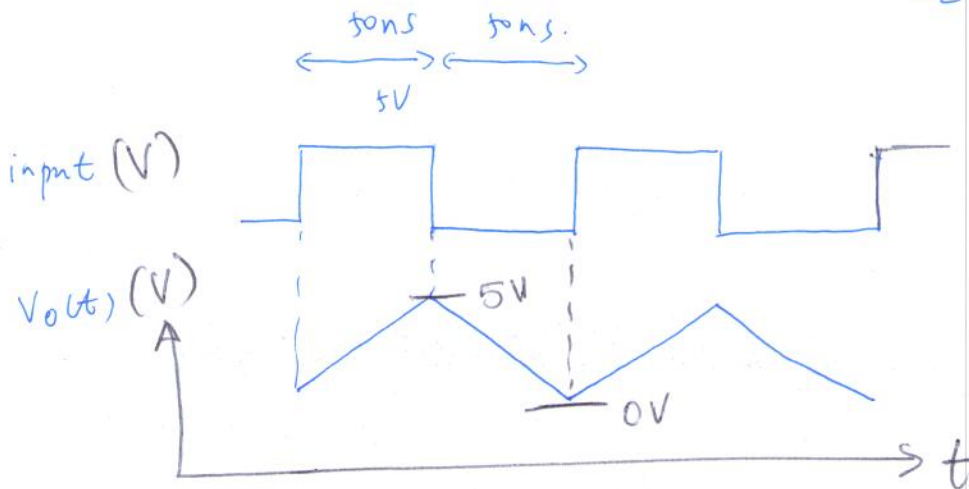

Frequency response
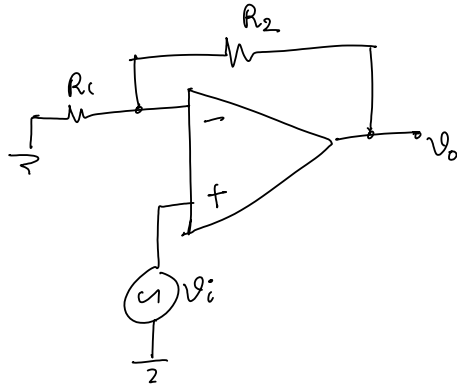
$$A(s) = \frac{A_0}{(1+s/\omega_{p1})(1+s/\omega_{p2})}$$



$$(v_+ - v_-)A(s) = v_o$$

$$\frac{v_- - v_o}{R_2} + \frac{v_-}{R_1} = 0$$

$$v_- = \frac{R_1}{R_1 + R_2} v_o \quad v_- = \beta v_o$$

$$\beta = \frac{R_1}{R_1 + R_2}$$

$$\Rightarrow (v_i - \beta v_o)A(s) = v_o$$

$$\frac{v_o}{v_i} = \frac{A(s)}{1 + \beta A(s)}$$

$$\text{loop gain} = A\beta = \frac{A_0\beta}{(1+s/\omega_{p1})(1+s/\omega_{p2})}$$

Since DC gain = 10^5 $\omega_{p1} = 200\pi$ rad/sec $\omega_{p2} = 4 \times 10^7 \pi$ rad/sec

$$\omega_{p1} \cdot A_{DC} = 2 \times 10^7 \pi \text{ rad/sec} < \omega_{p2}$$

$\omega_u \rightarrow$ At the unity gain frequency $\approx (1+A\beta)\omega_{p1} \rightarrow \omega_{p1}$
the phase introduced by first pole (ω_{p1}) $\approx 90^\circ$

$$-\tan^{-1}\left(\frac{\omega_u}{\omega_{p1}}\right) - \tan^{-1}\left(\frac{\omega_u}{\omega_{p2}}\right) = -100^\circ$$

$$-90 - \tan^{-1}\left(\frac{\omega_u}{\omega_{p2}}\right) = -100^\circ$$

$$\boxed{\omega_u = \omega_{p2} \tan 10^\circ}$$

The magnitude of loop gain = 1 @ ω_u

$$\left| \frac{A_o \beta}{\left(1 + j \frac{\omega_u}{\omega_{p1}}\right) \left(1 + j \frac{\omega_u}{\omega_{p2}}\right)} \right| = 1$$

ω_u

$$\frac{10^5 (\beta)}{\frac{\omega_{p2} \tan 10^\circ}{\omega_{p1}} \left| (1 + j \tan 10^\circ) \right|} = 1$$

$$\beta = \frac{\omega_{p2} \tan 10^\circ \left| 1 + j \tan 10^\circ \right|}{10^5 \omega_{p1}}$$

$$\frac{R_1}{R_1 + R_2} = \beta$$

$$\beta = \frac{4\pi \times 10^4}{2\pi \times 100 \times 10^3} \cdot \tan 10^\circ \left| 1 + j \tan 10^\circ \right|$$

$$\frac{R_2}{R_1 + R_1} = 1 - \beta$$

$$\beta = 2 \tan 10^\circ \left| 1 + j \tan 10^\circ \right|$$

$$\frac{R_2}{R_1} = \frac{(1 - \beta)}{\beta}$$

$$\beta = 0.36$$

$$\boxed{R_2 = \frac{(1 - \beta) R_1}{\beta}}$$

$$R_2 = 1.79 \text{ K}\Omega$$

$$R_1 = 1 \text{ K}\Omega$$

(b) $V_o(s) = V_i(s) \cdot H(s)$ $V_i(s) = 1/s$

$$H(s) = \frac{A(s)}{1 + \beta A(s)} = \frac{A_0}{\frac{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}{1 + \frac{\beta A_0}{(1 + s/\omega_{p1})(1 + s/\omega_{p2})}}}$$

Multiply by $\omega_{p1} \omega_{p2}$

$$= \frac{A_0}{(A_0 \beta) + \left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + s/\omega_{p2}\right)}$$

$$= \frac{A_0 \omega_{p1} \omega_{p2}}{(A_0 \beta) \omega_{p1} \omega_{p2} + (s + \omega_{p1})(s + \omega_{p2})}$$

$\omega_{p1} = 2\pi \times 10^2 \text{ rad/s}$
 $\omega_{p2} = 4\pi \times 10^7 \text{ rad/s}$

$$= \frac{A_0 \omega_{p1} \omega_{p2}}{s^2 + s(\omega_{p1} + \omega_{p2}) + \omega_{p1} \omega_{p2} (1 + A_0 \beta)}$$

$A_0 = 10^5$
 $\beta = \frac{R_1}{R_1 + R_2}$
 $\beta = \frac{1}{5}$

$$H(s) = \frac{A_0 \omega_{p1} \omega_{p2}}{(s+a)(s+b)}$$

$a = 1.416 \times 10^7 \text{ rad/sec}$
 $b = 11.1 \times 10^7 \text{ rad/sec}$

$$V_o(s) = \frac{A_0 \omega_{p1} \omega_{p2}}{s(s+a)(s+b)} = \frac{K_1}{s} + \frac{K_2}{s+a} + \frac{K_3}{s+b}$$

$$A_0 \omega_{p1} \omega_{p2} = K_1(s+a)(s+b) + K_2 s(s+b) + K_3 s(s+a)$$

Set $s=0$

$$K_1 = \frac{A_0 \omega_{p1} \omega_{p2}}{ab}$$

$$K_2 = \frac{s=-a}{-A_0 \omega_{p1} \omega_{p2}} = \frac{-A_0 \omega_{p1} \omega_{p2}}{a(b-a)}$$

$$K_3 = \frac{s=-b}{-A_0 \omega_{p1} \omega_{p2}} = \frac{-A_0 \omega_{p1} \omega_{p2}}{b(a-b)}$$

Taking inverse Laplace transform

$$V_o(t) = k_1 u(t) + k_2 e^{-at} u(t) + k_3 e^{-bt} u(t)$$

$$V_o(t) = A_0 \omega_{p1} \omega_{p2} \left(\frac{1}{ab} - \frac{e^{-at}}{a(b-a)} - \frac{e^{-bt}}{b(a-b)} \right) u(t)$$

$$A_0 = 10^5$$


$$a = 1.416 \times 10^7 \text{ rad/sec}$$

$$b = 11.15 \times 10^7 \text{ rad/sec}$$

$$\omega_{p1} = 200\pi \text{ rad/sec}$$

$$\omega_{p2} = 4\pi \times 10^7 \text{ rad/sec}$$

$$V_o(t) = 5 - 5.728 e^{-at} + 0.727 e^{-bt}$$


 See that gain is 5 if $t \rightarrow \infty$
