

Introduction to Digital Electronics

Professor Connie Chang-Hasnain and Dr. Wenbin Hsu

7/22/13, Midterm 1

EE42/100, Summer 2013

INSTRUCTIONS

- You have 100 minutes to complete the exam.
- The exam is closed book, closed notes, closed computer, closed calculator, except one hand-written 8.5" x 11" crib sheet of your own creation.
- Mark your answers ON THE EXAM ITSELF, and CIRCLE or BOX the final results
- Arrange your time wisely, move on if you get stuck on one question, and come back later

Last name	Key
First name	Key
SID	
TA & Section Time	
Name of the person to your left	
Name of the person to your right	
All the work on this exam is my own. (Please sign)	

For staff use only.

Q. 1	Q. 2	Q. 3	Q. 4	Q. 5	Q. 6	Total
/15	/24	/12	/24	/20	/5	/100

1. Phasors (15 points)

Write the following equations in phaser notation

5 1) $v_1(t) = 4 * \cos(10 \cdot 10^4 t + 10^\circ)$

$$V_1 = 4 \angle 10^\circ$$
$$= 4e^{j10^\circ}$$

5 2) $v_2(t) = 10 * \sin(3t - 45^\circ)$

$$= 10 \cos(3t - 45^\circ - 90^\circ)$$

$$V_2 = 10 \angle -135^\circ$$

$$= 10e^{-j135^\circ}$$

5 3) $v_3(t) = 3 * \sin(10 \cdot 10^4 t + 180^\circ)$

$$= 3 \cos(10 \cdot 10^4 t + 90^\circ)$$

$$V_3 = 3 \angle 90^\circ$$

$$= 3e^{j90^\circ}$$

both $r \angle \theta$ form and $re^{j\theta}$ form are right


Each: 5 pts for correct mag and phase

3 pts for only one is correct

1 pt for attempt
2

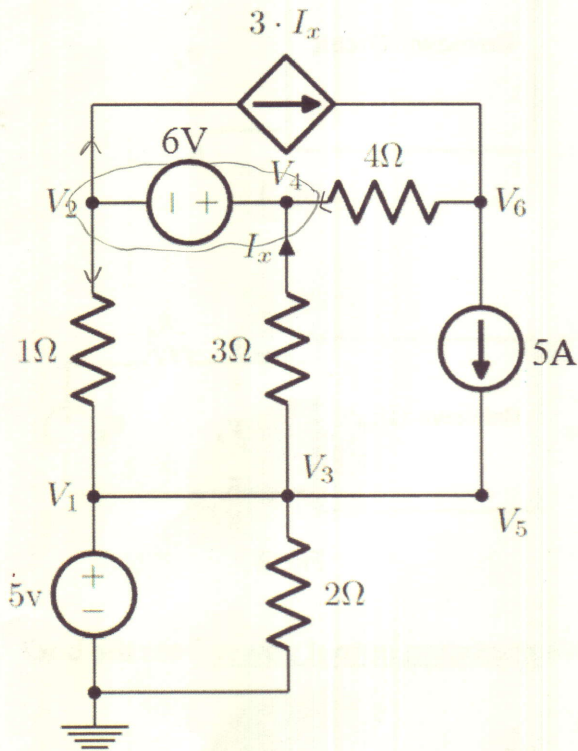2. Nodal Analysis (24 points)

Solving the following circuit using NODAL analysis. Find the value for V_2 (unit is V).



Node 1, 3, 5: $V_1 = V_3 = V_5 = 5V$

+2 recognize same voltage

Node 2 & 4: supernode

+2 recognize supernode

$$3I_x + \frac{V_2 - 5}{1} = I_x + \frac{V_6 - V_4}{4} \quad (1) \quad +5 \text{ most important function}$$

$$V_4 = V_2 + 6 \quad (2) \quad +3$$

Node 6: $\frac{V_6 - V_4}{4} + 5 = 3I_x \quad (3) \quad +5 \text{ 2nd important equation}$

$$I_x = \frac{5 - V_4}{3} \quad (4) \quad +3 \text{ solve for } I_x$$

\Rightarrow (2), (3), (4) substitute into (1)

$$3I_x + V_2 - 5 = 4I_x - 5$$

+2 going to the right direction

$$I_x = V_2 = 5 -$$

trying to reduce eqn. to only V_2

$$5 - (V_2 + 6) = 3V_2$$

$$V_2 = -0.25 V \quad +2 \text{ right result}$$

3. Equivalent Circuit (12 points)

Consider the unknown, linear circuit in Fig. 1. The box consists of dependent sources, resistors and independent sources. We measure the voltage V_x before the box is attached to anything else and find $V_x = 2V$.

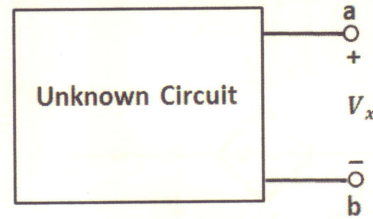


Fig. 1

Next, we connect the box to the circuit on Fig. 2 with $R_s = 500 \Omega$ and $V_s = 3V$. We measure $i_x = 1mA$:


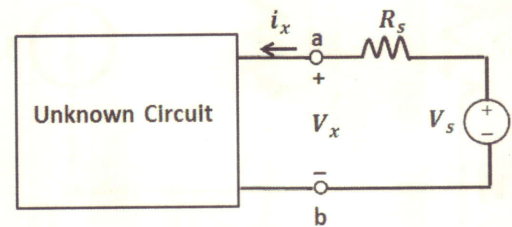


Fig. 2

Now we connect the box to a variable resistor R_L

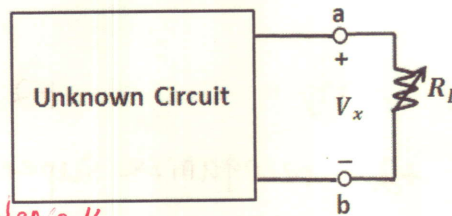
- (a) What value does R_L need to be in order to receive maximum output power from the box?
 (b) What is the maximum output power?



If said to find "Thevenin equivalence" without any calculation, +1 only get 1pt.

① $V_{Th} = V_x = 2V$ +2

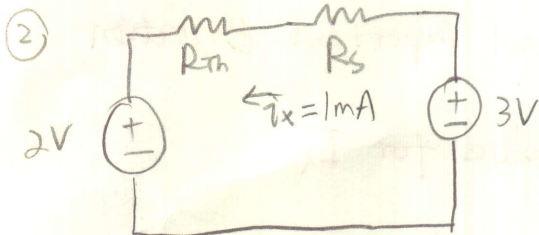③ (a) When $R_L = R_{Th} = 500 \Omega$ +3



(b) $P_{max} = \frac{(V_{Th})^2}{4R_L}$

$$= \frac{1}{0.5k\Omega}$$

$$= 2mW$$
 +3

$$R_{Th} + R_s = \frac{V_s - V_{Th}}{i_x} = \frac{3 - 2}{1m} = 1k\Omega$$

$$R_{Th} = 1k\Omega - 0.5k\Omega = 0.5k\Omega$$
 +4


right approach, wrong number -1 4

4. Operational Amplifiers (24 points)

This problem is about design of an integrator circuit, Figure below. Boxes A and B are unknowns for you to put in.

The input is a 5V unit-step source, $V_{in} = 5u(t)$. And the output, V_{out} , should integrate V_{in} at a rate of -0.2 V/s and **saturates** in 25 seconds.

$$V_{out}(0) = 0$$

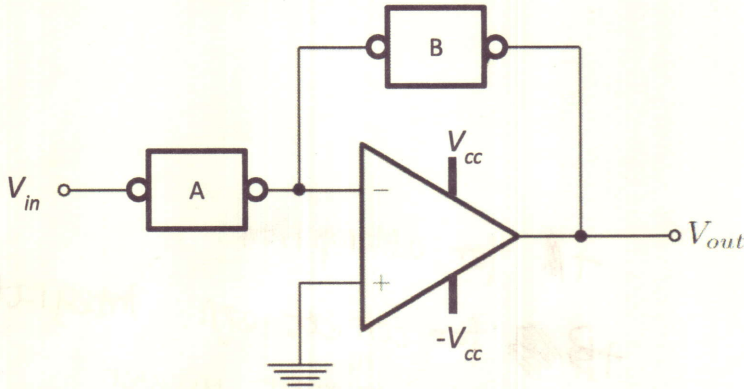

6pt ~~8pt~~ (a) What is V_{cc} ?

$$|V_{out}| \leq V_{cc} \quad +2$$

$$V_{out} = -0.2 \text{ V/s} * t = -0.2 t$$


$$t \leq 25 \text{ sec}$$

~~+~~ +2 understand what -0.2 V/s means

$$V_{out} \leq -0.2 \times 25 = -5 \text{ V}$$

$$V_{cc} = \underline{5 \text{ V}} \quad +2$$

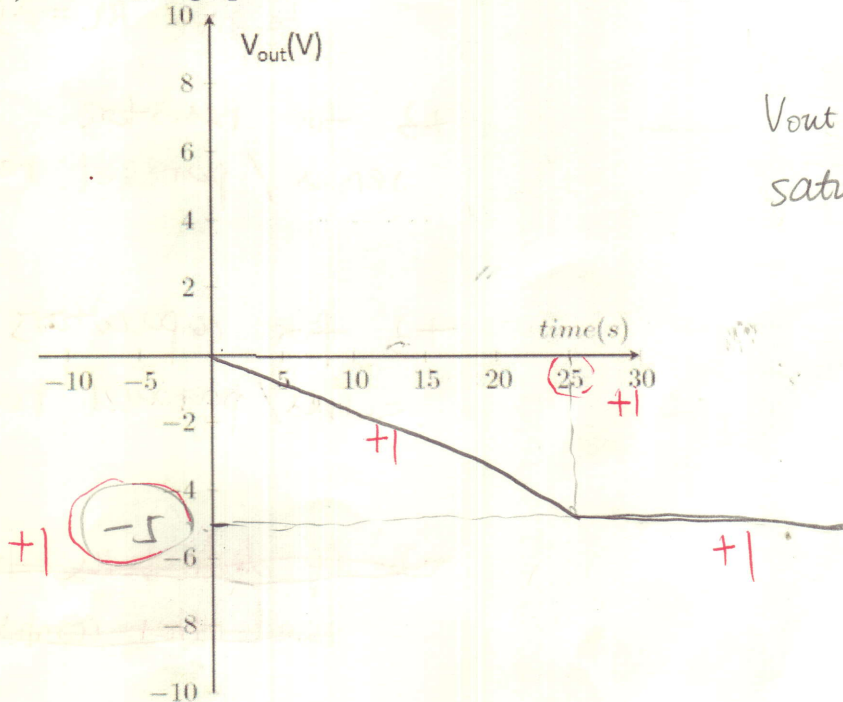4pt (b) Plot V_{out} in graph below for $t > 0$. Assume all voltages are 0 at $t=0$.



$$V_{out}(t) = -0.2 t$$

saturates at -5 V

6 pt (c) What is the RC constant needed for boxes A and B?

Integrator

$$V_{out} = -\frac{1}{RC} \int_0^t V_{in} dt$$

$$= -\frac{1}{RC} \int_0^t 5 dt$$

$$= -\frac{5t}{RC}$$

$$= -0.2t$$


$$RC = \frac{5}{0.2} = 25$$

+1 for attempt


+3 for correct eqn. integration
+2 for correct answer.

8 pt (d) You have an unlimited supply of 10MΩ resistors and 1μF capacitors. How will you use them to get the values needed for boxes A and B?

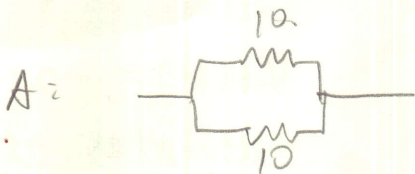$R = 5 \text{ M}\Omega$, $C = 5 \mu\text{F}$ +2. for correct R and C to give $RC = 25$



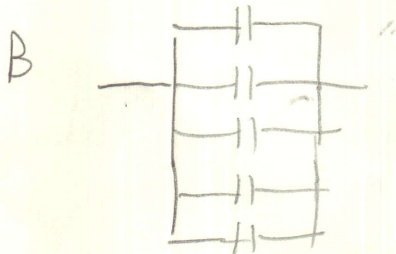+3 for resistors
series / parallel relation




+3 for capacitors
series / parallel relation

~~if didn't use 10MΩ / 1μF
used other combinations~~

only get 4 pts if ~~RC = 25~~
and used R.C ~~at~~ in the right
position, but single R.C

5. RLC Circuits (20 points)

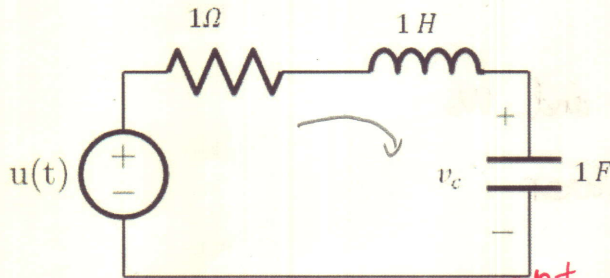- (a) A RLC series circuit is connected to a unit step input $u(t)$. Use KVL and write a second order & pt equation of $V_c(t)$ in response to the input.



$$i = i_c = C \frac{dv_c}{dt} \quad +2 \text{ for current}$$

$$V_R + V_L + V_C = u(t), \quad +2 \text{ KVL}$$

$$i_c \times 1 + L \frac{di}{dt} + V_C = u(t) \quad +2 \text{ for } V_L$$

$$C \frac{dv_c}{dt} + LC \frac{d^2v_c}{dt^2} + V_C = u(t) \quad +2 \text{ final form}$$

$$\frac{d^2v_c}{dt^2} + \frac{dv_c}{dt} + v_c = 1 \quad \text{okay if } u(t) = 1$$

- 4 pt (b) What is α , ω_0 ?

$$\alpha = \frac{R}{2L} = \frac{1\Omega}{2H} = 0.5 \quad \text{Np/sec} \quad +2$$

$$\omega_0 = \sqrt{\frac{1}{LC}} = 1 \quad \text{rad/sec} \quad +2$$

unit. missing -0.5

(C) Is this overdamped, underdamped, or critically damped?

4 pt

$\alpha < \omega_0$
underdamped

+2 if compare α and ω_0

+2 if correct answer

(d) What is the value of $V_c(\infty)$ as time goes to ∞ ?

4 pt

open circuit +2 for right direction


$V_c(\infty) = V(t) = |V$ +2 for correct answer

6. Resistor Networks (5 points)


A regular octahedron is a Platonic solid composed of eight equilateral triangles, four of which meet at each vertex.

Consider a resistor network connected in the form of octahedron with identical resistors of resistance R . What is the equivalent resistance between points A and B, which are opposite corners of an octahedron?

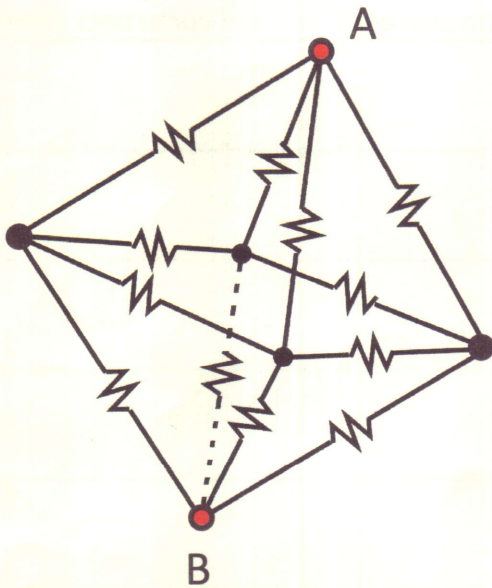Hint: Think about Wheatstone bridge. It should NOT include complex calculations.



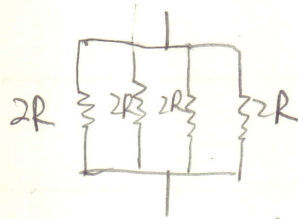4 resistors in between no use,
no current flowing across laterally
recognize wheatstone bridge +2



+ ~~1~~ equivalence

$$R_{eq} = \frac{2R}{4} = \frac{R}{2}$$

+ 1 correct answer