

PRINT your name and student ID: _____

[Extra page. If you want the work on this page to be graded, make sure you tell us on the problem's main page.]

Section 1: Warm-up questions (48 points)

3. **True or False** (2 pts for each question) For each question below, circle **T** on the left of each statement if you think the statement is true; else circle **F** (for false).

(a) [**T / F**] An ideal capacitor dissipates energy from the circuit in the form of heat.

Solutions: False. Ideal capacitors do not have non-idealities which dissipate heat, like series resistance.

(b) [**T / F**] An ideal “golden rules” op-amp behaves as though it has infinite gain.

Solutions: True. The golden rule where the positive and negative terminals have identical voltage in negative feedback holds true in the limit that $A \rightarrow \infty$.

(c) [**T / F**] A series RLC circuit connected with a DC input voltage/current in a single loop cannot exhibit voltage or current oscillations in time.

Solutions: We accept both *True* and *False* for this question, because we do not clarify the definition of a DC source during the exam. If you think a DC source should never change the value, then the answer is *True*.

However, if you think a DC voltage source can be $1V$ for $t < 0$ and $0V$ for $t \geq 0$, consider the circuit in Question 7(a), it exhibits oscillations. Hence the answer is *False*.

(d) [**T / F**] Given an impedance Z connected across a voltage source $v(t)$, it is possible for $i(t)$ to be in-phase (no phase shift) with a sinusoidal $v(t)$.

Solutions: True. A simple resistor has an impedance of R , which by Ohm’s law results in $v(t) = i(t)R$, where the voltage and the current are in phase.

(e) [**T / F**] Since the current across an open circuit must be zero, the voltage across the open circuit must also be zero by Ohm’s law.

Solutions: False. Ohm’s law applies only to resistors, and so the voltage across an open circuit could be anything. Furthermore, if we model the open circuit as a resistor with resistance $R \rightarrow \infty$, then we have $V = \infty * 0$ which is undefined.

(f) [**T / F**] The voltage across a constant current source must be zero.

Solutions: False. Consider a constant current source in series with a resistor. Then the voltage across the constant current source is no longer zero.

(g) [**T / F**] An electrical impedance across two terminals $Z = j\omega k$ (where ω is a positive angular frequency in rad/s and k is a positive real number) can be implemented using only capacitors.

Solutions: False. Without active elements or inductors, only impedances in the following form can be produced:

$$Z = \frac{1}{j\omega C_1} + \frac{1}{j\omega C_2} + \dots + \frac{1}{j\omega C_n}$$

$$Z = \frac{1}{j\omega} \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n} \right)$$

$$Z = \frac{k'}{j\omega}$$


This is not in the form $Z = j\omega k$.

PRINT your name and student ID: _____

4. Digital Circuits (9 pts)

Consider the circuit below:

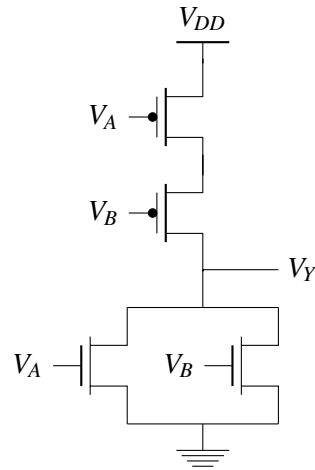- (a) (3 pts) The circuit below is a legal CMOS gate. A , B and Y are the Boolean values of the voltages, V_A , V_B and V_Y , respectively. Write down Y as a Boolean formula involving A and B .



Solutions: The circuit implements the NOR function. It pulls up when both A and B are zero. It pulls down on all other inputs.


PRINT your name and student ID: _____

Operator	Meaning
\neg	NOT
\vee	OR
\wedge	AND
\oplus	XOR

Table 1: Reminder: Logical Operators

Implement each of the following Boolean functions with a single CMOS gate (i.e. implemented using a pull-up network consisting of PMOS transistors connected to a pull-down network consisting of NMOS transistors) by drawing it, or state why the function cannot be implemented as a single CMOS gate in 1-3 sentences. You only have available V_A and V_B as inputs.

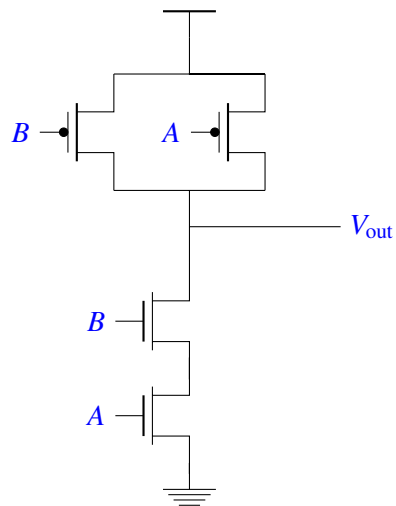(b) (3 pts) $\neg(A \wedge B)$. **Solutions:** The function is the NAND function.



- (c) (3 pts) $A \wedge B$. **Solutions:** Given the assignment $A = B = 0$, the pull-up network, being composed of PMOS transistors only, has to pull up the output to 1, no matter how the transistors are arranged. However, the output of $A \wedge B$ on this assignment is 0. Therefore this function cannot be implemented as a single CMOS gate.

PRINT your name and student ID: _____

5. Can you control me? (8pts)

We have a discrete time system that evolves according to $\vec{x}(t+1) = A\vec{x}(t) + B\vec{u}(t)$. For each part, **answer whether there exists a sequence of control vectors $\vec{u}(t)$ that will bring the state to the origin $\vec{0}$ in a finite number of steps no matter where it starts.**

(a) (4 pts) $A = \begin{bmatrix} 2 & 0 \\ 0 & 2 \end{bmatrix}$ and $B = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$.

Solutions: The controllability matrix

$$[B, AB] = \begin{bmatrix} 1 & 2 \\ 0 & 0 \end{bmatrix}$$

is not full-rank. This system is not controllable.

(b) (4 pts) $A = \begin{bmatrix} 1 & 2 \\ 1 & 2 \end{bmatrix}$ and $B = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$.

Solutions: The controllability matrix

$$[B, AB] = \begin{bmatrix} 1 & 1 \\ 0 & 1 \end{bmatrix}$$


is full-rank. This system is controllable.

PRINT your name and student ID: _____

6. Transfer Functions (9 pts)


Consider the circuit diagrams below. We define $H(\omega) = V_{\text{out}}/V_{\text{in}}$ as the voltage transfer function for each circuit. Here, assume that the input is connected to an ideal voltage source that applies a sinusoidal voltage. For each circuit, **provide an expression for $H(\omega)$** where ω is the frequency of the applied sinusoidal voltage in radians per second. Here the transfer functions should be expressed as functions of j , ω , constants and the physical constants (R , C , L) of the systems.

(a) (3 pts) $H(\omega) = ?$

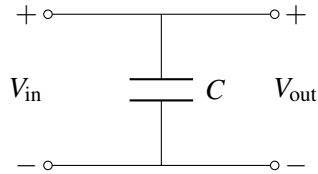

Solutions: Clearly, $V_{\text{out}} = V_{\text{in}}$, The transfer function is $H(\omega) = 1$.


(b) (3 pts) $H(\omega) = ?$

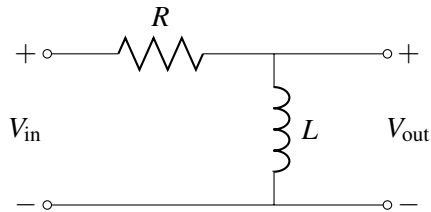

Solutions: This is a voltage divider. The transfer function is

$$H(\omega) = \frac{j\omega L}{R + j\omega L}$$


(c) (3 pts) $H(\omega) = ?$

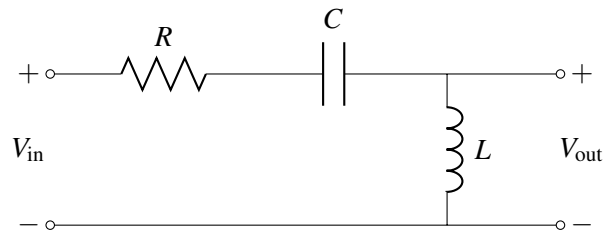

Solutions: This is a voltage divider. The transfer function is

$$H(\omega) = \frac{j\omega L}{R + \frac{1}{j\omega C} + j\omega L}$$

7. RLC Transient Matching (8pts)

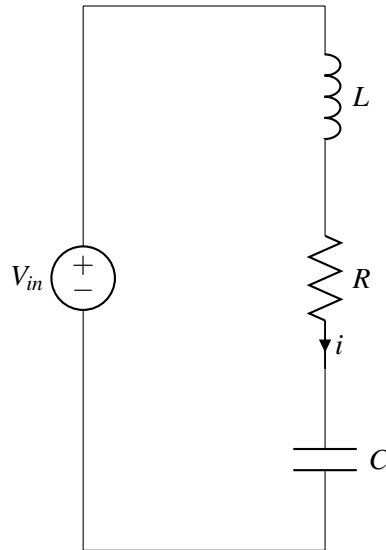

Throughout this problem, we assume $V_{in} = 1V$ for $t < 0$ and $0V$ for $t \geq 0$.

For this problem you are asked to **match** the transient behavior for **the current, i** , of the RLC circuit for various values of R , L , and C .

Circle your answer. There is no need to give any justification. However, 0 points will be awarded for an incorrect answer, 0.5 point will be awarded for leaving it blank and 4 points will be awarded for the correct answer

Solutions: In this circuit, we have the three equations to describe the current and voltage for each component: $v_R = i \times R$, $C \frac{dv_C}{dt} = i$ and $L \frac{di}{dt} = v_L$. By KVL, we have $V_{in} = v_L + v_R + v_C = L \frac{di}{dt} + i \times R + \int i dt$. Take derivative, we can get $L \frac{d^2i}{dt^2} + R \frac{di}{dt} + \frac{i}{C} = 0$.


To solve this second order differential equation, we could define $\vec{x} = \begin{pmatrix} i \\ \frac{di}{dt} \end{pmatrix}$. Therefore, we can get the following differential equations in the matrix form:

$$\begin{pmatrix} \frac{di}{dt} \\ \frac{d^2i}{dt^2} \end{pmatrix} = \begin{pmatrix} 0 & 1 \\ -\frac{1}{LC} & -\frac{R}{L} \end{pmatrix} \begin{pmatrix} i \\ \frac{di}{dt} \end{pmatrix}$$


Find the eigenvalues for the above circuit, you will get $\lambda = \frac{-R \pm \sqrt{R^2 - \frac{4}{LC}}}{2L}$

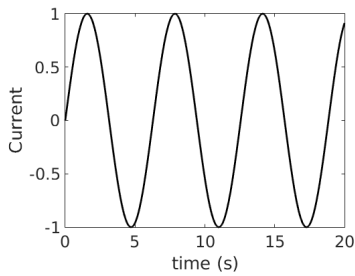- (a) (4 pts) For $R = 0\Omega$, $L = 1H$, $C = 1F$ Which one is the correct transient response of the current in the circuit?


Solutions: For $R = 0$, the eigenvalues are pure imaginary numbers, and this produces sinusoidal oscillation. The oscillation has period of $\frac{1}{\sqrt{LC}} = 1 \frac{rad}{s} = 2\pi \frac{1}{s}$. The initial conditions are that the current $i = 0$, therefore, the correct answer is part (A)




(A)

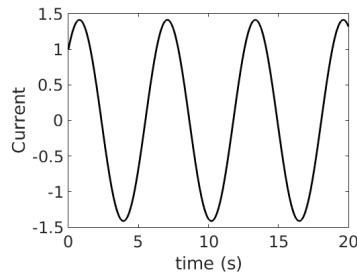


(B)

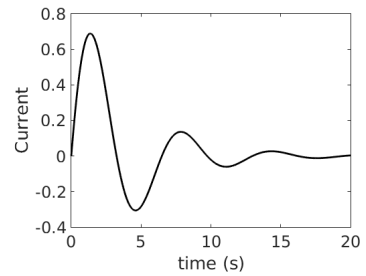


(C)

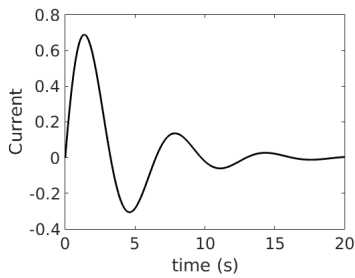

(A)

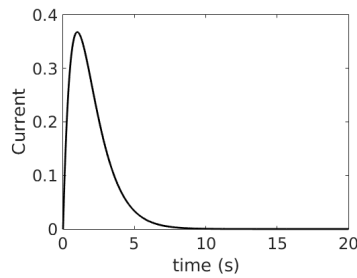

(B)

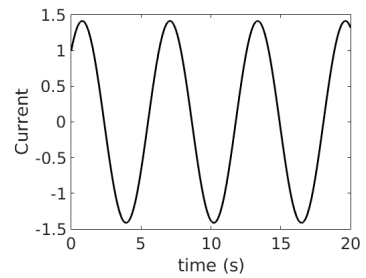

(C)

- (b) (4 pts) For $R = 0.5\Omega$, $L = 1H$, $C = 1F$ Which one is the correct transient response of the current in the circuit?


Solutions: For $R=0.5$, this circuit is in the underdamped stage. We can see this because the differential equation solution has oscillating terms if and only if $\frac{R}{2L} < \frac{1}{\sqrt{LC}}$. This case exhibits both negative real and imaginary eigenvalues and thus, should oscillate and decay with time. Initial conditions say the circuit should start out with 0 current, therefore part (A) is the correct answer again.

PRINT your name and student ID: _____

Section 2: In The Zone (59 points)

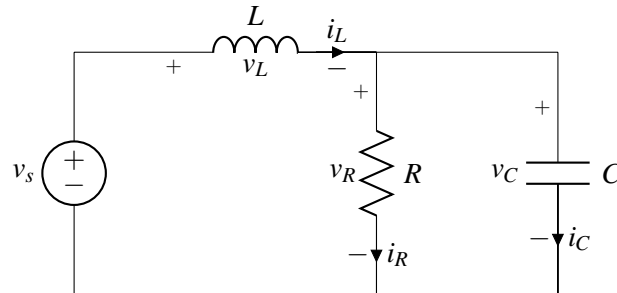8. RLC Problem (26 pts)

Consider the circuit below: let's try to analyze it with everything you know about circuits.



- (a) (3 pts) Assume $v_s = V_0$ for $t < 0$, and $v_s = 0$ for $t \geq 0$. **What is $v_C(0)$? What is $i_L(0)$?**

Solutions: Here C is an open circuit for the DC source while L works as short, so $v_C = v_R = V_0$. The current going through L is the same as that of R : $i_L = i_R = \frac{v_R}{R} = \frac{V_0}{R}$

- (b) (3 pts) If $v_s = 0$ (a constant) for any $t \geq 0$, **what is the steady state value of v_C ?** (i.e. $v_C(t \rightarrow \infty)$)
What is the steady state value of i_L ?

Solutions: Same as (a), $V_C = 0$, and $i_L = 0$.

- (c) (3 pts) **Write down the KCL equation on a node connecting the three passive components in terms of i_L , i_C and i_R .**

Solutions: $i_s = i_L = i_R + i_C$

(d) (3 pts) **Write down a KVL equation for the loop containing the voltage source, inductor and the capacitor in terms of v_s , v_L and v_C .**

Solutions: $v_s = v_L + v_C$

PRINT your name and student ID: _____

- (e) (6 pts) **Write down differential equations for v_C and i_L** using the relationships between the voltage across each component and the current through it, in addition to the equations obtained above. **Convert them into the following matrix form** (notice that $v_s = 0$ for any $t \geq 0$):

$$\begin{pmatrix} \frac{di_L}{dt} \\ \frac{dv_C}{dt} \end{pmatrix} = A \begin{pmatrix} i_L \\ v_C \end{pmatrix}$$

Solutions: We have (1) $v_R = i_R \times R = v_C$, (2) $C \frac{dv_C}{dt} = i_C$ and (3) $v_L = L \frac{di_L}{dt}$. Plug in the KCL equation, $i_L = \frac{v_C}{R} + C \frac{dv_C}{dt}$. Plug in the KVL equation, then $L \frac{di_L}{dt} + v_C = v_s$. because $v_s = 0$, we could drop out the constant term. Finally we could get the following matrix form:

$$\begin{pmatrix} \frac{di_L}{dt} \\ \frac{dv_C}{dt} \end{pmatrix} = \begin{pmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{RC} \end{pmatrix} \begin{pmatrix} i_L \\ v_C \end{pmatrix}$$

- (f) (8 pts) For the differential equations above, we know the solution can be obtained from the general solutions $c_1 e^{\lambda_1 t} \vec{v}_1 + c_2 e^{\lambda_2 t} \vec{v}_2$. **What are the values of λ_1 and λ_2 ? Express them in terms of R , L , C and constants.**

Solutions: λ_1 and λ_2 are eigenvalues of A . To find eigenvalues of A , we could find the roots of $\det(A - I\lambda) = -\lambda \times (-\lambda - \frac{1}{RC} + \frac{1}{LC}) = 0$. For $\lambda^2 + \frac{\lambda}{RC} + \frac{1}{LC} = 0$, the solutions should be $\lambda = \frac{-\frac{1}{RC} \pm \sqrt{\frac{1}{(RC)^2} - \frac{4}{LC}}}{2}$.

PRINT your name and student ID: _____

[Extra page. If you want the work on this page to be graded, make sure you tell us on the problem's main page.]

PRINT your name and student ID: _____

9. Hold me and linearize me (13 pts)

Consider a non-linear two-dimensional system with states x_0 and x_1 and scalar input u that evolves according to the following coupled differential equations

$$\begin{aligned}\frac{d}{dt}x_0(t) &= \dot{x}_0 = x_1(t) \\ \frac{d}{dt}x_1(t) &= \dot{x}_1 = 4 - \left(\frac{u(t)}{x_0(t)}\right)^2\end{aligned}\tag{1}$$

- (a) (5 pts) **Find an input u_e so that if the system starts in state vector $\vec{x}_e = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$ and we apply the input $u(t) = u_e$, the system will always stay in that same state. Solutions:**
The non-linear system is given in vector form as

$$\frac{d}{dt}\vec{x}(t) = \vec{f}(\vec{x}(t), u(t)) = \begin{bmatrix} x_1(t) \\ 4 - \left(\frac{u(t)}{x_0(t)}\right)^2 \end{bmatrix}$$

Now setting $\frac{d}{dt}\vec{x}_e(t) = \vec{f}(\vec{x}_e(t), u_e(t)) = \vec{0}$ we have

$$u_e(t)^2 = 4$$

Thus, we have

$$\vec{x}_e = \begin{bmatrix} 1 \\ 0 \end{bmatrix} \text{ and } u_e(t) = \pm 2$$

- (b) (8 pts) **Write linearized state-space equations around \vec{x}_e and u_e . Convert them into the following form and find the matrices A and B .**

$$\frac{d}{dt}\vec{x}(t) = A(\vec{x} - \vec{x}_e) + B(u(t) - u_e)$$

Solutions: We find the Jacobian matrices for both the state vector and the input. Thus,

$$\frac{\partial \vec{f}}{\partial \vec{x}} = \begin{bmatrix} 0 & 1 \\ 2\frac{u_e(t)^2}{x_0(t)^3} & 0 \end{bmatrix} = A_e$$

and

$$\frac{\partial \vec{f}}{\partial \vec{u}} = \begin{bmatrix} 0 \\ -2u_e(t) \end{bmatrix} = B_e$$

The system evolves as

$$\frac{d}{dt} \vec{x}(t) = A_e(\vec{x} - \vec{x}_e) + B_e(\vec{u} - \vec{u}_e)$$

For $u_e = 2$,

$$A = \begin{bmatrix} 0 & 1 \\ 8 & 0 \end{bmatrix}$$

and

$$B = \begin{bmatrix} 0 \\ -4 \end{bmatrix}$$

For $u_e = -2$,

$$A = \begin{bmatrix} 0 & 1 \\ 8 & 0 \end{bmatrix}$$

and

$$B = \begin{bmatrix} 0 \\ 4 \end{bmatrix}$$

PRINT your name and student ID: _____

[Extra page. If you want the work on this page to be graded, make sure you tell us on the problem's main page.]


PRINT your name and student ID: _____

10. Circuit Design (8 pts)


In this problem, you will find a circuit where several components have been left *blank* for you to fill in.

Assume the op-amp is *ideal*.

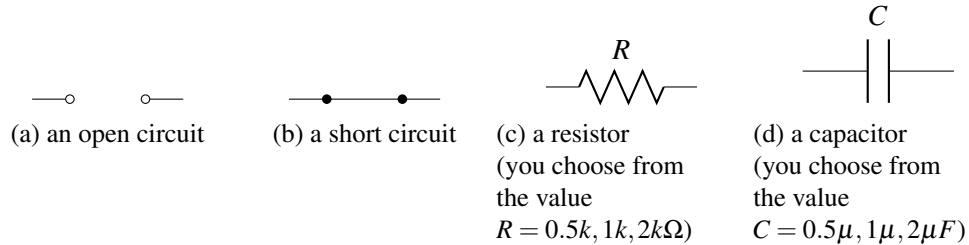You have at your disposal *only one of each* of the following components:



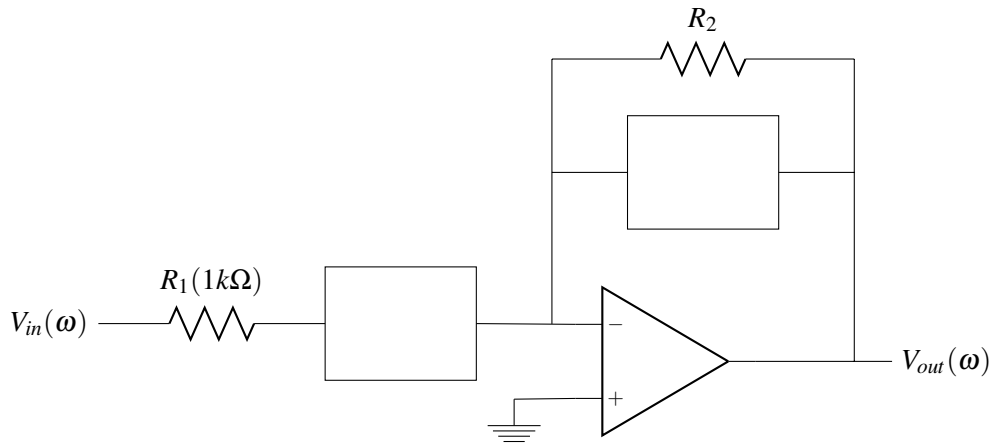Consider the circuit below. The voltage source $v_{in}(t)$ has the form $v_{in}(t) = v_0 \cos(\omega t + \phi)$. The labeled voltages $V_{in}(\omega)$ and $V_{out}(\omega)$ are the phasor representation of $v_{in}(t)$ and $v_{out}(t)$. The transfer function $H(\omega)$ is defined as $H(\omega) = V_{out}(\omega)/V_{in}(\omega)$.



Let R_1 be $1k\Omega$. **Fill in the boxes and determine the value of R_2** so that

- It is a high-pass filter.
- $|H(\infty)| = 2$.
- $|H(10^3)| = \sqrt{2}$.

Solutions:

Let the left box be Z_1 and the right box be Z_2 . The circuit should be a high-pass filter, so Z_2 cannot be a short circuit or a capacitor (otherwise $V_{out}(\infty) = 0$). Since Z_2 cannot be capacitors, Z_1 must be a capacitor (otherwise it is not a filter). Z_2 is either an open circuit or a resistor. Let $R_f = R_2 \parallel Z_2$ and $Z_1 = C$. The transfer function is given by

$$H(\omega) = -\frac{R_f}{R_1 + \frac{1}{j\omega C}} = -\frac{j\omega R_f C}{1 + j\omega R_1 C} = -\frac{R_f}{R_1} \frac{j\omega R_1 C}{1 + j\omega R_1 C}$$


Observing the transfer function, we know $H(0) = 0$ and $H(\infty) = -\frac{R_f}{R_1}$ so it is a high-pass filter. From $|H(\infty)| = 2$, we know $R_f = 2R_1 = 2k\Omega = R_2 \parallel Z_2$. Because of the limited choices of resistors, Z_2 must be an open circuit and $R_2 = 2k\Omega$.

From $H(10^3) = \sqrt{2}$, we have (let $x = 10^3 R_1 C$)

$$\sqrt{2} = 2 \frac{\sqrt{x^2}}{\sqrt{1+x^2}} \Rightarrow \frac{1}{2} = \frac{x^2}{1+x^2} \Rightarrow x^2 = 1 \Rightarrow 10^3 R_1 C = 1 \Rightarrow C = \frac{1}{10^3 R_1} = 1\mu F$$

Thus,

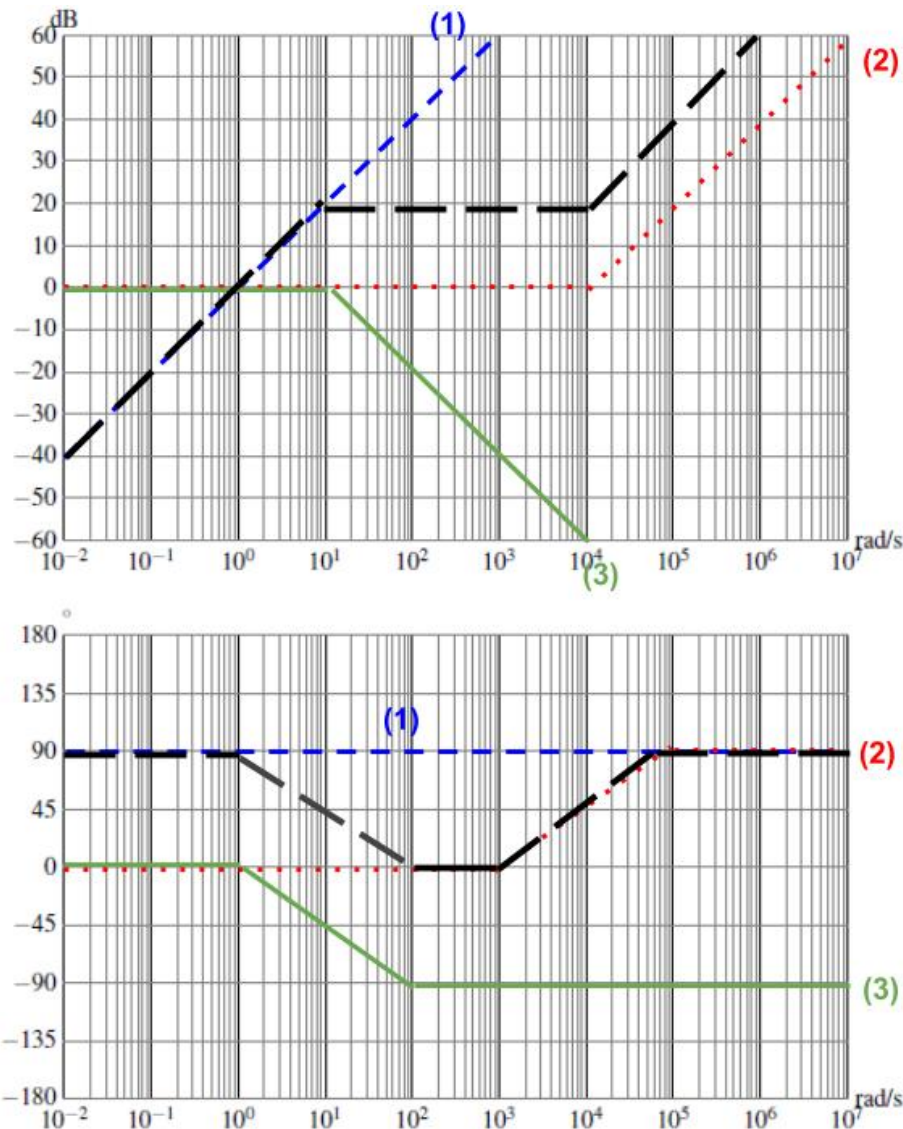- $R_2 = 2k\Omega$.
- The right box : an open circuit.
- The left box : a capacitor with $C = 1\mu F$.



PRINT your name and student ID: _____


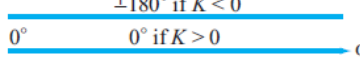
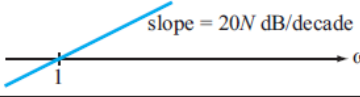
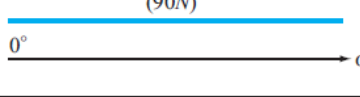
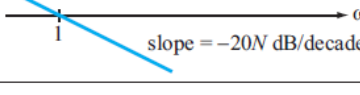
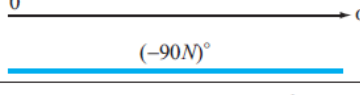
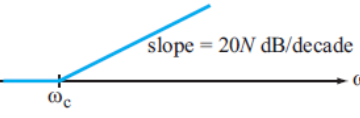
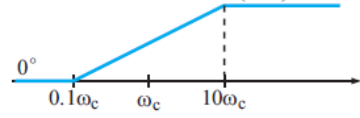
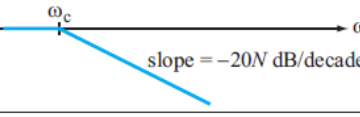
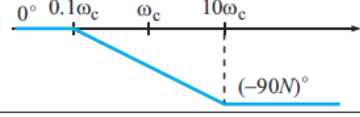
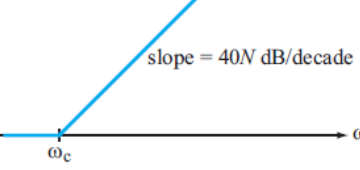
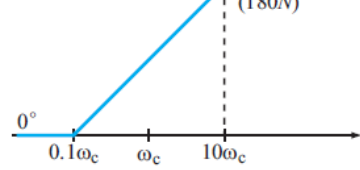
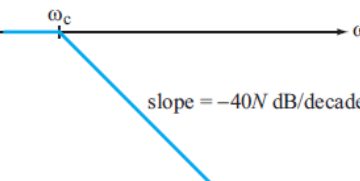
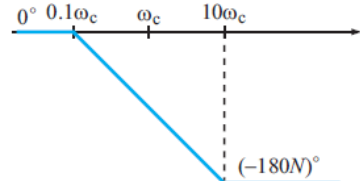
11. Bode plot (12 pts)

Draw the Bode plot for the transfer function $H(\omega) = \frac{(j\omega \times 10)(10 + j\omega \times 10^{-3})}{(100 + j\omega \times 10)}$ Remember you have the Bode plot table in the next page!

Solutions:

$$H(\omega) = \frac{(j\omega \times 10)(10 + j\omega \times 10^{-3})}{(100 + j\omega \times 10)} = \frac{j\omega(1 + \frac{j\omega}{10^4})}{(1 + \frac{j\omega}{10})}$$

Therefore, we should draw three lines and perform superposition among them. In the following graph, line (1) is $j\omega$, line (2) is $(1 + \frac{j\omega}{10^4})$, and line (3) is $(1 + \frac{j\omega}{10})^{-1}$.

Factor	Bode Magnitude	Bode Phase
Constant K	$20 \log K$ 0 dB 	$\pm 180^\circ$ if $K < 0$ 0° if $K > 0$ 
Zero @ Origin $(j\omega)^N$	0 dB 1 slope = $20N$ dB/decade 	$(90N)^\circ$ 0° 
Pole @ Origin $(j\omega)^{-N}$	0 dB 1 slope = $-20N$ dB/decade 	0° $(-90N)^\circ$ 
Simple Zero $(1 + j\omega/\omega_c)^N$	0 dB ω_c slope = $20N$ dB/decade 	0° $0.1\omega_c$ ω_c $10\omega_c$ $(90N)^\circ$ 
Simple Pole $\left(\frac{1}{1 + j\omega/\omega_c}\right)^N$	0 dB ω_c slope = $-20N$ dB/decade 	0° $0.1\omega_c$ ω_c $10\omega_c$ $(-90N)^\circ$ 
Quadratic Zero $[1 + j2\xi\omega/\omega_c + (j\omega/\omega_c)^2]^N$	0 dB ω_c slope = $40N$ dB/decade 	0° $0.1\omega_c$ ω_c $10\omega_c$ $(180N)^\circ$ 
Quadratic Pole $\frac{1}{[1 + j2\xi\omega/\omega_c + (j\omega/\omega_c)^2]^N}$	0 dB ω_c slope = $-40N$ dB/decade 	0° $0.1\omega_c$ ω_c $10\omega_c$ $(-180N)^\circ$ 

[Doodle page! Draw us something if you want or give us suggestions or complaints. You can also use this page to report anything suspicious that you might have noticed.]