


Name: Pramod / Siva Student ID #: 

**University of California at Berkeley
Electrical Engineering and Computer Science
EE105 Midterm Examination #1
March 5, 2014
(50 minutes)**


CLOSED BOOK; Two standard 8.5" x 11" sheet of notes (both sides) permitted

IMPORTANT NOTES

- Read each problem completely and thoroughly before beginning to work on it
- Summarize all your answers in the boxes provided on these exam sheets
- Show your work in the space provided so we can check your work and scan for partial credit
- Remember to put your name in the space above

| Problem # | Points Possible | Score |
|--------------|-----------------|-------|
| 1 | 20 | |
| 2 | 40 | |
| 3 | 40 | |
| Total | 100 | |

a

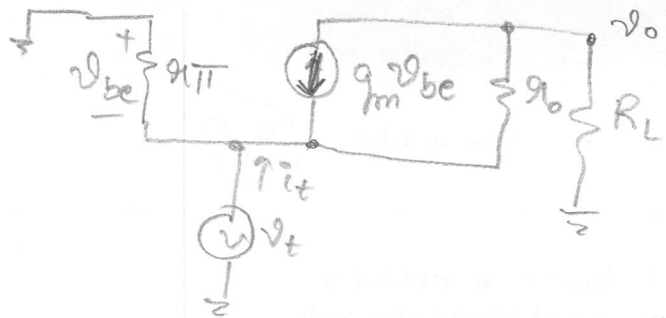

$$i_t = \frac{v_t}{r_{\pi}} + g_m v_t$$

$$\frac{v_t - v_o}{r_o}$$

$$\frac{v_o - v_t}{r_o} + \frac{v_o}{R_L} - g_m v_t = 0$$

$$v_o \left(\frac{1}{R_L} + \frac{1}{r_o} \right) = v_t \left(\frac{1}{r_o} + g_m \right)$$

$$v_o = v_t \frac{(1 + g_m r_o)}{(1 + r_o/R_L)}$$

$$i_t = \frac{v_t}{r_{\pi}} + g_m v_t + \frac{v_t}{r_o} - \frac{v_t}{r_o} \frac{(1 + g_m r_o)}{(1 + r_o/R_L)}$$

$$\frac{i_t}{v_t} = \frac{1}{r_{\pi}} + g_m + \frac{1}{r_o} - \frac{1}{r_o} \frac{(1 + g_m r_o)}{(1 + r_o/R_L)}$$

$$Z_{in} = \left(\frac{i_t}{v_t} \right)^{-1}$$

b

$$\text{Gain} = g_m R_L = \frac{I_c \cdot R_L}{V_T} \Rightarrow \frac{(V_{CC} - V_{CEQ}) R_L}{R_L V_T} \Rightarrow \frac{V_{CC} - V_{CEQ}}{V_T}$$

$$\text{If } V_{CEQ} = \frac{V_{CC} + V_{CE,sat}(=0)}{2} = V_{CC}/2$$

$$\text{Gain} = \frac{V_{CC}}{2V_T}$$


1. True/False questions (20 points)

For each of the following statements, state "T" for true or "F" for false. No explanation necessary. Correct answers are worth +2 point and incorrect answers yield -2 point. 0 points for unanswered questions. Your minimum total score on this problem is zero points.

| | |
|---|---|
| (a) The input resistance of a common-base stage depends on the load resistance, R_L . (Include r_o) | T |
| (b) Assuming a constant current source load, the voltage gain, A_V , of a cascode common-emitter amplifier is twice as large as that of a common-emitter amplifier without cascode. | F |
| (c) The Early voltage of a BJT can be increased by increasing the doping density in the base region. | T |
| (d) In an abrupt-junction pn diode, the depletion region is greater on the more lightly doped side. | T |
| (e) In an abrupt-junction pn diode, the potential drop is greater on the more lightly doped side. | T |
| (f) In a common-emitter amplifier with a fixed load resistance, R_L , properly biased for maximum signal swing at the output, the voltage gain is doubled as the power supply voltage, V_{CC} , is doubled. Assume $V_{CE(sat)} = 0V$ | T |
| (g) Cascoding can be used to increase the small-signal output resistance of a common-emitter stage. | T |
| (h) In a common-collector amplifier with an ideal current source connected from the emitter to ground, the small-signal input resistance is r_π . | F |
| (i) The combination of a degenerated common-emitter amplifier cascaded with a common-collector amplifier is suitable for current amplification. | T |
| (j) Oski got his/her undergraduate degree at Stanford. | F |

2 @ $\beta_1 = \beta_2 = \infty \Rightarrow$ No base current

4

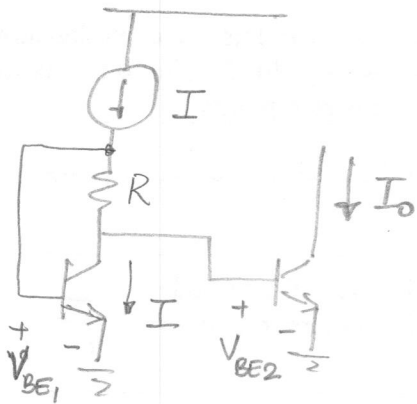

$$I = I_s \left(e^{V_{BE1}/V_T} - 1 \right)$$

$$I_O = I_s \left(e^{(V_{BE1} - IR)/V_T} - 1 \right)$$

$$V_{BE2} = V_{BE1} - IR$$

Plugging in values $I = 1\text{mA}$ $I_s = 10^{-17}$
 $R = 100$


$$V_{BE1} = V_T \ln \left(\frac{I}{I_s} + 1 \right) = 0.8252 \text{ V}$$

$$V_{BE2} = 0.7252 \text{ V}$$

$$I_O = 20.11 \mu\text{A}$$

2(b)

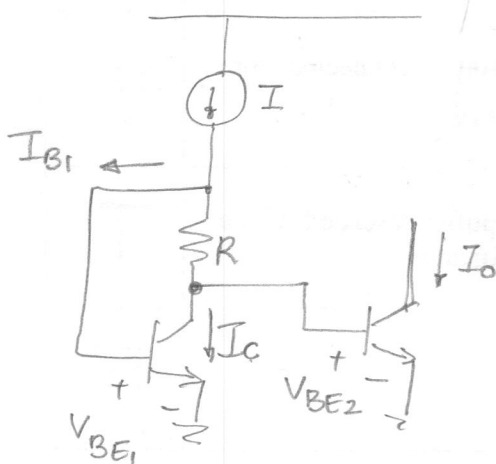when $\beta_1 = 100 \Rightarrow I_{B1} \neq 0$



$$I_C + I_{B1} = I$$


$$I_C = I - I_{B1} = I - \frac{I_C}{\beta}$$

$$I_C \left(1 + \frac{1}{\beta} \right) = I$$

$$I_C = \frac{I}{\left(1 + \frac{1}{\beta} \right)} = 0.9901 \text{ mA}$$

$$V_{BE1} = V_T \ln \left(\frac{I_C}{I_s} + 1 \right) = 0.82499 \text{ V}$$

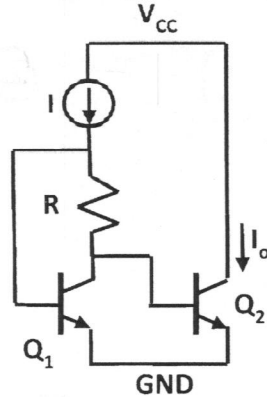2. DC Bias Circuits (40 points). In the circuit below, all devices operate in the forward-active region (FAR). In all cases, assume $I_{S1} = I_{S2} = 10^{-17}$ A, $I = 1$ mA and $R = 100 \Omega$.




(a) Find the value of I_o with $\beta_1 = \beta_2 = \infty$.

$$\begin{aligned}
 V_{BE2} &= V_{BE1} - I_o R \\
 &= 0.82499 - 0.9901 \times 10^{-3} \times 100 \\
 &= 0.82499 - 0.09901 = 0.72598 \text{ V} \\
 I_o &= I_S (e^{V_{BE2}/V_T} - 1) \\
 I_o &= 20.70 \mu\text{A}
 \end{aligned}$$

2 (c) $\beta_2 = 100 \Rightarrow I_{B2} \neq 0$

$$I = I_{B2} + I_c$$

$$I_{B2} = \frac{I_o}{\beta}$$

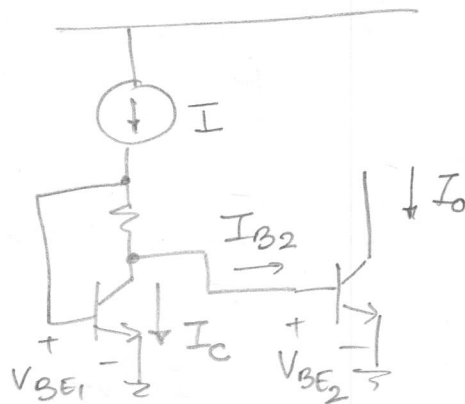

| | |
|-------------|--|
| (a) $I_o =$ | |
|-------------|--|

$$I = \frac{I_0}{\beta} + I_c \rightarrow (1)$$

$$I_c = I_s (e^{V_{BE1}/V_T} - 1) \rightarrow (2)$$

$$V_{BE1} = V_{BE2} + IR$$

$$V_{BE1} = V_T \ln\left(\frac{I_0}{I_s} + 1\right) + IR \rightarrow (3)$$

From (1), (2) and (3)

$$I - \frac{I_0}{\beta} = I_s \left(e^{IR/V_T} \cdot e^{\ln\left(\frac{I_0}{I_s} + 1\right)} - 1 \right)$$

$$\Rightarrow I - \frac{I_0}{\beta} = I_s \left[e^{IR/V_T} \left(\frac{I_0}{I_s} + 1 \right) - 1 \right]$$


$$I - \frac{I_0}{\beta} = I_0 e^{IR/V_T} + I_s e^{IR/V_T} - I_s$$

$$\frac{I - I_s e^{IR/V_T} + I_s}{1/\beta + e^{IR/V_T}} = I_0$$

$$I_0 = 20.112 \mu A$$

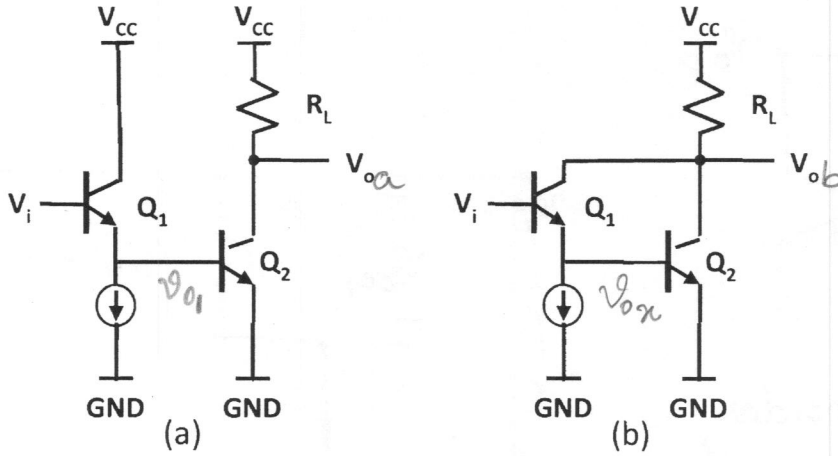3. (40 points) **Small-signal gain calculations.** In the circuits below, all devices operate in the forward-active region (FAR). In both cases, assume for DC $V_{BE1} = V_{BE2}$, $\beta_1 = \beta_2 = \infty$ and $V_{A1} = V_{A2} = \infty$.


Derive expressions for the small-signal voltage gains, $A_v = V_o/V_i$ and compute the value of the ratio of the two gains, $A_v(b)/A_v(a)$.



For first stage. (a)

$$\beta = \infty \Rightarrow r_{\pi} \Rightarrow \infty$$

(a)

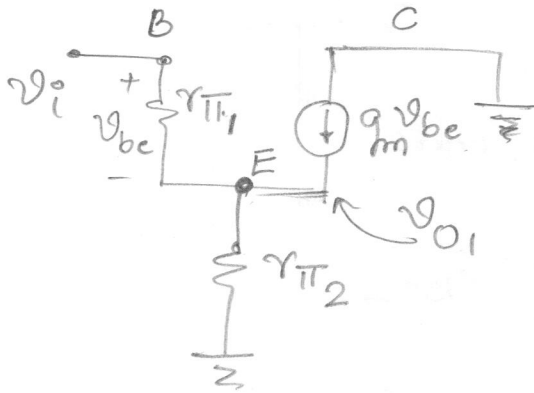

$$\frac{v_{o1} - v_i}{r_{\pi 1}} - g_m (v_i - v_{o1}) + \frac{v_{o1}}{r_{\pi 2}} = 0$$

$$v_{o1} \left(\frac{1}{r_{\pi 1}} + g_m + \frac{1}{r_{\pi 2}} \right) = \left(g_m + \frac{1}{r_{\pi 1}} \right) v_i$$

$$\frac{v_{o1}}{v_i} = \frac{g_m + 1/r_{\pi 1}}{1/r_{\pi 1} + g_m + 1/r_{\pi 2}}$$

Since $r_{\pi 1}$ and $r_{\pi 2} \rightarrow \infty$



$$\boxed{\frac{v_{o1}}{v_i} = 1}$$

$$\boxed{\frac{v_{oa}}{v_{o1}} = -g_{m2} R_L}$$

$$\boxed{A_{va} = \frac{v_{oa}}{v_{o1}} = -g_{m2} R_L}$$

Should be derived

⑥ For Case 2

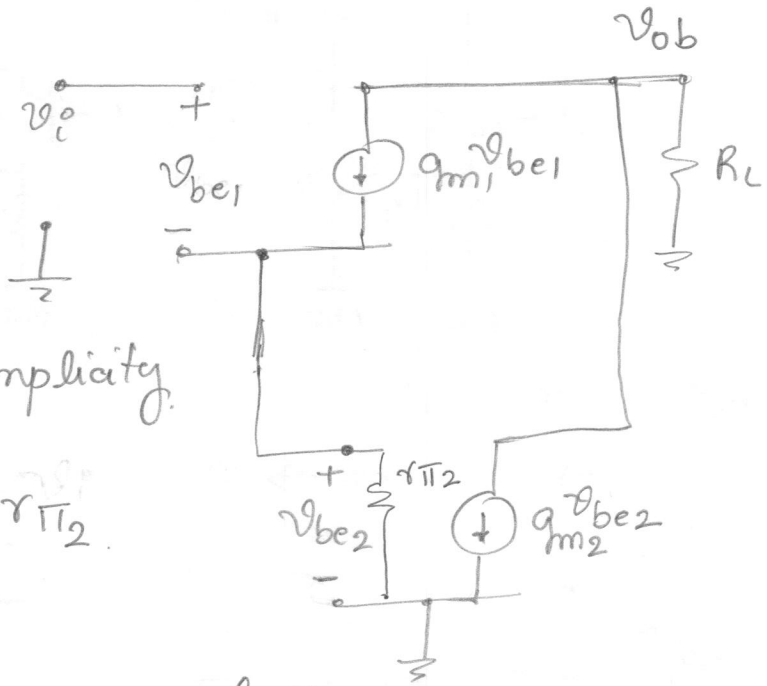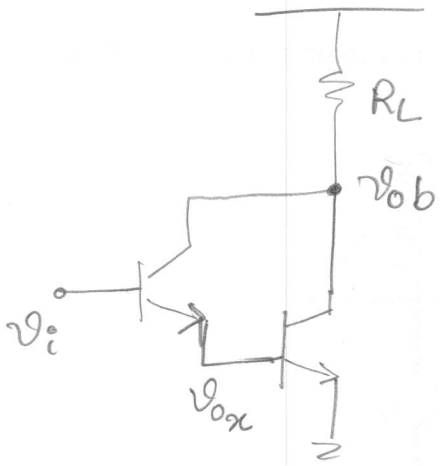

Let us consider only $r_{\pi 2}$ for simplicity.

$$v_{be2} = (g_{m1} v_{be1}) r_{\pi 2}$$

Since $r_{\pi 2} \rightarrow \infty$

$v_{be1} \rightarrow 0$ since v_{be2} is finite.

$$\Rightarrow v_i = v_{be1} + v_{be2} \approx v_{be2}$$

$$v_{ob} = -v_{be2} g_{m2} R_L = -v_i g_{m2} R_L$$

$$A_{vb} \left[\frac{v_{ob}}{v_i} = -g_m R_L \right]$$

$$\left[\frac{A_{vb}}{A_{vb}} = 1 \right]$$