

University of California at Berkeley
College of Engineering
Dept. of Electrical Engineering and Computer Sciences

EE 105 Midterm 2

Spring 2006

Prof. Ming C. Wu

April 6, 2006

Guidelines

- Closed book and notes.
- Two pages of information sheets allowed.
- Total time = 90 minutes

- (1) For the circuit shown in Fig. 1, $W/L = 2$ for both M_1 and M_2 , $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$, $\lambda = 0.05 \text{ V}^{-1}$, $V_{Tn} = 1\text{V}$, $V_{DD} = 5\text{V}$.
- [5 pt] Find the DC drain current at M_2 when $V_{OUT} = 3\text{V}$. Use $\lambda = 0$ for this part.
 - [5 pt] Find the DC gate bias (V_G) of M_2 such that the DC output voltage $V_{OUT} = 3\text{V}$. Use $\lambda = 0$ for this part.
 - [5 pt] Draw the small-signal equivalent circuit. Find the values of all circuit elements in the small signal circuit (e.g., g_m , r_0 , ...).
 - [5 pt] Find the voltage gain, $A_V = v_{out} / v_s$.
 - [5 pt] Find the output resistance of the circuit (both expression and numeric value).
 - [5 pt] Find the input resistance, and construct the two-port model of this voltage amplifier.

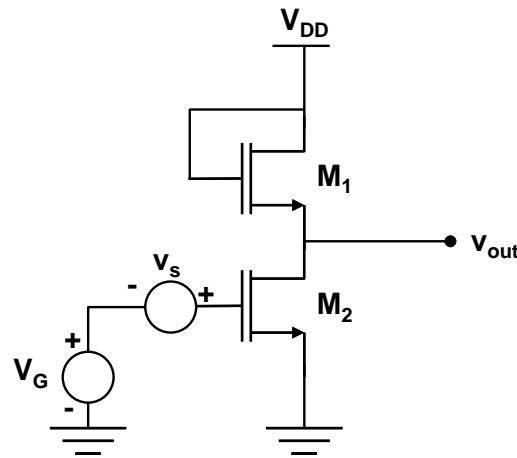


Fig. 1

- (2) Consider the following circuit with $(W/L)_1 = 2$, $(W/L)_2 = 1$, $\mu_p C_{ox} = 50 \mu\text{A}/\text{V}^2$, $\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$, $\lambda_n = \lambda_p = 0.05 \text{ V}^{-1}$, $V_{Tn} = 1\text{V}$ and $V_{Tp} = -1\text{V}$, $V_{DD} = 5\text{V}$:
- [10 pt] The gate is biased at 2.5V DC. Show that both transistors are in saturation regime. Find the expression and numeric value of small-signal voltage gain, $A_V = v_{out} / v_s$.
 - [10 pt] Find the maximum and the minimum voltage at the output of this circuit when both transistors stay in saturation regime.

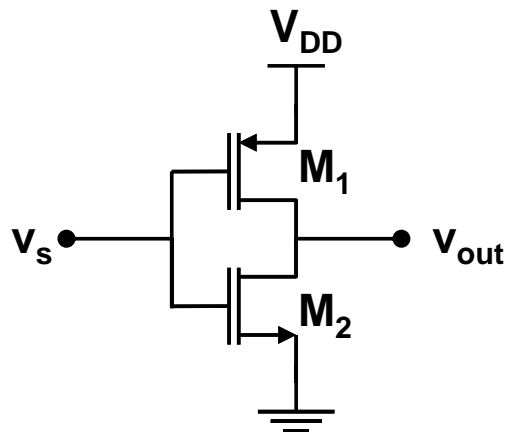


Fig. 2

- (3) Consider the following circuit with 3 PMOS transistors: $(W/L)_1 = 10$, $(W/L)_2 = 20$, $(W/L)_3 = 100$, $\mu_p C_{ox} = 50 \mu\text{A}/\text{V}^2$, $\lambda = 0.05 \text{ V}^{-1}$, $V_{Tp} = -1 \text{ V}$, $I_{REF} = 10 \mu\text{A}$, $V_+ = 3 \text{ V}$, $V_- = -3 \text{ V}$, $R_L = 100 \text{ K}\Omega$.
- [5 pt] Can you identify any functional block in this circuit (i.e., any portion of the circuit that performs a known function)? Replace that functional block, and draw a simplified circuit of the amplifier.
 - [10 pt] Find the expression of the voltage gain, $A_v = v_{out} / v_s$, and then find its numerical value.
 - [10 pt] Find both the expression and the numeric value of the output resistance of the amplifier.

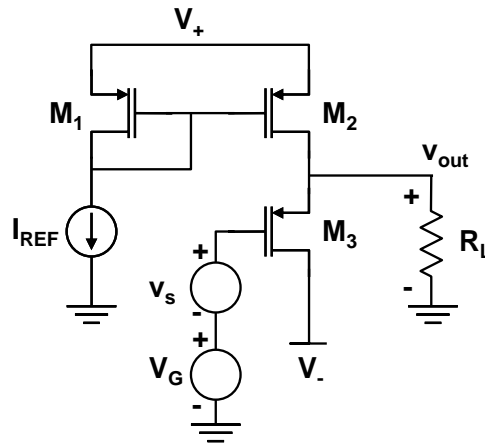


Fig. 3

- (4) The frequency response of an amplifier is shown in the figure below.

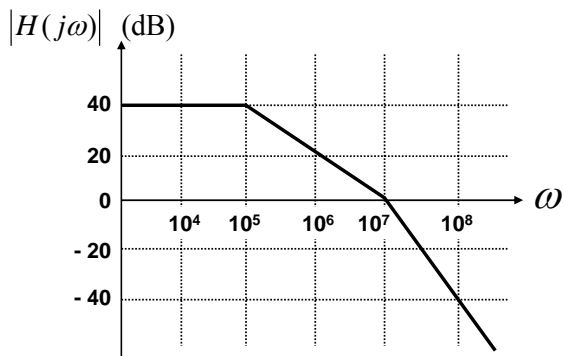


Fig. 4A

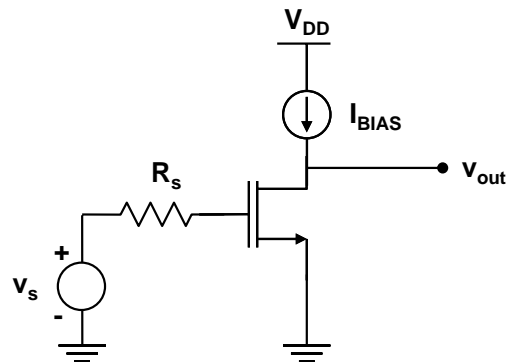


Fig. 4B

- [8 pt] Find the transfer function of the frequency response shown in Fig. 4A.
- [7 pt] This transfer function can be realized by the circuit in Fig. 4B. Draw the small-signal circuit that includes C_{gd} . For simplicity, we will neglect C_{gs} . Analysis of this circuit can be simplified by Miller approximation. Draw the simplified small-signal equivalent circuit. Show the Miller capacitances explicitly in terms of other circuit parameters.
- [10 pt] The following parameters of the circuit are given:
 $I_{BIAS} = 10 \mu\text{A}$, $\lambda = 0.1 \text{ V}^{-1}$, $r_{oc} = \infty$ (ideal current source).
 If the frequency response of the amplifier matches the transfer function shown in Fig. 4A, find the numeric values of the transistor parameters: C_{gd} , r_0 , g_m , and the circuit parameter, R_s .

Some equations

Threshold voltage (NMOS)

$$V_{Tn} = V_{FB} - 2\phi_p + \frac{1}{C_{ox}} \sqrt{2q\epsilon_s N_a (-2\phi_p)}$$

$$V_{Tn} = V_{Tn0} + \gamma \left(\sqrt{V_{SB} - 2\phi_p} - \sqrt{-2\phi_p} \right)$$

$$\phi_p = -\frac{kT}{q} \ln \frac{N_a}{n_i}$$

NMOS equations:

$$I_D = 0, \quad V_{GS} < V_{Tn}$$

$$i_D = \frac{W}{L} \mu C_{ox} \left(V_{GS} - V_{Tn} - \frac{V_{DS}}{2} \right) V_{DS} (1 + \lambda V_{DS}), \quad V_{GS} > V_{Tn}, \quad V_{DS} < V_{GS} - V_{Tn}$$

$$i_D = \frac{W}{L} \frac{\mu C_{ox}}{2} (V_{GS} - V_{Tn})^2 (1 + \lambda V_{DS}), \quad V_{GS} > V_{Tn}, \quad V_{DS} > V_{GS} - V_{Tn}$$

MOS capacitances in saturation $C_{GS} = (2/3)WLC_{ox} + C_{ov}$ $C_{ov} = L_D W C_{ox}$

MOS signal parameters:

$$g_m = \left. \frac{\partial i_D}{\partial V_{GS}} \right|_{V_{GS}, V_{DS}} = \mu C_{ox} \frac{W}{L} (V_{GS} - V_{Tn}) (1 + \lambda V_{DS})$$

$$\approx \mu C_{ox} \frac{W}{L} (V_{GS} - V_{Tn})$$

$$= \sqrt{2i_D \left(\frac{W}{L} \right) \mu C_{ox}}$$

$$r_o = \left(\left. \frac{\partial i_D}{\partial V_{DS}} \right|_{V_{GS}, V_{DS}} \right)^{-1} \approx \frac{1}{\lambda I_{DS}}$$

$$g_{mb} = \left. \frac{\partial i_D}{\partial V_{BS}} \right|_Q = \frac{\gamma g_m}{2\sqrt{-V_{BS} - 2\phi_p}}$$