

Problem 1 - Short Answers (8 points)

If you make any assumption that you think might be unclear to the grader, mark that question with an asterisk (*) in the right-hand margin and explain your assumption on the back of the page. Note that some of the non-true/false questions may have more than one correct answer.

[1 pt.] (a) T F The peak value of the AC voltage at the wall outlets in your lab in Cory Hall is 170 volts.

[1 pt.] (b) T F An ideal discharged capacitor is a nonlinear component.

[1 pt.] (c) T F A phasor voltage V is a function of time.

[1 pt.] (d) Name a component or device that turns a steady current into a steady voltage.

Answer: Resistor

[1 pt.] (e) Name a two-terminal component that can never pass a steady current with a steady voltage applied.

Answer: Capacitor

[2 pts.] (f) Name two components or devices that can increase the amplitude of an AC voltage.

Answer: Transformer; amplifier; MOSFET


[1 pt.] (g) Name a component or device that can use a steady voltage to control a steady current.

Answer: MOSFET; voltage-controlled current source

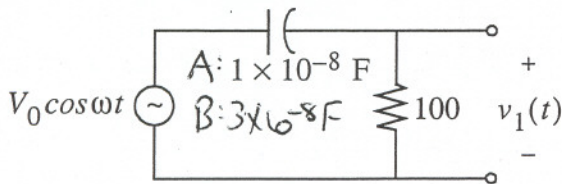Problem 2 – Phasors (13 points)

KEY

[6 pts.] (a) Determine the Thévenin equivalent of the following circuit using phasors:



$$V_{oc} = V_{TH} = V_0 \cdot \frac{R}{R + 1/j\omega C} = \frac{j\omega RC}{1 + j\omega RC} V_0$$

where $\omega = 10^6$ rad/sec

$$= V_0 \cdot \frac{j\omega RC}{1 + j\omega RC} \cdot \frac{1 - j\omega RC}{1 - j\omega RC} = \frac{\omega^2 R^2 C^2 + j\omega RC}{1 + \omega^2 R^2 C^2} V_0$$

A: $C = 10^{-8} F$, $\omega RC = 1$ B: $C = 3 \times 10^{-8} F$, $\omega RC = 3$

A: $V_{TH} = \frac{1 + j}{2} V_0$

$Z_{TH} = \frac{100 - 100j}{2}$

$Z_{TH} = \frac{R \cdot 1/j\omega C}{R + 1/j\omega C} = \frac{R}{1 + j\omega RC}$

(Express answers in simplest rectangular form $A + Bj$.)

B: $V_{TH} = \frac{9 + 3j}{10} V_0$

$Z_{TH} = \frac{100 - 300j}{10} = 10 - 30j$

$Z_{TH} = \frac{R(1 - j\omega RC)}{1 + \omega^2 R^2 C^2}$

[3 pts.] (b) What is the time average power in the 100 ohm resistor?

A: $P_{ave} =$

$= \frac{1}{2} \text{Re}[VI^*] = \frac{1}{2} \text{Re}\left[\frac{V_{TH}}{R} \cdot \frac{V_{TH}^*}{R}\right]$

A: $\frac{1}{200} \cdot \left(\frac{1 \cdot \sqrt{2}}{2} V_0\right)^2 = \frac{V_0^2}{400}$

$= \frac{1}{2R} \frac{1}{2R} |V_{TH}|^2$, $|V_{TH}| = \frac{\sqrt{\omega^4 R^4 C^4 + \omega^2 R^2 C^2} V_0}{1 + \omega^2 R^2 C^2}$

B: $\frac{1}{200} \cdot \left(\frac{3 \cdot \sqrt{10}}{10} V_0\right)^2 = \frac{9 V_0^2}{2000}$

$= \frac{\omega RC \sqrt{\omega^2 R^2 C^2 + 1}}{1 + \omega^2 R^2 C^2} V_0$

[4 pts.] (c) The output voltage is of the form $v_1(t) = V_1 \cos(\omega t + \phi)$. Determine V_1 and ϕ .

$V_1 = |V_{TH}|$

$\phi = \angle V_{TH}$

$\angle V_{TH} = \angle \frac{j\omega RC}{1 + j\omega RC} = \angle \frac{1}{1 - j\omega RC}$

(Express answers in simplest rectangular form $A + Bj$.)


A: $|V_{TH}| = \frac{\sqrt{2}}{2} V_0$

$\angle V_{TH} = \tan^{-1} 1$

B: $|V_{TH}| = \frac{3\sqrt{10}}{10} V_0$


$\angle V_{TH} = \tan^{-1} 1/3$

Problem 3 – Phasors (18 points)

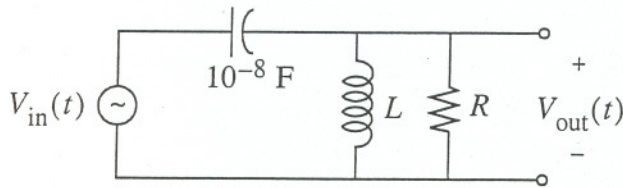

where $V_{in}(t) = \cos(\omega t)$ and $L = 2 \times 10^{-4}$ H, $R = 200 \Omega$



[2 pts.] (a) What is $|V_{out}(t)|$ for $\omega = 0$?

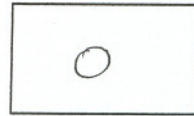


Since C is open circuit

[2 pts.] (b) What is $|V_{out}(t)|$ for $\omega \rightarrow \infty$?

C is short circuit

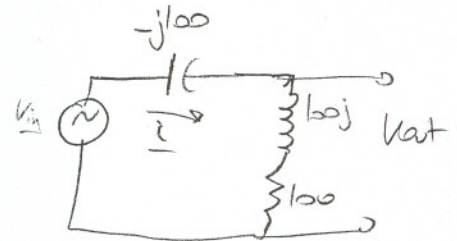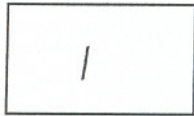


[8 pts.] (c) What is $|V_{out}(t)|$ for $\omega = 10^6$?

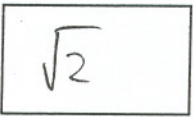

$$i = \frac{V_{in}}{100}$$
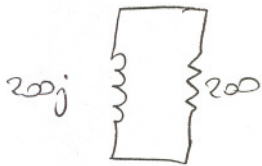
$$V_{out} = \frac{V_{in}}{100} \cdot (100 + 100j) = V_{in} \cdot (1 + j)$$




$$\frac{200 \cdot 200j}{200 + 200j} = \frac{200j}{1+j} = \frac{200j(1-j)}{2} = 100 + 100j = \text{---} \text{---} \text{---}$$

$$\left| \frac{V_{out}}{V_{in}} \right|_{\omega=10^6} = \sqrt{2}$$

[6 pts.] (d) Let $G(\omega) = \frac{V_{out}}{V_{in}}$. Sketch the general behavior of $|G(\omega)|$ vs. ω on axes provided. (Note linear scales.)

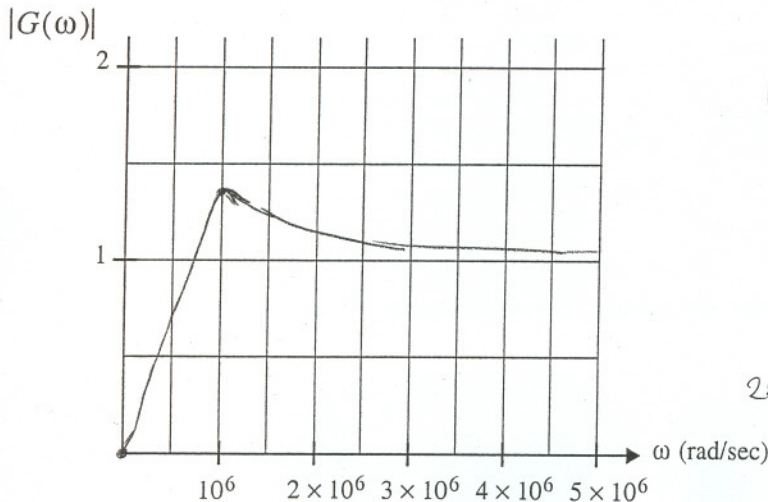check $G(\omega=5 \times 10^6) \approx 1$




$$\begin{aligned} & \frac{200 \cdot 100j}{200 + 100j} = \frac{1000j}{1+5j} \\ & = \frac{(1000j)(1-5j)}{1+25} = \frac{5000 + 1000j}{26} \\ & \approx 200 + 40j \end{aligned}$$


Problem 4 – Short Answers (15 points)

A circuit made with three ideal op amps is shown below:

version A

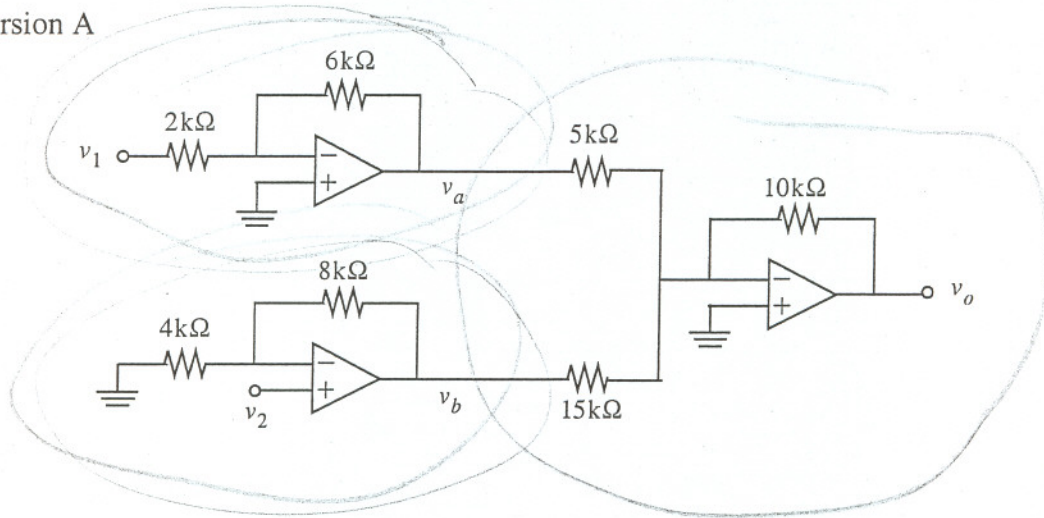

version B

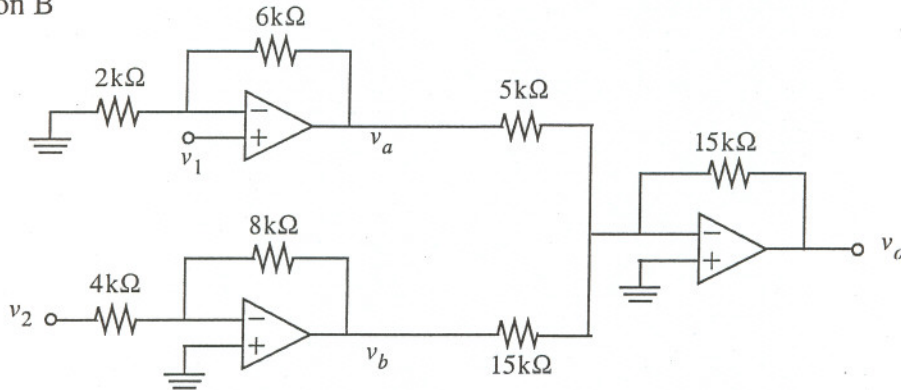

[6 pts.] (a) Of what three basic op-amp circuits is this circuit composed? (Circle them individually.)

Sub-circuit with output v_a is an inverting amplifier

Sub-circuit with output v_b is non-inverting amplifier

Sub-circuit with output v_o is Inverting summing amplifier

[9 pts.] (b) Find the voltages v_a , v_b , and v_o in terms of v_1 and v_2 . Make your methods clear to the grader.

$$v_a = \frac{-3v_1}{1} \quad \frac{v_1}{2k} = -\frac{v_a}{6k}, \quad v_a = -3v_1$$

$$v_b = \frac{3v_2}{1} \quad v_b \cdot \frac{4}{8} = v_2, \quad v_b = 3v_2$$

$$v_o = \frac{6v_1 - 2v_2}{1} \quad -\frac{v_o}{10k} = \frac{v_a}{5k} + \frac{v_b}{15k}$$


$$v_o = -2v_a - \frac{2}{3}v_b$$

$$= 6v_1 - 2v_2$$

Problem 5 (20 points)

An ideal op amp is shown with its input sources and its power supplies.

version A

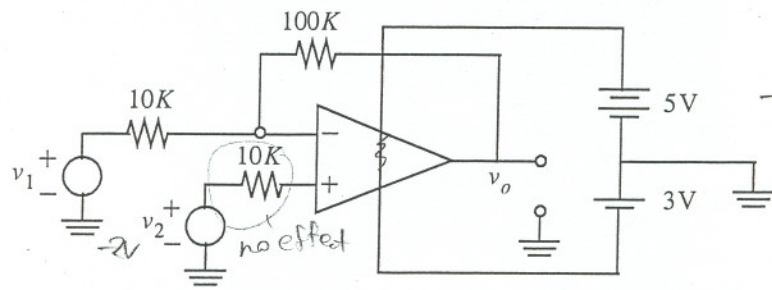


$$-3V < v_o < 5V$$

$$-3V < -10v_i - 22 < 5V$$

$$19V < -10v_i < 27V$$

$$-1.9V > v_i > -2.7V$$

version B

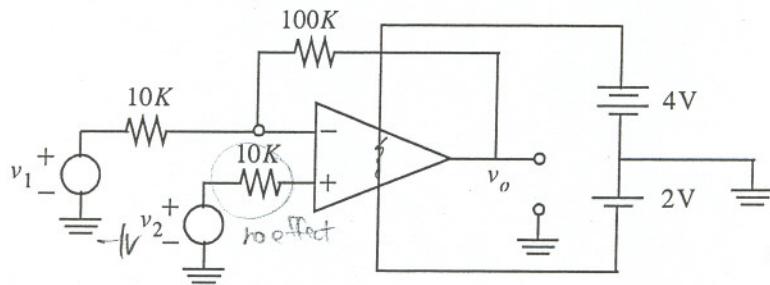


$$-2V < v_o < 4V$$

$$-2V < -5v_i - 6 < 4V$$

$$4V < -5v_i < 10V$$


$$-4/5 > v_i > -2V$$

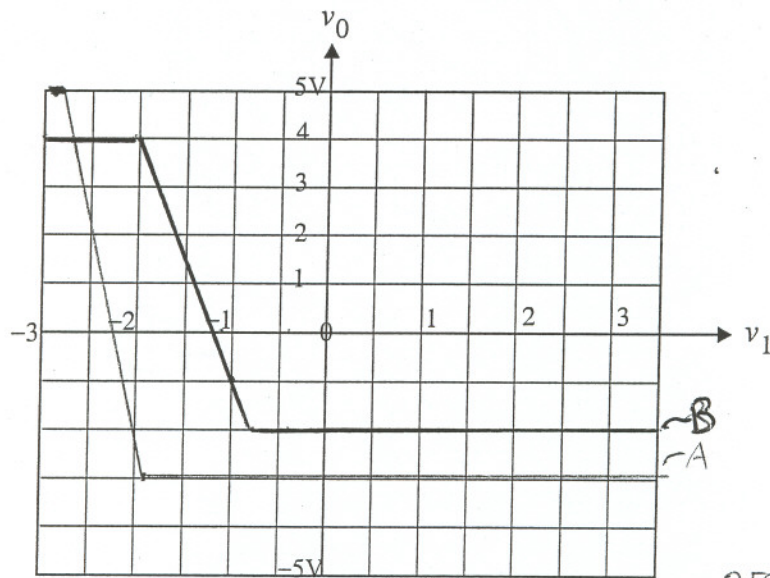Given $v_2 = \begin{cases} -2V \\ -1V \end{cases}$ plot V_0 vs. V_1 for $-3 \leq v_1 \leq 3$ volts.




Version A

in negative feedback $v_- \approx v_+$

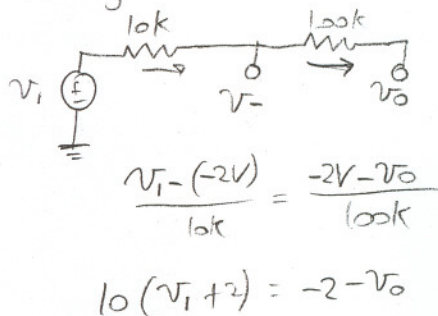

$$v_o = -10v_i - 22$$


version B

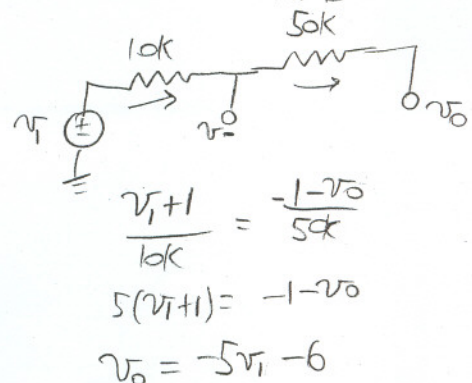

Problem 6 (10 points)

A DC circuit that was connected up one week ago is shown attached to a Very Strange Component whose I-V characteristic is shown. find I and V for this circuit. Make your method clear for the grader and state any assumptions you make.

version A

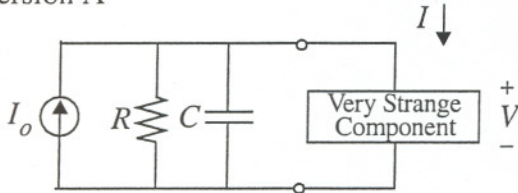


$I_o = 0.5 \text{ mA}$
 $R = 10 \text{ k}\Omega$
 $C = 300 \mu\text{F}$


load line by KCL

$I_o - \frac{V}{R} - I = 0, I = I_o - \frac{V}{R}$

version B

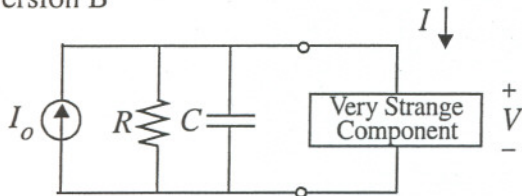

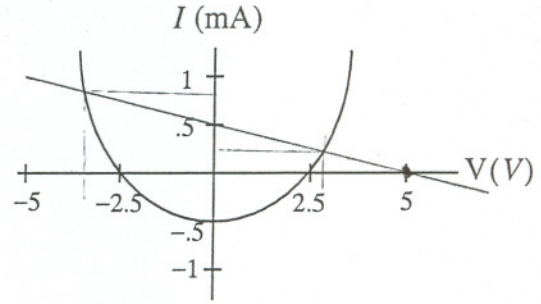$I_o = 1 \text{ mA}$
 $R = 3 \text{ k}\Omega$
 $C = 100 \mu\text{F}$




$I = 0.3 \text{ mA}$

$V = 2.7 \text{ V}$

or $I = 0.8 \text{ mA}$

$V = -3.5 \text{ V}$

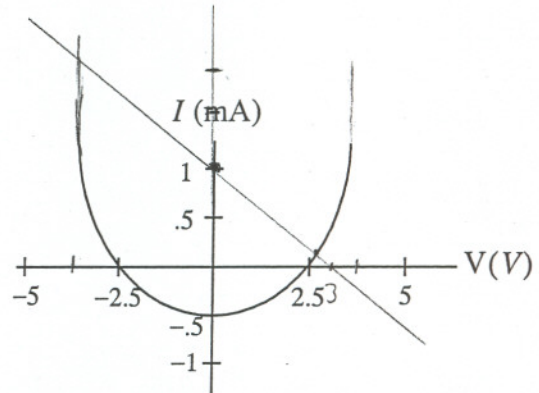Bistable - circuit could be in either state.



$I = 0.1 \text{ mA}$


$V = 2.6 \text{ V}$

or $I = 2 \text{ mA}$

$V = -3.7 \text{ V}$

Problem 7 (16 points)

KEY

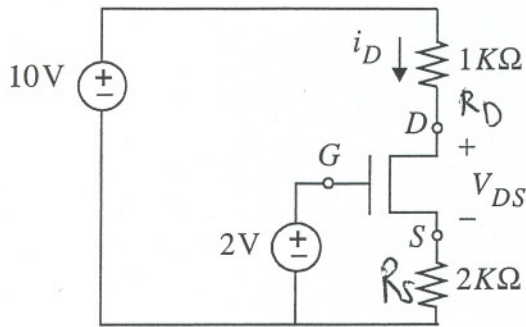

$V_{t0} = 1\text{V}$ (threshold voltage)

$K = \frac{500\mu\text{A}}{\text{V}^2}$

[3 pts.] (a) What is i_D as a function of V_{DS} ?

~~By KVL~~

$$i_D = \frac{10\text{V} - V_{DS}}{3\text{k}\Omega}$$

[3 pts.] (b) What is V_{GS} as a function of i_D ?

$$V_{GS} = 2\text{V} - i_D (2\text{k}\Omega)$$

[10 pts.] (c) What is V_{DS} at quiescent point?

(Hint: $i_D = K(V_{GS} - V_{t0})^2$. If needed,

you may use $\sqrt{2} \approx 1.4$, $\sqrt{3} \approx 1.7$.)

$$i_D = K(V_{GS} - V_{t0})^2$$

substitute $i_D = \frac{2\text{V} - V_{GS}}{2000}$ from (b).

$$\frac{2\text{V} - V_{GS}}{2000} = K(V_{GS} - 1)^2$$

$$2\text{V} - V_{GS} = V_{GS}^2 - 2V_{GS} + 1$$

$$V_{GS}^2 - V_{GS} - 1\text{V} = 0$$

$$V_{GS} = \frac{1 \pm \sqrt{1+4}}{2} = \frac{1 \pm \sqrt{5}}{2}$$

$$V_{DS} \approx 9.46 \text{ volts}$$

$\sqrt{5} \approx 2.2$, so $V_{GS1} = \frac{1}{2}(1-2.2) < 0$
not possible.

$$V_{GS2} = \frac{1}{2}(1+2.2) = \frac{3.2}{2} = 1.6\text{V}$$

Now solve for i_D

$$i_D = K(1.6 - 1)^2 \quad (\text{note } 6 \times 6 = 36)$$

$$= (500 \times 10^{-6})(0.36)$$

$$= (1000 \times 10^{-6})(0.18) \quad (\frac{18}{2 \times 36})$$

$$= 0.18\text{mA}$$

Now

$$V_{DS} = 10\text{V} - (3000)(0.18\text{mA})$$

$$= 10\text{V} - 0.54 = 9.46$$

($2 \times 3 \times 9 = 54$)