

UNIVERSITY OF CALIFORNIA  
College of Engineering  
Department of Electrical Engineering  
and Computer Sciences

EE 42 / 100

Midterm 2

Spring 2008

Name:

Solutions

SID:

Section:


Name of student left of you:

Name of student right of you:

Problem	Score
1	
2	
3	
4	
Total	

- Check the units of your results.
- Closed book, closed notes.
- No calculators.
- Leave pack, books, and electronic devices (e.g. cell phones) in isle.
- Take off caps or hats.
- Copy your answers into marked boxes on exam sheets.
- Simplify numerical and algebraic results as much as possible.
- Be kind to the graders and write legibly. No credit for illegible results.
- No credit for multiple differing answers to the same question.
- The UC rules on dishonesty apply.

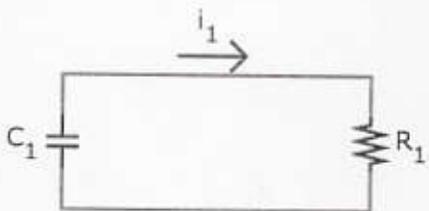1. [25 points] A capacitor  $C_1$  is used to power a model airplane, represented in the circuit diagram below by resistor  $R_1$ . Initially the capacitor is charged to voltage  $V_1$ . Calculate the fraction  $r$  of the initial energy remaining on the capacitor when the current  $i_1$  has decreased to half its initial value.



$$r = \frac{1}{4}$$

The energy stored in a capacitor is given by

$$E_{\text{stored}} = \frac{1}{2} C V^2$$

$$E_0 = \frac{1}{2} C_1 V_0^2 = \frac{1}{2} C_1 V_1^2$$


$$E_f = \frac{1}{2} C_1 V_f^2 = \frac{1}{2} C_1 (I_f R_1)^2 = \frac{1}{2} C_1 \left(\frac{I_1 R_1}{2}\right)^2 = \frac{1}{2} C_1 \left(\frac{V_1}{2}\right)^2$$

$$r = \frac{E_f}{E_0} = \frac{\frac{1}{2} C_1 \left(\frac{V_1}{2}\right)^2}{\frac{1}{2} C_1 V_1^2} = \frac{1}{4}$$

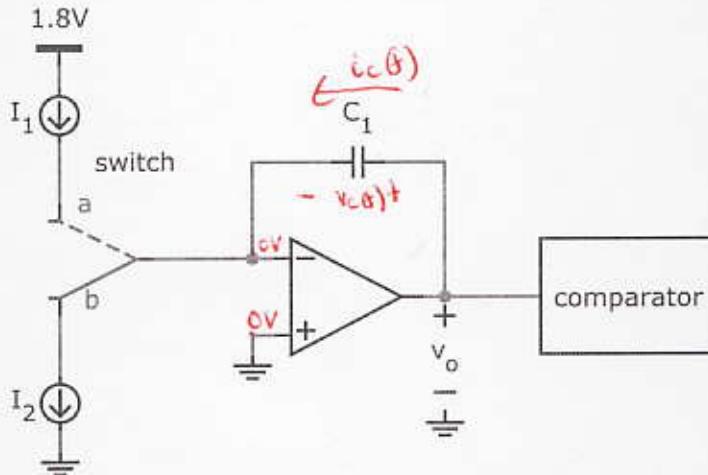2. [25 points] In the circuit below  $C_1$  represents a touch sensor. The comparator controls the position of the switch as follows: Whenever  $V_o$  reaches the value  $V_{ref}$ , the switch is set to position  $a$ . After  $V_o$  drops to zero, the switch is set to position  $b$ . Touch is detected by measuring the frequency  $f_o$  at which the switch position changes.

Derive an analytical expression for  $f_o$ . Assume that the operational amplifier is ideal.

Suggestion: sketch  $v_o(t)$  and mark the knowns and unknowns in the graph.



$$f_o = \frac{I_1 \cdot I_2}{C \cdot V_{ref} (I_1 + I_2)}$$

The op-amp is in negative feedback.

$$v_p = v_n = 0 \quad v_p = v_n = 0V$$

Let's define the current & voltage through  $C_1$  as  $i_c(t) + v_c(t)$

$$i = C \frac{dv}{dt} \Rightarrow v_c(t) = \frac{1}{C} \int_0^t i_c(x) dx + v_c(0)$$

Charge Cycle (switch is set to b)

$$V_{ref} = \frac{1}{C} \int_0^{T_a} i_c(x) dx + v_c(0)$$

$$V_{ref} = \frac{1}{C} I_2 T_a + 0V$$

$$T_a = \frac{C \cdot V_{ref}}{I_2}$$

Discharge Cycle (switch is set to a)


$$0V = \frac{1}{C} \int_{T_a}^{T_a+T_b} i_c(x) dx + v_c(t_a)$$

$$0V = \frac{1}{C} (-I_2) T_b + V_{ref}$$

$$T_b = \frac{C \cdot V_{ref}}{I_1}$$

$$T = T_a + T_b \Rightarrow f = \frac{1}{T_a + T_b}$$
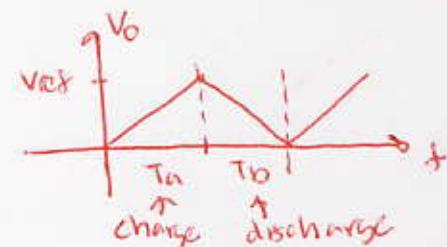
$$f = \frac{1}{I_1} + \frac{1}{I_2} = \frac{I_1 \cdot I_2}{C \cdot V_{ref} (I_1 + I_2)}$$




Note:  $C_1$  charges through  $I_2$  & discharges through  $I_1$ .

-blank-

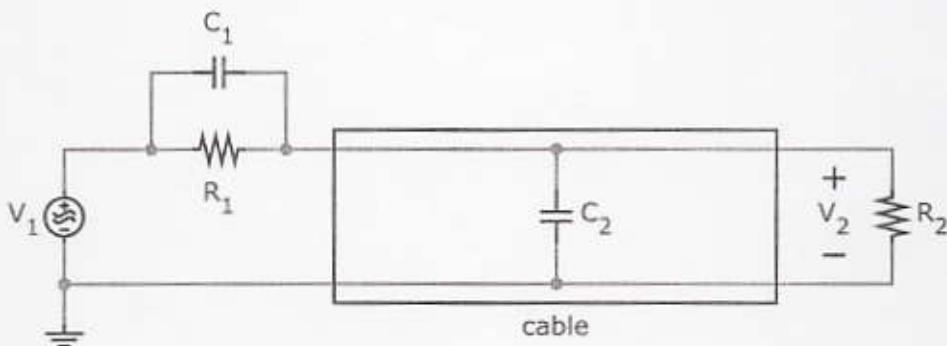3. [25 points] The circuit below shows a simple model of a wired Ethernet connection.  $V_1$  is the signal source and  $R_1$  represents its impedance. The cable is modelled by capacitor  $C_2$  and  $R_2$  represents the receiver's input impedance. The capacitor  $C_1$  has been added to enable higher frequency transmission at low error rates.

Derive an expression for  $C_1$  as a function of  $R_1$ ,  $R_2$ , and  $C_2$  for which  $\frac{V_2(j\omega)}{V_1(j\omega)}$  has a constant value that is independent of frequency.

Note: This technique is used in many transceivers including 100 Mbit Ethernet.



$$C_1 = \frac{C_2 R_2}{R_1}$$

### Short Solution

The impedance at low frequencies should equal the impedance at high frequencies. Since the caps are open at low freqs & close shorts at high freqs

$$Z(10) = Z(\infty)$$

$$\frac{R_2}{R_1 + R_2} = \frac{\frac{1}{j\omega C_2}}{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}}$$

$$\frac{R_2}{R_1 + R_2} = \frac{C_1}{C_1 + C_2}$$


$$R_2(C_1 + C_2) = C_1(R_1 + R_2)$$

$$C_1 = \frac{C_2 R_2}{R_1}$$

PROB 5)
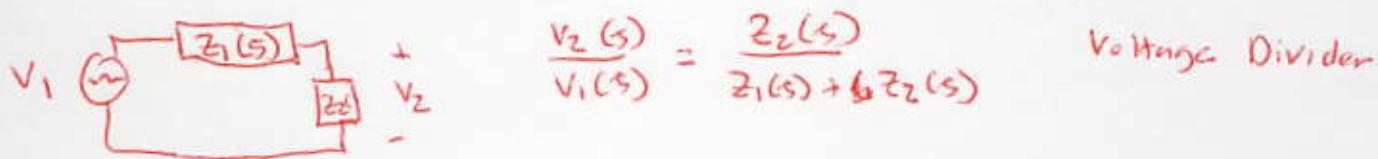
### "Long" Solution

- Let's find the transfer function  $V_2(s)/V_1(s)$



$$\text{Where } Z_1(s) = \frac{R_1 \cdot \frac{1}{sC_1}}{R_1 + \frac{1}{sC_1}} = \frac{R_1}{1+sR_1C_1} \quad Z_2(s) = \frac{R_2 \cdot \frac{1}{sC_2}}{R_2 + \frac{1}{sC_2}} = \frac{R_2}{1+sR_2C_2}$$

$$\begin{aligned} \frac{V_2(s)}{V_1(s)} &= \frac{\frac{R_2}{1+sR_2C_2}}{\frac{R_1}{1+sR_1C_1} + \frac{R_2}{1+sR_2C_2}} = \frac{R_2(1+sR_1C_1)}{R_1(1+sR_2C_2) + R_2(1+sR_1C_1)} \\ &= \frac{R_2}{R_1+R_2} \cdot \frac{(1+sR_1C_1)}{1+s\frac{R_1R_2}{R_1+R_2}(C_1+C_2)} \end{aligned}$$

In order for the transfer to be independent of frequency, the coefficients of  $s$  should be equal.

$$\therefore R_1C_1 = \frac{R_1R_2}{R_1+R_2}(C_1+C_2)$$


$$R_1C_1(R_1+R_2) = R_1R_2(C_1+C_2)$$

$$C_1 \frac{R_1}{R_1+R_2} = C_2 \frac{R_2}{R_1+R_2}$$

$$C_1 = C_2 \frac{R_2}{R_1}$$

4. [25 points] An audio system suffers from high frequency interference. Design a circuit consisting of a resistor  $R$  and capacitor  $C$  that passes low frequency signals ( $\left| \frac{V_o(j\omega)}{V_i(j\omega)} \right|_{\omega=0} = 1$ ) and attenuates high frequency signals ( $\left| \frac{V_o(j\omega)}{V_i(j\omega)} \right|_{\omega>0} < 1$ ).

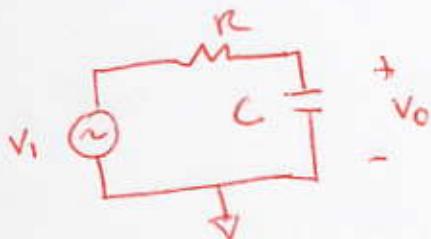- (a) Draw a diagram of a circuit with these characteristics, consisting of  $R$  and  $C$ . Clearly mark the input and output voltages  $V_i$  and  $V_o$  with plus and minus signs.



$$\frac{V_o}{V_i} = \frac{\frac{1}{sC}}{\frac{1}{sC} + R} = \frac{1}{1 + sRC}$$

- (b) Derive a symbolic expression for the value of  $C$  as a function of  $R$  that results in 26 dB attenuation at a given frequency  $f_0$ .

Hint: draw the Bode plot (piece-wise linear approximation of magnitude response) of the circuit. Mark what is known and unknown in the graph.

$C = \frac{10}{\pi f_0 R}$	(assume $f_0$ is in Hz)	$= \frac{20}{f_0 R}$	(assume $f_0$ is in rad/s)
----------------------------	-------------------------	----------------------	----------------------------

Bode Plot for  $H(s) = \frac{1}{1 + sRC} = \frac{1}{1 + s/w_p}$  where  $w_p = \frac{1}{RC}$



The transfer function of a first-order system is given by  $H(j\omega) = \frac{1}{1 + j\omega RC} = \frac{1}{1 + j\omega w_p}$ . If  $\omega \gg w_p$  (large), the imaginary term in the denominator dominates, and we have

$$H(j\omega) \approx \frac{1}{j\omega w_p}$$

$$G_{\text{attdB}}(\omega) = 20 \log_{10} |H(j\omega)|$$

Prob 4 cont.

The gain difference at  $\omega = \omega_0$  (frequency) 10 times  $w_p$  is

$$\begin{aligned} & \text{Gain}_{dB}(10w_p) - \text{Gain}_{dB}(w_p) \\ &= -20\log_{10}(10w_p) + 20\log_{10}(w_p) \\ &= -20\log_{10}(10) - 20\log_{10}(w_p) + 20\log_{10}(w_p) \\ &= -20\log_{10}(10) = -20dB \quad (\text{at 10 times } w_p) \end{aligned}$$

The gain difference at  $\omega = \omega_0$  2 times  $w_p$  is

$$\begin{aligned} & \text{Gain}_{dB}(2w_p) - \text{Gain}_{dB}(w_p) \\ &= -20\log_{10}(2w_p) + 20\log_{10}(w_p) \\ &= -20\log(2) - 20\log(w_p) + 20\log(w_p) \\ &= -20\log(2) = -6dB \quad (\text{at 2 times } w_p) \end{aligned}$$

Now for our problem, we have 26 dBs attenuation

$$\begin{aligned} 26dB &= 20dB + 6dB \\ &\quad \uparrow \quad \uparrow \\ &= \text{Gain}_{dB}(10x) + \text{Gain}_{dB}(2x) \\ &= \text{Gain}_{dB}(20 \cdot w_p) \end{aligned}$$

$$\omega_0 = 20 \cdot w_p = 20 \cdot \frac{1}{RC}$$

$$\Rightarrow C = \frac{20}{R \cdot \omega_0}$$

$$\text{Since } \omega_0 = 2\pi f_0$$

$$C = \frac{20}{2\pi f_0 R} = \boxed{\frac{10}{\pi f_0 R}}$$