

## **THIS IS A CLOSED BOOK QUIZ**

Electromagnetic Fields and Waves -- EE117. Quiz 1.

SPRING 2021

Instructor: Prof. Boubacar Kanté

9:40am-11:00am 02/18/2021

- The solution should be scanned (if written on paper) and submitted to Gradescope "Quiz 1", similar to previous homework submissions.
- The submission deadline is 11am at the end of the class, with additional 5 mins grace period for scanning & submission.
- The quiz is closed book, but one-page cheat sheet is allowed. No online resource is allowed.
- Partial credits will be given if the derivation is correct but the answer is wrong.
- Please keep camera on during the quiz.
- If you have questions during the quiz, please post it in Zoom chat.

Honor Pledge: I have neither given nor received any aid on this quiz.

Signature: \_\_\_\_\_

**Problem 1 [Transmission lines]. (50 points)**

Consider a system in Fig. 1(a) that operates under the frequency  $f = 3 \text{ GHz}$ . The system comprises a feeding transmission line (TL1) of characteristic impedance  $Z_{01} = 50 \Omega$  that is connected to two identical transmission lines (TL3a and TL3b) through a transmission line TL2 of impedance  $Z_{02}$ . The length of TL2 is  $l_2 = \lambda/4$  and the length of TL3(a) and TL3(b) is  $l_3 = 5\lambda/2$ . The transmission lines TL3a and TL3b are terminated by load impedance  $Z_L$ . The system is excited by an incident wave of voltage amplitude of  $1 \text{ V}$  in TL1.

- 1) The load impedances are given by  $Z_L = 70 \Omega$ . The characteristic impedance of TL2 is  $Z_{02} = 50 \Omega$ . Find the input impedance and reflection coefficient at port  $AA'$ . Give expressions for the phasor and instantaneous voltage and current in TL1.
- 2) The load impedances are again  $Z_L = 70 \Omega$ . Find a value of the characteristic impedance  $Z_{02}$  that leads to no reflected wave in TL1 (i.e. perfect matching between TL1 and the rest of the system).
- 3) With the matching conditions in item 2 in place, is there a standing wave in TL1? Is there a standing wave in TL2?
- 4) Now, the load impedances are replaced with complex impedances  $Z_L = 70 \Omega - j20 \Omega$  and the characteristic impedance  $Z_{02}$  is given by  $Z_{02} = 50 \Omega$ . A matching circuit is inserted at the port  $AA'$ . It consists of a reactive (imaginary) impedance  $jX$  and resistive (real) impedance  $R$  connected as shown in Fig. 1(b). Find the values of the reactance ( $X$ ) and resistance ( $R$ ) leading to matching between TL1 and the rest of the system (on the right).

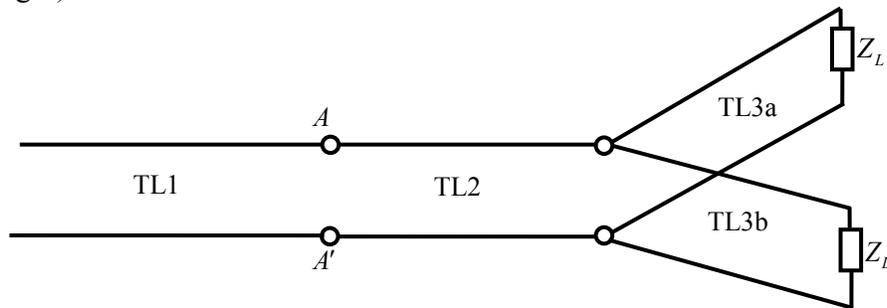


Fig. 1(a)

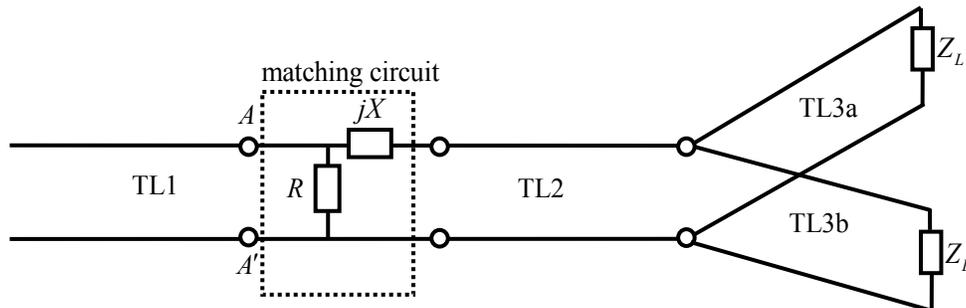


Fig. 1(b)

**Problem 2 [electrostatic]. (50 points)**

Consider a sphere of radius  $R$ , and total charge  $Q$ . The total charge is uniformly distributed through the volume of the sphere.

- 1) Establish an expression of the electric field inside the sphere.
- 2) Establish an expression of the electric field outside the sphere
- 3) Plot the electric field  $E$  as a function of  $r$  with  $r < R$  and  $r > R$  on the same plot. Is  $E(r)$  continuous at  $r=R$ ? Plot the potential  $V(r)$ .
- 4) Same questions 1-3 with the charge  $Q$  only on the surface of the sphere with a uniform surface charge density.