

**UNIVERSITY OF CALIFORNIA**  
**College of Engineering**  
**Department of Electrical Engineering**  
**and Computer Sciences**


**B. E. BOSER**

**Final Exam**  
**May 17, 2000**


**EECS 240**  
**SPRING 2000**

*Show derivations and mark results with box around them. Erase or cross-out erroneous attempts. Mark your name and SID at the top of the exam sheet.*

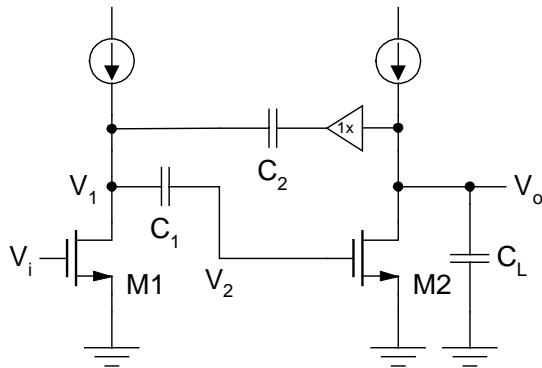1. [30 points] All component values in the amplifiers below are identical except for  $g_{m2}$ , which is adjusted for 63 degrees phase margin with unity-gain feedback. Calculate the ratio of  $g_{m2}$  for amplifier A to  $g_{m2}$  for amplifier B as a function of  $C_{GS1}$ ,  $C_{GS2}$ ,  $C_1$ ,  $C_2$ ,  $C_L$ . Treat all non-given parameters as ideal.




Amplifier A

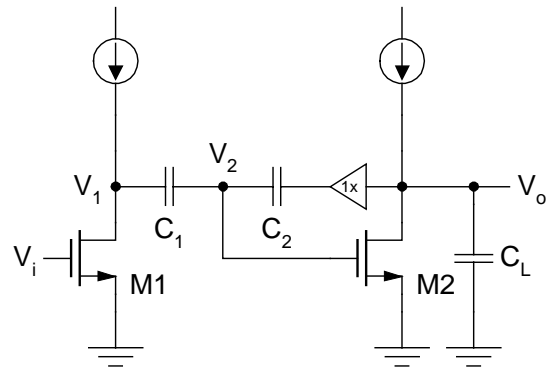


Amplifier B

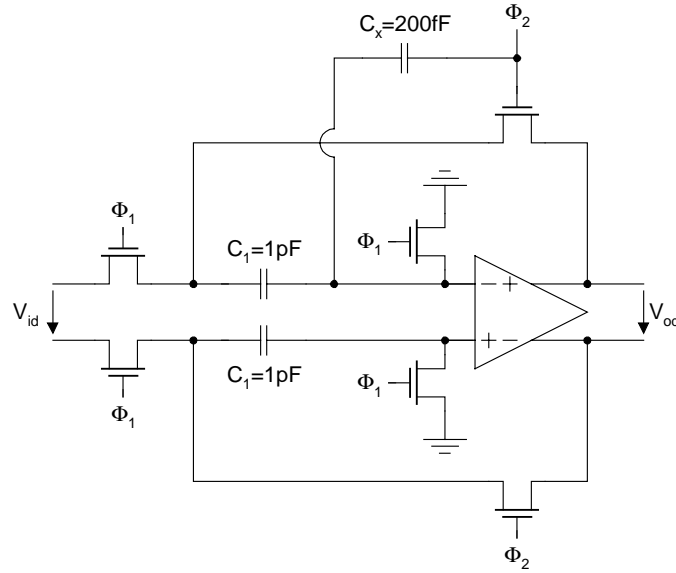2. [15 points] The circuit below is “perfectly” symmetrical except for capacitor  $C_x$  that was inadvertently added due to a layout error. Calculate  $V_{od}$  for  $V_{id}=0$  just before the end of phase  $\Phi_2$ . All transistors are NMOS, the amplifier is ideal, and  $\Phi_1$  and  $\Phi_2$  are 0V to 3V non-overlapping clocks.



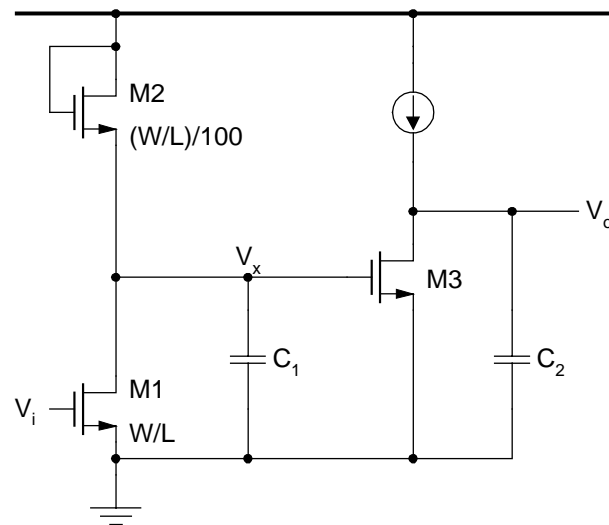3. [30 points] The amplifier below is placed in a negative unity-gain feedback loop (i.e.  $v_i = -v_o$ ).
- Calculate the total output noise delivered to  $C_2$  in V-rms as a function of  $g_{m1}$ ,  $g_{m3}$ ,  $C_1$ ,  $C_2$ . *Ignore the noise from M3, flicker noise and all capacitors except  $C_1$  and  $C_2$ .* All devices operate in the forward-active region and  $g_{m1} r_{o1} \gg 1$ .
- Note:** M3 usually contributes more noise than M1 and M2 combined, but the math is a little too tedious to be appropriate for an exam: do only if you are done with all other problems.
- Calculate the ratio  $g_{m1}/g_{m3}$  required for a 63-degree phase margin with unity-gain feedback.



4. [25 points] All transistors in the circuit below operate in the forward active region, have nominally the same  $W/L$ , and are biased at  $V_{dsat}=200\text{mV}$  (assume “square-law characteristics”). All devices are subject to the following random variations:  $\sigma_{V_{TH0}}=2\text{mV}$ ,  $\sigma_{\Delta(W/L)/(W/L)}=0.2\%$ ,  $\sigma_{\Delta R/R}=0.5\%$ ,  $\sigma_{\gamma}=0.01\text{V}^{1/2}$ .  
 Device Parameters:  $\Phi_f=0.3\text{V}$ ,  $\lambda \rightarrow \text{infinity}$ .
- a) Calculate the standard deviation of the input referred offset voltage,  $\sigma_{V_{os}}$  at low frequency for  $V_X=0\text{V}$  and  $V_X=3\text{V}$ . Assume that the mismatch is small compared to the mean for all parameters.
- b) Assuming  $\sigma_{V_{os}}=5\text{mV}$  (not the correct answer for part a), what is the fraction of amplifiers with an offset voltage less than  $2\text{mV}$ ?

