

NAME \_\_\_\_\_

SID \_\_\_\_\_

UNIVERSITY OF CALIFORNIA  
College of Engineering  
Department of Electrical Engineering  
and Computer Sciences

B. E. BOSER

Final Exam  
May 21, 2002

EECS 240  
SPRING 2002


Show derivations and **mark results** with box around them. Erase or cross-out erroneous attempts. Mark your name and SID at the top of the exam sheet.

1. [25 points] MOS S/H


The circuit below operates from a two-phase non-overlapping 0V/3V clock. The switch  $\Phi_{1\text{late}}$  opens shortly after the switch clocked with  $\Phi_1$ .

- Calculate the maximum value of  $W$  for which the charge injected onto  $C$  results in a sampling error of less than 50mV. Assume fast gating and that the channel charge splits equally between source and drain.
- Assuming that the source  $V_i$  has zero output resistance and  $W=10\mu\text{m}$  (not the correct answer for a), what is the **worst-case** relative settling accuracy for  $t_{\text{settle}}=5\text{ns}$  (ignore charge injection)?

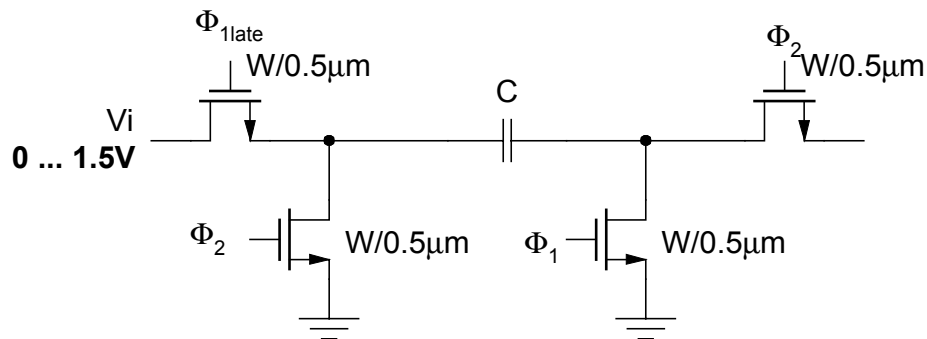Parameter:  $V_{\text{THN}}=1\text{V}$ ,  $\mu_n C_{\text{ox}}=200\mu\text{A}/\text{V}^2$ ,  $C_{\text{ox}}=5\text{fF}/\mu\text{m}^2$ ,  $C_{\text{ol}}'=0.2\text{fF}/\mu\text{m}$ ,  $C=1\text{pF}$ .  
Assume square-law and ignore the body-effect.




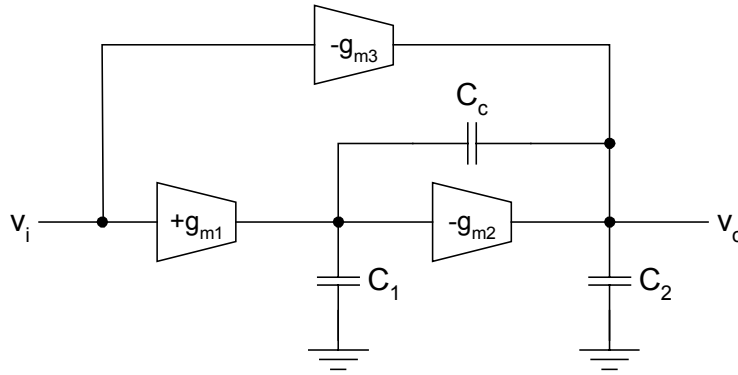2. [25 points] The diagram below illustrates an alternative method for removing the feedforward zero arising from Miller compensation.
- Find the value of  $g_{m3}$  that moves the zero of  $V_o(s)/V_i(s)$  to infinity as a function of  $g_{m1}$ ,  $g_{m2}$ ,  $C_1$ ,  $C_2$ , and  $C_c$ . Simplify your result, but do not make assumptions regarding the relative value of component sizes.
  - Compare this approach to using a nulling resistor. List key advantages or disadvantages of the proposed solution.



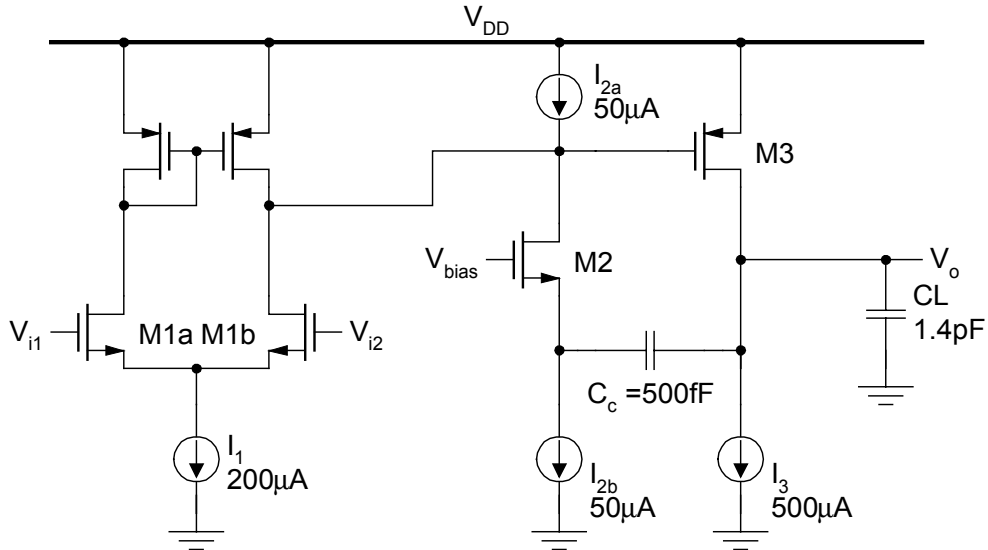3. [25 points] For the amplifier below find
- The positive and negative slew-rate at the output.
  - The input referred offset if  $I_{2a}$  and  $I_{2b}$  are mismatched by 10%; i.e.
 
$$I_{2a} - I_{2b} = 0.05(I_{2a} + I_{2b}).$$

Ignore all capacitors except those shown explicitly, transistor output impedance.  $g_{m1}=1\text{mS}$ ,  $g_{m2}=5\text{mS}$ . M2 and M3 can source very large currents.



4. [25 points] Find a reasonably simplified analytical expression for the low-frequency CMRR of the circuit below as a function of

$$R_L = \frac{R_{L1} + R_{L2}}{2} \quad R_S = \frac{R_{S1} + R_{S2}}{2} \quad \text{and } R_X.$$

$$\Delta R_L = R_{L1} - R_{L2} \quad \Delta R_S = R_{S1} - R_{S2}$$

Assume  $G_m R_i \gg 1$  for  $i=L, S, X$ .

What is the fraction of amplifiers having CMRR=60dB or better?

Parameter:  $g_{m1}=g_{m2}=1\text{mS}$ ,  $R_S=10\text{k}\Omega$ ,  $R_X=10\text{k}\Omega$ ,  $R_L=100\text{k}\Omega$ ,  $\sigma_{\Delta R/R}=0.12\%$ .

