

EECS 240
B. E. BOSSER

FINAL
SOLUTION

SPRING 199

$$1. \quad R_{on} = \left(\mu C_{ox} \frac{W}{L} \cdot (V_{GS} - V_{TH}) \right)^{-1} = \frac{1}{g_m} \quad 2$$

$$B = (2\pi R_{on} \cdot C_H)^{-1} \quad 3$$

$$\Rightarrow C_H = g_m / 2\pi B$$

$$\Delta V = \frac{Q_{CHAN}}{C_H} = \frac{WL C_{ox} (V_{GS} - V_{TH})}{C_H} \quad 5$$

$$= \frac{1.5 C_{GS} \cdot (V_{GS} - V_{TH})}{g_m} \cdot 2\pi B$$

$$= \frac{1.5 (V_{GS} - V_{TH}) \cdot 2\pi B}{2\pi f_T}$$

$$\begin{aligned} \therefore f_T &= B \cdot \frac{1.5 (V_{GS} - V_{in} - V_{TH})}{\Delta V} \quad 10 \\ &= 50 \text{ MHz} \cdot 1.5 \cdot \frac{3 - 1 - 1}{0.02} \\ &= 3.75 \text{ GHz} \approx 4 \text{ GHz} \end{aligned}$$

Reference:D:\Users\Bernhard\Lib\MathCAD\Default\defaults.mcd

corrected

Thermal Noise in 2-Stage OTA

Unilateral Feedback through C_c

given

$$s \cdot C_c \cdot (v_x - v_o) + i_1 - v_o \cdot g_{m1} \cdot F = 0$$

$$g_{m2} \cdot v_x + s \cdot C_L \cdot v_o + i_2 = 0$$

$$v_o = \frac{1}{F \cdot g_{m1}} \cdot \frac{1}{s \cdot C_c + \frac{s^2 \cdot C_c \cdot C_L}{F \cdot g_{m1} \cdot g_{m2}}} \cdot \left(i_1 - i_2 \cdot \frac{s \cdot C_c}{g_{m2}} \right)$$

$$v_o = \frac{1}{F \cdot g_{m1}} \cdot \frac{\omega_o^2}{s^2 + s \cdot \frac{\omega_o}{Q} + \omega_o^2} \cdot \left(i_1 - i_2 \cdot \frac{s \cdot C_c}{g_{m2}} \right)$$

with $\omega_o = \sqrt{\frac{F \cdot g_{m1} \cdot g_{m2}}{C_c \cdot C_L}}$ $Q = \frac{1}{\omega_o} \cdot \frac{F \cdot g_{m1}}{C_c}$

Noise from M2:

$$N_2 = \int_0^\infty 4 \cdot k_B \cdot T_r \cdot \frac{2}{3} \cdot g_{m2} \cdot \left(\frac{1}{F \cdot g_{m1}} \right)^2 \cdot \left(\frac{\omega_o \cdot C_c}{g_{m2}} \right)^2 \cdot \left(\frac{s \cdot \omega_o}{s^2 + s \cdot \frac{\omega_o}{Q} + \omega_o^2} \right)^2 df$$

RESULT: $N_2 = \frac{k_B \cdot T_r \cdot C_c^2}{C_c \cdot C_L} \cdot \frac{2}{3}$

FYI: $\frac{N_2}{N_1} = F \cdot \frac{C_c}{C_c + C_L} \cdot \frac{g_{m1}}{g_{m2}}$ (usually < 1, esp. for small F)

$$3. \quad \Delta i_{1-2} = \frac{V_{dd}}{R_{SS}} \cdot \frac{\Delta g_m}{g_m}$$

↑ tail c.s. ↑ current divider

$$\Delta i_{3-4} = V_{dd} \cdot \Delta g_m$$

$$A_{dm} = g_m \cdot R_o$$

$$A^{++} = \frac{V_{od}}{V_{dd}} = \frac{\Delta i \cdot R_o}{V_{dd}}$$

$$\therefore PSRR = g_m / \Delta i \cdot V_{dd}$$

$$\frac{\Delta i}{V_{dd}} = \Delta g_m \cdot \left(1 + \frac{1}{R_{SS} \cdot g_m} \right)$$

$$PSRR = \frac{g_m}{\Delta g_m} \cdot \frac{1}{1 + \frac{1}{R_{SS} \cdot g_m}} \approx \underline{\underline{31.6}}$$

$$\Delta g_m = g_m \cdot \frac{\Delta V_{TH}}{V_d^{sat}}$$

$$\Rightarrow \frac{g_m}{\Delta g_m} = \frac{V_d^{sat}}{\Delta V_{TH}} = 31.6$$

$$g_m \cdot R_{SS} = 15.8$$

using


$$g_m = 316 \mu S$$

$$V_d^{sat} = 316 mV$$


contribution from
 M₃₋₄ dominates
 since V_{TH} is
 connected "WRONG"

a) $\epsilon \approx \frac{1}{A_0 F} = \underline{\underline{0.25\%}}$

5pts

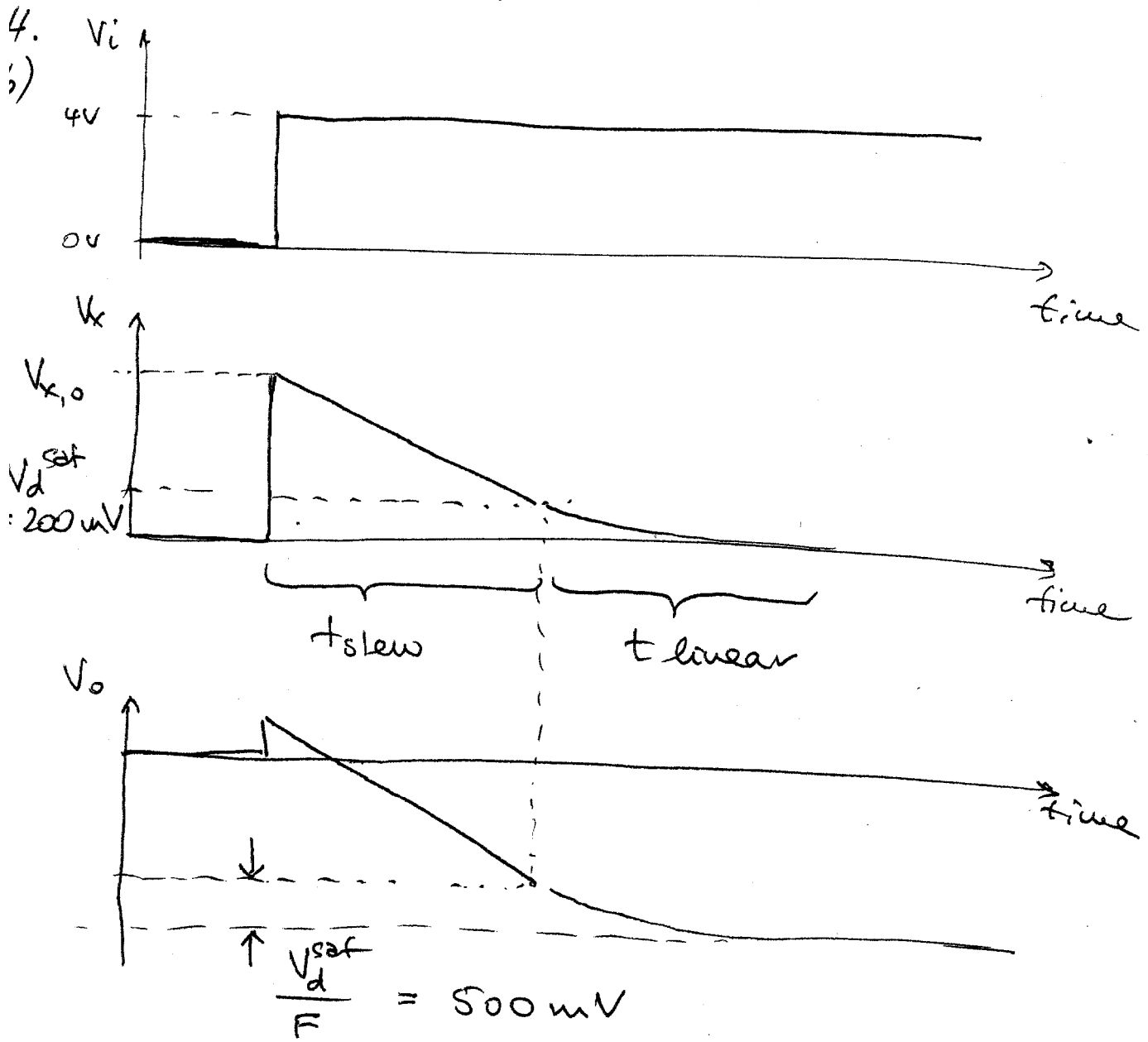

model during slewing:

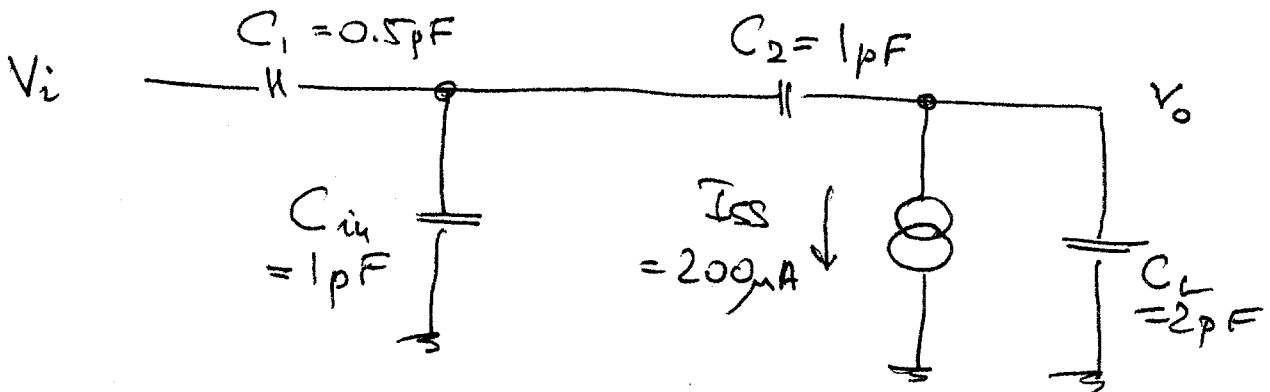

$$c = \frac{C_1}{C_2} = 0.5$$

$$F = \frac{C_2}{C_1 + C_2 + C_{in}} = \frac{1}{2.5} = 0.4$$

$$V_d^{sat} = \frac{2V_D}{g_m} = \frac{I_{SS}}{g_m} = 200 \text{ mV}$$

A) Calculate initial step:

$$V_{x,0} = V_{step} \cdot \frac{C_1}{(C_2 \parallel C_c) + C_{in} + C_L} = 923 \text{ mV}$$

B) Slew rate:

$$\begin{aligned} C_L^* &= C_L + C_2 \parallel (C_1 + C_{in}) = 2.6 \text{ pF} \\ &= C_L + F \cdot (C_1 + C_{in}) = C_L + C_2(1-F) \end{aligned}$$

$$SR = \frac{I_{SS}}{C_L^*} = 77 \text{ V}/\mu\text{sec.}$$

$t_{slew} = \frac{\Delta V_o}{SR} = 23.5 \text{ nsec.}$	10 pts
$\Delta V_o = \frac{V_{x0} - V_d^{sat}}{F} = 1808 \text{ mV}$	

c) linear settling

$$V_{\text{error}} = \varepsilon \cdot 2V$$

$$\varepsilon^* = \frac{V_{\text{error}}}{0.5V} = \varepsilon \cdot \frac{2V}{0.5V} = 0.4\%$$

↑ final change of output after steering

$$\tau = \frac{C_L + (1-F) \cdot C_2}{F \cdot g_m} = \frac{2.6 \text{ pF}}{0.4 \text{ mS}} = 6.5 \text{ ns}$$

$$t_{\text{linear}} = -\tau \cdot \ln \varepsilon^* = 36 \text{ usec.}$$

10pts

$$t_{\text{settle}} = t_{\text{steer}} + t_{\text{lin}} \approx 60 \text{ nsec.}$$